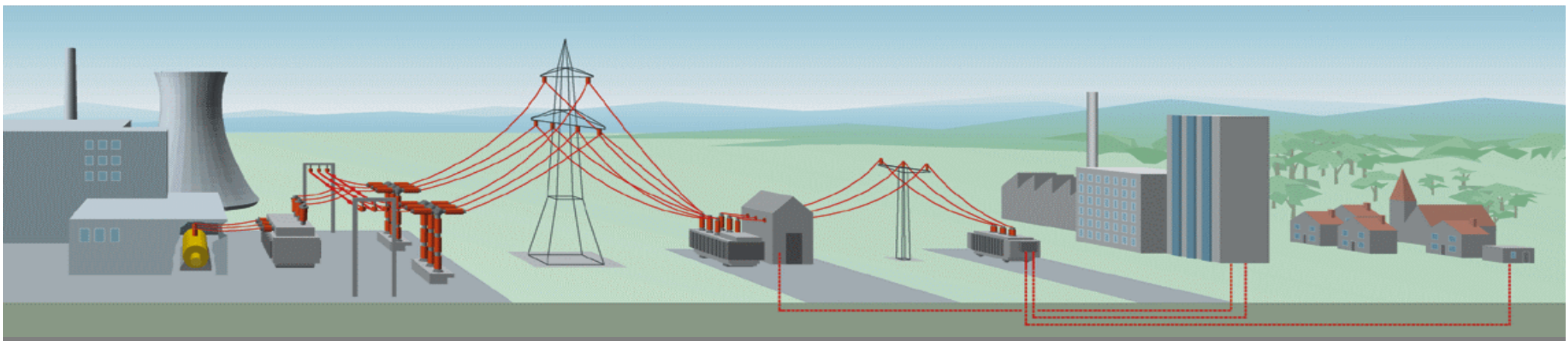


# Digital Differential Protection

G. Ziegler



## Differential Protection: Discussion Subjects

- ∅ Mode of operation
- ∅ Measuring technique
- ∅ Current transformers
- ∅ Communications
- ∅ Generator and motor differential protection
- ∅ Transformer differential protection
- ∅ Line differential protection
- ∅ Busbar differential protection



# Digital Differential Protection

## Principles and Application

Gerhard Ziegler

SIEMENS

## Contents

	Pages
Mode of operation	3 - 27
Measuring technique	28 - 45
Current transformers	46 - 86
Communications	87 - 115
Generator and motor differential protection	116 - 122
Transformer differential protection	123 - 178
Line differential protection	179 - 216
Busbar differential protection	217 - 247
7UT6 product features	248 - 264



# Digital Differential Protection


## Mode of operation

Gerhard Ziegler

**SIEMENS**
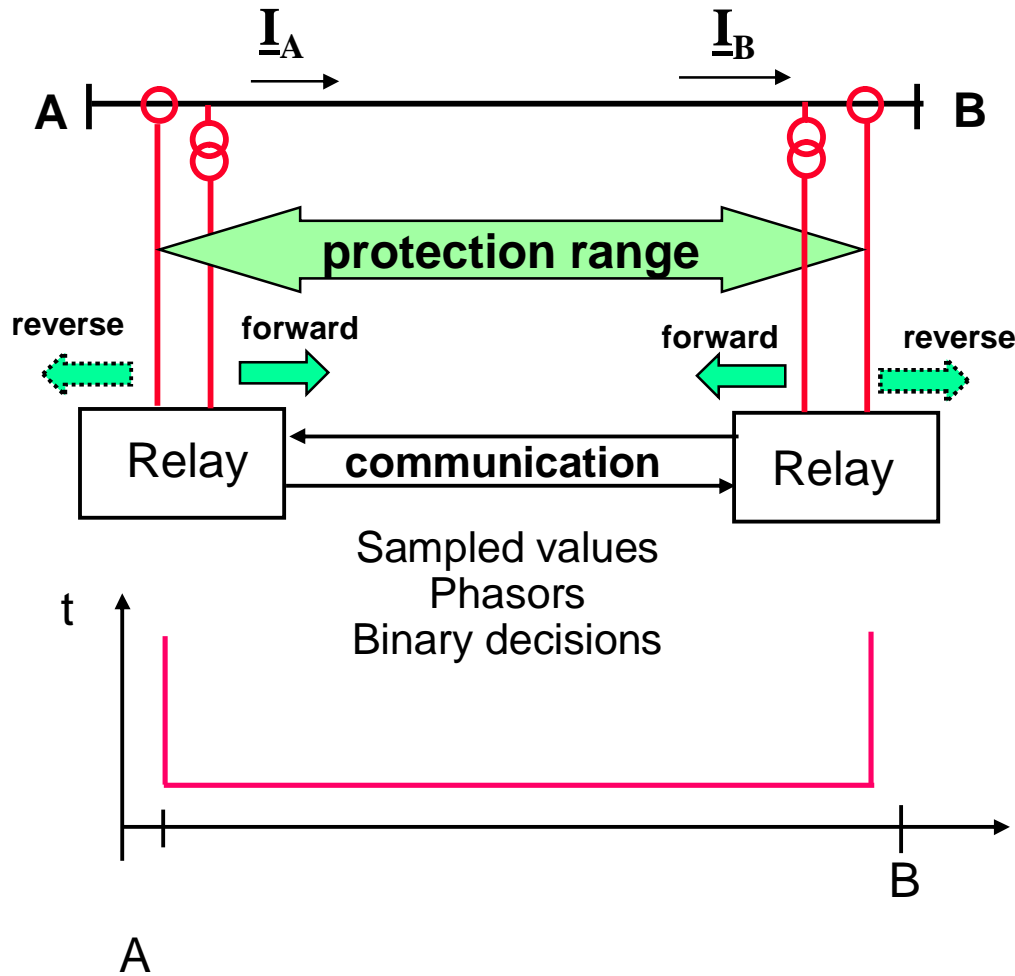
# Comparison protection - Principles


Absolute selectivity by using communications



• Directional comparison

Exchange of YES / NO signals  
(fault forward / reverse)

• Current comparison

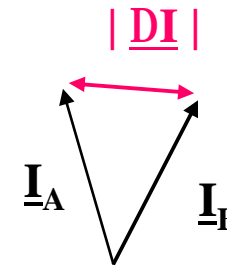


• comparison of momentary values or phasors

•  $|\underline{\Delta I}| = |\underline{I}_A - \underline{I}_B| > \text{limiting value}$

## Protection Criterion “current difference“ (differential protection)


- n Kirchhoff's law:  $I_{\underline{1}} + I_{\underline{2}} + I_{\underline{3}} + \dots + I_{\underline{n}} = I_{\text{diff}} = 0$ ;  
Current difference indicates fault
- n Security by through-current dependent restraint  
 $|I_1| + |I_2| + \dots + |I_n| = I_{\text{Res}}$

- n Characteristic:

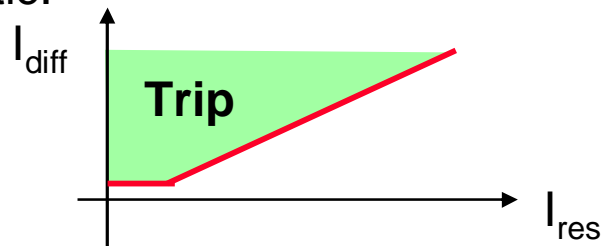


- n Absolute zone selectivity (limits: CT locations)  
No “back-up“ for external faults

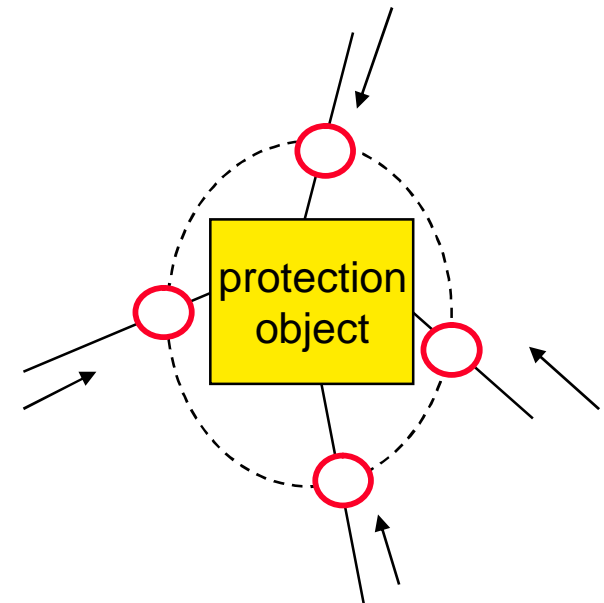
- n **Differential protection:** for generators, motors, transformers, lines and busbars


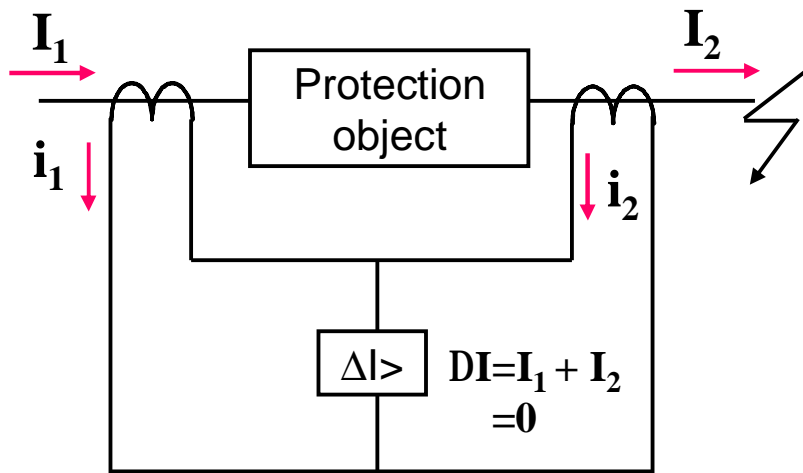
# Current differential protection: Basic principle



external fault or load

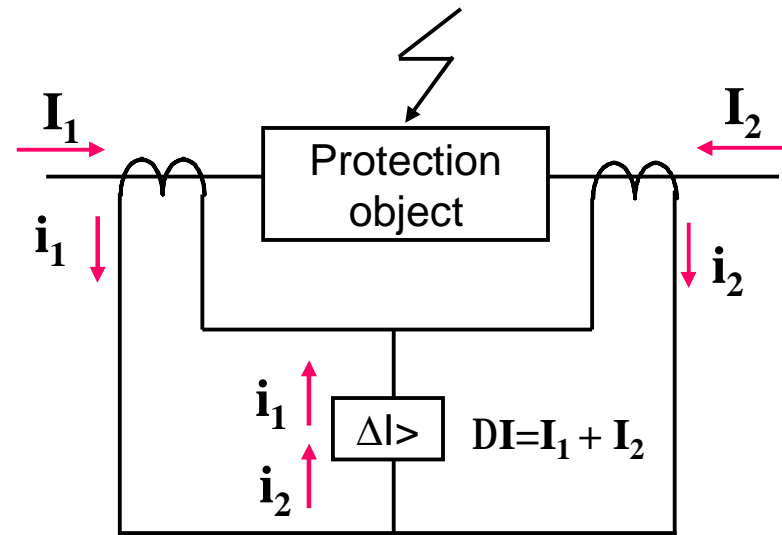


internal fault



# Differential protection: Connection circuit


Traditional technique

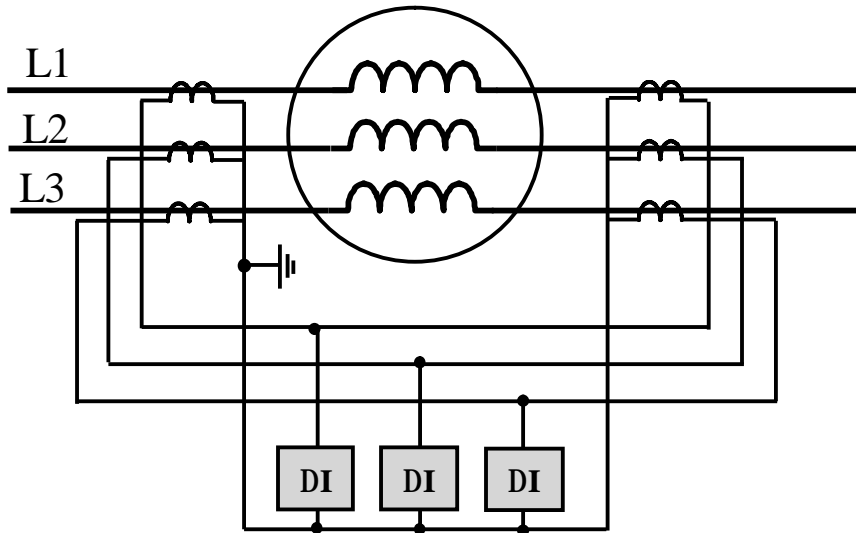

Galvanically connected circuits must only be earthed once!

Different CT ratios need to be adapted by auxiliary CTs!



Digital technique

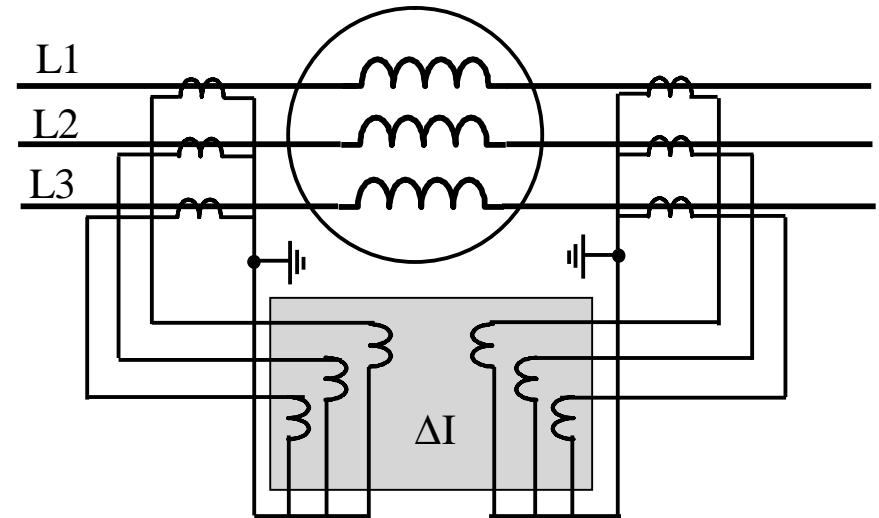


CT circuits of digital relays are segregated and must each be earthed !

Digital relays have integrated numerical ratio adaptation !
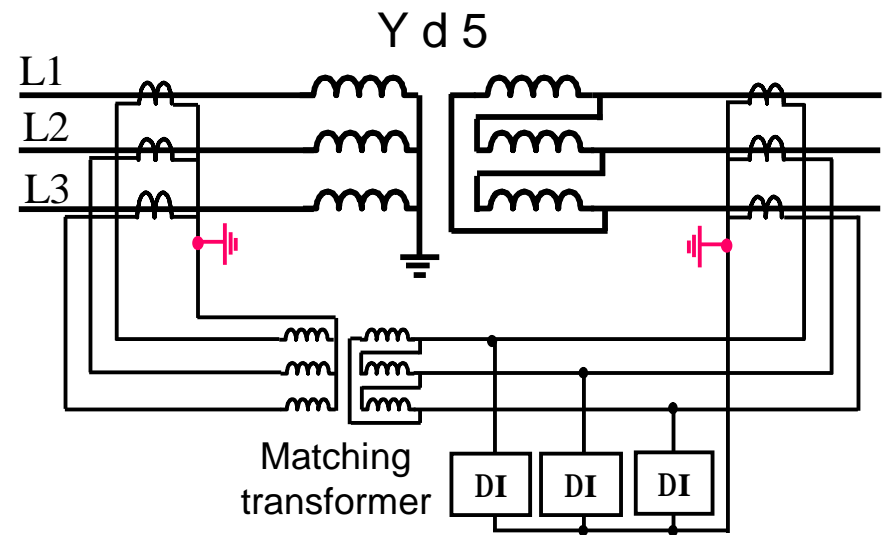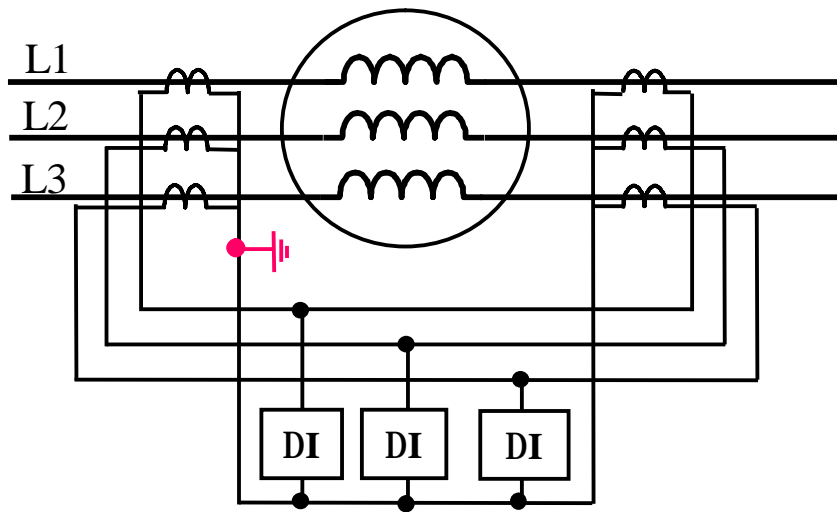
# Generator and transformer differential protection




# Transformer differential protection

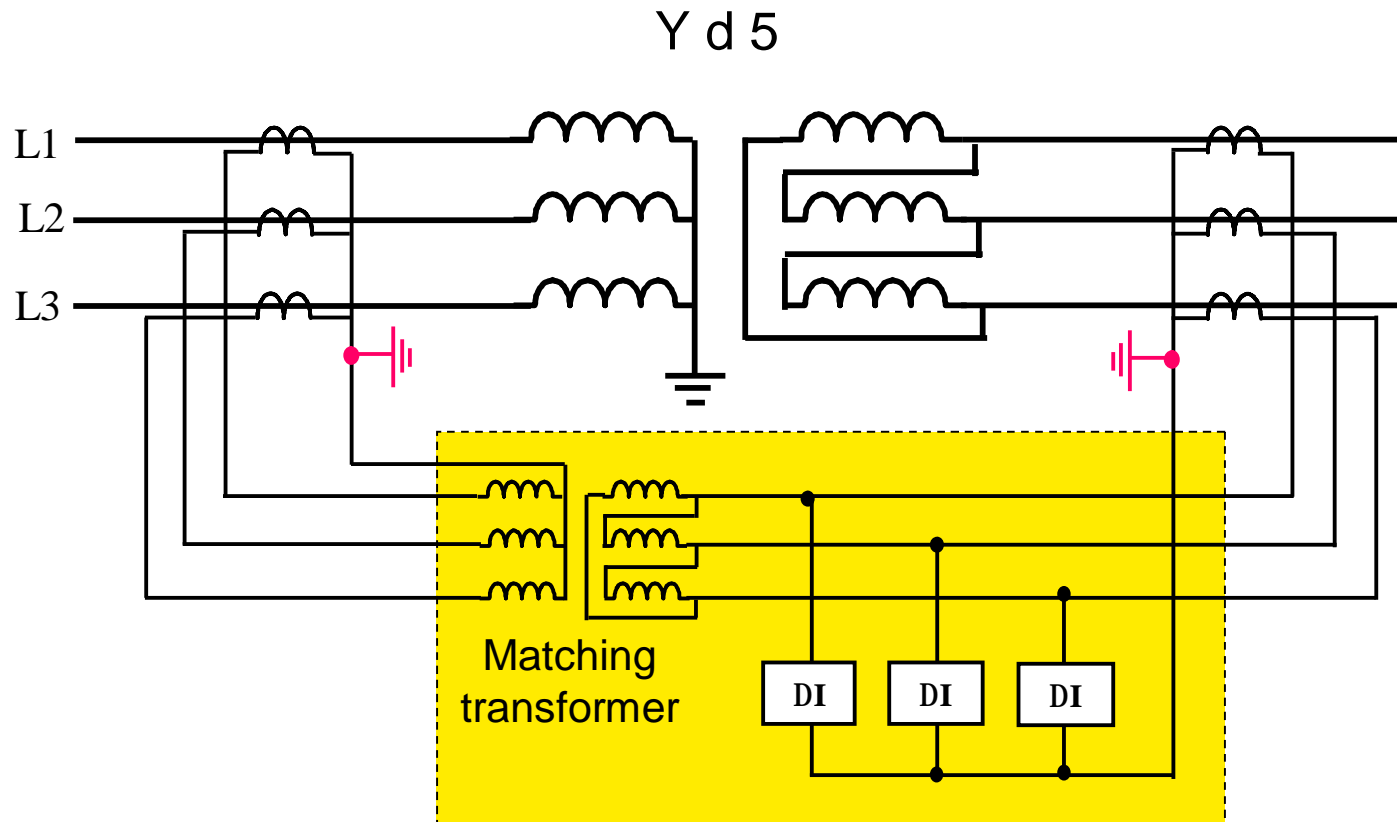


# Current transformer:

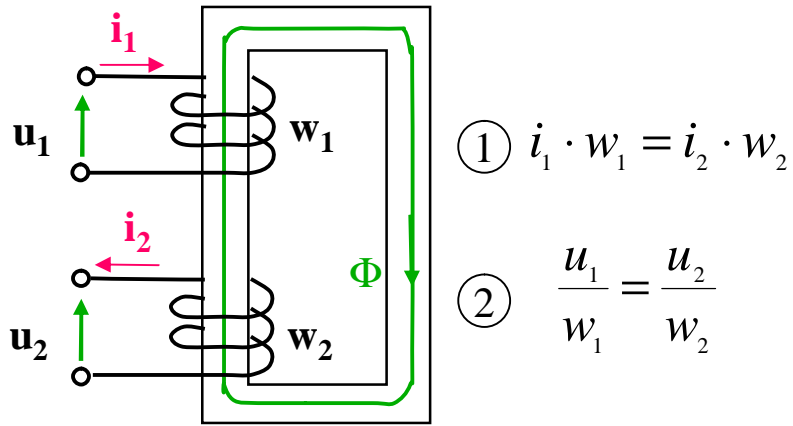
## Principle, transformation ratio, polarity




Function principle

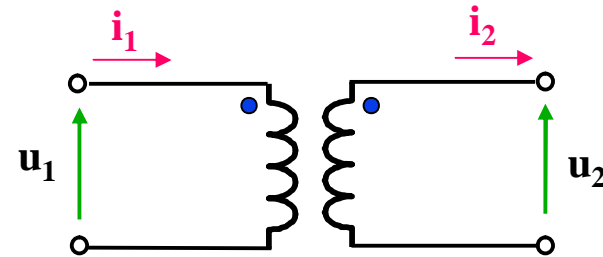

Polarity marks

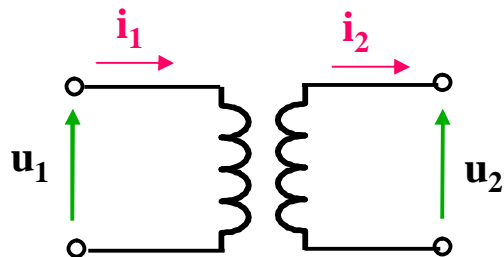


Equivalent electrical circuit

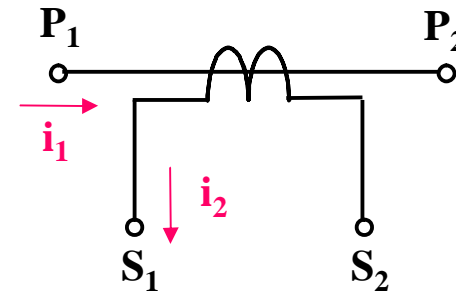


Designation of CT terminals according to IEC 60044-1
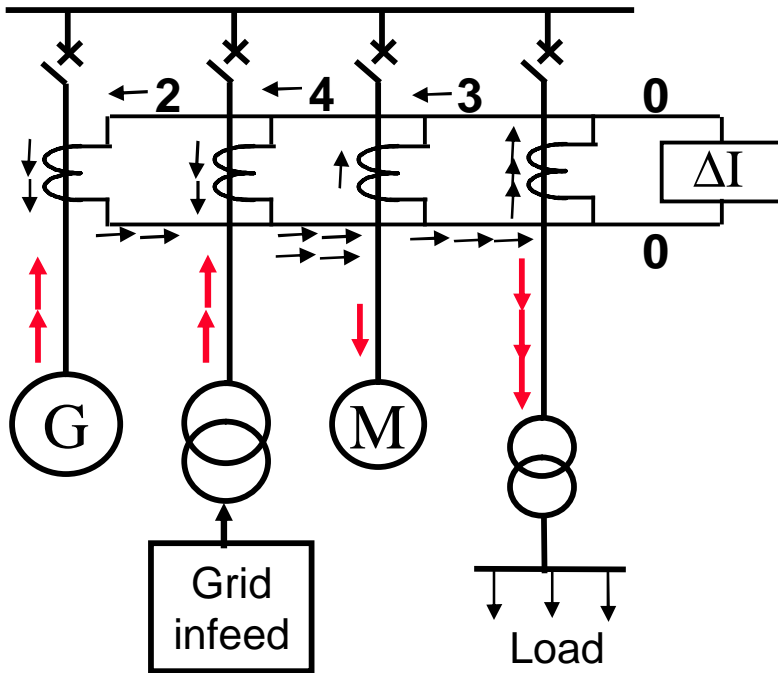
# Busbar differential protection

Analog protection **7SS10/11/13**  
**7SS600** with digital measuring relay ( $\Delta I$ )




Digital protection **7SS52**

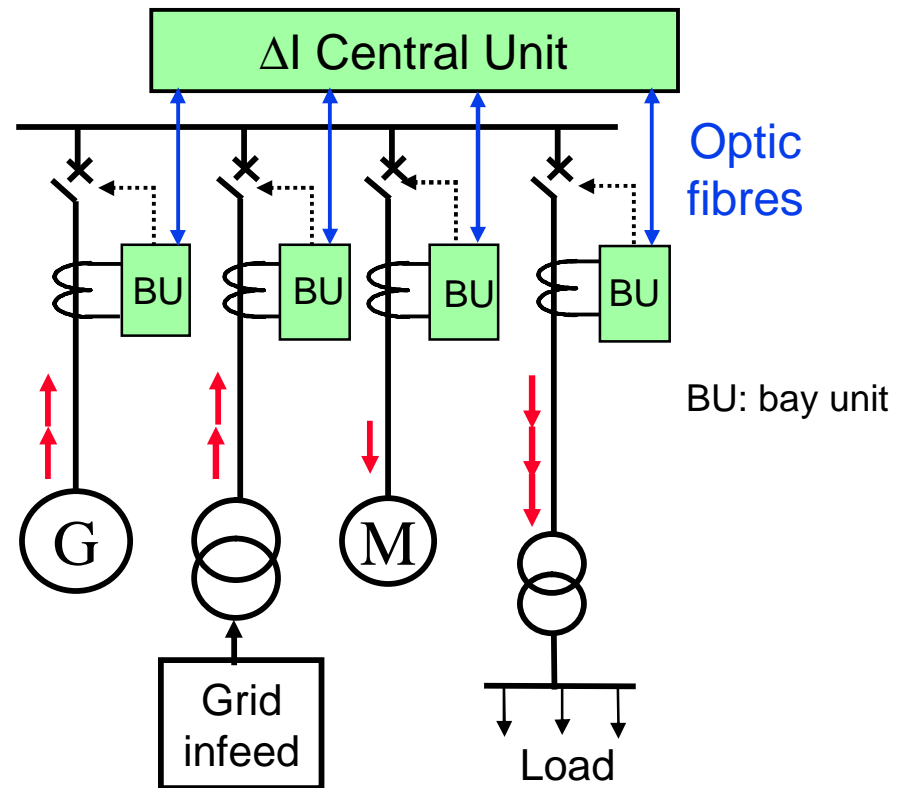

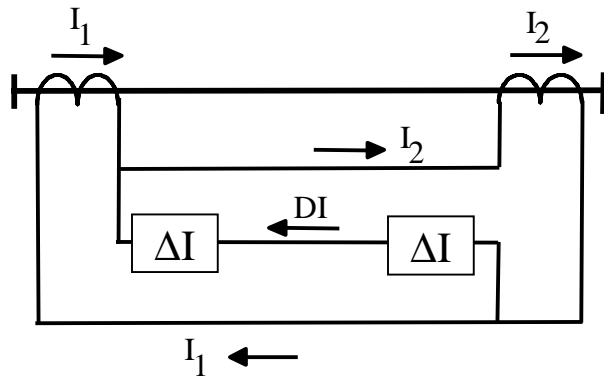
# Line differential protection

50/60 Hz current comparison through wire connection





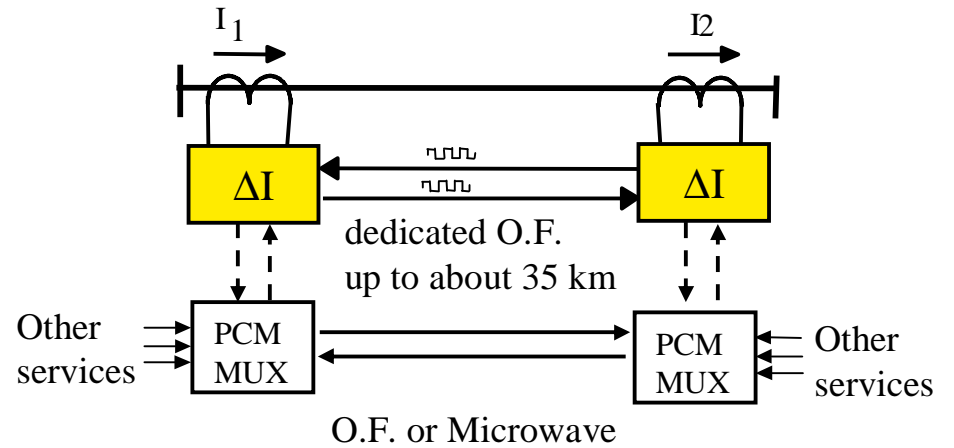Phasor with digital communication via OF, microwave or pilot wires




# Two wire (pilot wire) line differential protection

## Voltage comparison principle

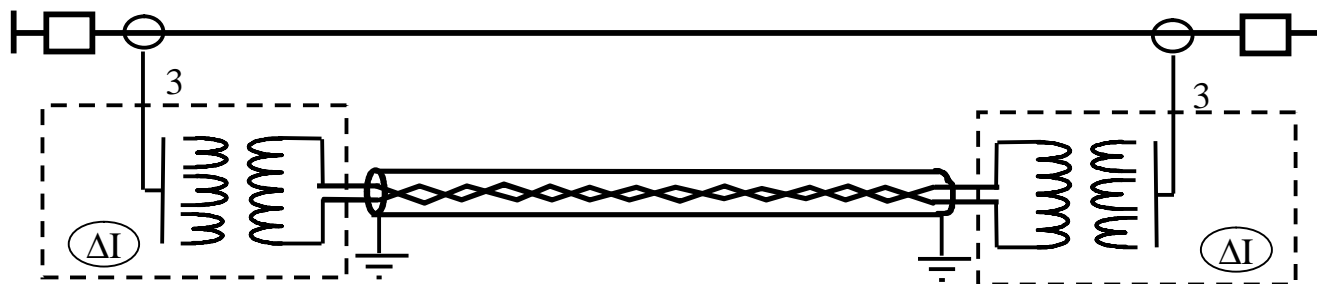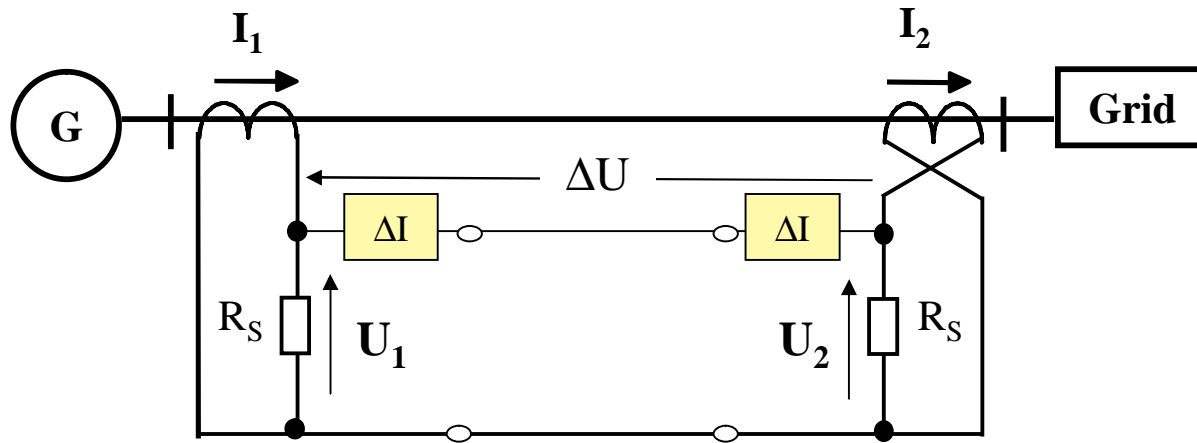

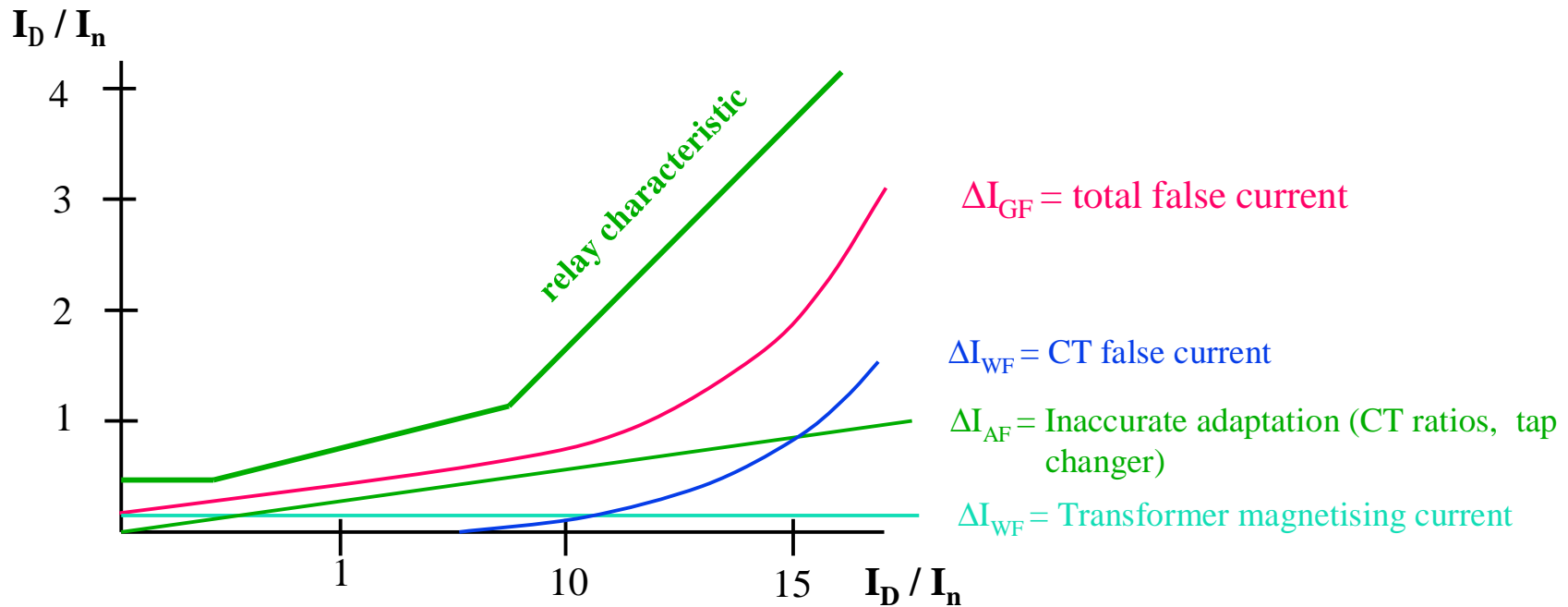
# False differential currents during load or external faults






# Percentage differential relay

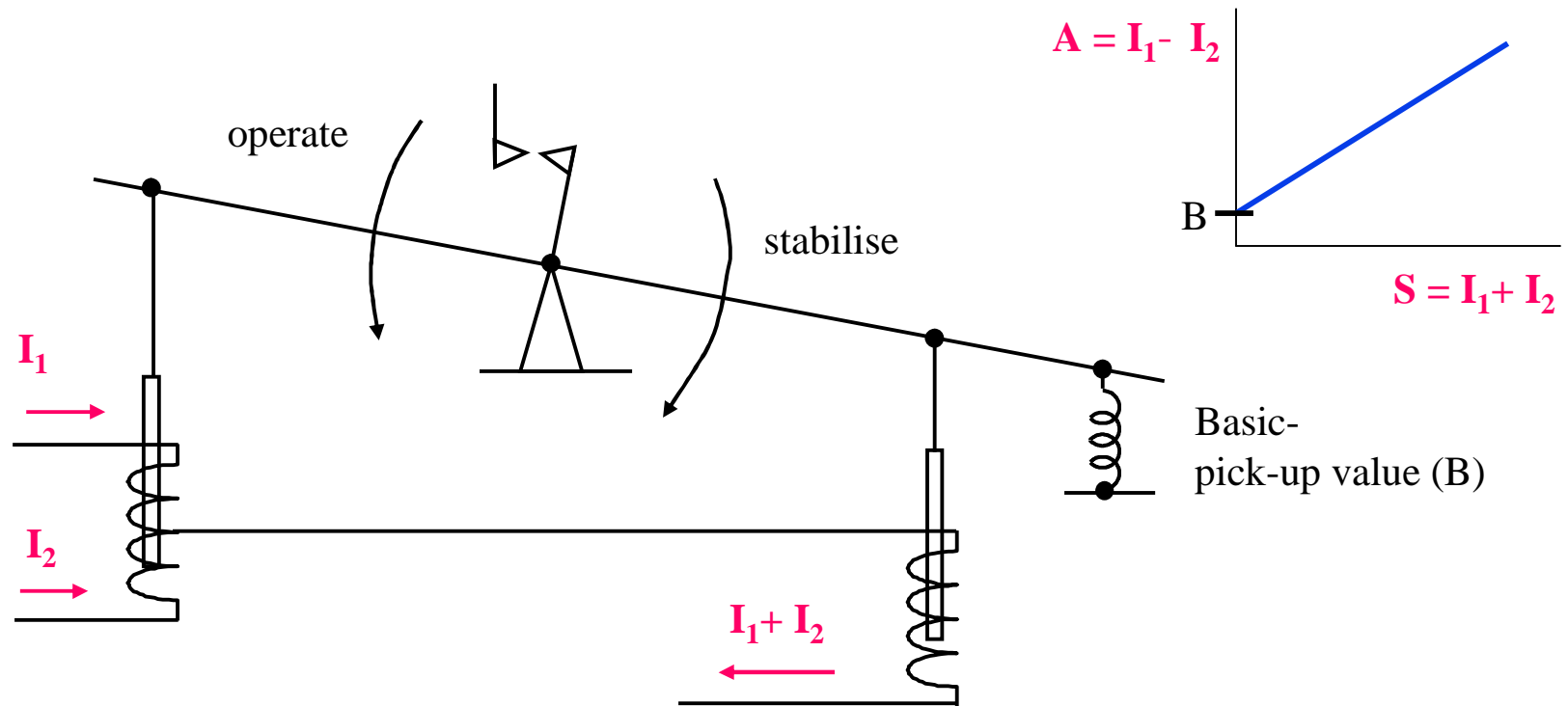


# Differential protection: analog measuring circuit
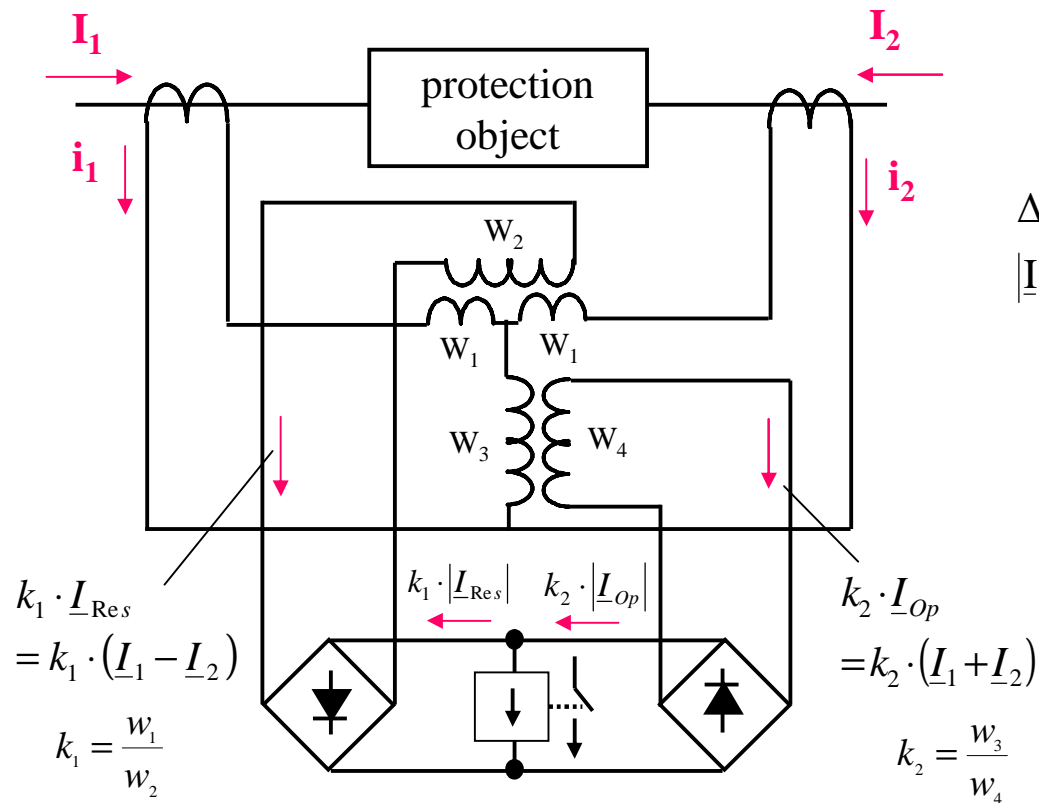
## Rectifier bridge comparator with moving coil relay



$$\Delta I = |\underline{I}_1 - \underline{I}_2|$$

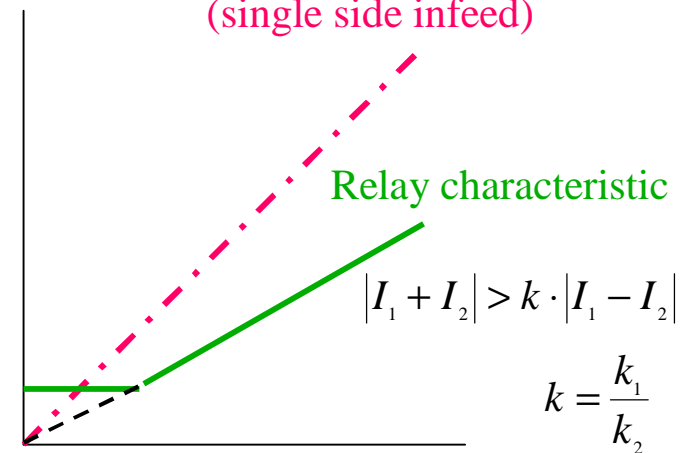
Fault characteristic (single side infeed)



$$\Sigma I = |\underline{I}_1 + \underline{I}_2|$$

with digital relays:  $\Sigma I = |\underline{I}_1| + |\underline{I}_2|$



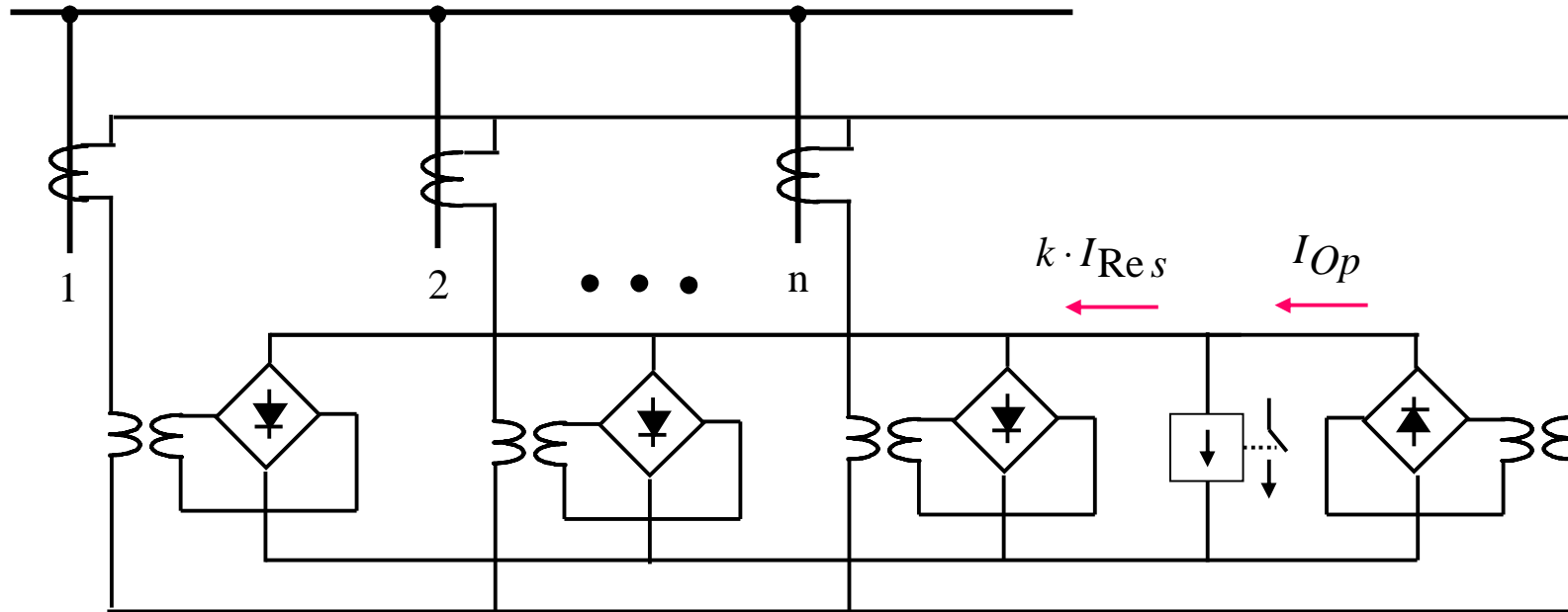
# Multi-end differential protection: Analog measuring principle



$$I_{Op} = |\underline{I}_1 + \underline{I}_2 + \dots + \underline{I}_n| = \Sigma |\underline{I}|$$

$$I_{Res} = |\underline{I}_1| + |\underline{I}_2| + \dots + |\underline{I}_n| = |\Sigma \underline{I}|$$

# Optimised relay characteristic

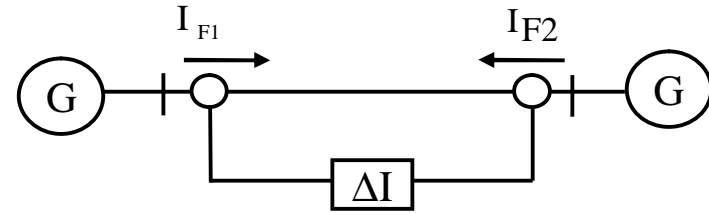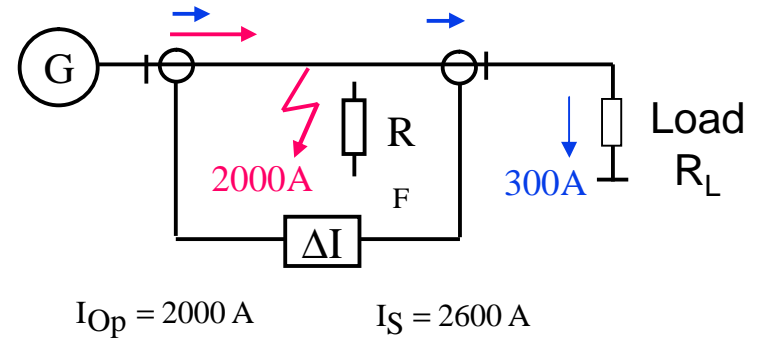
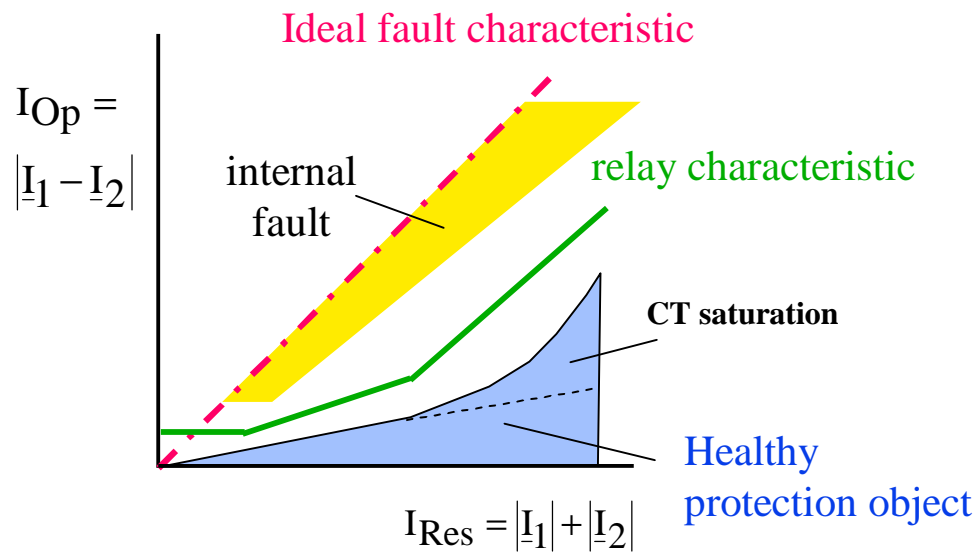


$$I_{Res} = 2 \cdot |I_F|$$

The vector diagram shows two vectors originating from the same point. The resultant vector is labeled  $I_{Op} = 2 \cdot |I_F| \cdot \cos \frac{\delta}{2}$ , where  $\delta$  is the angle between the two vectors.

# Digital differential protection: Relay characteristic

Positive current polarity

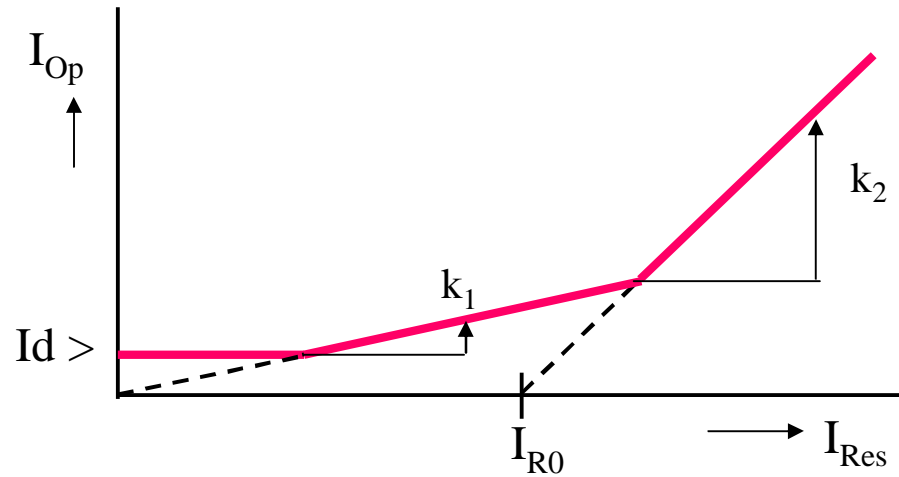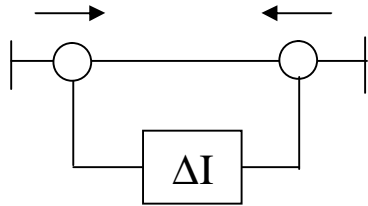


$$I_{Op} = |\Sigma I| = |I_{-1} + I_{-2}|$$

$$I_{Res} = \Sigma |I| = |I_{-1}| + |I_{-2}|$$

Settings:

- Pick-up value  $I_d >$
- slope  $k_1$
- slope  $k_2$  with footing point  $I_{R0}$
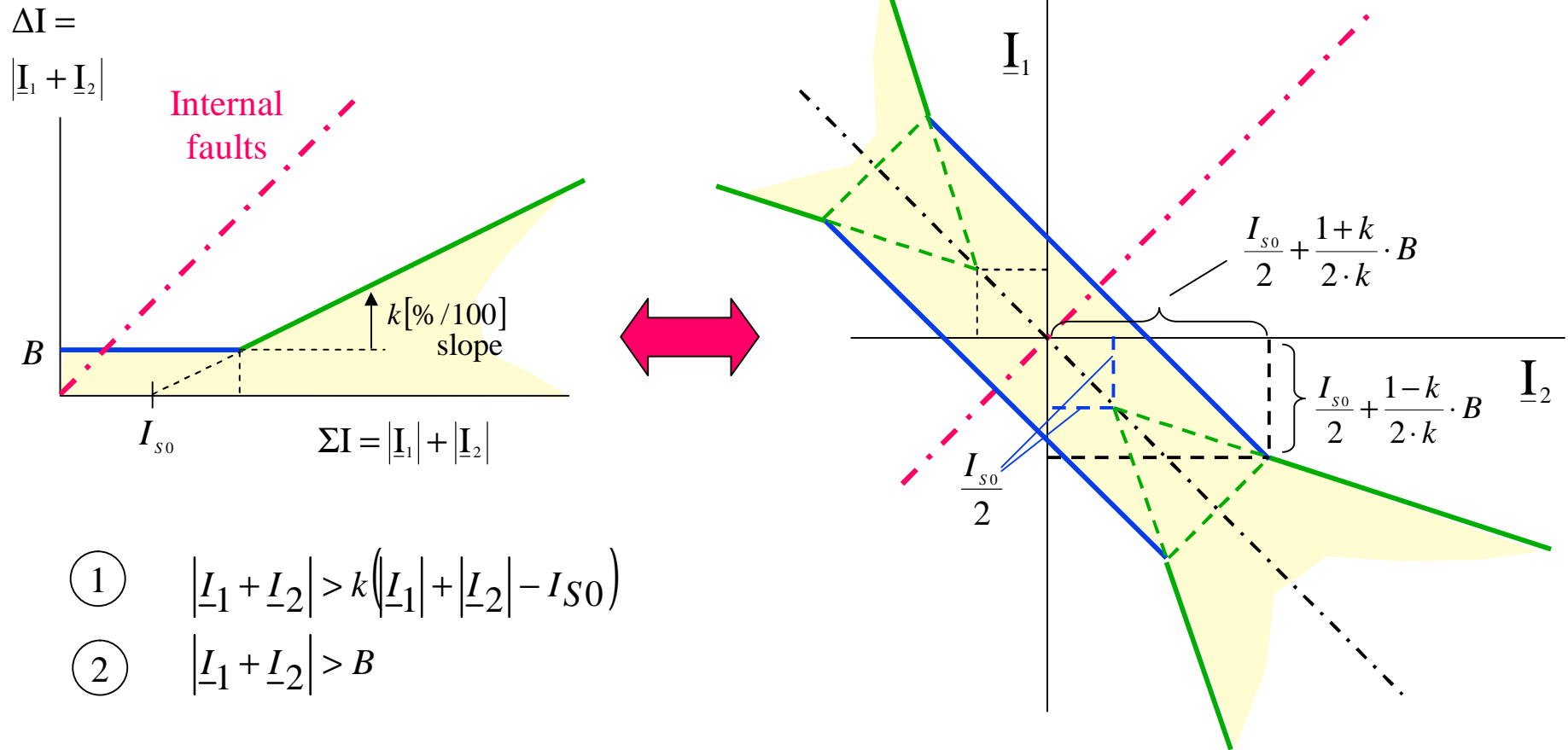
# $\Delta I / \Sigma I$ und $I_1 / I_2$ diagram




# Polar diagram of differential protection

$$|\underline{I}_1 + \underline{I}_2| > k \cdot |\underline{I}_1 - \underline{I}_2|$$

$\beta$ -Plane (remote/local current)

$$\left| \frac{1 + \frac{\underline{I}_2}{\underline{I}_1}}{1 - \frac{\underline{I}_2}{\underline{I}_1}} \right| > k \quad \text{or} \quad \left| \frac{1 + \underline{\beta}}{1 - \underline{\beta}} \right| > k$$

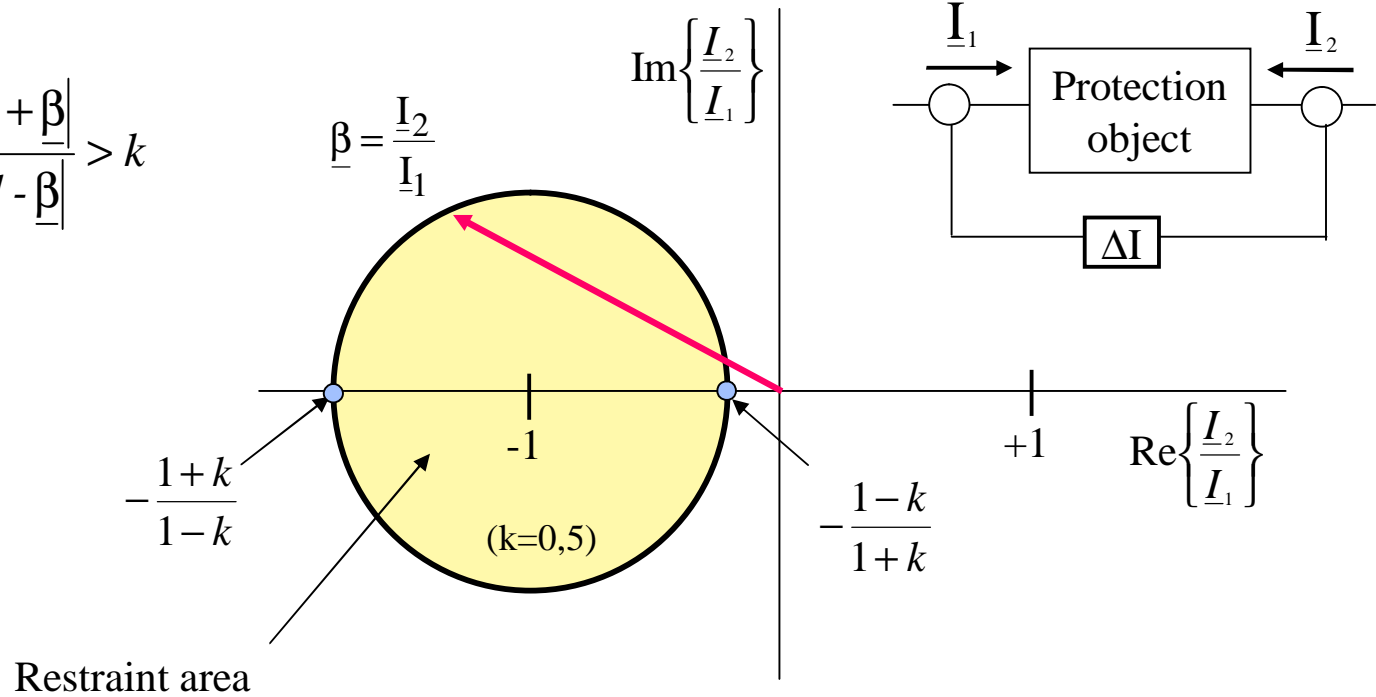with  $\underline{\beta} = \frac{\underline{I}_2}{\underline{I}_1}$




# Polar diagram of digital differential protection: Basic pick-up value $B > 0$

$$|\underline{I}_1 + \underline{I}_2| > k \cdot (|\underline{I}_1| + |\underline{I}_2|) + B$$

or


$$\left| 1 + \frac{\underline{I}_2}{\underline{I}_1} \right| > k \cdot \left( 1 + \left| \frac{\underline{I}_2}{\underline{I}_1} \right| \right) + \frac{B}{|\underline{I}_1|}$$

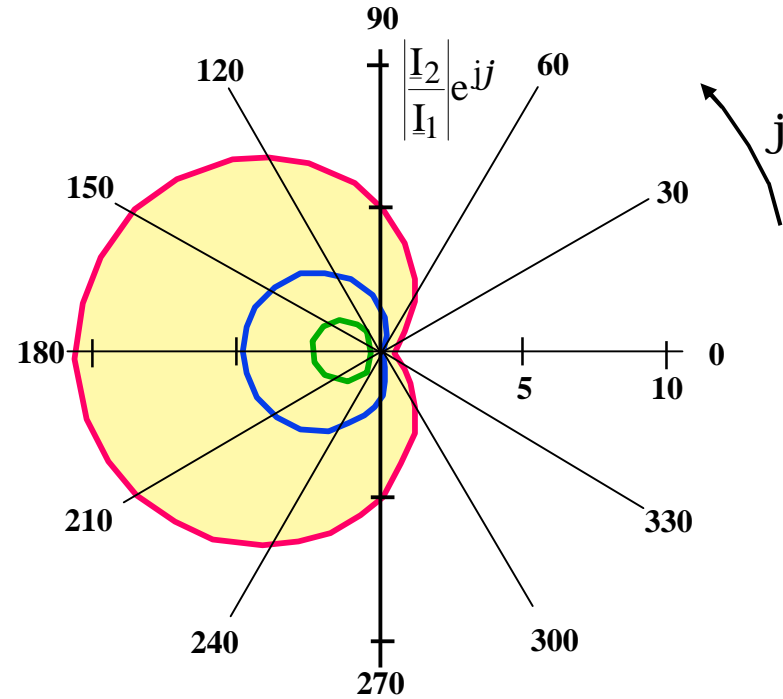

- $B/I_1 = 0,3$      $a1(F): k=0,3$     —
- $a2(F): k=0,6$     —
- $a3(F): k=0,8$     —


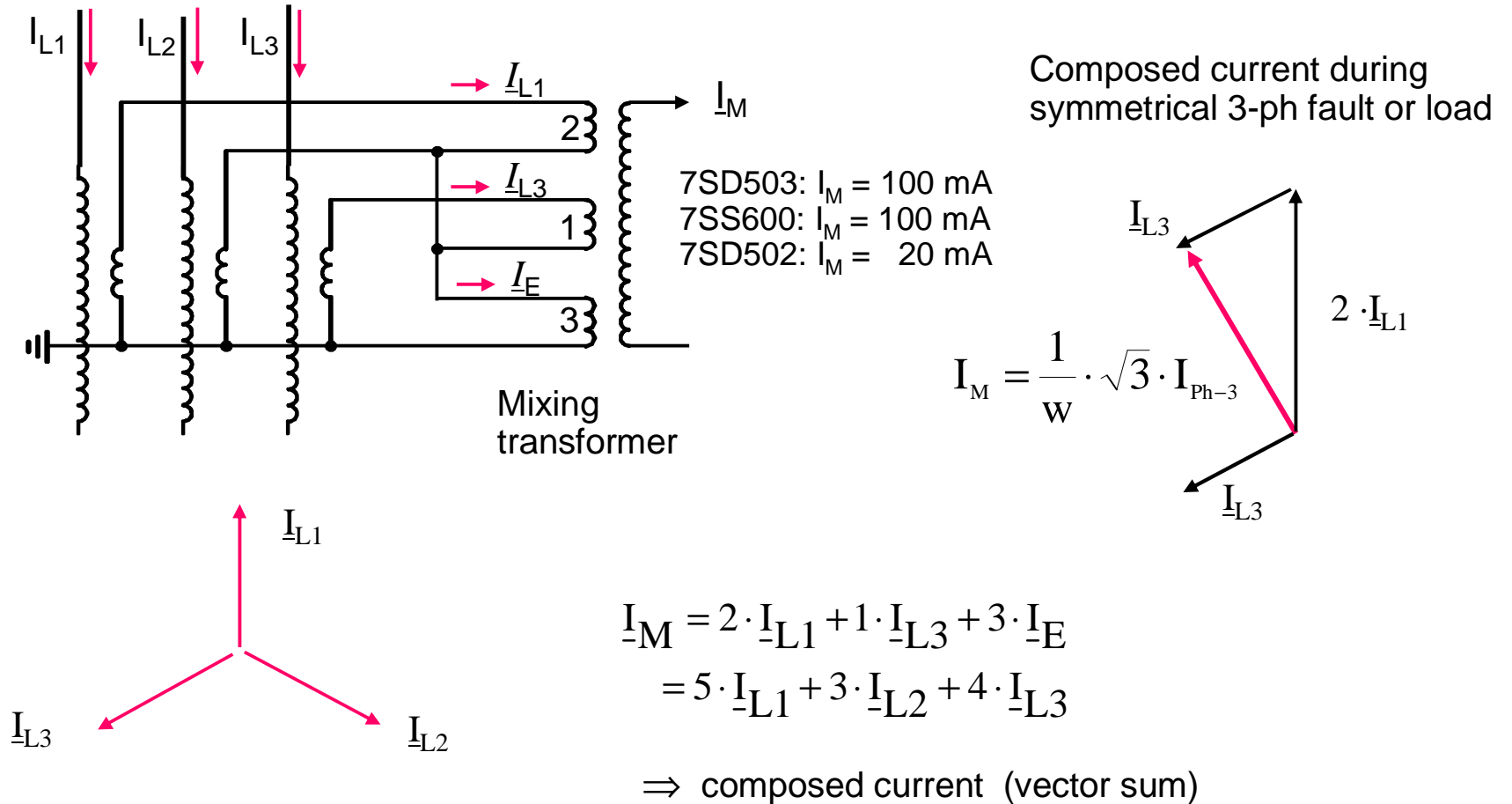
# Mixing transformer of composed current differential protection




# Mixing transformer:

Pickup sensitivity of standard connection ( $I_M = 2I_{L1} + I_{L3} + 3I_E$ )

Fault type	Composed current		Per unit composed current related to 3-phase symmetrical current
L1-E	$I_{ML1-E} = 5 I_{L1}$	$I_{L2} = I_{L3} = 0$	$I_{ML1-E} / I_M = 5 / \sqrt{3} = 2.9$
L2-E	$I_{ML2-E} = 3 I_{L2}$	$I_{L1} = I_{L3} = 0$	$I_{ML2-E} / I_M = 3 / \sqrt{3} = 1.73$
L3-E	$I_{ML3-E} = 4 I_{L3}$	$I_{L1} = I_{L2} = 0$	$I_{ML3-E} / I_M = 4 / \sqrt{3} = 2.3$
L1-L2	$I_{ML12} = 5 I_{L1} + 3 I_{L2}$	$I_{L3} = 0$	$I_{ML12} / I_M = 2 / \sqrt{3} = 1.15$
L2-L3	$I_{ML23} = 3 I_{L2} + 4 I_{L3}$	$I_{L1} = 0$	$I_{ML23} / I_M = 1 / \sqrt{3} = 0.58$
L1-L3	$I_{ML13} = 5 I_{L1} + 4 I_{L3}$	$I_{L2} = 0$	$I_{ML13} / I_M = 1 / \sqrt{3} = 0.58$
L1-L2-L3	$I_{ML123} = 5 I_{L1} + 3I_{L2} + 4I_{L3}$	$ I_{L1}  =  I_{L2}  =  I_{L3} $	$I_{ML123} / I_M = \sqrt{3} / \sqrt{3} = 1$

Highest sensitivity
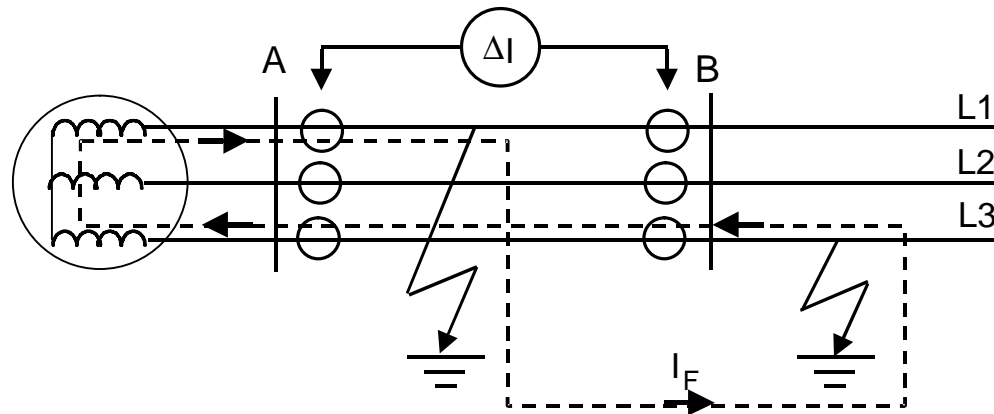
# Composed current differential protection Behaviour during cross country fault (isolated/compensated network)



**L1 internal und L3 external:**

$$I_{M-A} = 5 \cdot I_F - 4 \cdot I_F = 1 \cdot I_F \text{ und } I_{M-B} = + 4 \cdot I_F$$

$$\Delta I = |I_{M-A} + I_{M-B}| = 5 I_F \text{ und } \Sigma I = |I_{M-A}| + |I_{M-B}| = 5 \cdot I_F$$

$$\Delta I / \Sigma I = 5/5 = 1.0$$

Tripping

**L2 internal, L3 external**

$$I_{M-A} = - 1 \cdot I_F \text{ und } I_{M-B} = + 4 \cdot I_F$$


$$\Delta I = |I_{M-A} + I_{M-B}| = 3 \cdot I_F \text{ und } \Sigma I = |I_{M-A}| + |I_{M-B}| = 5 \cdot I_F$$

$$\Delta I / \Sigma I = 3/5 = 0.6$$

Tripping if k-setting < 0.6

# Composed current differential protection
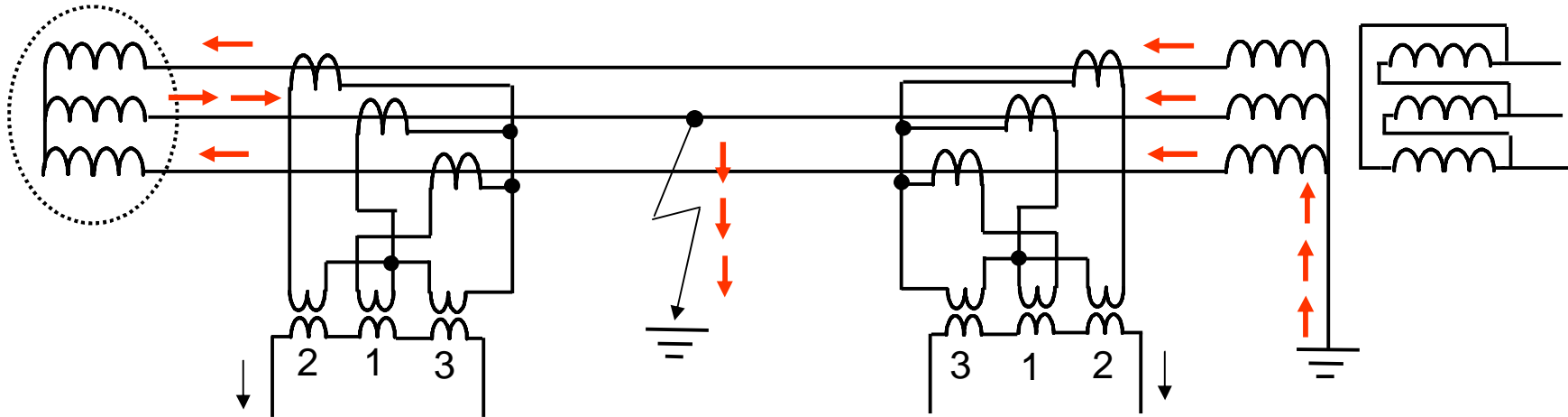
## Through current stabilisation with unsymmetrical earthing conditions



$$I_{M1} = 2 \cdot I_{L1} + 1 \cdot I_{L3} + 3 \cdot I_E$$

$$= 2 \cdot (-I_F) + 1 \cdot (-I_F) + 3 \cdot 0 = -3 \cdot I_F$$

$$I_{M2} = 2 \cdot I_{L1} + 1 \cdot I_{L3} + 3 \cdot I_E$$


$$= 2 \cdot I_F + 1 \cdot I_F + 3 \cdot 3I_F = +12 \cdot I_F$$

$$\left. \begin{aligned} I_{Op} &= |I_{M1} + I_{M2}| = 9 \cdot I_F \\ I_{Res} &= |I_{M1}| + |I_{M2}| = 15 \cdot I_F \end{aligned} \right\} k = 9/15 = 0.6$$

Faults in other phases:

$$\left. \begin{aligned} \text{Fault L1-E: } I_{Op} &= (3+12) \cdot I_F = 15 \cdot I_F \\ I_{Res} &= (3+12) \cdot I_F = 15 \cdot I_F \end{aligned} \right\} k=1$$

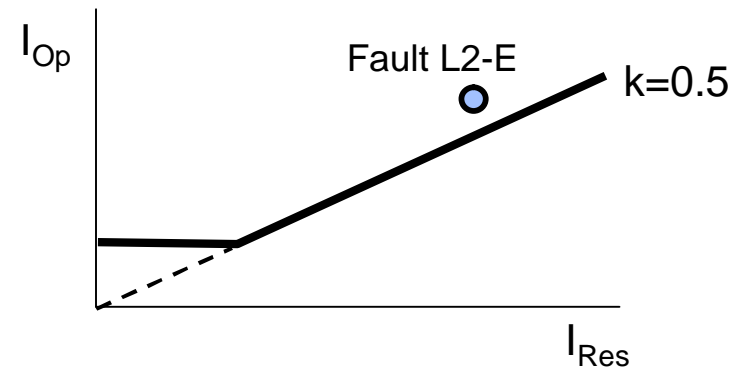
$$\left. \begin{aligned} \text{Fault L3-E: } I_{Op} &= (0+12) \cdot I_F = 12 \cdot I_F \\ I_{Res} &= (0+12) \cdot I_F = 12 \cdot I_F \end{aligned} \right\} k=1$$



# High impedance differential protection: Principle

## Behaviour during external fault

with ideal current transformers

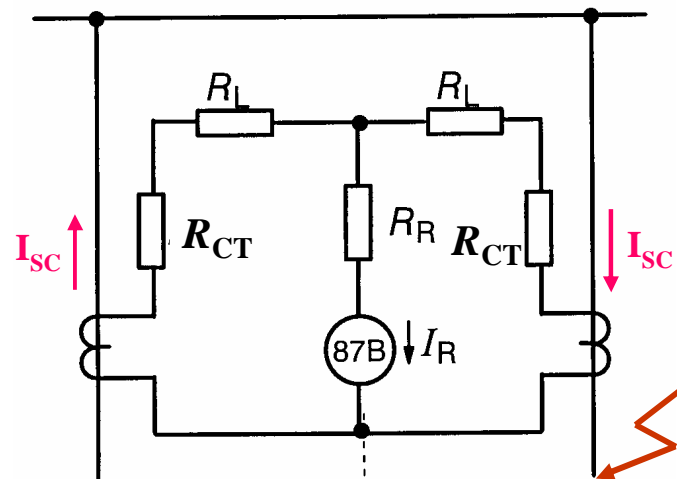


$$E_{CT-1} = (R_L + R_{CT}) \cdot i_{sc}$$

$$U_R = 0$$

$$E_{CT-2} = (R_L + R_{CT}) \cdot i_{sc}$$

with CT saturation

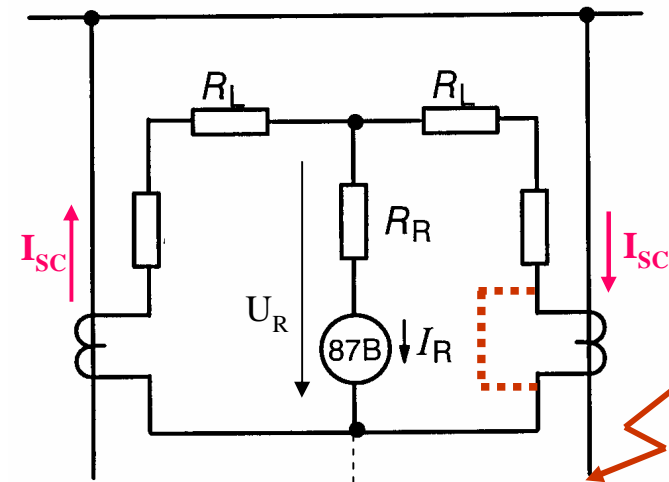

$$E_{CT-1} = 2 \cdot (R_L + R_{CT}) \cdot i_{sc}$$

$$U_R = (R_L + R_{CT}) \cdot i_{sc}$$

## High impedance differential protection: Calculation example (busbar protection)

---

Given:  $n = 8$  feeders  
 $r_{CT} = 600/1$  A  
 $U_{KN} = 500$  V  
 $R_{CT} = 4$  Ohm  
 $I_{mR} = 30$  mA (at relay pick-up value)

$R_L = 3$  Ohm (max.)  
 $I_{R-pick-up} = 20$  mA (fixed value)  
 $R_R = 10$  kOhm  
 $I_{var} = 50$  mA (at relay pick-up value)

Pick-up sensitivity:

$$I_{F-min} = r_{CT} \cdot (I_{R-pick-up} + I_{Var} + n \cdot I_{mR})$$

$$I_{F-min} = \frac{600}{1} \cdot (0.02 + 0.05 + 8 \cdot 0.03)$$

$$I_{F-min} = 186 \text{ A} \cdot (31\%)$$

Stability:

$$I_{F-through-max} < r_{CT} \cdot \frac{R_R}{R_L + R_{SW}} \cdot I_{R-pick-up}$$

$$I_{F-through-max} < \frac{600}{1} \cdot \frac{10,000}{3+4} \cdot 0.02$$

$$I_{F-through-max} < 17 \text{ kA} = 28 \cdot I_n$$



# Digital Differential Protection


## Measuring Technique

Gerhard Ziegler

**SIEMENS**

# Merz and Price differential protection


Patent dated 1904

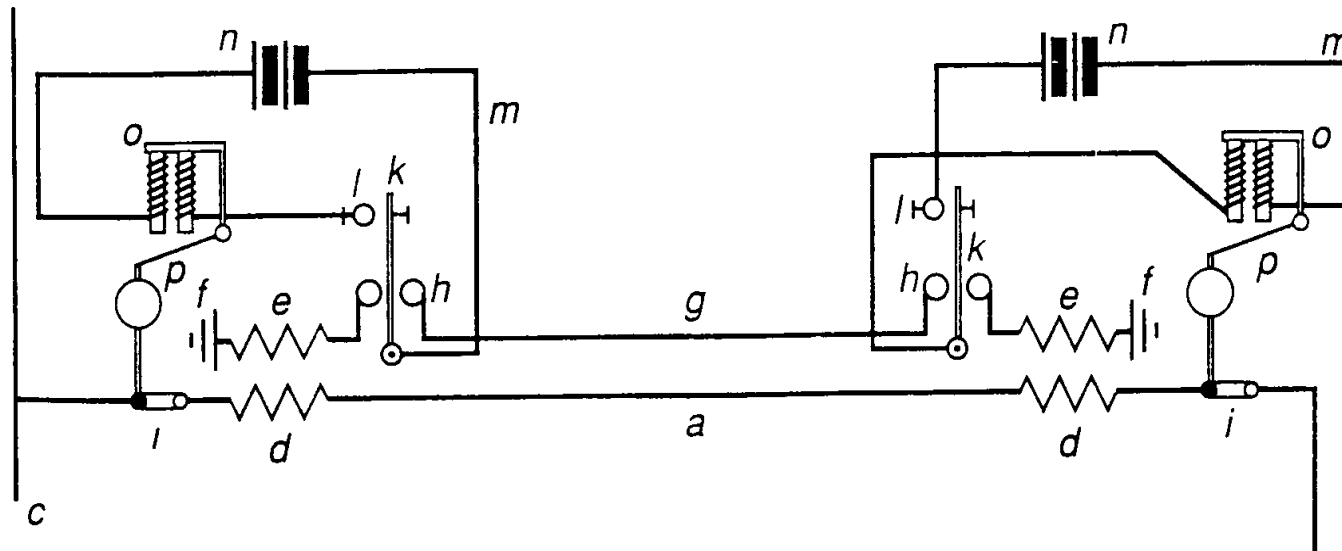

a: feeder, b: generator, c: substation, d: primary winding of CT, e: secondary winding of CT, f: earth or return conductor, g: pilot wire, h: relay windings, i: circuit breakers, k,l: movable and fixed relay contacts, m: circuit, n: battery, o: electromagnetic device with armature p.



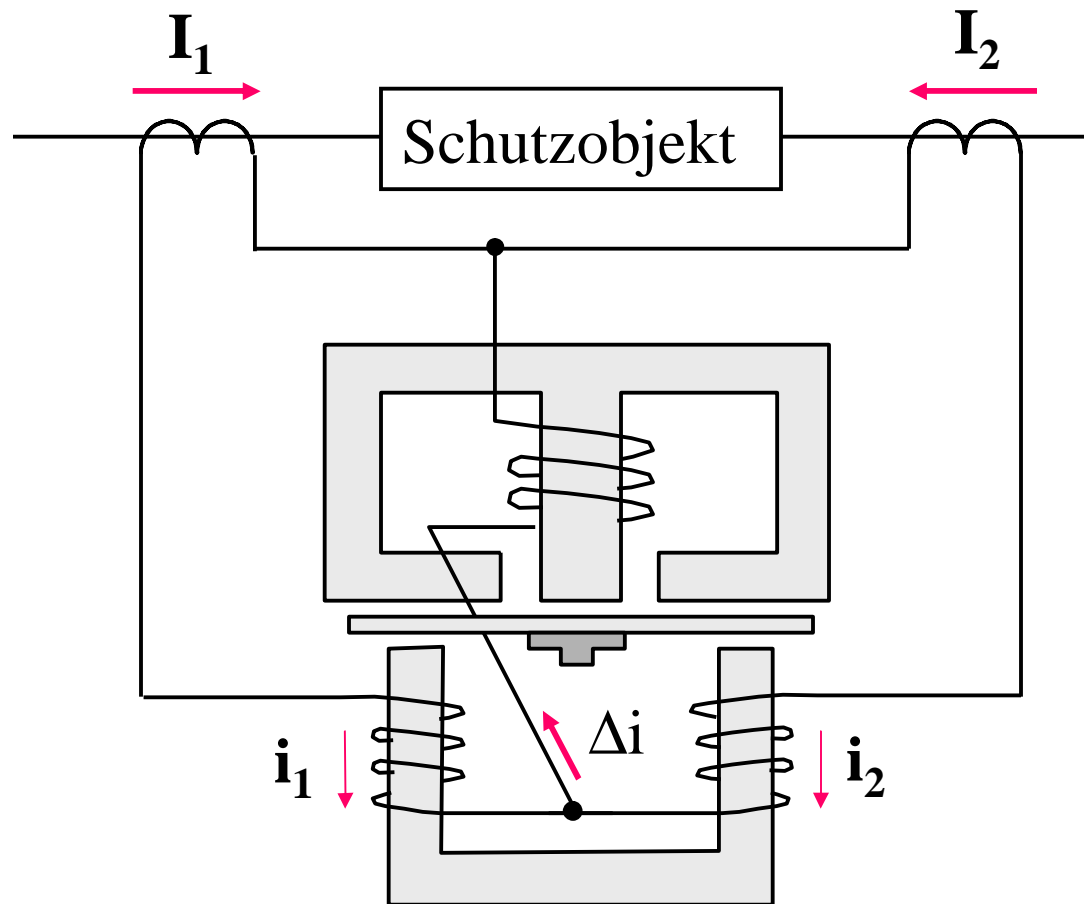
# Electro-mechanical differential protection based on induction relay




# Electro-mechanical differential protection
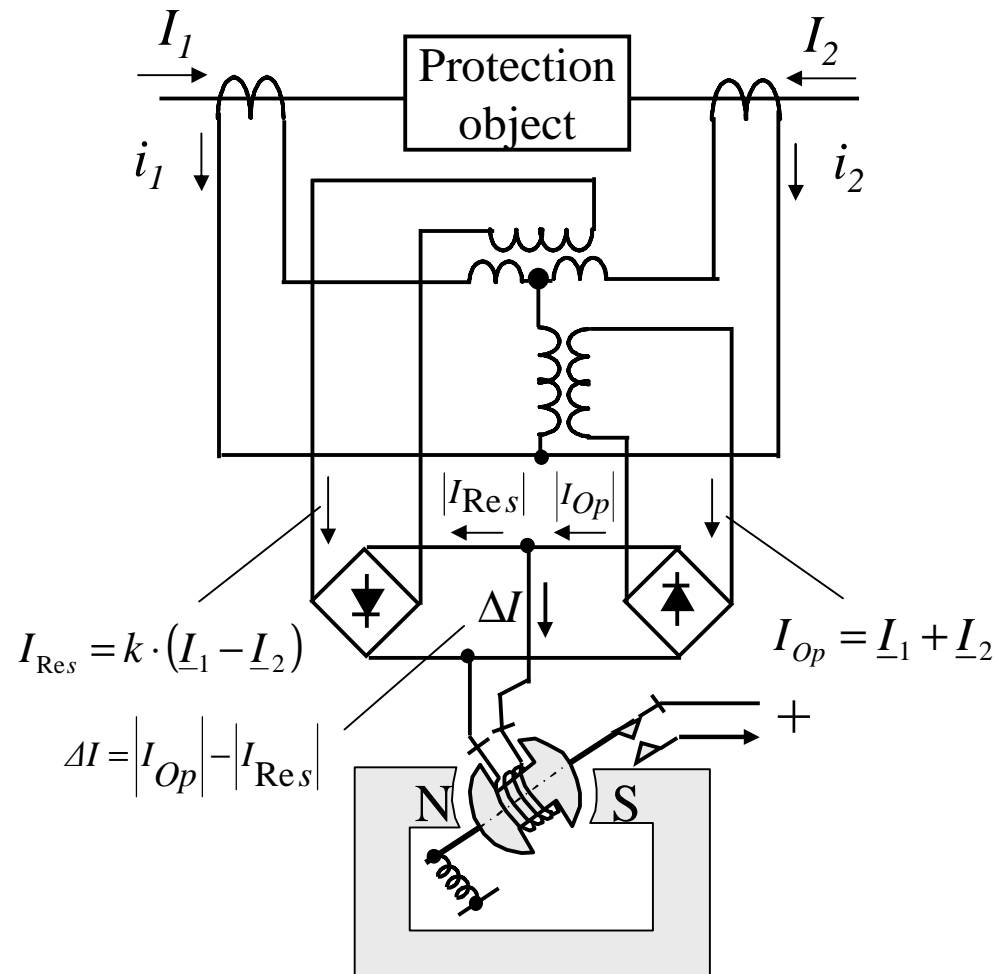
## Rectifier bridge comparator with moving coil relay




# Differential protection

## Analog static measuring circuit

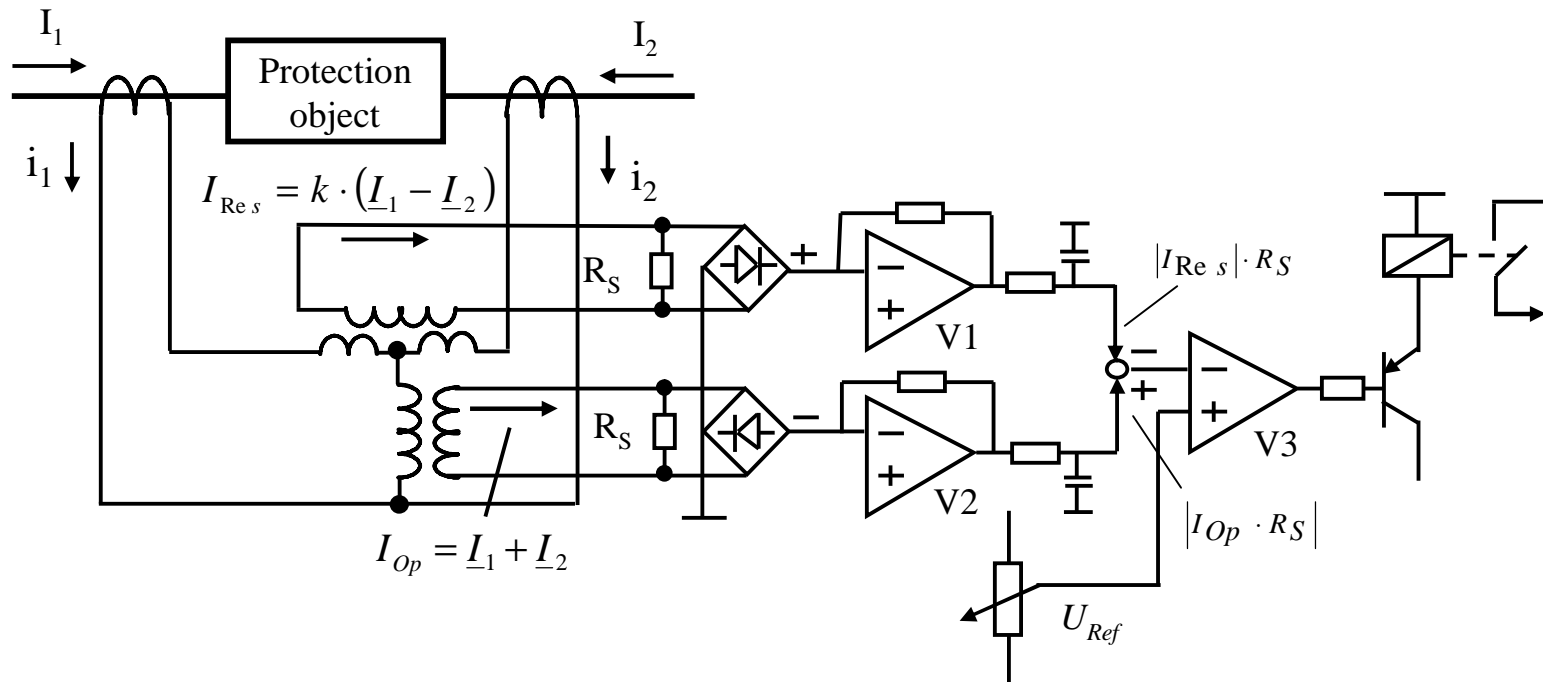


# Digital differential protection
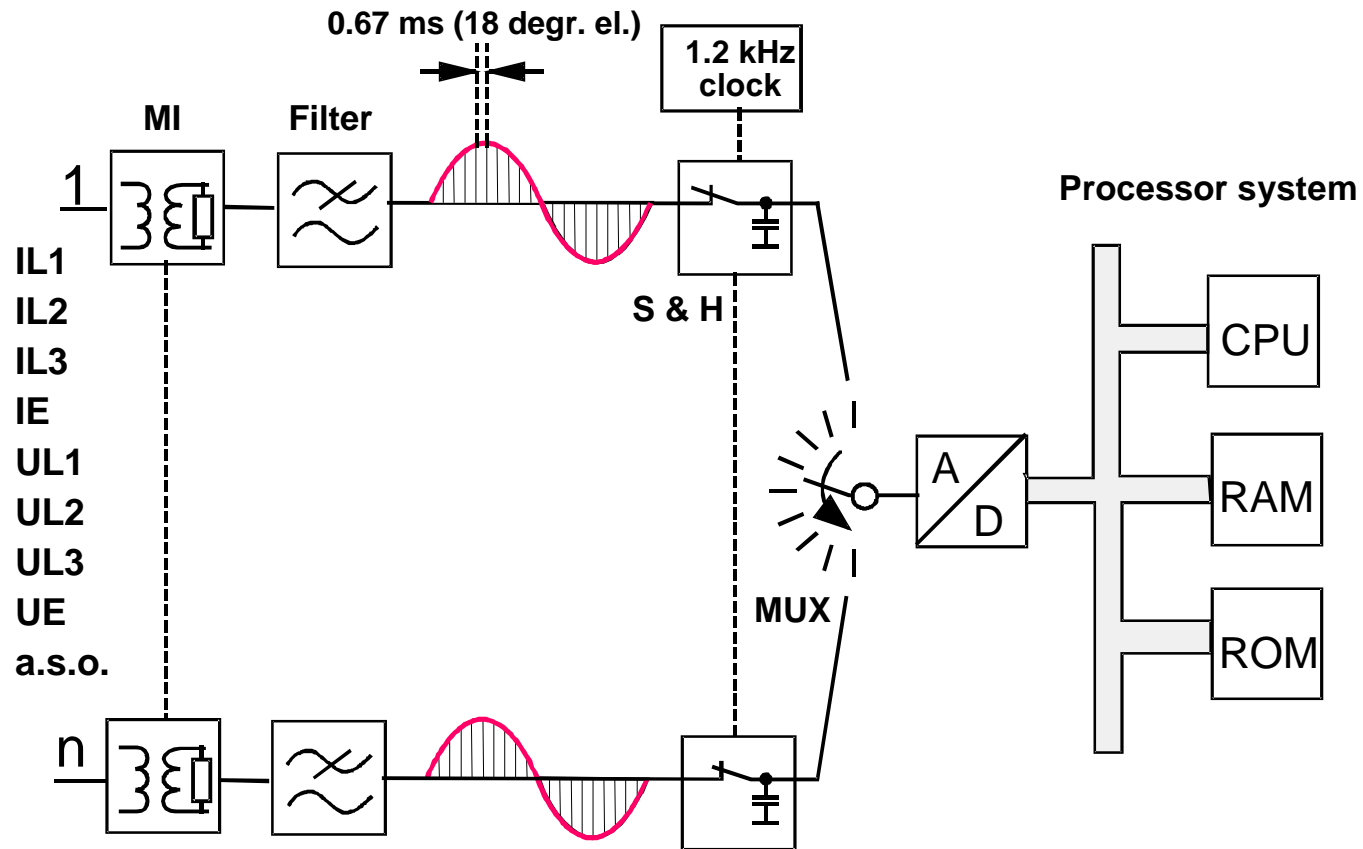
## Measuring value acquisition and processing


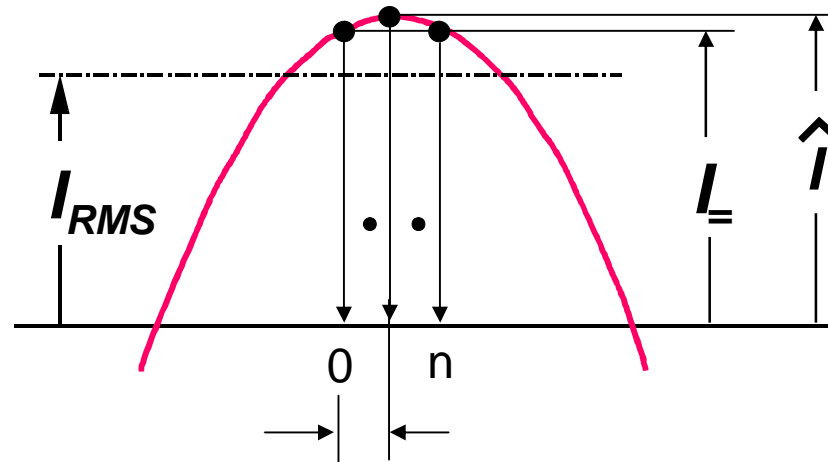
# Digital protection: Measurement based on momentary values



$\Delta T_{\text{samp.}}$  corresponds to  $\Delta\varphi$  ( 60Hz: 0.67 ms = 18° el.)


$$\hat{I} = \frac{I_{=}}{\cos\left(\frac{n-1}{2} \cdot \Delta j\right)}$$

when n sampled values exceed the pick-up limit  $I_{=}$

$$I_{RMS} = \frac{\hat{I}}{\sqrt{2}}$$


$$\Delta j = w \cdot \Delta T_{\text{samp.}} = \frac{f_N}{f_A} \cdot 360^\circ$$
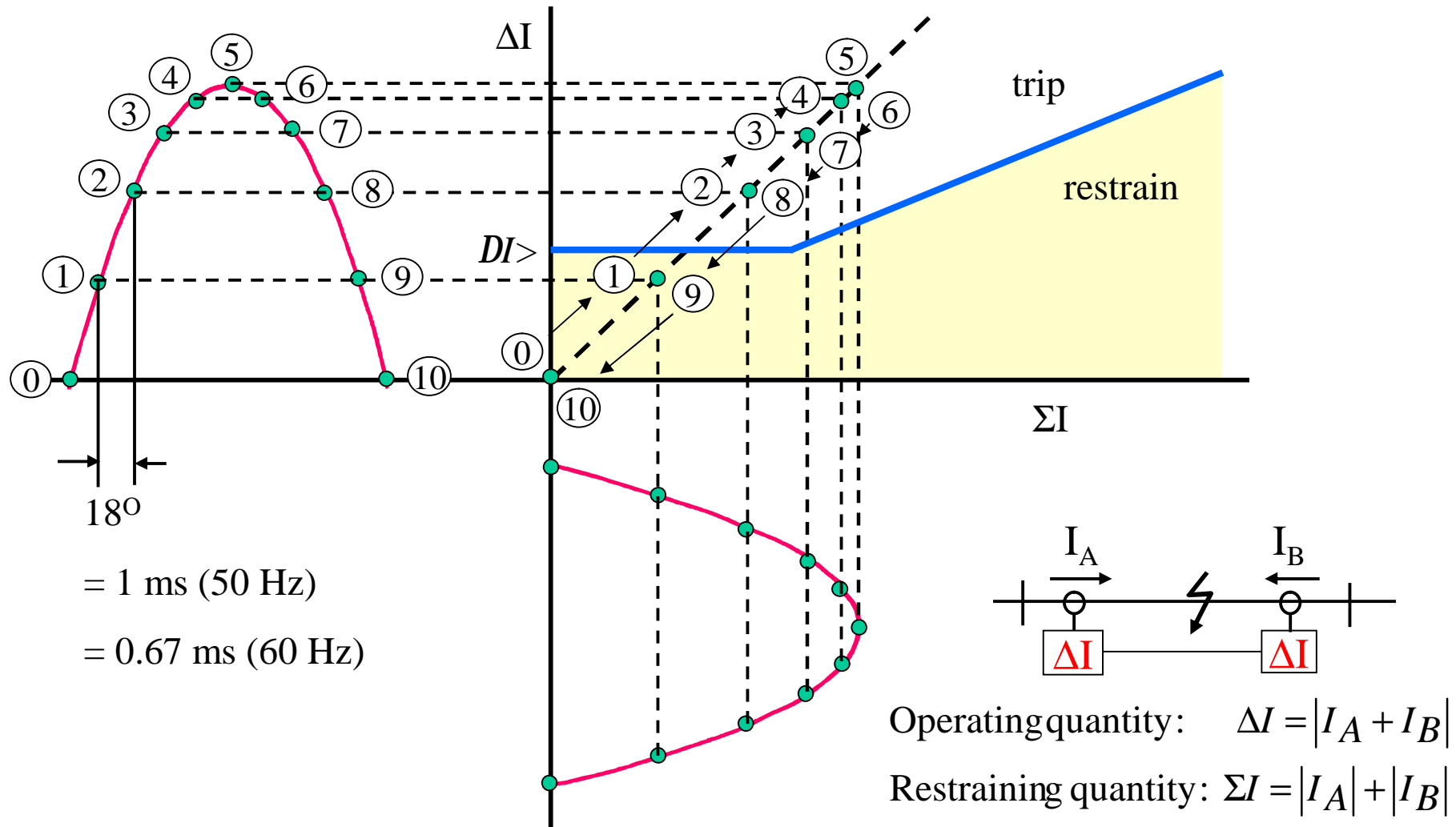
# Digital differential protection: Measurement based on momentary values



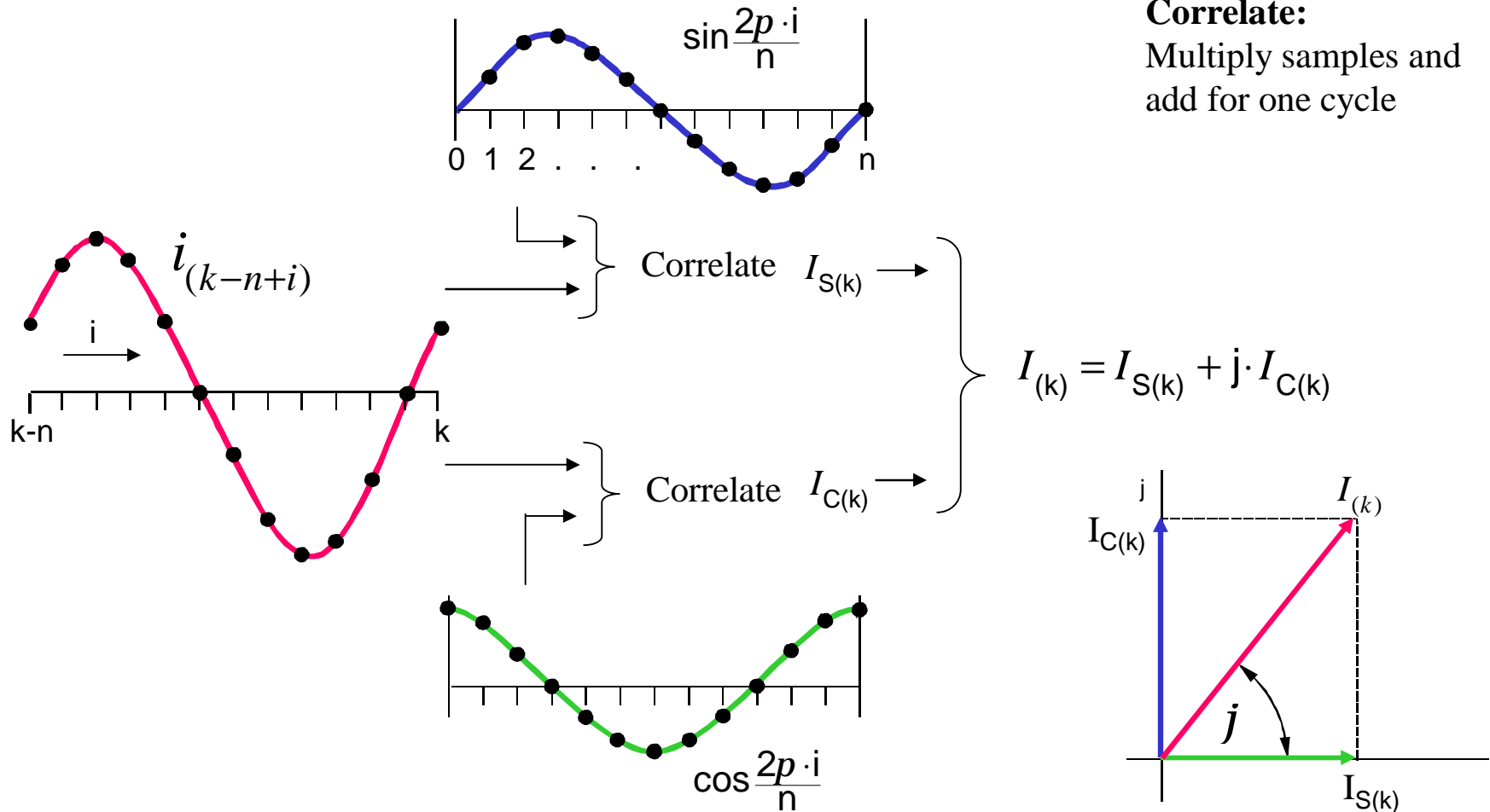
# Discrete Fourier-Transformation (Principle)

**Correlate:**  
Multiply samples and add for one cycle


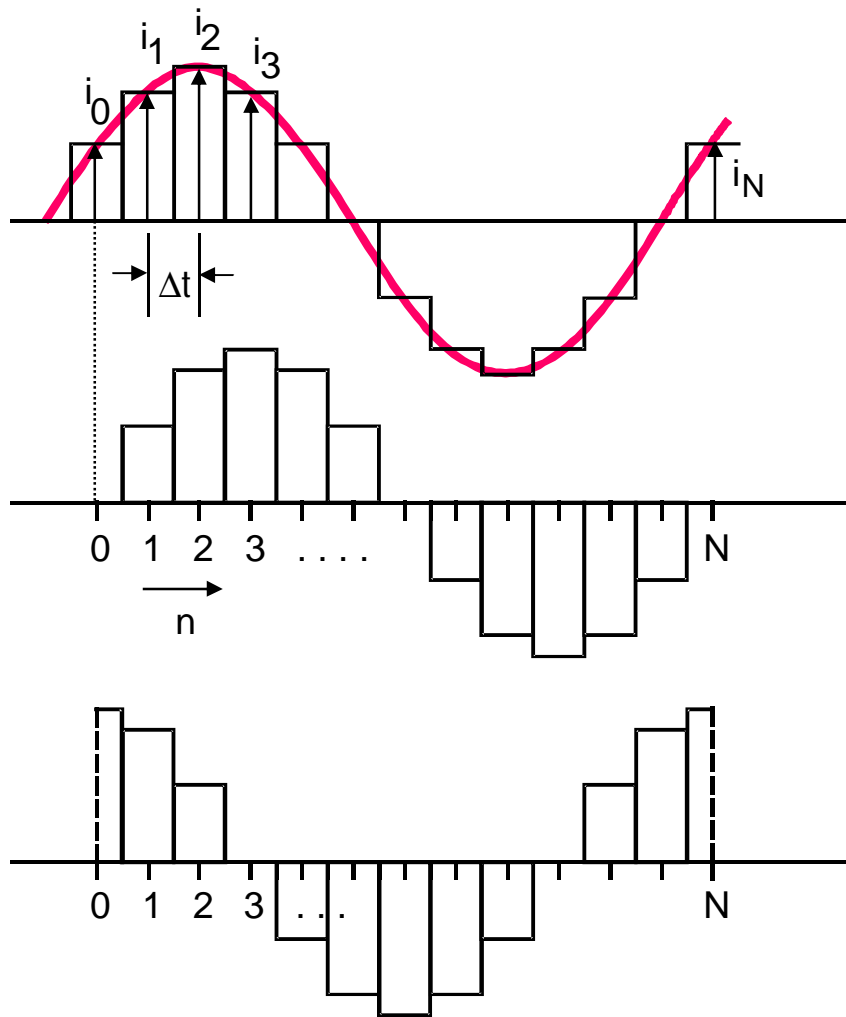
# Discrete Fourier-Transformation (calculation formulae)




$$I_s = \frac{2}{N} \left[ \sum_{n=1}^{N-1} \sin(\omega \cdot n \cdot \Delta t) i_n \right]$$

$$I_c = \frac{2}{N} \left[ \frac{i_0}{2} + \frac{i_N}{2} + \sum_{n=1}^{N-1} \cos(\omega \cdot n \cdot \Delta t) i_n \right]$$



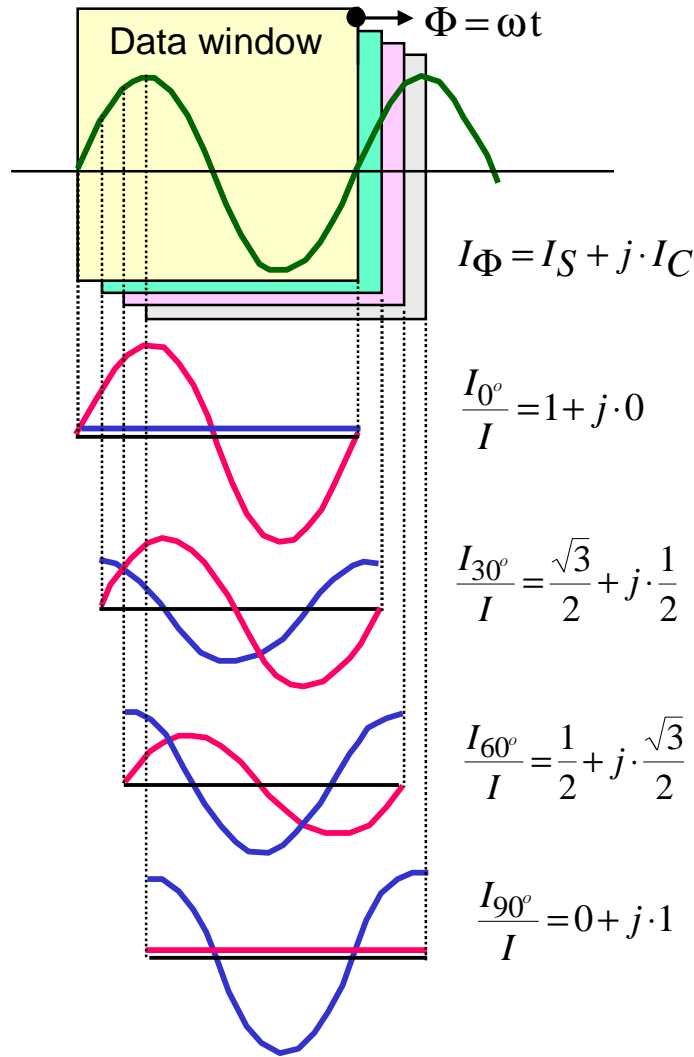
# Orthogonal components of a current phasor dependent on the position of the data window




$$I_S = \frac{1}{2p} \cdot \int_{\Phi-360^\circ}^{\Phi} I(\omega \cdot t) \cdot \sin \omega t \cdot dt$$
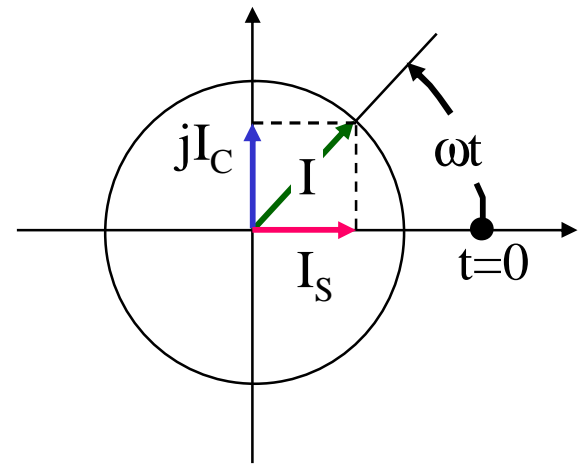
$$I_C = \frac{1}{2p} \cdot \int_{\Phi-360^\circ}^{\Phi} I(\omega \cdot t) \cdot \cos \omega t \cdot dt$$



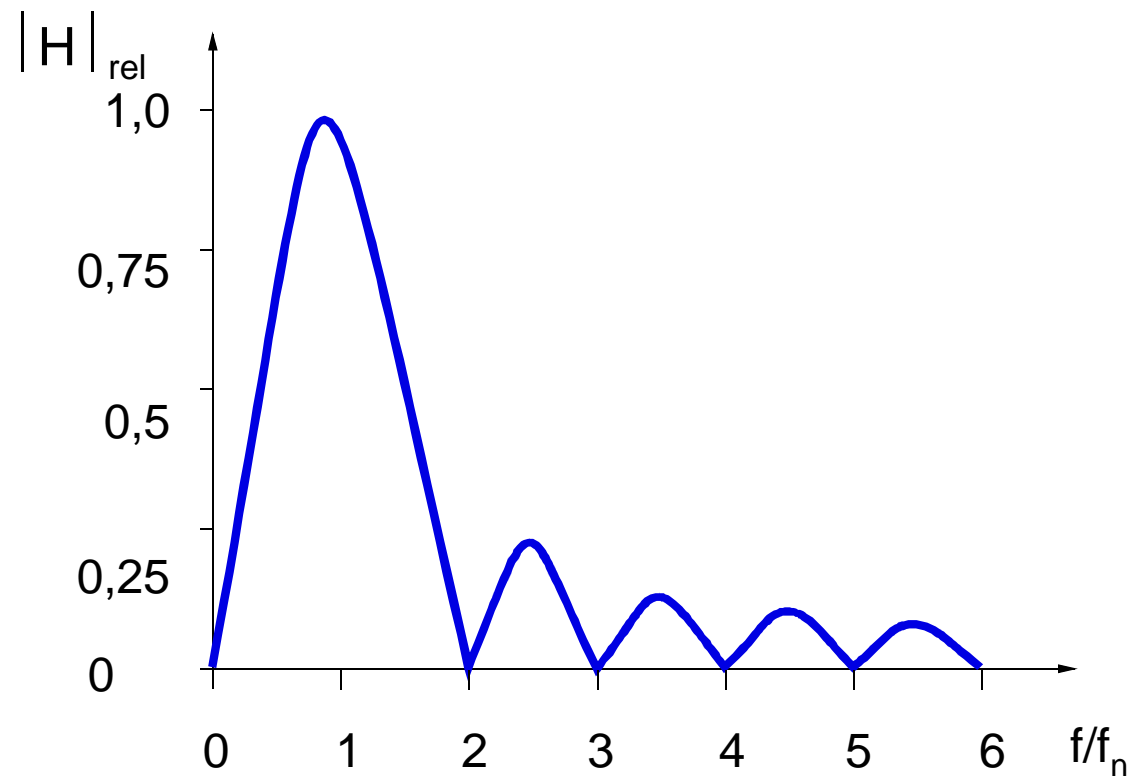
## Transfer function of a one cycle Fourier-filter



# Digital protection

## Fast current phasor estimation

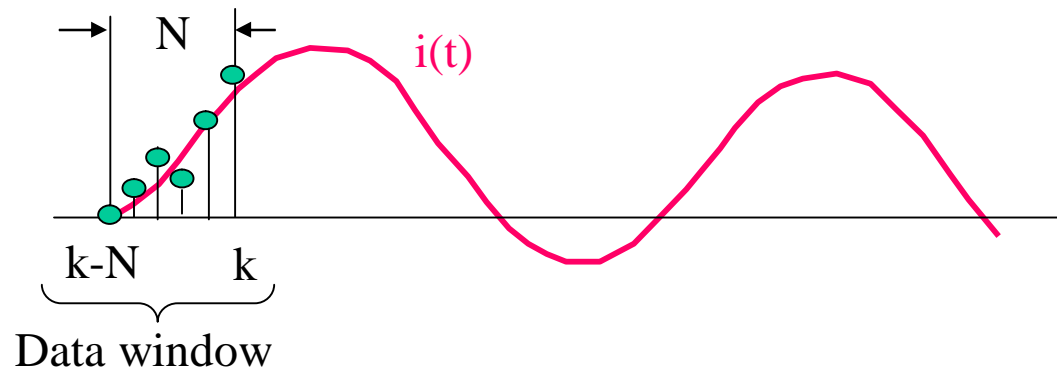

$$i(t) = A \cdot \sin(\omega t) + B \cdot \left( \cos(\omega t) - e^{-\frac{t}{\tau}} \right) + C \cdot \cos(\omega t)$$

**Task:** Estimation of the coefficients A, B, C on basis of measured currents and voltages



**Method:** Gauß's *Minimization of error squares*:

- Delta = quality value
- k = sampling number
- N = length of data window
- n = variable
- $\Delta T$  = sampling interval

$$Delta = \sum_{n=k-N}^k \left( i_{(n \cdot \Delta T)} - f_{(n)} \right)^2 \quad \rightarrow \quad \text{MIN}$$

← sampled values
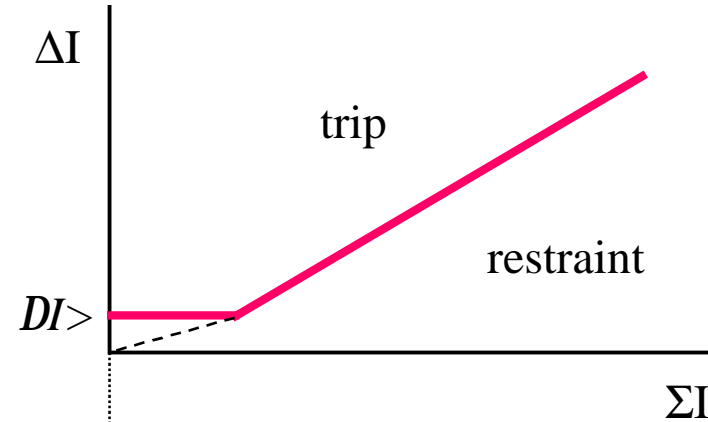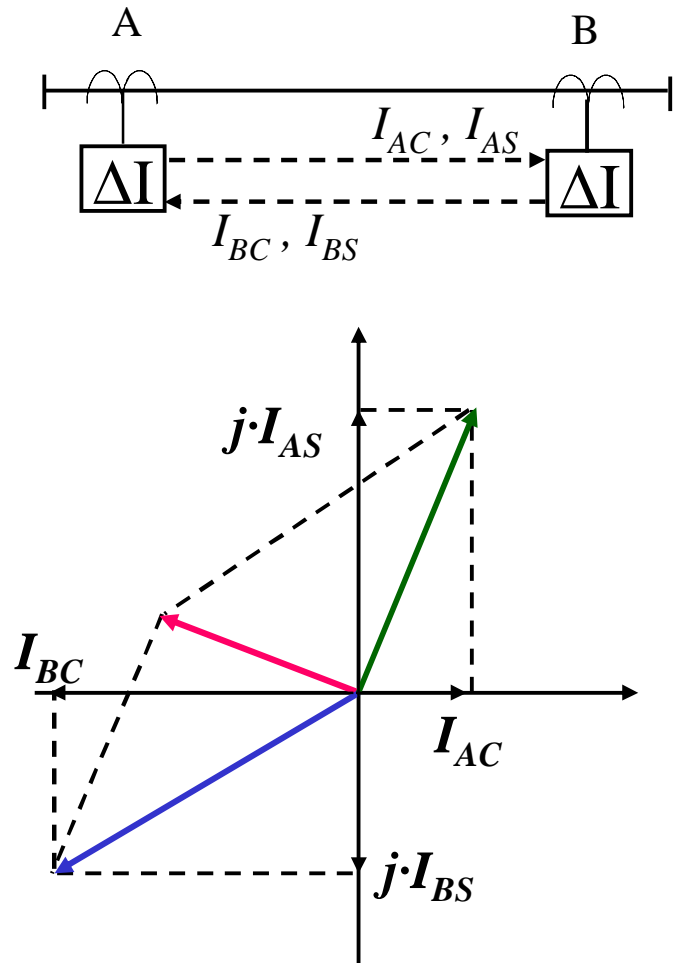
# Differential protection with phasors (principle)





Operating quantity :  $\Delta I = |I_A + I_B|$

Restraining quantity :  $\Sigma I = |I_A| + |I_B|$

# Digital line differential protection
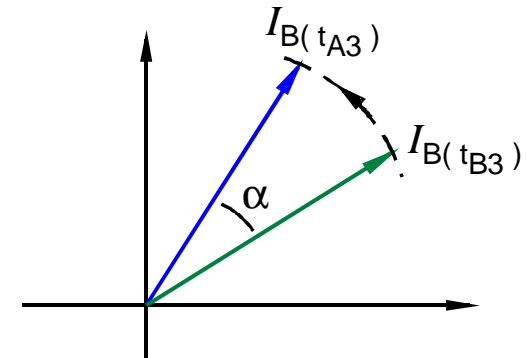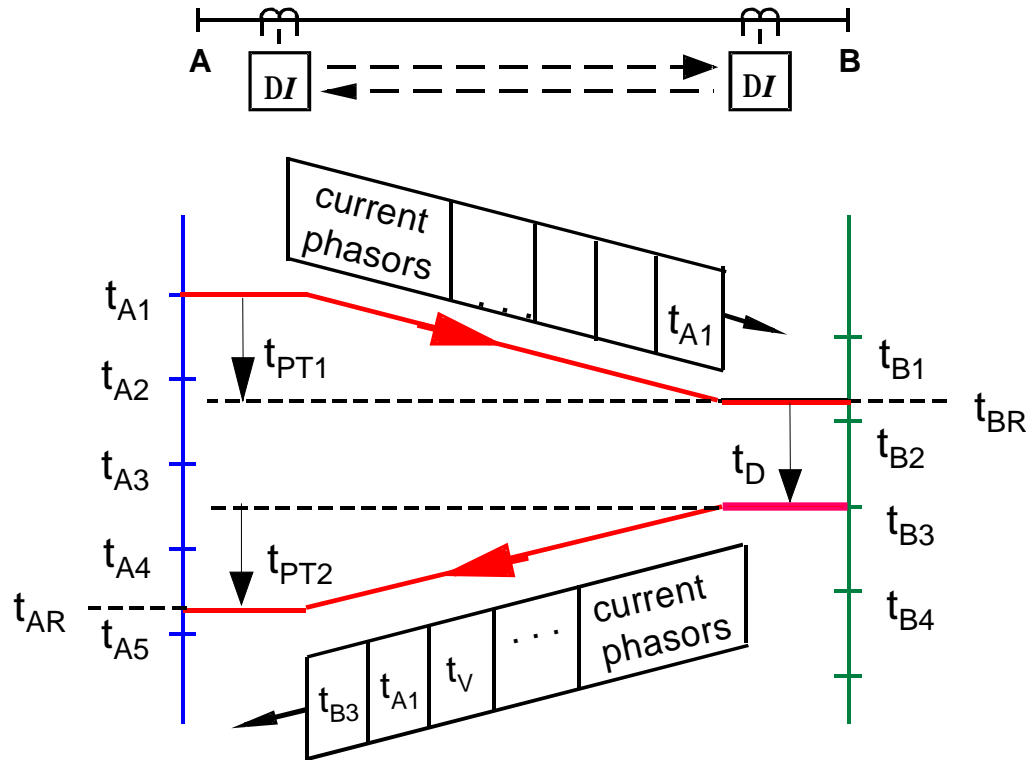
## Synchronisation of phasors (ping-pong time alignment)




$$\alpha = \frac{t_{B3} - t_{A3}}{T_P} \cdot 360^\circ$$

Signal transmission time:  $t_{PT1} = t_{PT2} = \frac{1}{2} (t_{A1} - t_{AR} - t_D)$

Sampling instant:  $t_{B3} = t_{A3} - t_{PT2}$
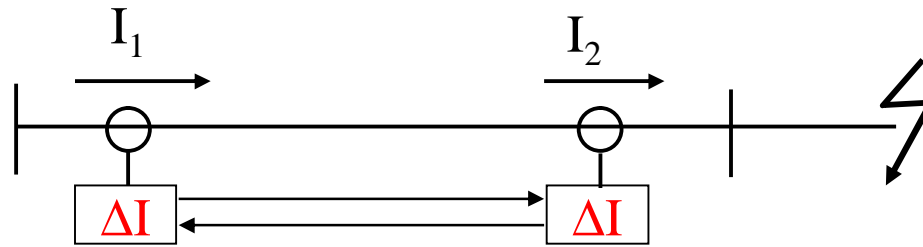
# Split path data transmission Impact of unsymmetrical propagation time




$$\Delta I = I \cdot \sin \frac{\alpha}{2} = I \cdot \sin \frac{\Delta T[\text{ms}] \cdot \frac{180^\circ}{10\text{ms}}}{2}$$

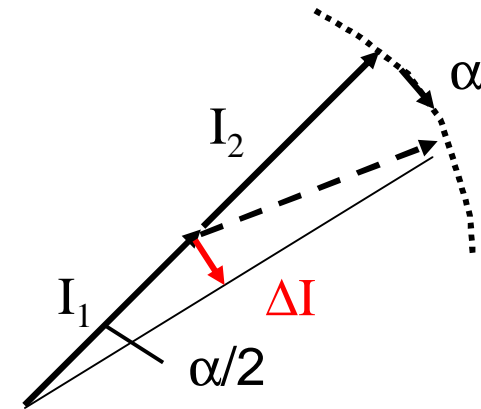Example:

Transmit channel time 3 ms  
 Receive channel time 4.2 ms  
 → time difference  $\Delta = 1.2 \text{ ms}$

$$\Delta I = I \cdot \sin \frac{1.2\text{ms} \cdot \frac{180^\circ}{10\text{ms}}}{2} = I \cdot 0.19 \quad \Delta I = 19\%$$




To keep the false differential current below about 2 to 5%, the propagation time difference should not exceed about 0.1 to 0.25 ms!

Otherwise:

- more insensitive relay setting
- or GPS synchronisation
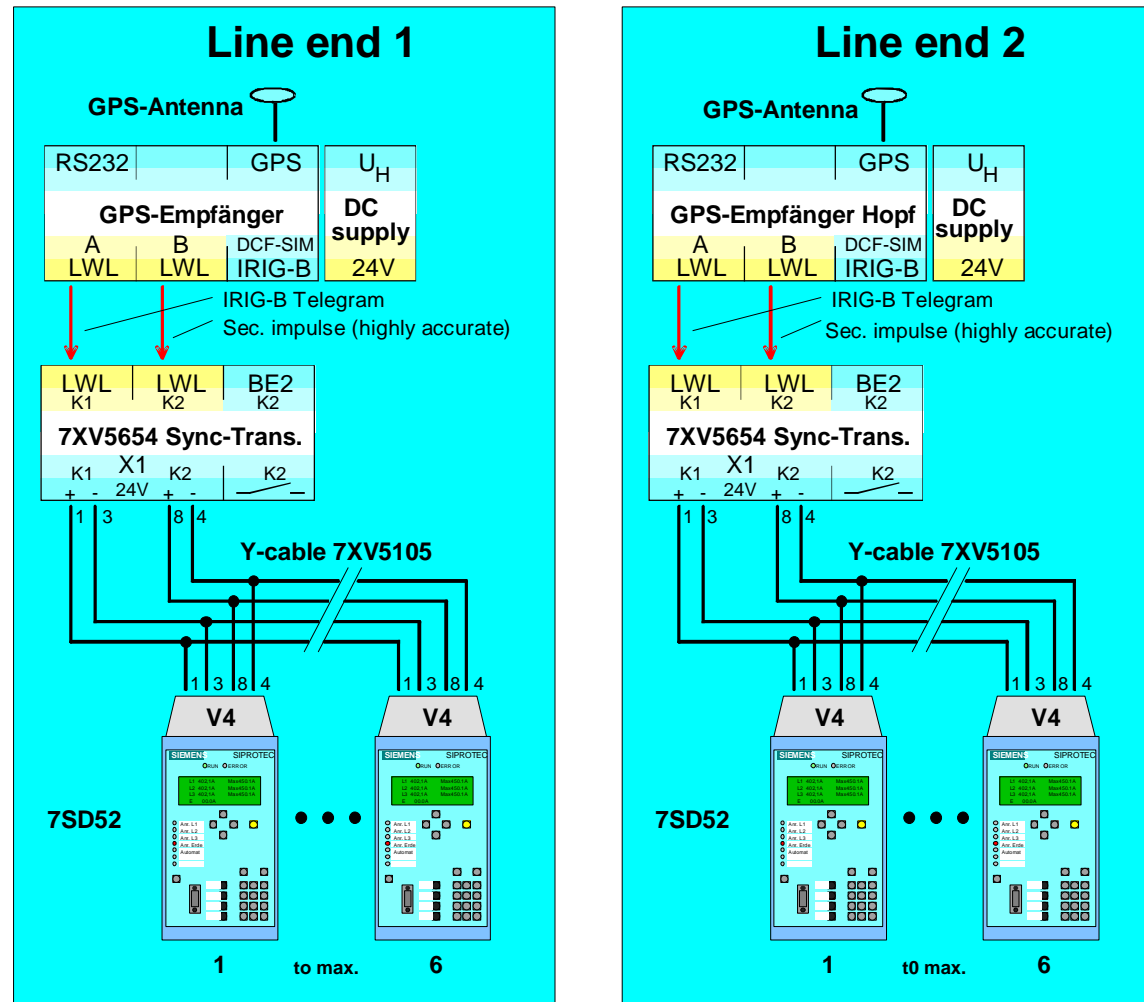
# Synchronisation of Differential relays via GPS




## Devices for GPS time synchronisation

- n GPS receiver with 2 optical outputs (7XV5664-0AA00).  
Output for IRIB-B telegram and output for second/minute pulse
- n Galvanic separation between the receiver and the transceiver 7XV5654
- n Optic/electric signal conversion in the transceiver
- n Distribution of the electrical signals via Y-bus cable to port A of the relays (telegram)
- n Electronic contact for the minute pulse in case of synchronisation through binary input with battery voltage



GPS receiver  
7XV5664

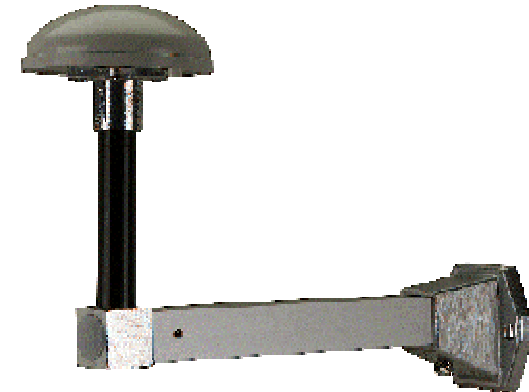

Outdoor antenna  
FG4490G10 for GPS




Transceiver  
7XV5654




## Additional components for SICAM SAS GPS-System

---

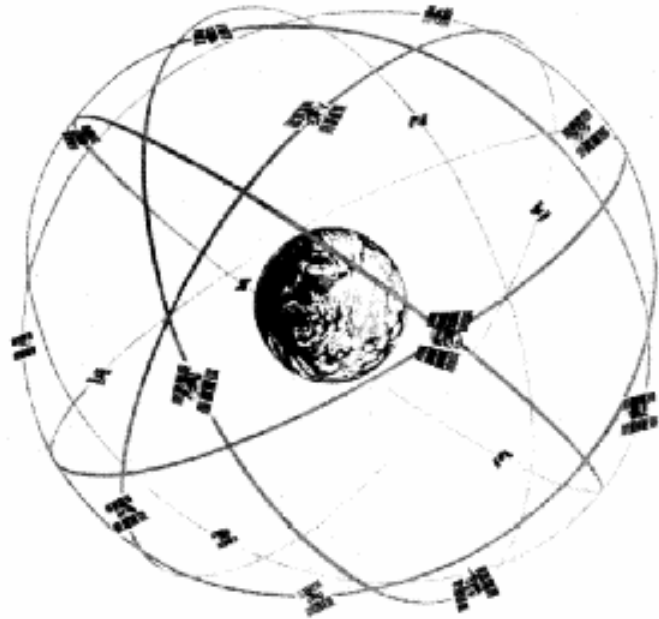



- 24 satellites move in a height of 20 000km on 6 different paths
- Transmission frequency 1,57542GHz
- For a continuous time reception min. 4 satellites is necessary
- High accuracy : 1 usec
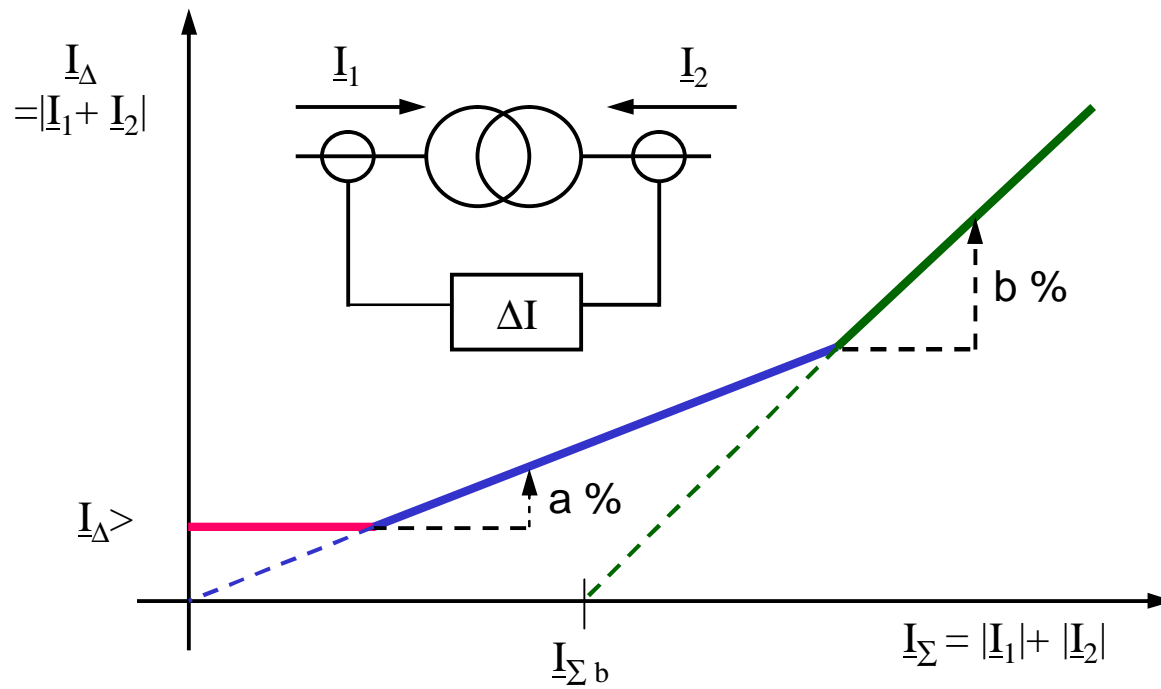
# Operating characteristic of digital differential relays



# Differential protection

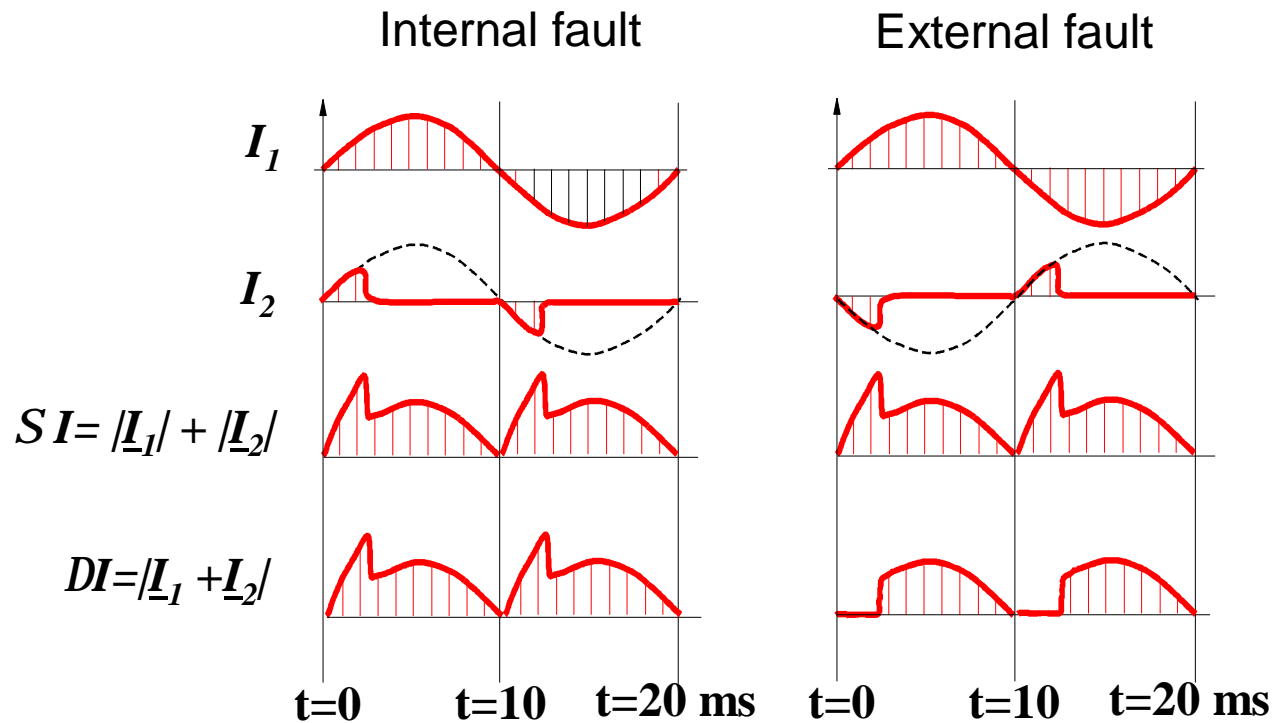
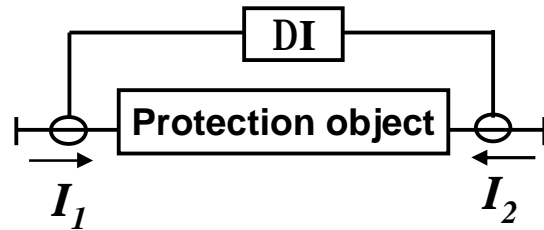
## CT saturation with internal and external faults




# Saturation detector:

Locus of  $\Delta I/\Sigma I$  for external faults without and with CT saturation

$$i_{Op(n)} = |i_{1(n)} + i_{2(n)}|$$

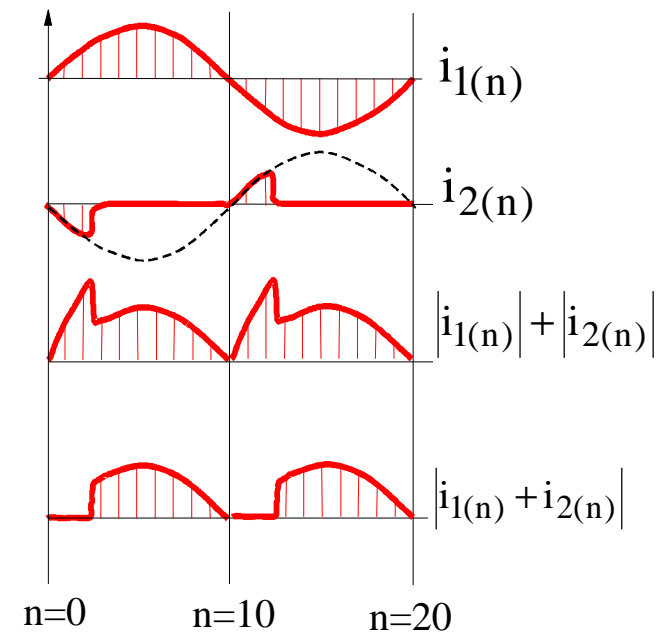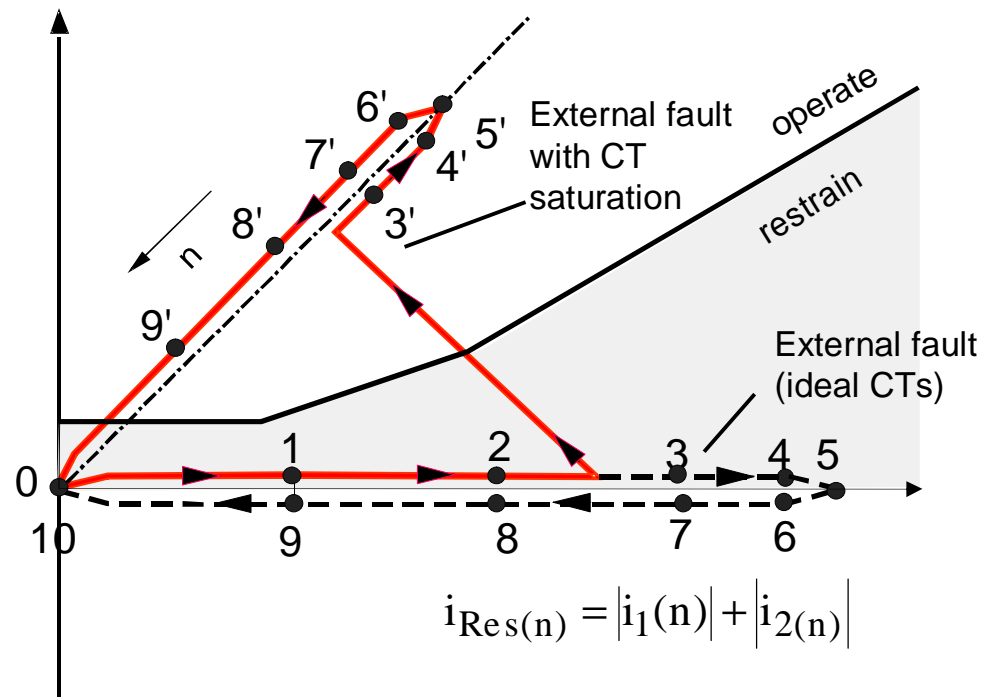
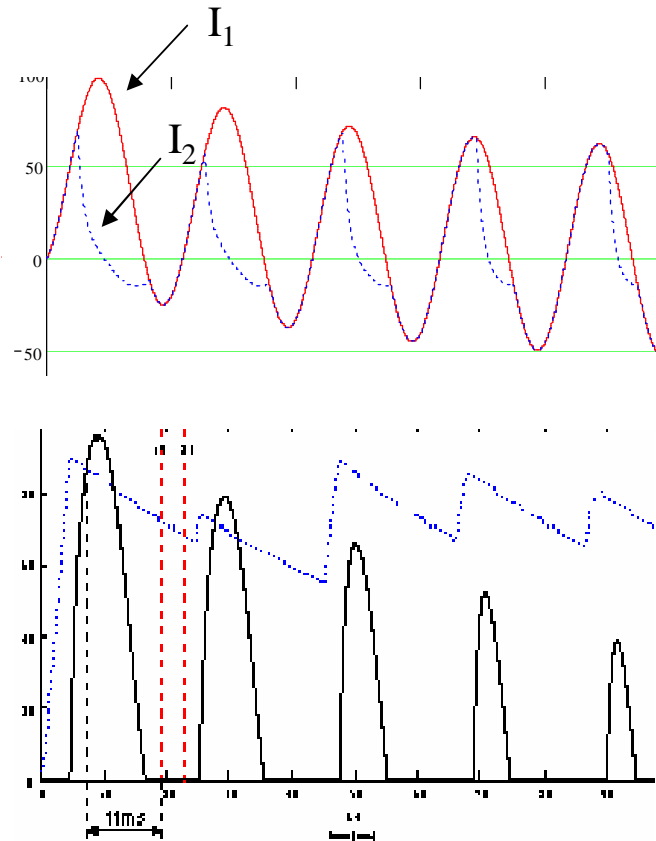
# Differential current caused by transient CT saturation (ext. fault) with operating and restraint current of busbar protection 7SS5




$$I_{Res.} = |I_1| + |I_2|$$


$$I_{Op} = |I_1 + I_2|$$

Differential current appears only every second half wave!


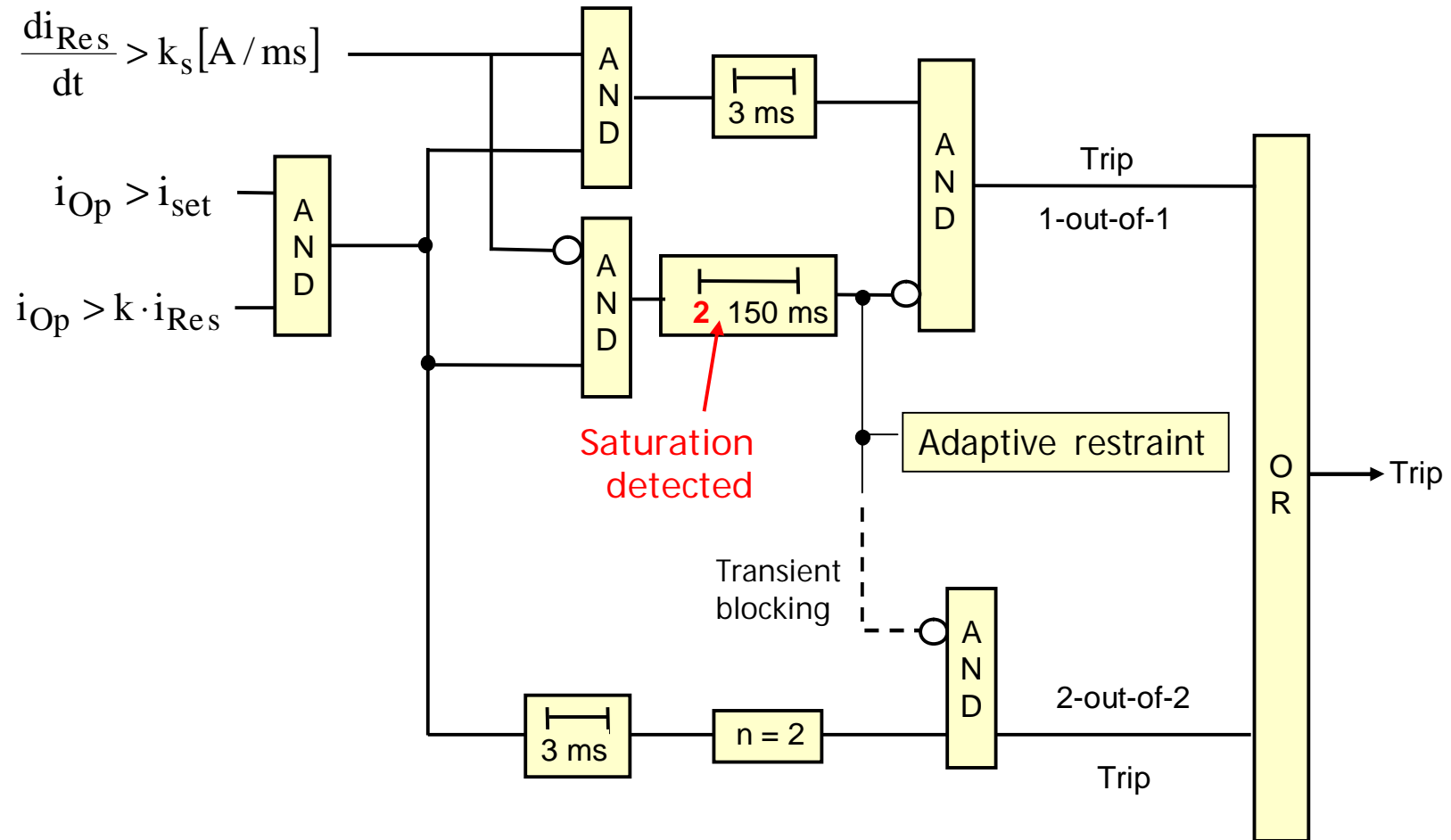
# Tripping logic of digital busbar protection 7SS600/7SS5 with saturation detector (simplified)


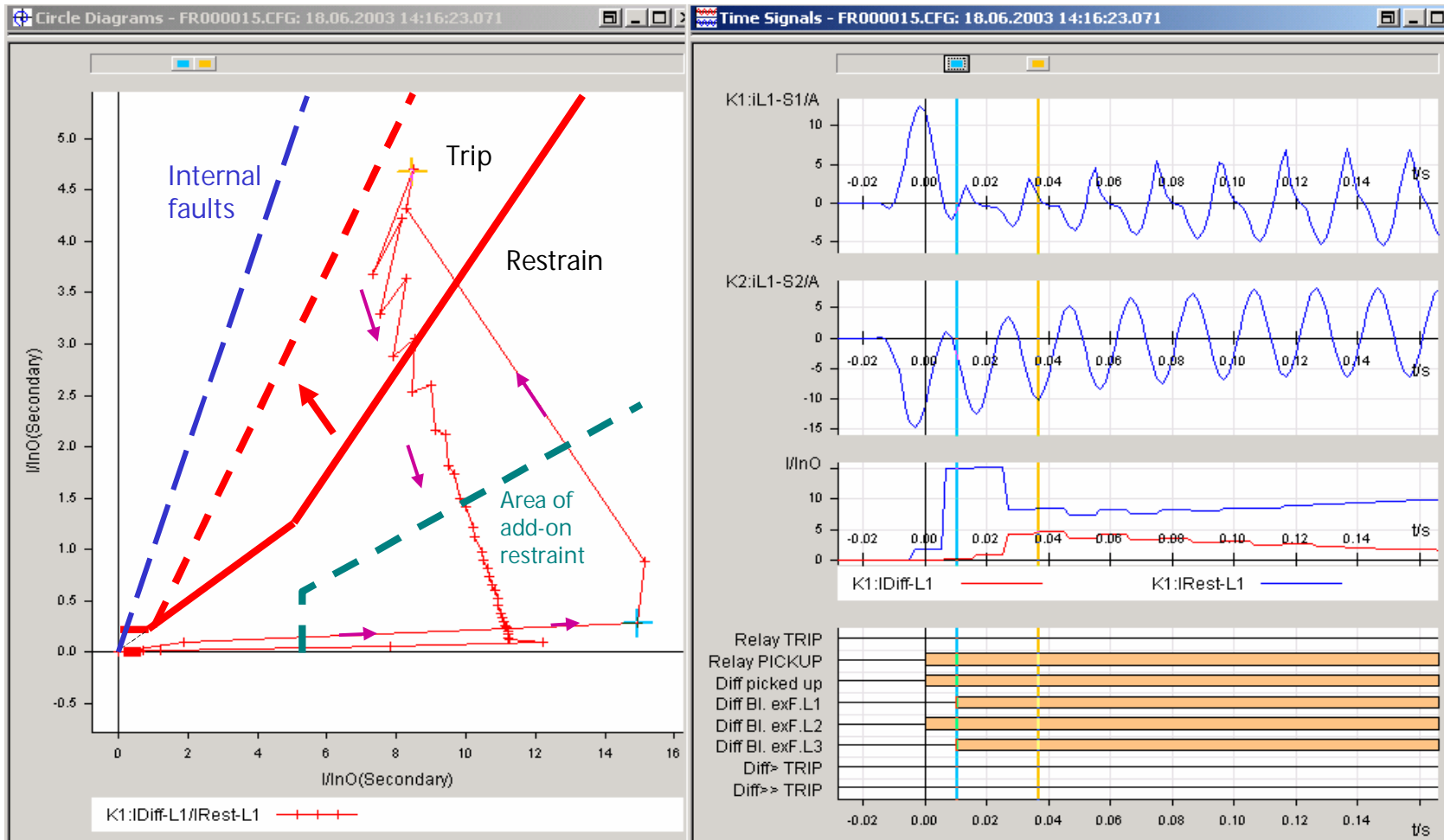
# Transformer differential protection 7UT6: Saturation detection and automatic increase stabilisation


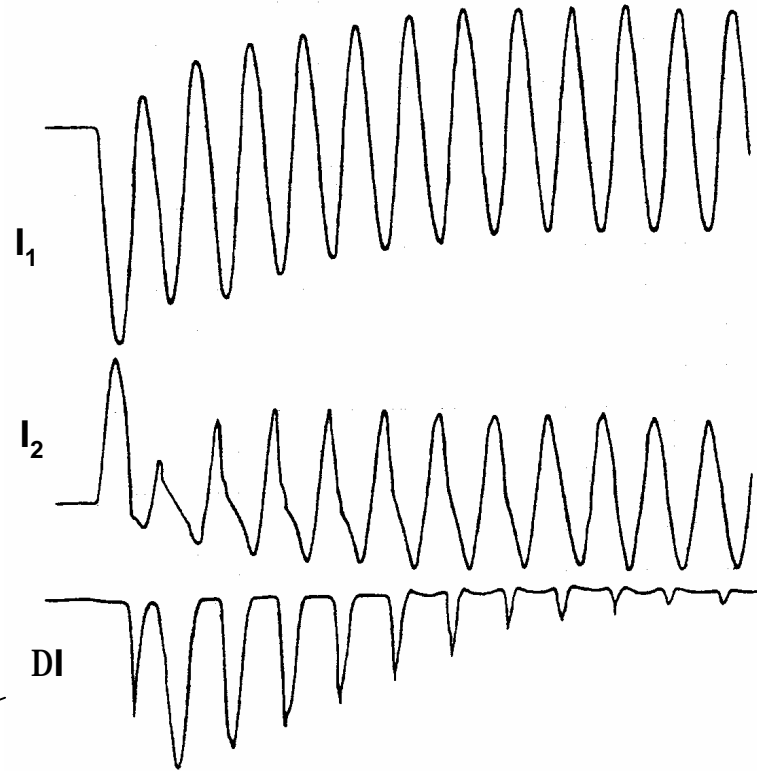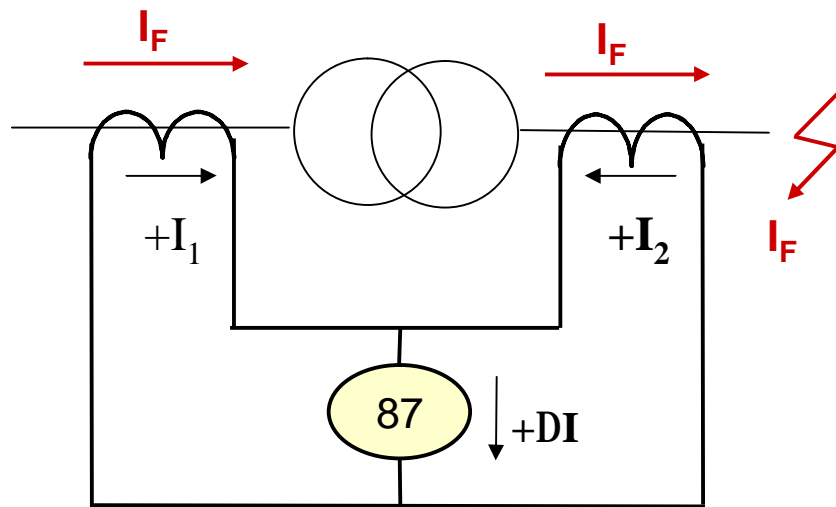
# Transient CT saturation causes false differential currents




Wave shape similar to transformer inrush current ?




# Adaptive restraint against CT errors (7SD52/61)


CT Error approximation (no-saturation)

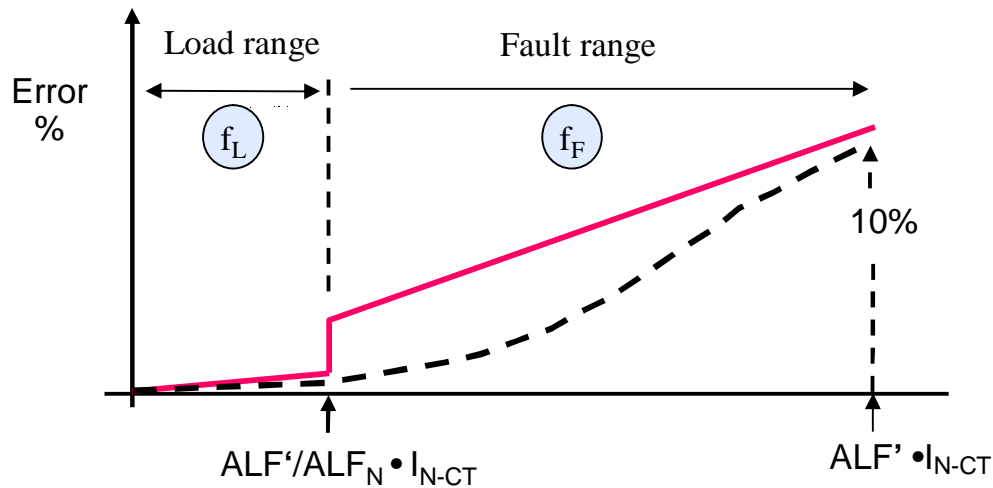

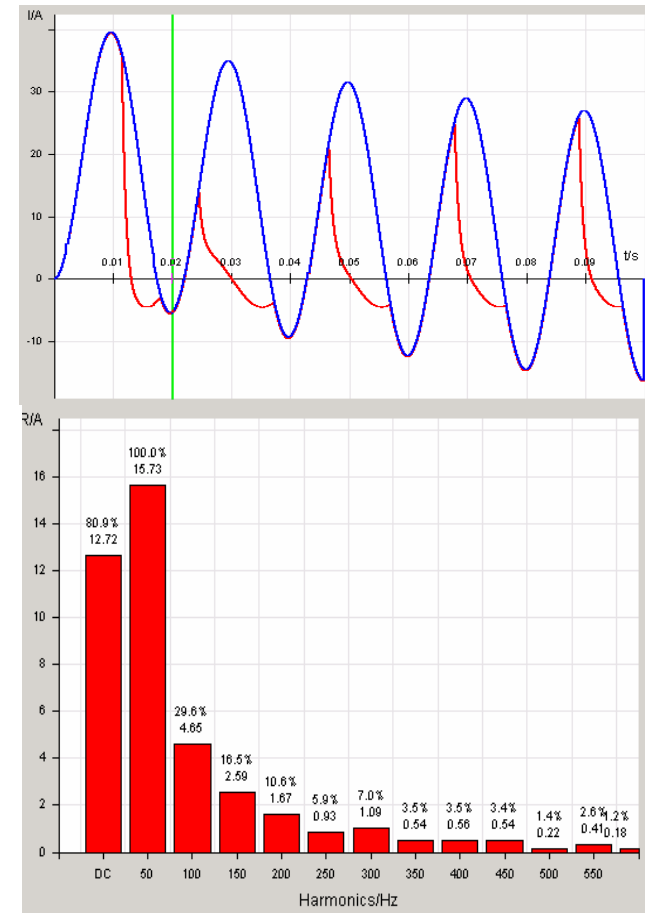Detection of CT saturation (wave shape analysis)




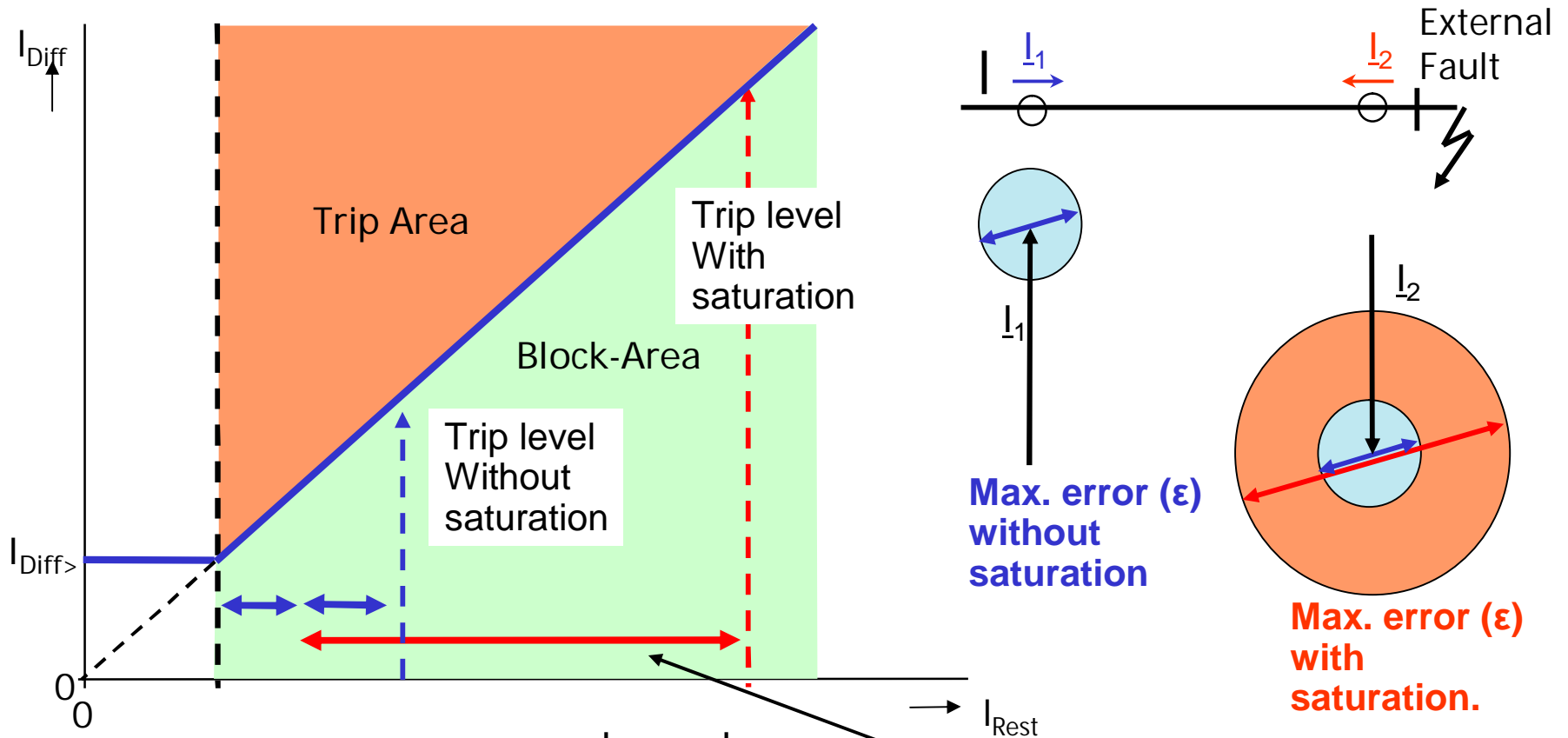
# Adaptive 87 restraint (7SD52/61) considers current CT- errors




**Current summation:**  $I_{Diff} = |I_1 + I_2|$

**Max. error summation:**  $I_{Rest} = S I_{Error} = I_{Diff} > + \epsilon_{CT1} \cdot I_1 + f_{Sat} \cdot \epsilon_{CT2} \cdot I_2$
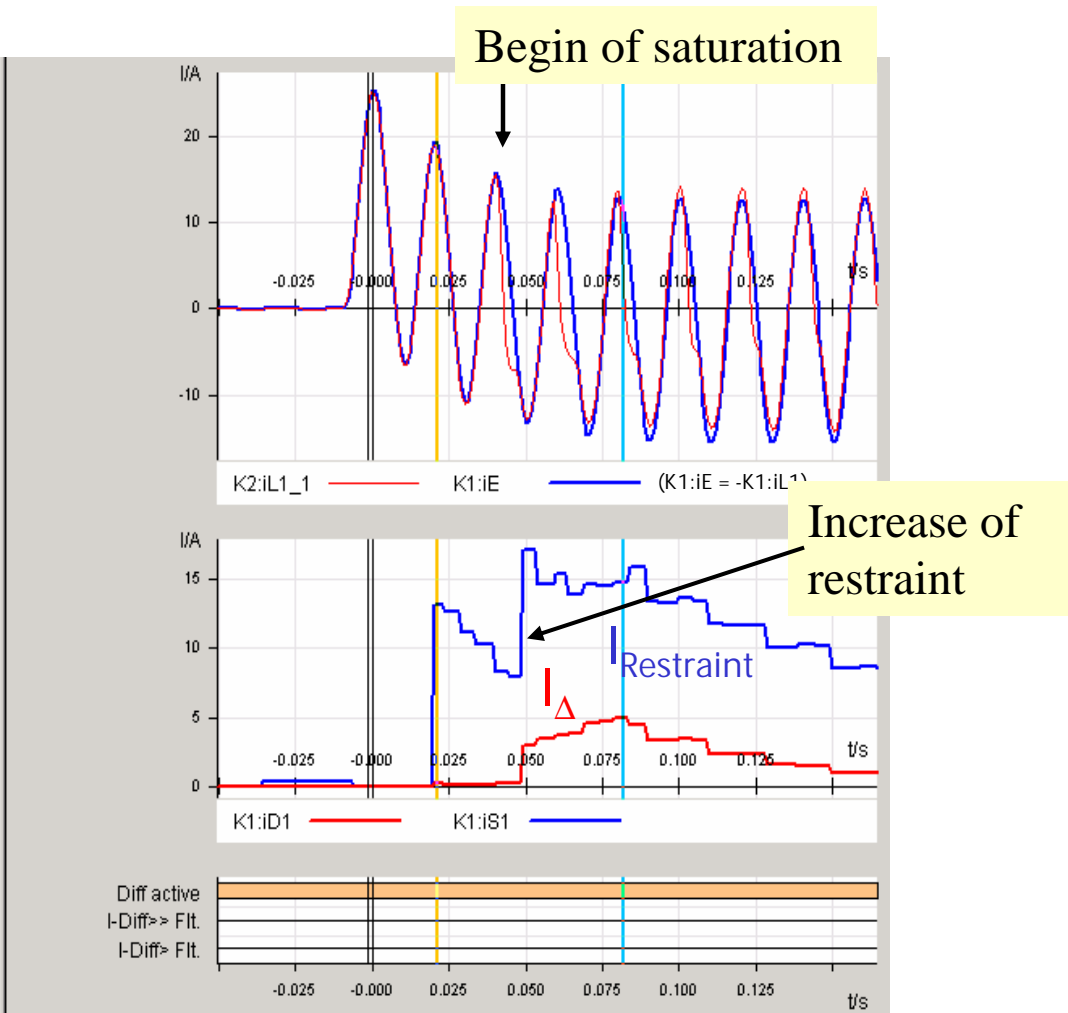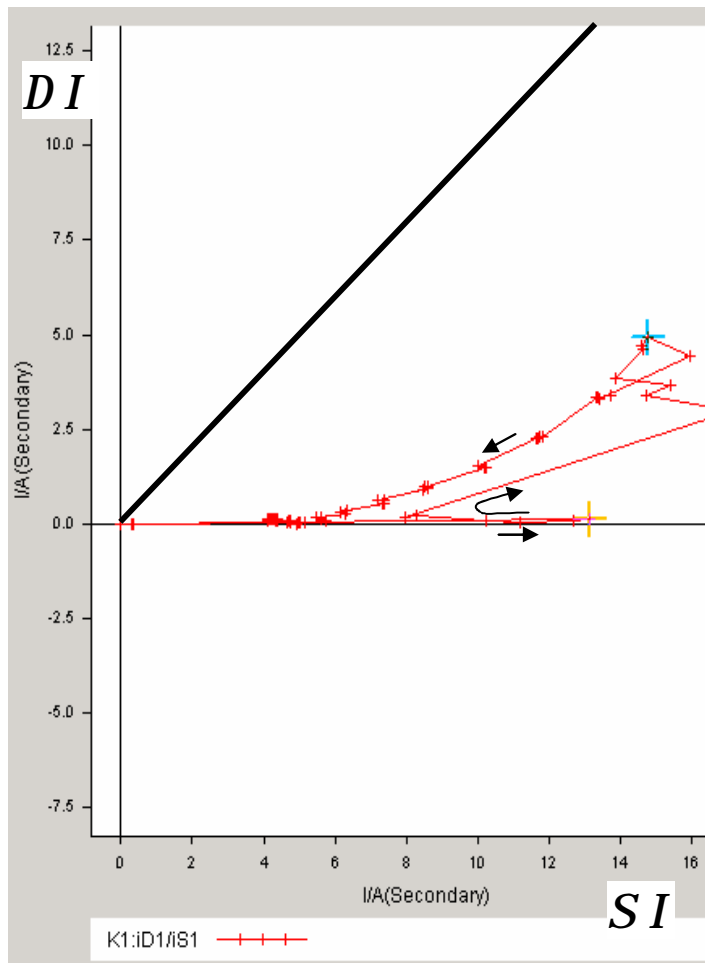
# External fault Increase of stabilisation after detection of saturation



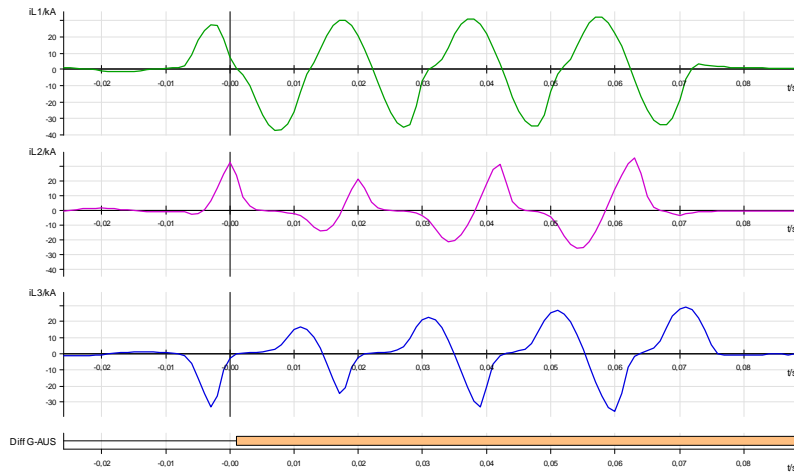
# Fast charge comparison supplement speeds up phasor based line differential protection (7SD52/61)



1 cycle data windows for phasor comparison




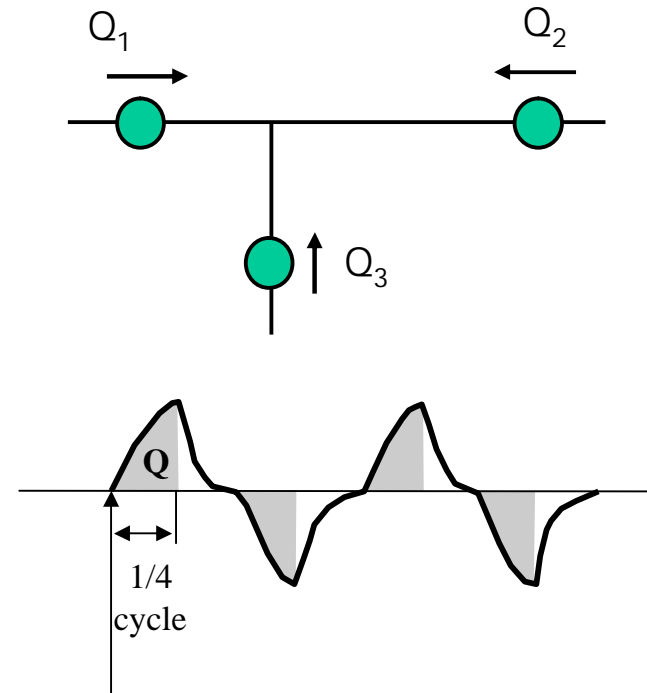1/4 cycle data windows of fast charge comparison



- Synchronized with fault inception
- Released by  $I_{diff} >>$
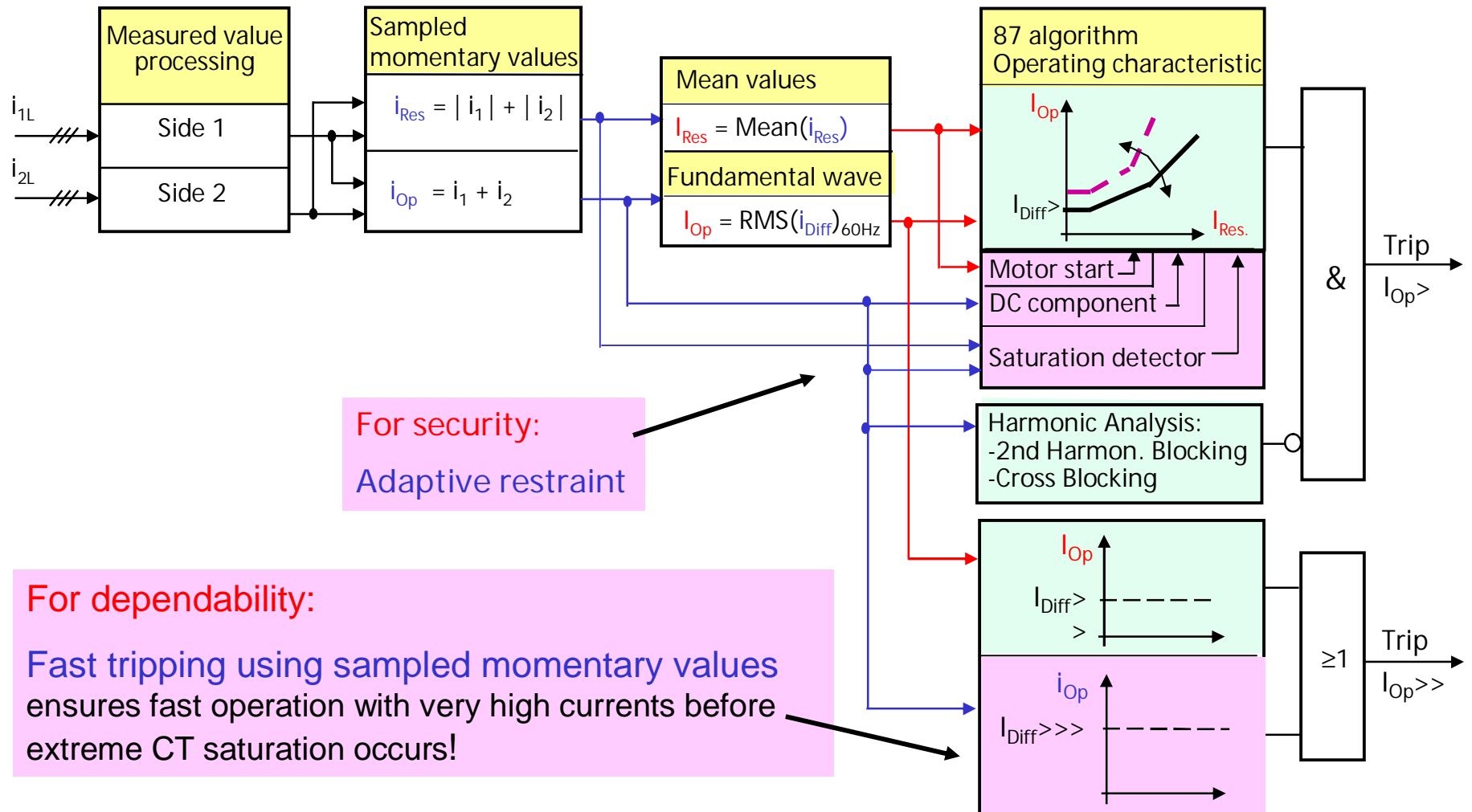
# Generator, Motor and Transformer protection: Adaptive algorithms to upgrade relay stability and dependability with CT saturation (7UT6)






# Current Transformers for Differential Relaying Requirements and Dimensioning

Gerhard Ziegler

SIEMENS
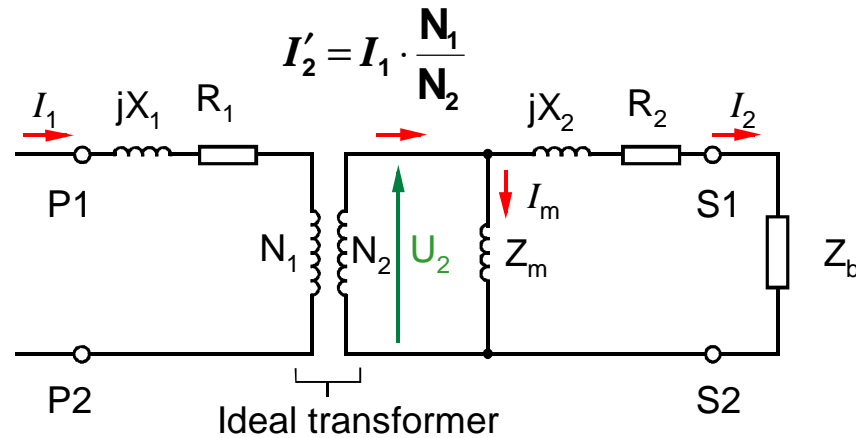
## Equivalent current transformer circuit




$X_1$  = Primary leakage reactance  
 $R_1$  = Primary winding resistance  
 $X_2$  = Secondary leakage reactance  
 $Z_0$  = Magnetising impedance  
 $R_2$  = Secondary winding resistance  
 $Z_b$  = Secondary load

**Note:** Normally the leakage fluxes  $X_1$  and  $X_2$  can be neglected

Current transformer:

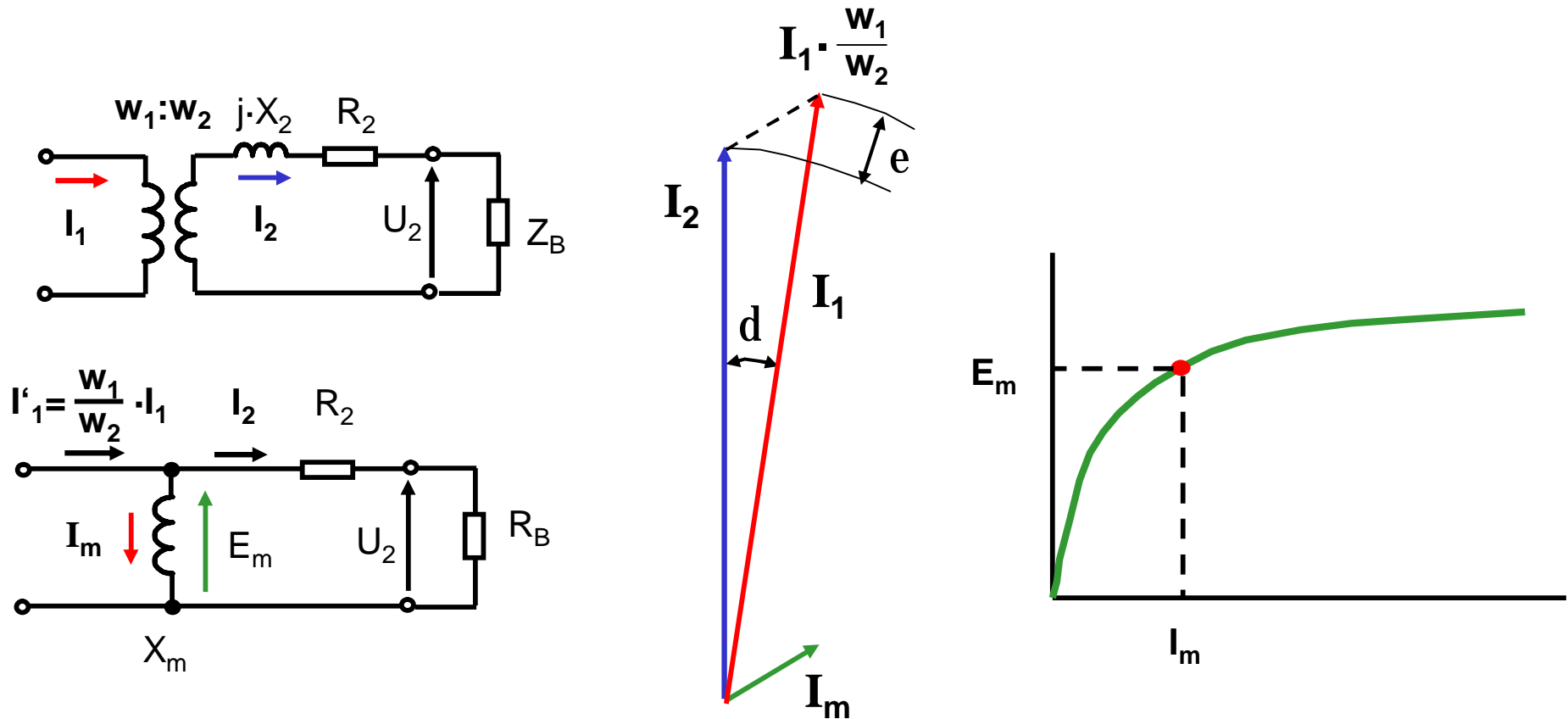Phase displacement ( $\delta$ ) and current ratio error ( $\epsilon$ )





# Dimensioning of CTs for differential protection

CT classes to IEC 60044-1: 5P or 10P

**Specification: 300/1 A 5P10, 30 VA R<sub>CT</sub> £ 5 Ohm**

Ratio  $I_{n-Prim} / I_{n-Sek.}$

5% accuracy  
at  $I = n \times I_n$

5P10

Accuracy  
limit factor **ALF**

30 VA

Rated burden  
(nominal power)  $P_N$

$$P_i = I_{sec.}^2 \times R_{CT}$$

R<sub>CT</sub>

£ 5 Ohm

Actual accuracy limit factor  
in operation is higher as the CT  
is normally under-burdened :  
Operating ALF: **ALF'**

$$ALF' = ALF \times \frac{P_i + P_N}{P_i + P_B}$$

Dimension criterium:

$$ALF' \geq \frac{I_{SC-max}}{I_n} \times K_{TF}$$

$K_{TF}$  (over-dimensioning factor) considers the single sided CT over-magnetising due to the d.c. component in short circuit current  $I_{SC}$ .

$K_{TF}$  values required in practice depend on relay type and design.

Recommendations are provided by manufacturers (see Application Guide)

## Current transformer, Standard for steady-state performance

---

IEC 60044-1 specifies the following classes:


<b>Accuracy class</b>	<b>Current error at nominal current (<math>I_n</math>)</b>	<b>Angle error <math>\delta</math> at rated current <math>I_n</math></b>	<b>Total error at <math>n \times I_n</math> (rated accuracy limit)</b>
<b>5P</b>	$\pm 1 \%$	$\pm 60$ minutes	<b>5 %</b>
<b>10P</b>	$\pm 5\%$	—————	<b>10 %</b>

## Current transformers, Standard for transient performance

IEC 60044-6 specifies four classes:

Class	Error at rated current		Maximum error at rated accuracy limit	Remanence
	Ratio error	Angle error		
TPX (closed iron core)	$\pm 0,5 \%$	$\pm 30 \text{ min}$	$\hat{\epsilon} \leq 10\%$	no limit
TPY with anti-remanence air-gap	$\pm 1,0 \%$	$\pm 30 \text{ min}$	$\hat{\epsilon} \leq 10\%$	$< 10 \%$
TPZ linear core	$\pm 1,0 \%$	$\pm 180 \pm 18 \text{ min}$	$\hat{\epsilon} \leq 10\%$ (a.c. current only)	negligible
TPS closed iron core	Special version for high impedance protection (Knee point voltage, internal secondary resistance)			No limit
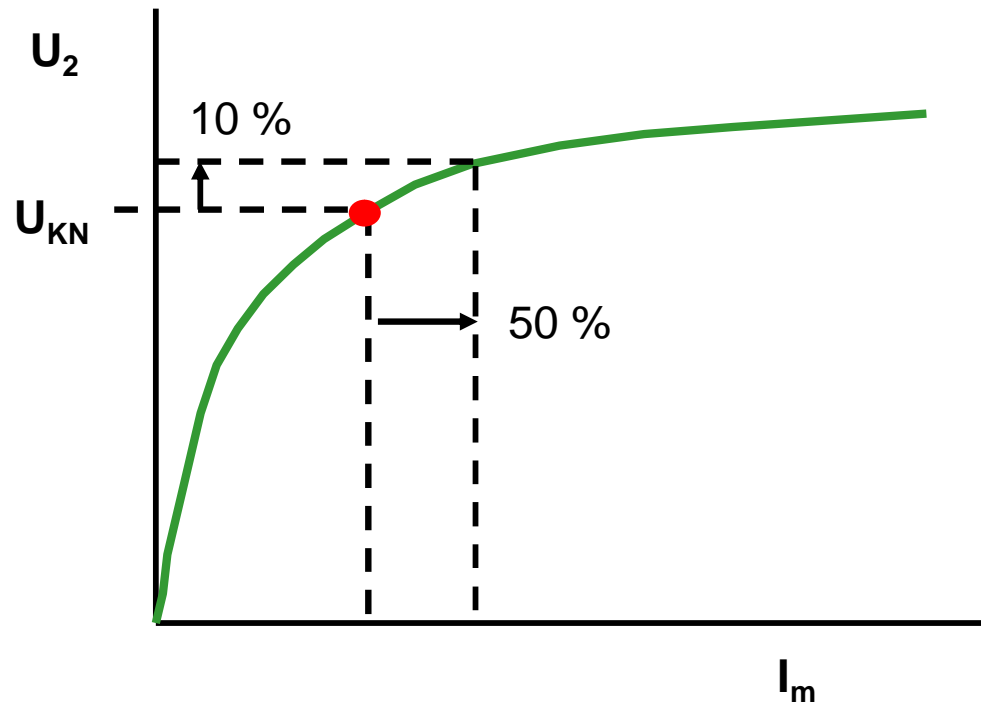
## Definition of the CT knee-point voltage (BS and IEC)



British Standard BS3938: Class X

or

IEC 60044-1 Amendment 2000/07:  
Class PX


Specify:

Knee point voltage

Secondary resistance  $R_{CT}$

$$U_{KN} \geq K_{TF} \cdot (R_{CT} + R_{B-connected}) \cdot \frac{I_{SC-max.}}{I_{n-CT}}$$
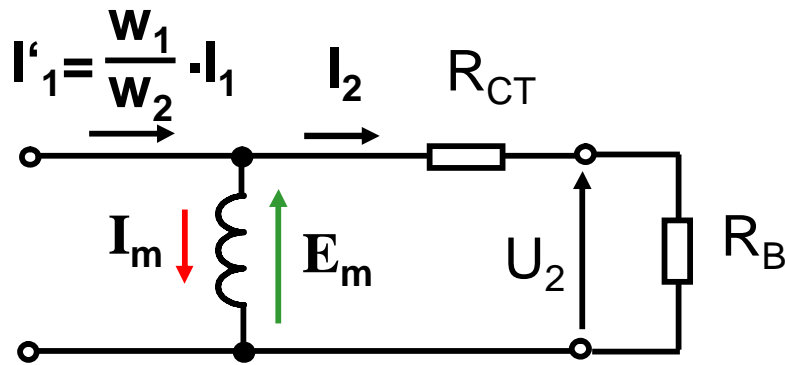
# CT specification according to ANSI C57.13




ANSI C57.13 specifies:

- Secondary terminal voltage  $U_2$  at 20 times rated current ( $20 \times 5 = 100$  A) and rated burden
- Error < 10%

Example:

800/5 A, C400 ( $R_B = 4 \Omega$ )

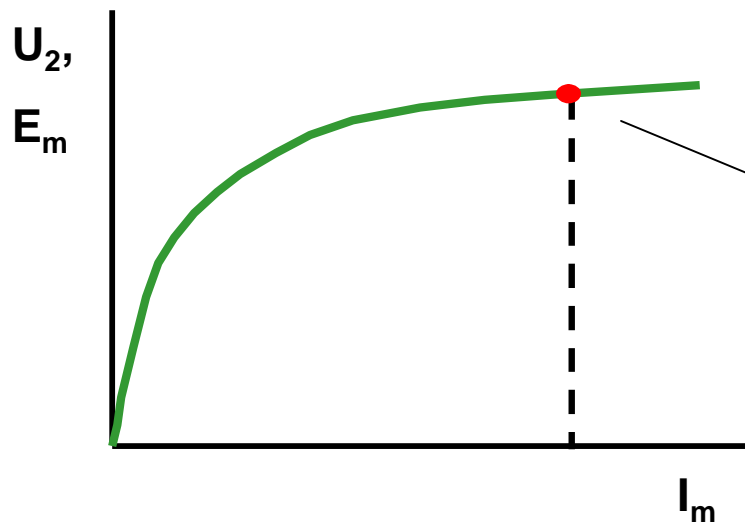


Resulting magnetising voltage:

$$E_{al} \approx (U_{ANSI} + 20 \cdot 5 \cdot R_{CT})$$


$$= (20 \cdot 5 \cdot Z_{B-rated} + 20 \cdot 5 \cdot R_{CT})$$

## Current transformer saturation

---

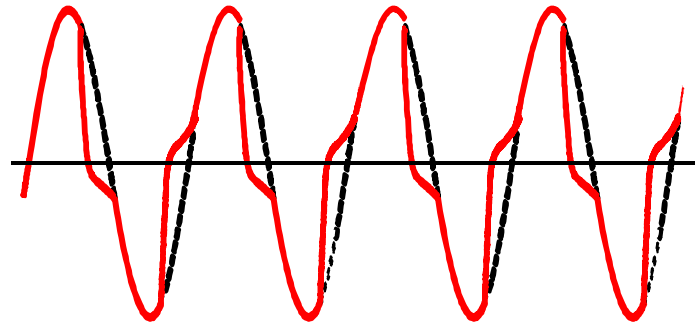


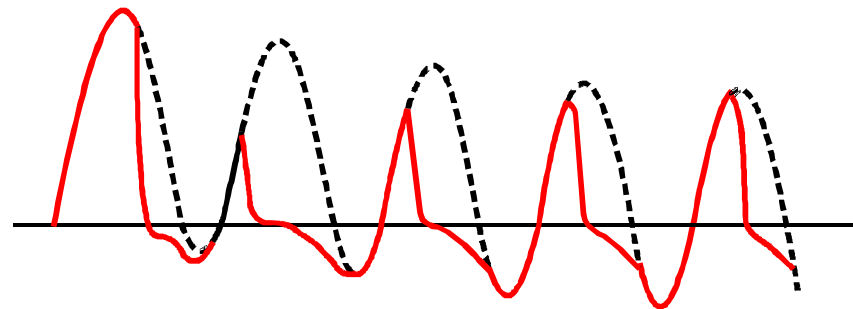Steady-state saturation with a.c. current




Transient saturation with offset current

# CT saturation Currents and magnetising

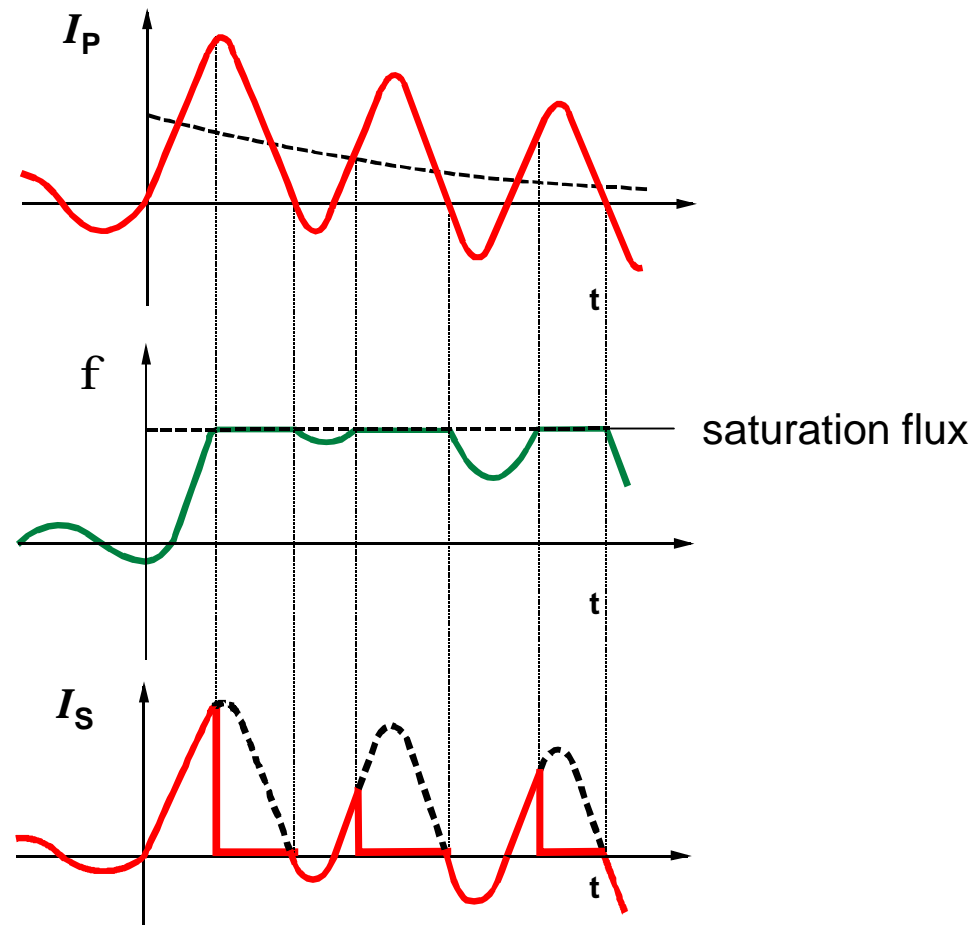

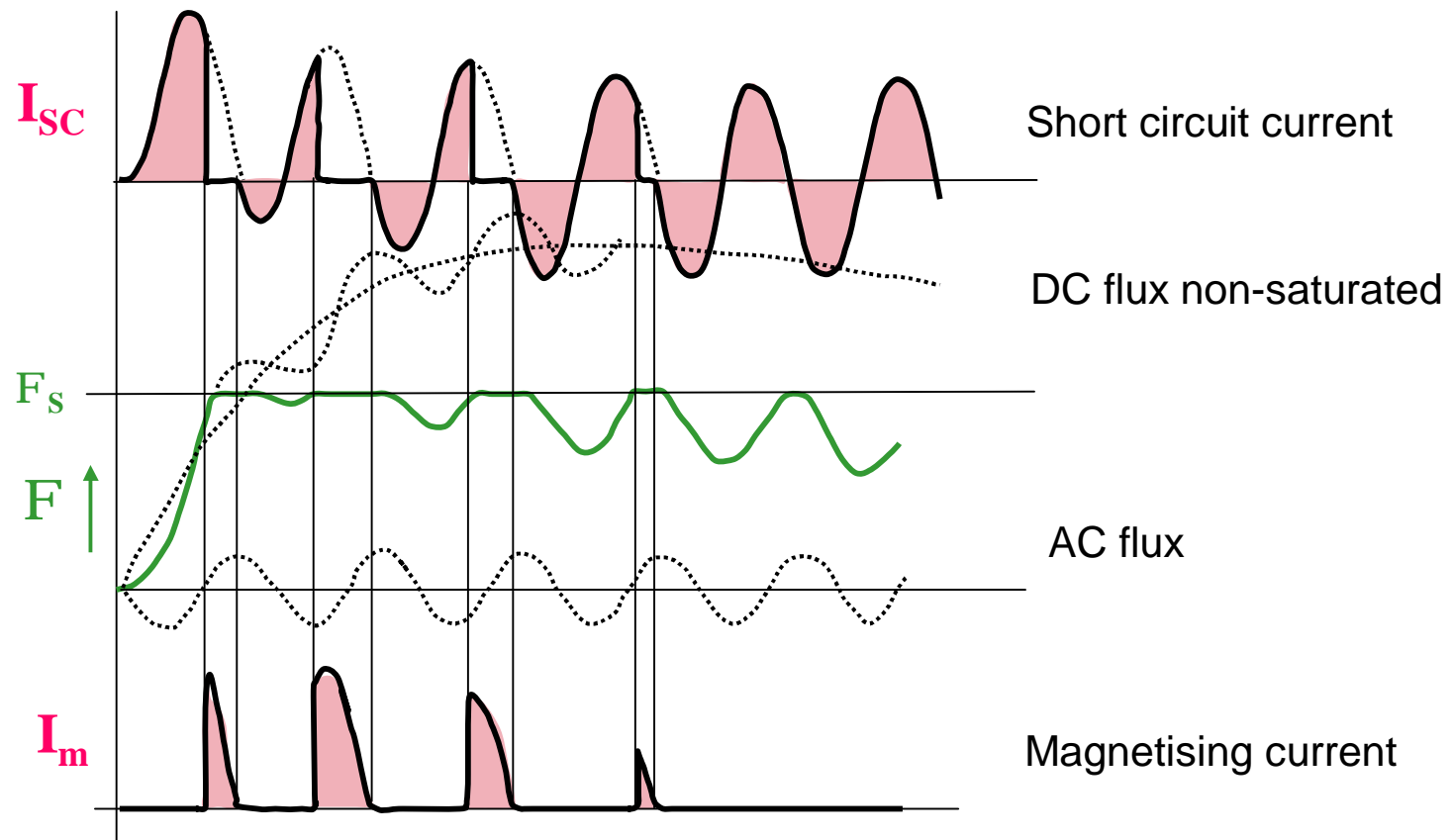
# Transient CT saturation due to DC component




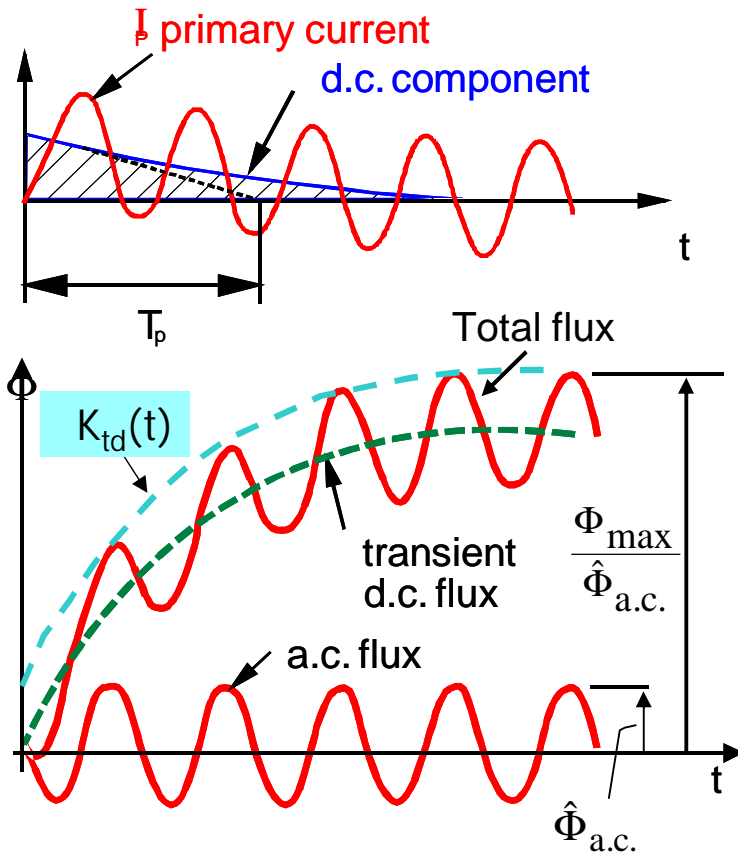
## Course of CT-flux during off-set short-circuit current




$$i_p(t) = \sqrt{2} \cdot I_p \cdot \left[ e^{-\frac{t}{T_p}} - \cos(\omega t) \right]$$

$$\frac{\Phi}{\hat{\Phi}_{\text{a.c.}}} = \frac{\omega T_p T_s}{T_p - T_s} (e^{-\frac{t}{T_p}} - e^{-\frac{t}{T_s}}) - \sin \omega t$$

$$K_{\text{td}}(t) = \frac{\Phi_{\max}}{\hat{\Phi}_{\text{a.c.}}} = \frac{\omega T_p T_s}{T_p - T_s} (e^{-\frac{t}{T_p}} - e^{-\frac{t}{T_s}}) + 1$$


$$K_{\text{td-max}} = 1 + \omega T_p = 1 + \frac{X_p}{R_p}$$
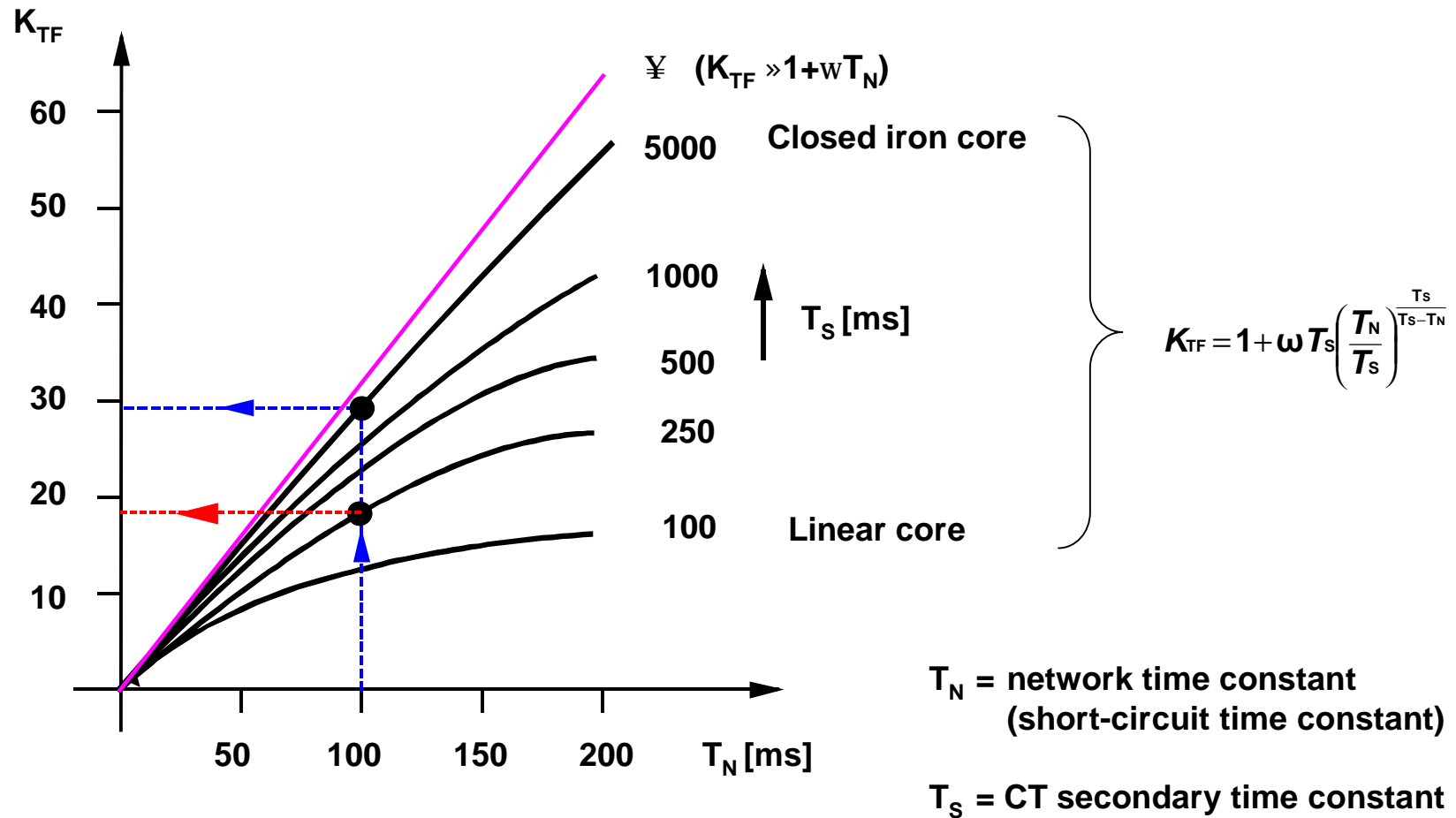
# Theoretical CT over-dimensioning factor $K_{TF}$



CT with closed iron core,

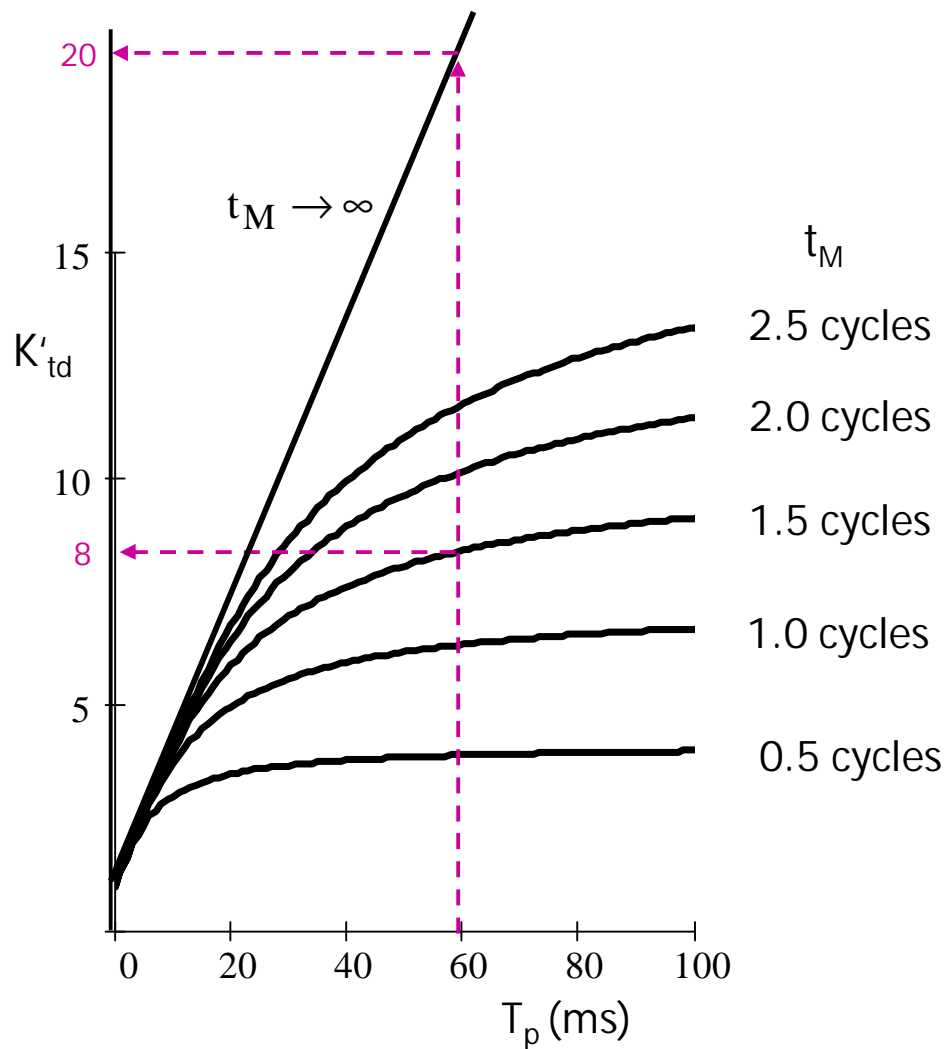Over-dimensioning factor  $K_{TF}'$  for specified time to saturation ( $t_M$ )





$$K'_{td} = 1 + wT_p \cdot \left( 1 - e^{-\frac{t_M}{T_p}} \right)$$

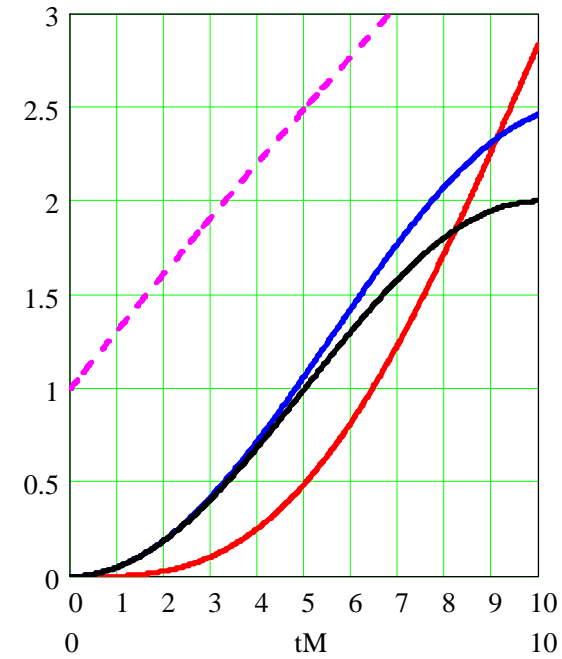
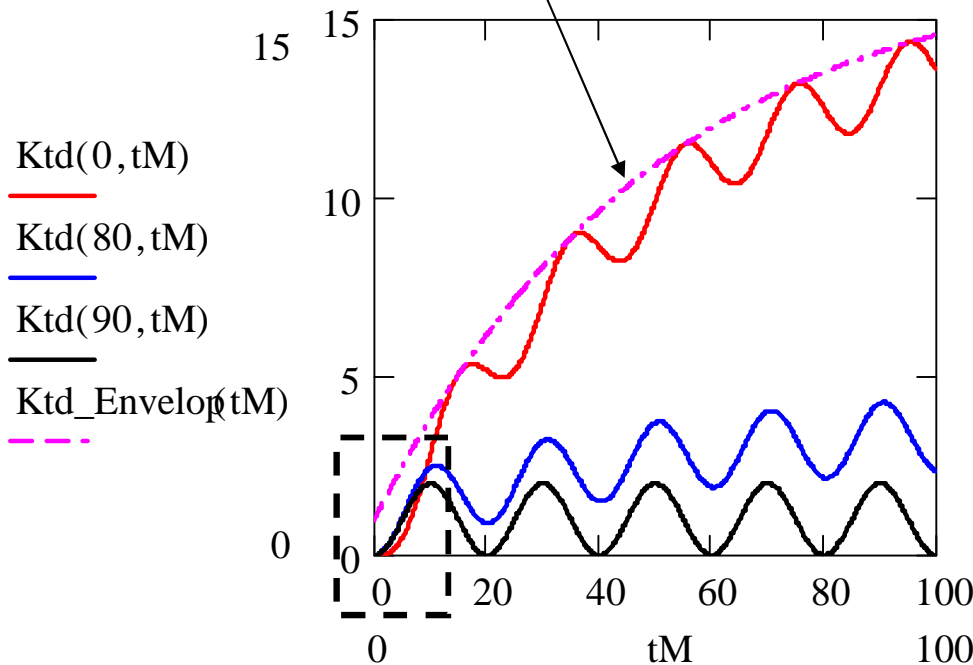
# Transient dimensioning factor $K''_{td}$ for short time to saturation $t_M$

$$K_{td-Envelop} = 1 + \omega T_p \cdot \left( 1 - e^{-\frac{t_M}{T_p}} \right)$$

$$K''_{td}(\Theta, t_M) = \omega \cdot T_p \cdot \cos \theta \cdot \left( 1 - e^{-\frac{t_M}{T_p}} \right) + \sin \Theta - \sin(\omega t_M + \Theta)$$



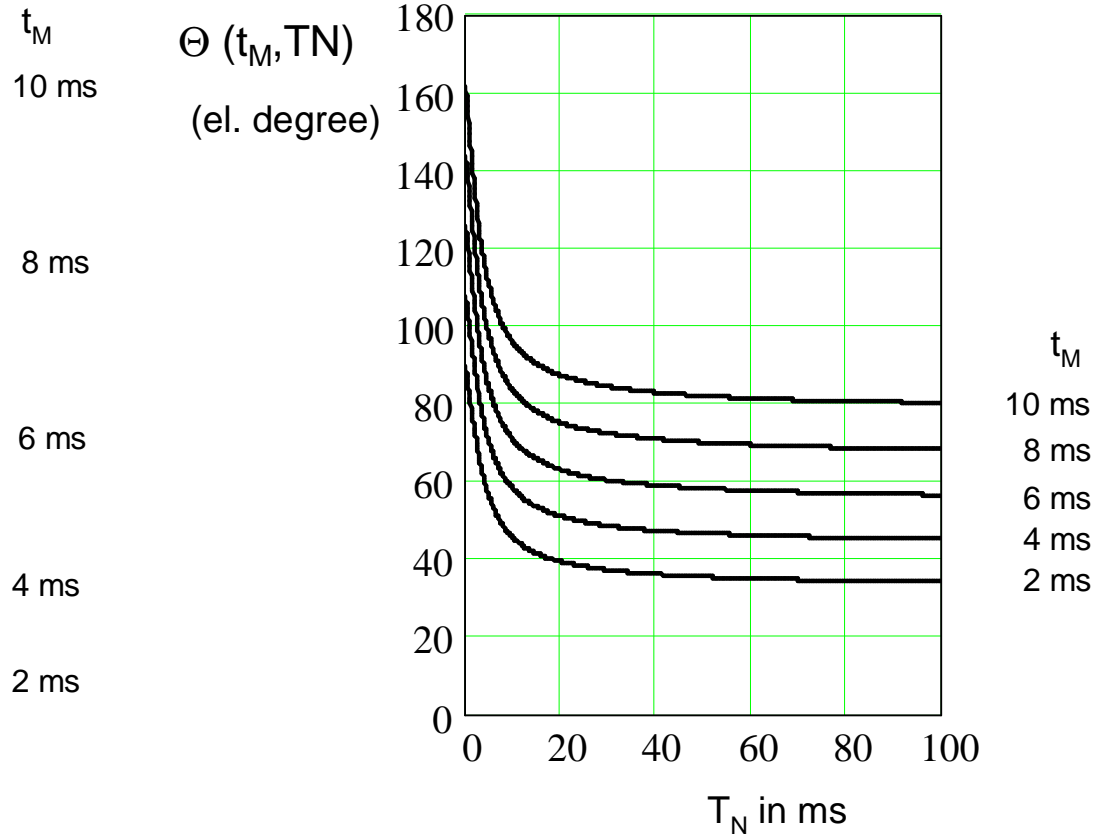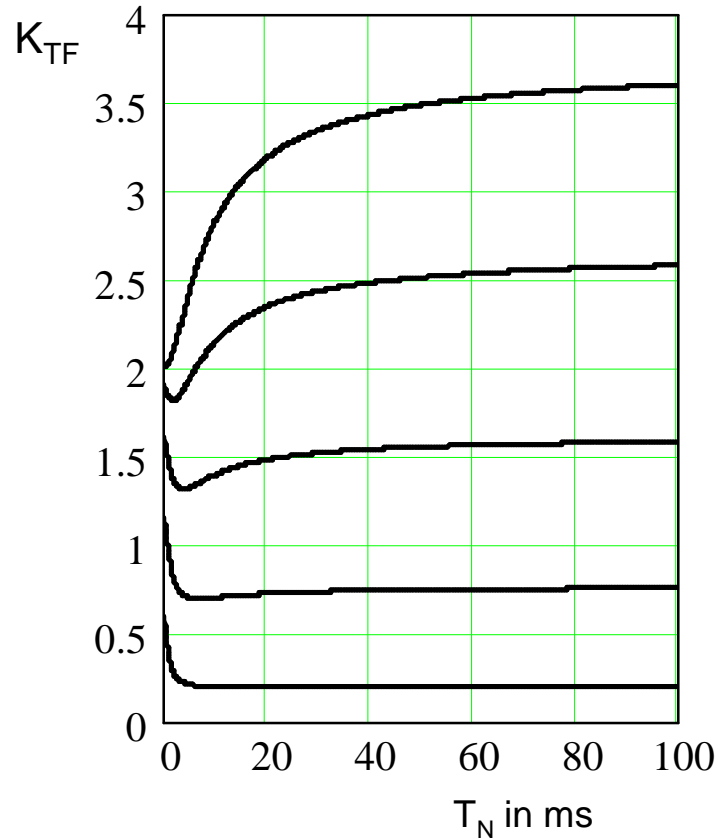
# CT over-dimensioning factor $K_{TF}(t_M, T_N)$ in the case of short time to saturation ( $t_M$ )




# Current transformer

## Magnetising and de-magnetising

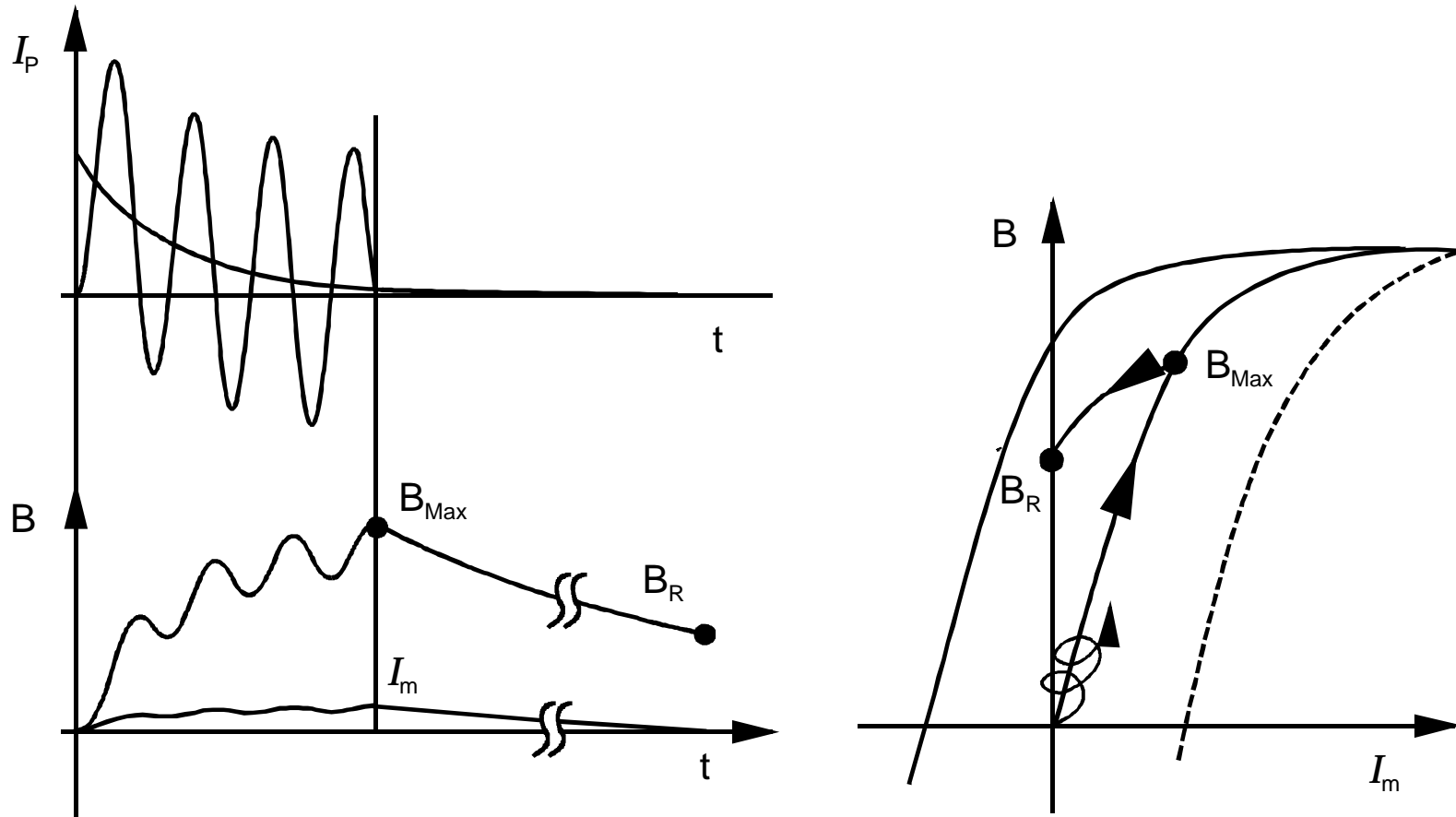

# Current transformer
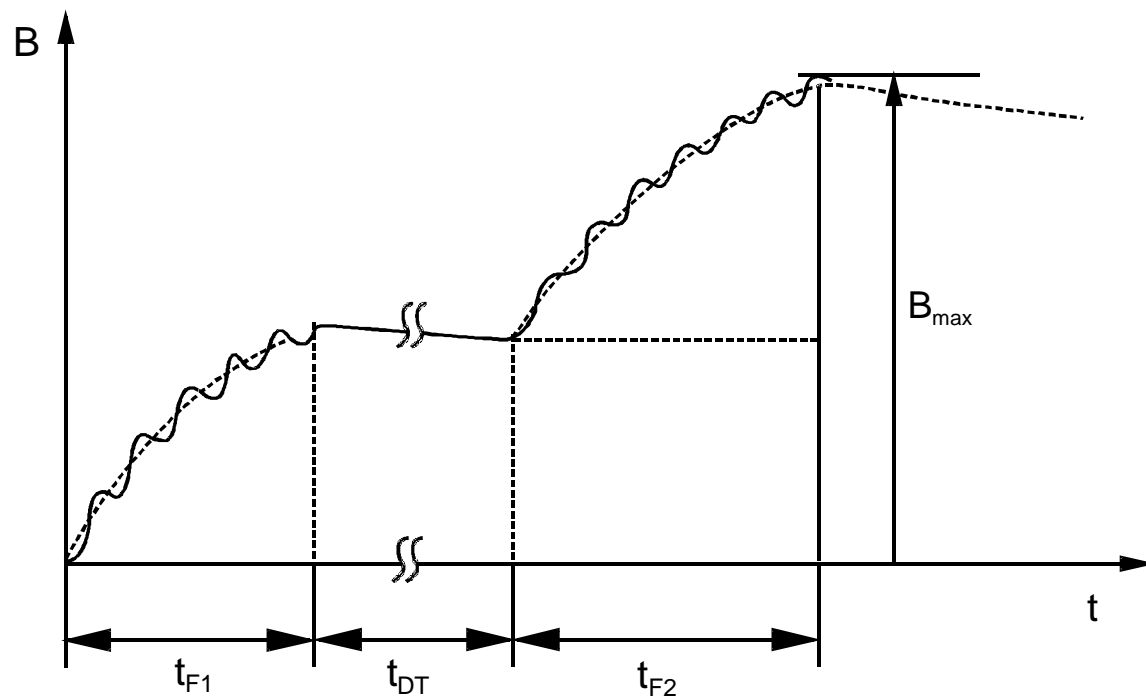
## Course of flux in the case of non-successful auto-reclosure



$t_{F1}$  = duration of 1st fault


$t_{DT}$  dead time

$t_{F2}$  =duration of 2nd fault

$$\frac{B_{max}}{\hat{B}_{\sim}} = \left[ 1 + \frac{\omega \cdot TN \cdot TS}{TN - TS} \left( e^{-\frac{t_{F1}}{TN}} - e^{-\frac{t_{F1}}{TS}} \right) \right] \cdot e^{-\frac{t_{DT} + t_{F2}}{TS}} + \left[ 1 + \frac{\omega \cdot TN \cdot TS}{TN - TS} \left( e^{-\frac{t_{F2}}{TN}} - e^{-\frac{t_{F2}}{TS}} \right) \right]$$

# Current transformer

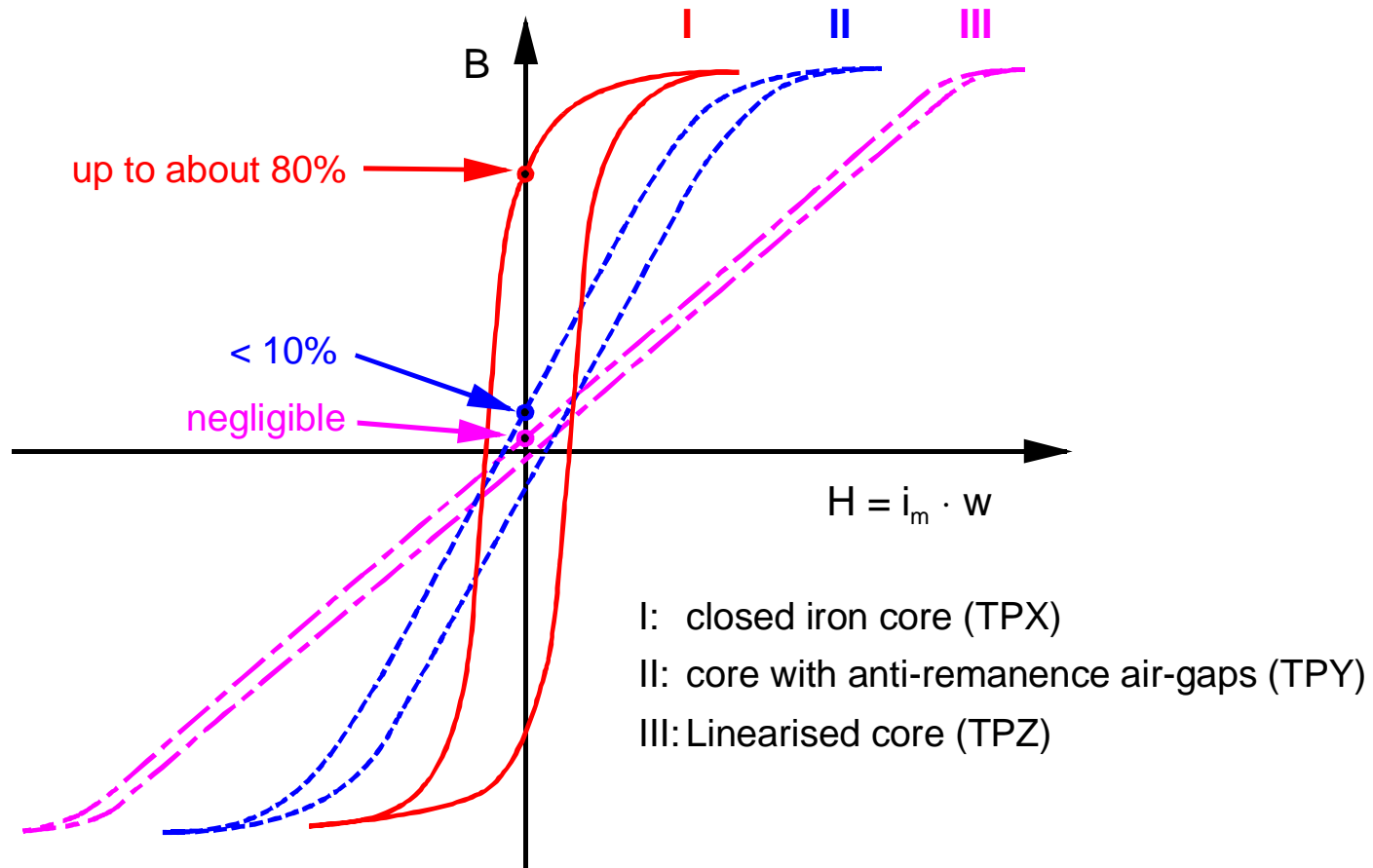
## Magnetising curve and point of remanence






# Current transformers TPX und TPY
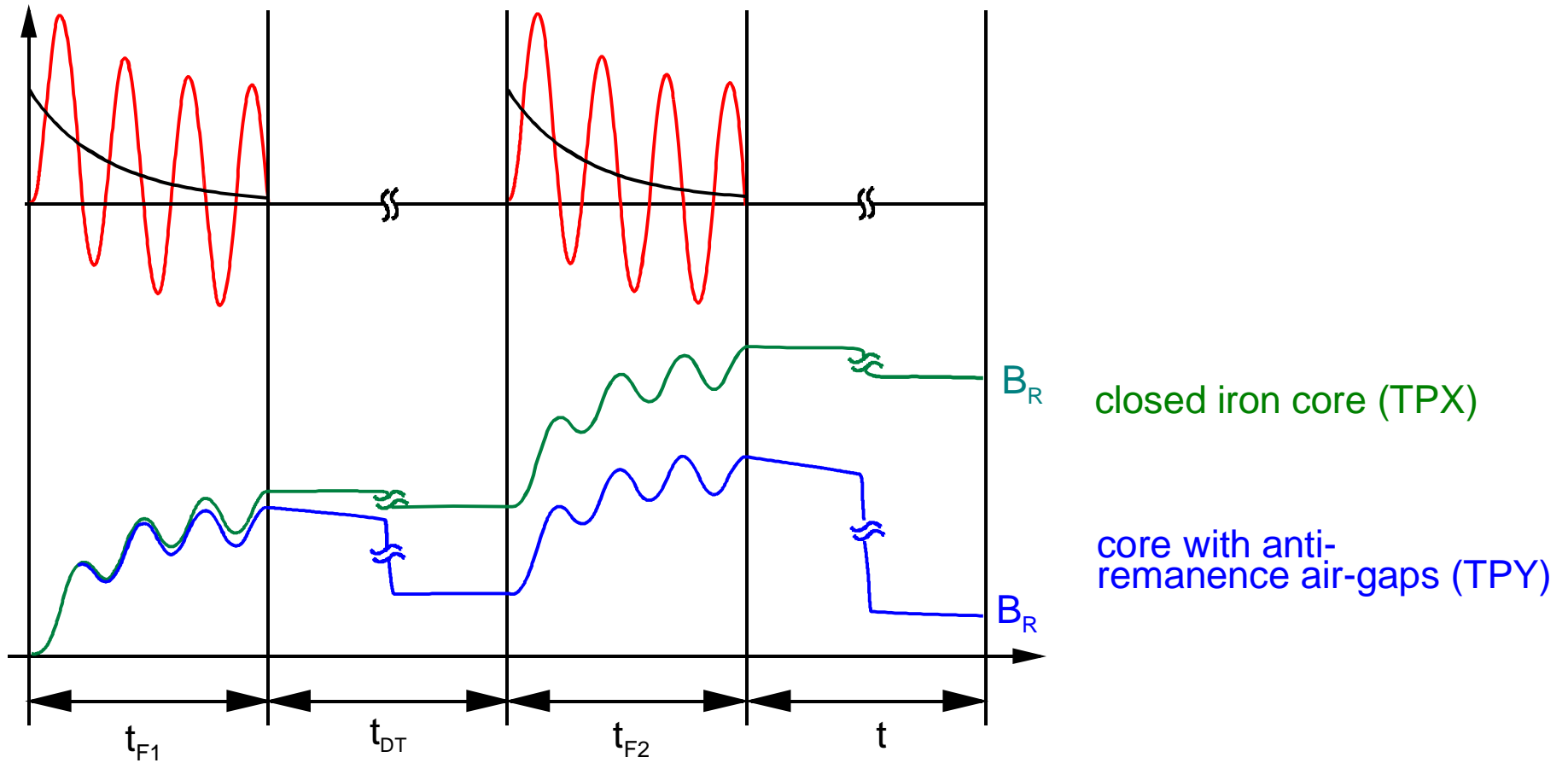
## Course of the flux with non-successful auto-reclosure


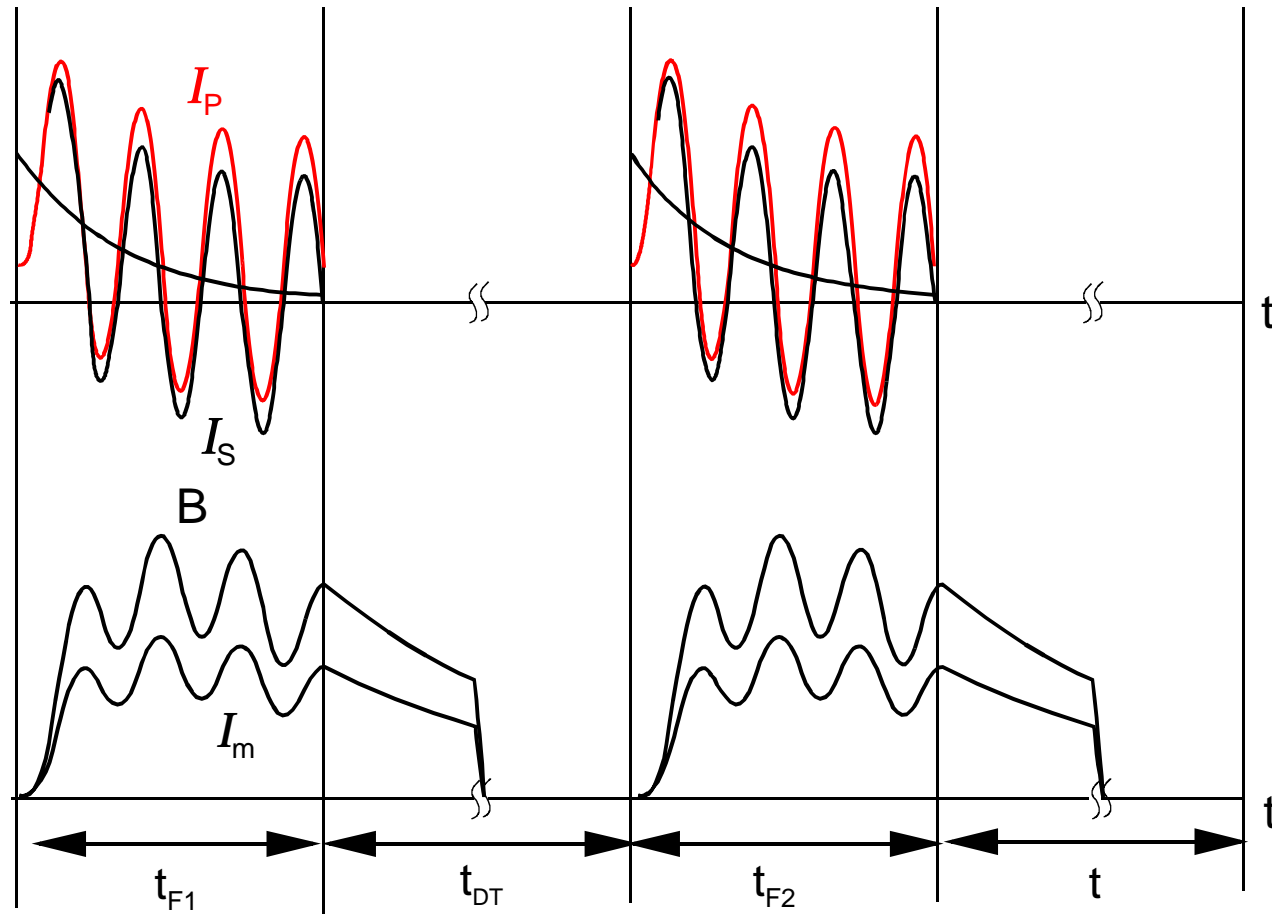
# Current transformer with linear core (TPZ), Course of the flux with non-successful auto-reclosure



## Dimensioning of CTs for protection application

$$ALF' = ALF \cdot \frac{P_1 + P_N}{P_1 + P_B} = n \cdot \frac{R_i + R_N}{R_i + R_B}$$

$$ALF = ALF' \cdot \frac{P_1 + P_B}{P_1 + P_N} = ALF' \cdot \frac{R_i + R_B}{R_i + R_N}$$

Rated CT burden:  $P_N$   
 Internal CT burden:  $P_i = R_i \cdot I_{2N}^2$   
 Actually connected burden :  $P_B = R_B \cdot I_{2N}^2$

with:  $R_B = R_L + R_R =$  total burden resistance  
 $R_L =$  resistance of connecting cable  
 $R_R =$  relay burden resistance

with  $ALF' \geq K_{OD} \cdot \frac{I_{SC}}{I_N}$

Where  $K_{OD}$  is the total over-dimensioning factor:

$$K_{OD} \geq K_{TF} \cdot K_{Rem}$$

$$K_{Rem} = 1 + \frac{\% \text{ remanence}}{100}$$

Theory:

No saturation during total fault duration:  $K'_{TF} = \frac{B_{Max}}{\hat{B}} = 1 + wT_N = 1 + \frac{X_N}{R_N}$

No saturation for the specified time  $t_M$ :  $K''_{TF} = \left[ 1 + \frac{\omega \cdot T_N \cdot T_S}{T_N - T_S} \left( e^{\frac{t_M}{T_N}} - e^{\frac{t_M}{T_S}} \right) \right]$

**Practice:**  $K_{OD} = K_{TF}$

Remanence only considered in extra high voltage systems (EHV)

$K_{TF}$ -values acc. to relay manufacturers' guides

## Practical CT dimensioning using dimensioning factors $K_{td}$ (required minimum time to saturation)

### IEC 60044-1 and 60044-6

300/5 A, 5P20, VA ( $R_b = 1.0 \Omega$ ),  
 $R_{ct} = 0.15 \Omega$

$$ALF' \geq K_{SSC} \cdot K_{td}$$

$$ALF' = \frac{R_{ct} + R_{b-rated}}{R_{ct} + R_{b-connected}} \cdot ALF$$

$$ALF \geq K_{td} \cdot \frac{I_{F-max}}{I_{pn}} \cdot \frac{R_{ct} + R_{b-connected}}{R_{ct} + R_{b-rated}}$$

### BS 3839 (IEC: 60044-1 addendum)

$$E_{al} = \frac{I_{F-max}}{I_{pn}} \cdot K_{td} \cdot (R_{ct} + R_{b-con.}) \cdot I_{sn-CT}$$

$$U_{KN} \approx (0.8 \dots 0.85) \cdot E_{al}$$

### ANSI C57.13

300/5 A, C100 ( $R_b = 1 \Omega$ )

$$\begin{aligned} E_{al} &\approx (U_{ANSI} + 20 \cdot 5 \cdot R_{ct}) \\ &= (20 \cdot 5 \cdot Z_{b-rated} + 20 \cdot 5 \cdot R_{ct}) \end{aligned}$$

$$20 \geq K_{td} \cdot \frac{I_{F-max}}{I_{pn}} \cdot \frac{R_{ct} + R_{b-connected}}{R_{ct} + R_{b-rated}}$$

Transient dim. factor:  $K_{td}$

No saturation:  $1 + X/R = 1 + \omega \cdot T_p$

Differential relays: 1 (87BB: 0.5)

Distance relays: 2 to 4 close-in faults  
5 to 10 zone end

faults

O/C relays:  $I >> ALF' > (I >>_{set} / I_n)$

# Coordination of CTs and digital relays


## Summary

---

- ü Digital relays use intelligent algorithms and are therefore highly tolerant against CT saturation.
- ü In particular differential relays allow short time to saturation of  $\frac{1}{4}$  cycle and below.
- ü Determination of transient dimensioning factors for short time to saturation must consider the real flux course after fault inception.
- ü With time to saturation  $< 10$  ms, the critical point on wave of fault inception is not close to voltage zero-crossing (fully offset current), but varies and is closer to voltage maximum (a.c. current).
- ü CT dimensioning is normally based on relay specific  $K_{td}$  factors provided by manufacturers
- ü In practice, fully offset s.c. current has been assumed while remanence has been widely neglected for CT dimensioning.
- ü A new dimensioning factor is discussed in CIGRE WG B5.02, composed of more probable transient and remanence factors.

## CT dimensioning for differential protection (1)

## 1. Calculation of fault currents

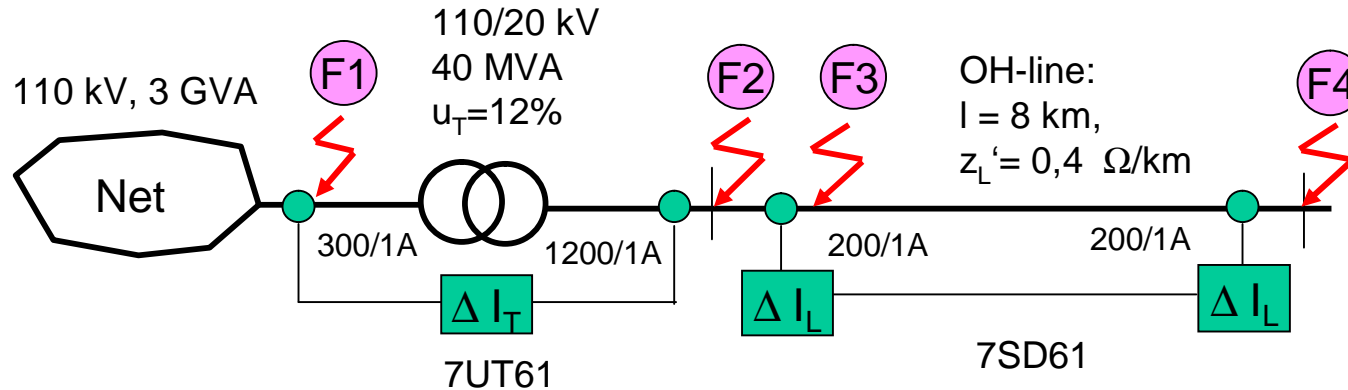

## Impedances related to 110 kV:

$$\text{Net : } Z_N = \frac{U_N^2 [\text{kV}^2]}{S_{SC}'' [\text{MVA}]} = \frac{110^2}{3000} = 4.03 \text{ } \Omega$$

$$\text{Transf. : } Z_T = \frac{U_N^2 [\text{kV}^2]}{P_{N-T} [\text{MVA}]} \cdot \frac{u_T [\%]}{100} = \frac{110^2}{40} \cdot \frac{12\%}{100} = 36.3 \text{ } \Omega$$

## Impedances related to 20 kV:

$$\text{Net : } Z_N = \frac{U_N^2 [\text{kV}^2]}{S_{SC}'' [\text{MVA}]} = \frac{20^2}{3000} = 0.13 \text{ } \Omega$$

$$\text{Transf. : } Z_T = \frac{U_N^2 [\text{kV}^2]}{P_{N-T} [\text{MVA}]} \cdot \frac{u_T [\%]}{100} = \frac{20^2}{40} \cdot \frac{12\%}{100} = 1.2 \text{ } \Omega$$

$$\text{Line : } Z_L = l [\text{km}] \cdot z_L' [\Omega/\text{km}] = 8 \cdot 0,4 = 3,2 \text{ } \Omega$$

## CT dimensioning for differential protection (2)

$$\text{F1} \quad I_{F1} = \frac{1.1 \cdot U_N / \sqrt{3}}{Z_N} = \frac{1.1 \cdot 110 \text{ kV} / \sqrt{3}}{4.03 \Omega} = 17.3 \text{ kA}$$

$$\text{F3} \quad I_{F3} = \frac{1.1 \cdot U_N / \sqrt{3}}{Z_N + Z_T} = \frac{1.1 \cdot 20 \text{ kV} / \sqrt{3}}{0.13 \Omega + 1.2 \Omega} = 9.55 \text{ kA}$$

$$\text{F2} \quad I_{F2} = \frac{1.1 \cdot U_N / \sqrt{3}}{Z_N + Z_T} = \frac{1.1 \cdot 110 \text{ kV} / \sqrt{3}}{4.03 \Omega + 36.3 \Omega} = 1.73 \text{ kA}$$

$$\text{F4} \quad I_{F4} = \frac{1.1 \cdot U_N / \sqrt{3}}{Z_N + Z_T + Z_L} = \frac{1.1 \cdot 20 \text{ kV} / \sqrt{3}}{0.13 \Omega + 1.2 \Omega + 3.2 \Omega} = 2.8 \text{ kA}$$

**Dimensioning of the 110 kV CTs for the transformer differential protection:**

**Manufacturer recommends for relay 7UT61:**

- 1) Saturation free time <sup>3</sup> 4ms for internal faults
- 2) Over-dimensioning factor  $K_{TF}$  <sup>3</sup> 1,2  
for through flowing currents (external faults)

The saturation free time of 3 ms  
corresponds to  $K_{TF} \geq 0,75$   
See diagram, page 59

**Criterion 1) therefore reads:**

$$ALF' \geq K_{TF} \cdot \frac{I_{F1}}{I_N} = 0,75 \cdot \frac{17300}{300} = 43$$

**For criterion 2) we get:**

$$ALF' \geq K_{TF} \cdot \frac{I_{F2}}{I_N} = 1,2 \cdot \frac{1730}{300} = 7$$

The 110 kV CTs must be dimensioned according to criterion 1).

## CT dimensioning for differential protection (3)

We try to use a CT type: 300/1, 10 VA, 5P?, internal burden 2 VA.

$$ALF \geq \frac{P_i + P_{operation}}{P_i + P_{rated}} \cdot ALF' = \frac{2 + 2.5}{2 + 10} \cdot 43 = 16.1 \quad (\text{Connected burden estimated to about 2.5 VA})$$

Chosen, with a security margin : 300 /1 A, 5P20, 10 VA,  $R_2 \leq 2 \text{ Ohm}$  ( $P_i \leq 2\text{VA}$ )

### Specification of the CTs at the 20 kV side of the transformer:

It is good relaying practice to choose the same dimensioning as for the CTs on the 110 kV side:

1200/1, 10 VA, 5P20,  $R_2 \leq 2 \text{ Ohm}$  ( $P_i \leq 2\text{VA}$ )

### Dimensioning of the 20 kV CTs for line protection:

For relay 7SD61, it is required:

- 1') Saturation free time <sup>3</sup> 3ms for internal faults
- 2') Over-dimensioning factor  $K_{TF}$  <sup>3</sup> 1.2  
for through flowing currents (external faults)

The saturation free time of 3 ms  
corresponds to  $K_{TF} \geq 0.5$   
See diagram, page 59

Criterion 1') therefore reads:

$$ALF' \geq K_{TF} \cdot \frac{I_{F3}}{I_N} = 0.5 \cdot \frac{9550}{200} = 24$$

For criterion 2') we get:

$$ALF' \geq K_{TF} \cdot \frac{I_{F4}}{I_N} = 1.2 \cdot \frac{2800}{200} = 16.8$$

The 20 kV line CTs must be dimensioned according to criterion 1').



## CT dimensioning for differential protection (4)

---

For the 20 kV line we have considered the CT type: 200/5 A, 5 VA, 5P?, internal burden ca. 1 VA


$$ALF \geq \frac{P_i + P_{operation}}{P_i + P_{rated}} \cdot ALF' = \frac{1+1}{1+5} \cdot 24 = 8 \quad (\text{Connected burden about 1 VA})$$

### Specification of line CTs:

We choose the next higher standard accuracy limit factor  $ALF=10$  :


Herewith, we can specify: CT Type TPX, 200/5 A, 5 VA, 5P10,  $R_2 \leq 0.04 \text{ Ohm}$  ( $P_i \leq 1 \text{ VA}$ )

## Interposing CTs, Basic versions

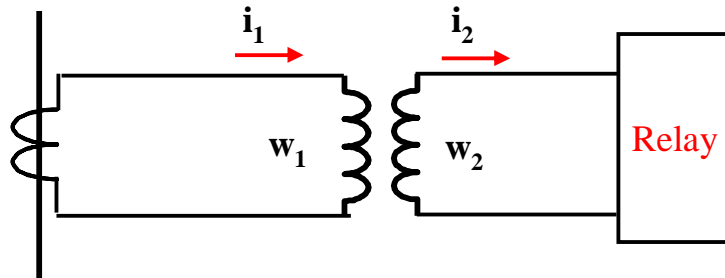

separate winding connection

$$i_2 = \frac{w_1}{w_2} \cdot i_1$$

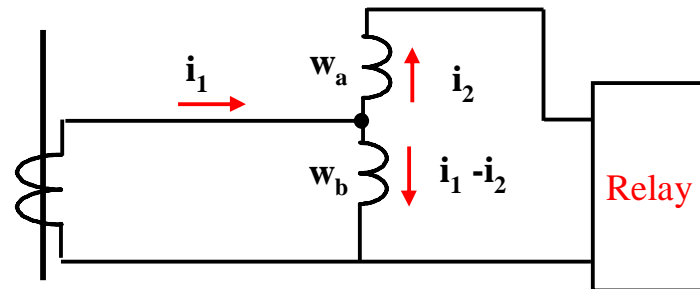


auto-transformer connection



$$i_2 = \frac{w_b}{w_a + w_b} \cdot i_1$$

No galvanic separation!

## Interposing CTs, Example

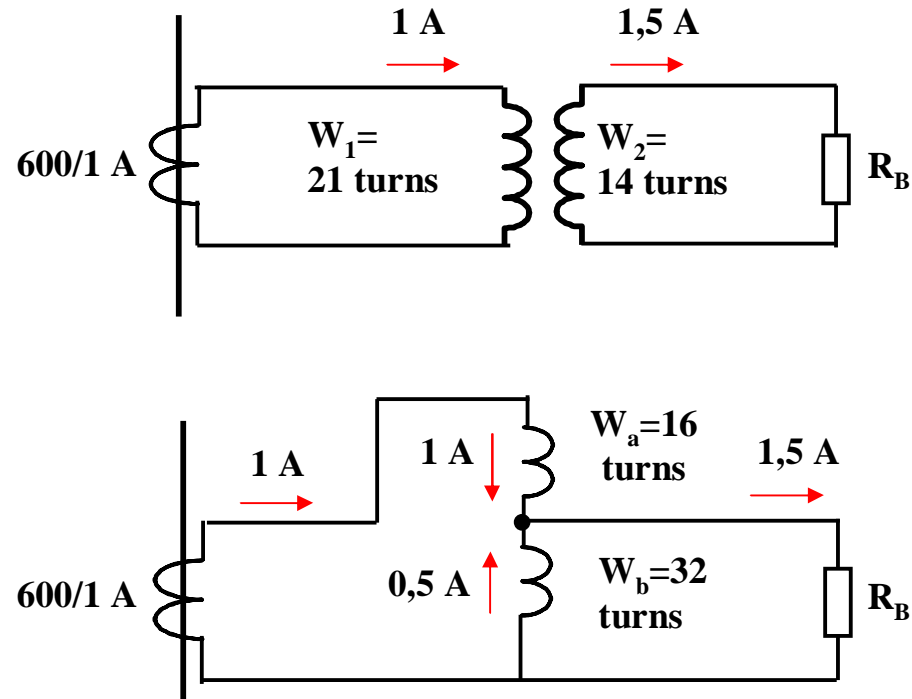


# Interposing CTs in Y-Δ-connection

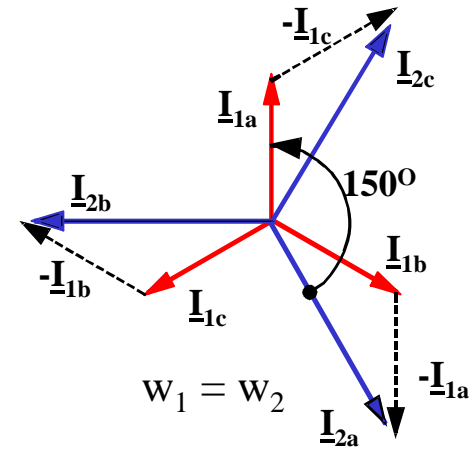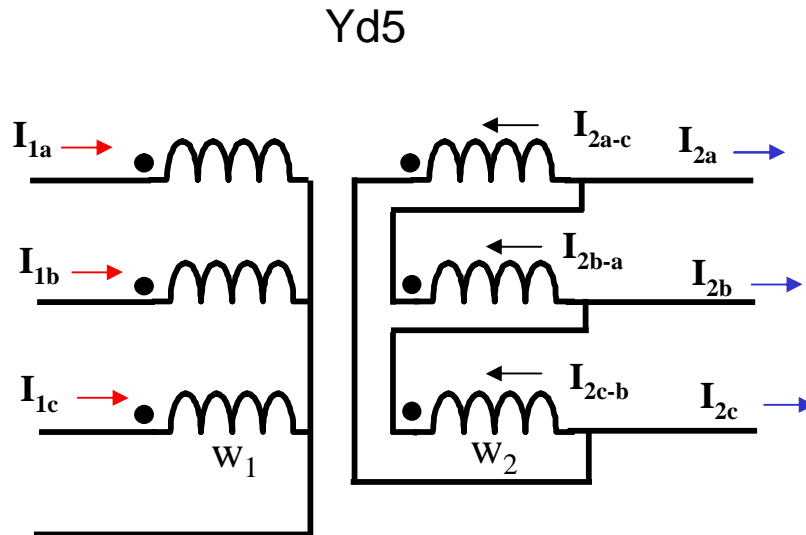


$$I_1 = \frac{1}{\sqrt{3}} \cdot I_2 \cdot \frac{w_2}{w_1} \cdot e^{j \cdot (n \cdot 30^\circ)}$$
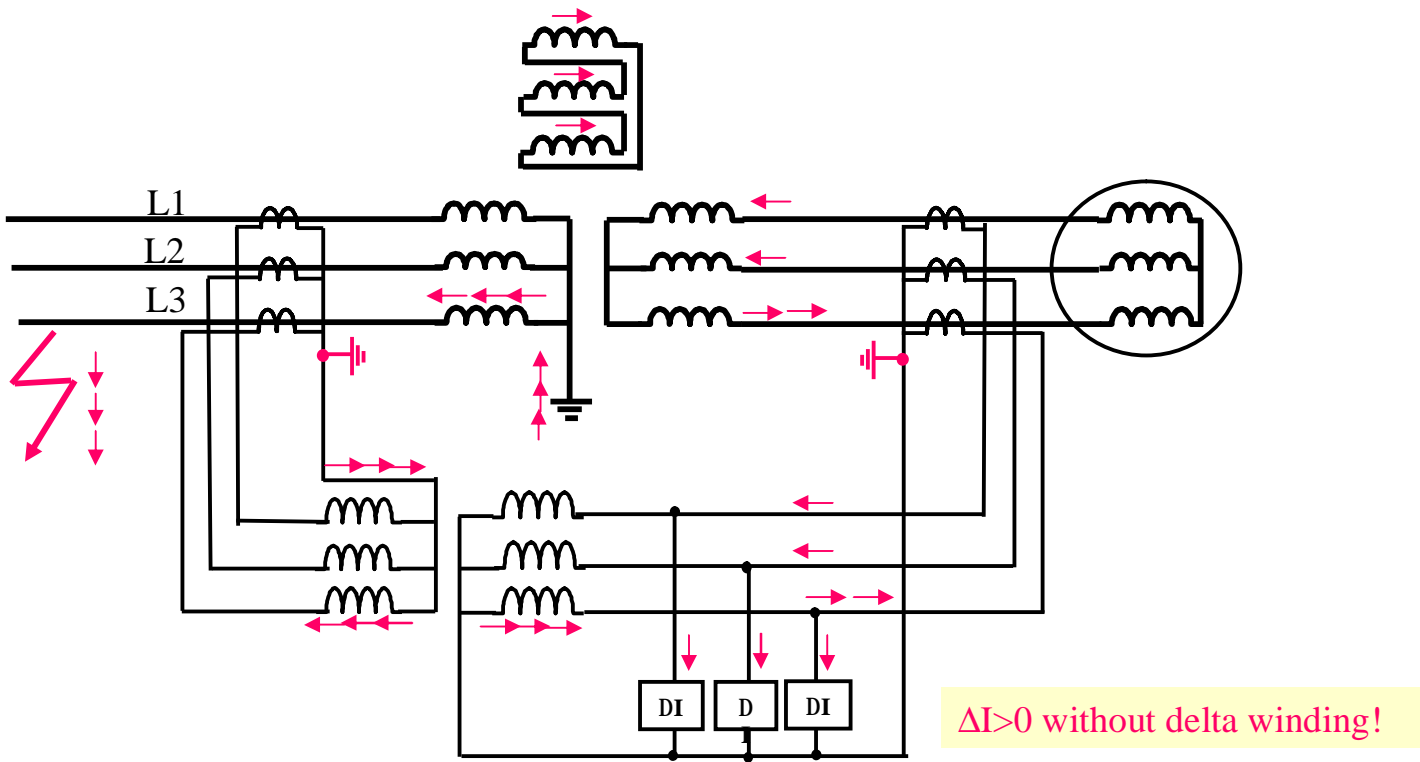
# False operation during external fault of transformer differential protection without zero-sequence current filter




## Zero-sequence current filter

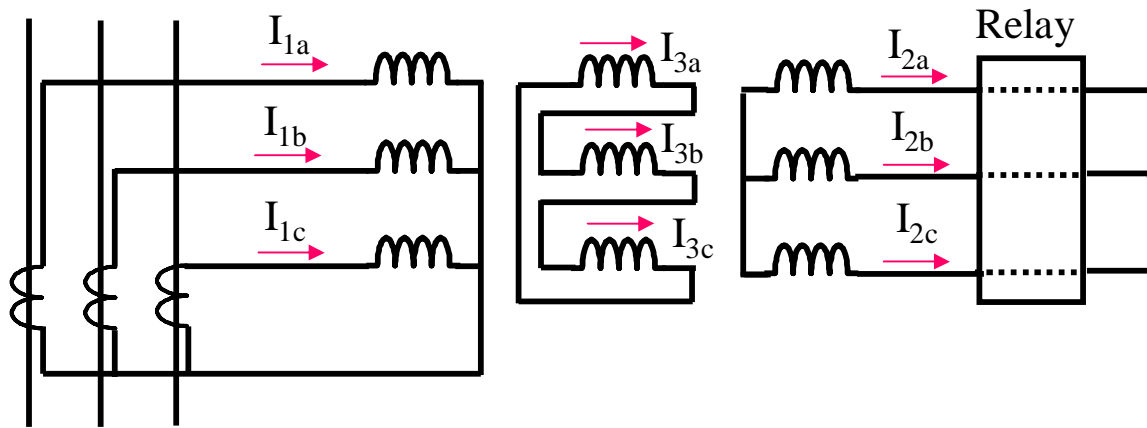

$$\left. \begin{aligned} I_{1a} \cdot w_1 + I_{2a} \cdot w_2 + I_{3a} \cdot w_3 &= 0 \\ I_{1b} \cdot w_1 + I_{2b} \cdot w_2 + I_{3b} \cdot w_3 &= 0 \\ I_{1c} \cdot w_1 + I_{2c} \cdot w_2 + I_{3c} \cdot w_3 &= 0 \\ I_{3a} &= I_{3b} = I_{3c} \\ I_{2a} + I_{2b} + I_{2c} &= 0 \end{aligned} \right\}$$


$$\begin{aligned} I_{3a} = I_{3b} = I_{3c} &= \frac{w_1}{w_3} \cdot \frac{I_{1a} + I_{1b} + I_{1c}}{3} = \frac{I_E}{3} \\ I_{2a} &= \frac{w_1}{w_2} \left( I_{1a} - \frac{I_{1a} + I_{1b} + I_{1c}}{3} \right) \\ I_{2b} &= \frac{w_1}{w_2} \left( I_{1b} - \frac{I_{1a} + I_{1b} + I_{1c}}{3} \right) \\ I_{2c} &= \frac{w_1}{w_2} \left( I_{1c} - \frac{I_{1a} + I_{1b} + I_{1c}}{3} \right) \end{aligned}$$
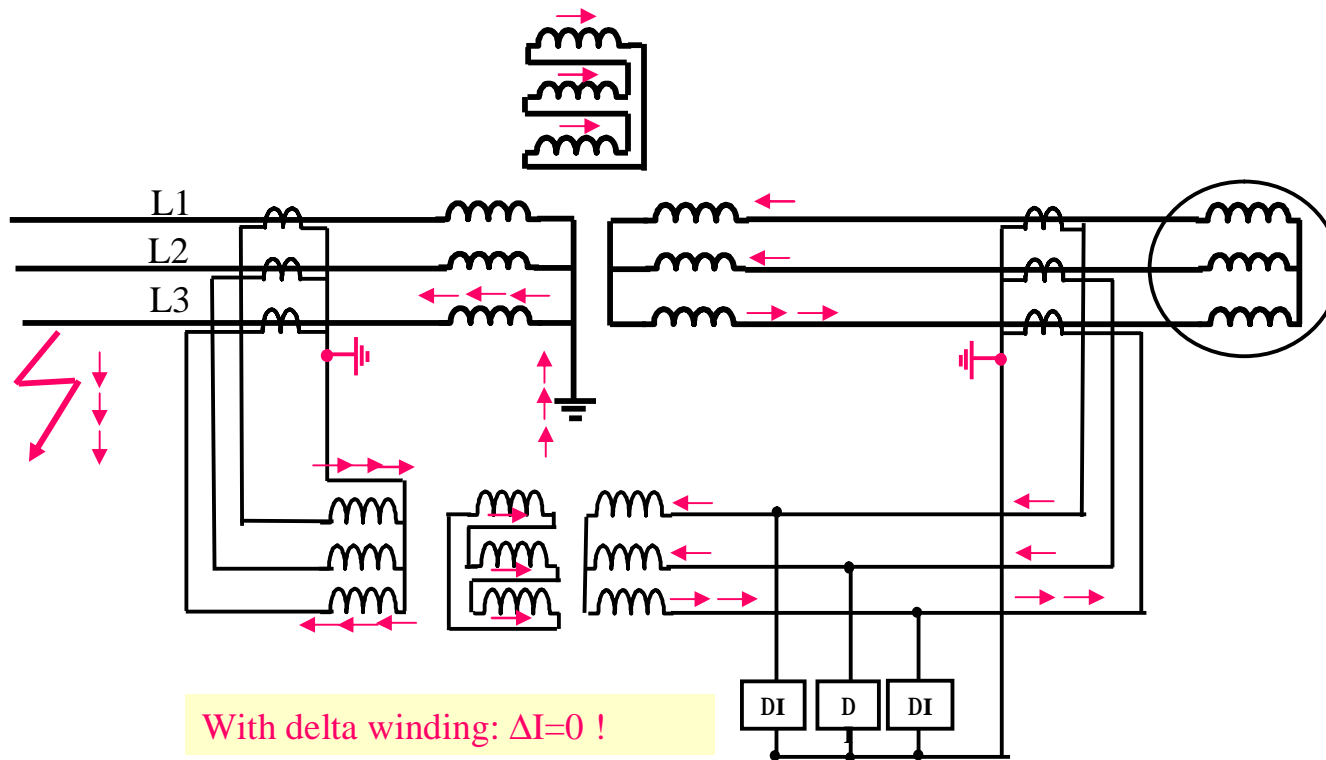
# Biasing of transformer differential protection during external earth fault with zero-sequence current filter (closed delta winding)



# Current matching with interposing CTs (1)

## Calculation example

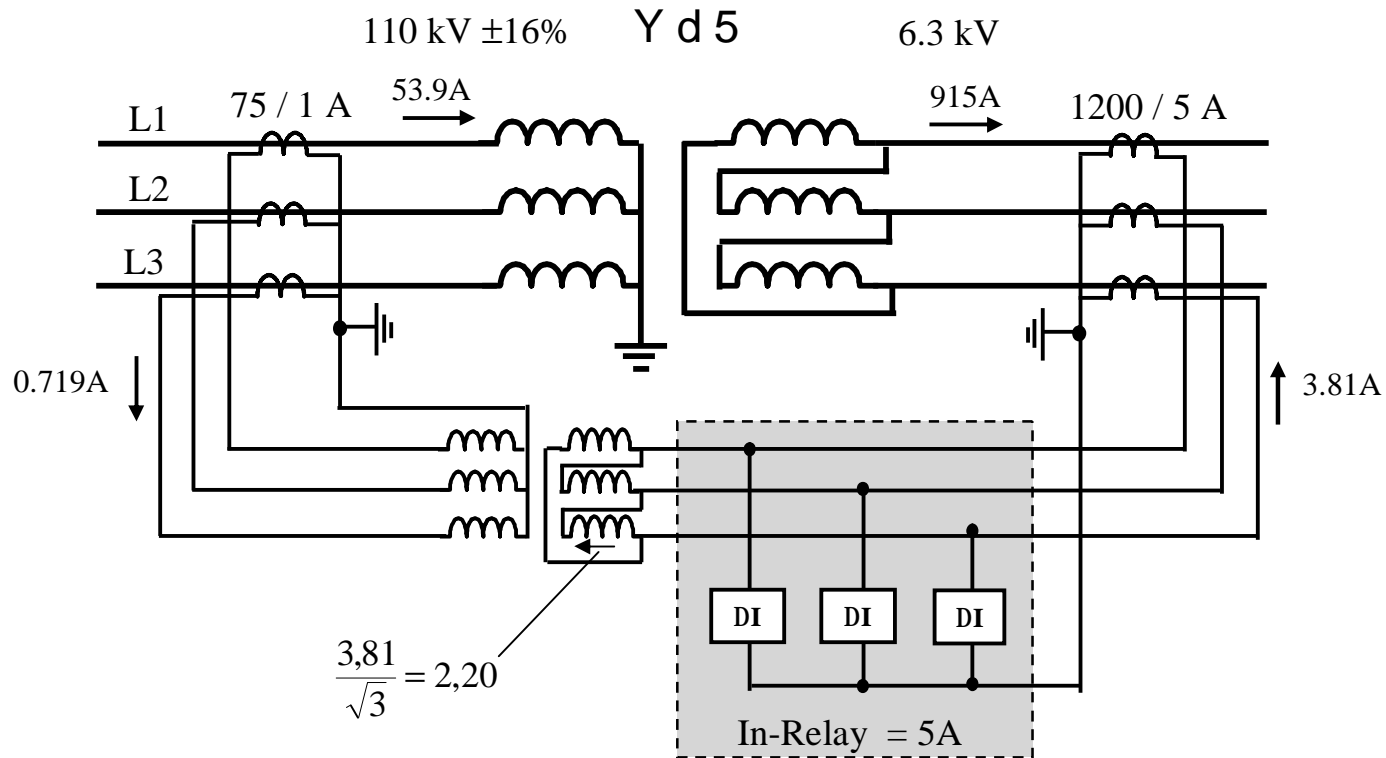



## Current matching with interposing CTs (2)

### Calculation example

---

Current transformation ratio:

We take through flowing rated current as reference:

:

110kV-side:

Mean current value of upper and lower tap changer position:

$$I_1 = \frac{10,000\text{kVA}}{\sqrt{3} \cdot (110\text{kV} + 16\%)} = 45.2\text{A} \quad I_1' = \frac{10,000\text{kVA}}{\sqrt{3} \cdot (110\text{kV} - 16\%)} = 62.5\text{A} \quad I_{1-\text{mean}} = \frac{45.2 + 62.5}{2} = 53.9\text{A}$$

6 kV-side:

$$I_2 = \frac{10,000\text{kVA}}{\sqrt{3} \cdot 6.3\text{kV}} = 915\text{A}$$

The corresponding secondary currents are:

$$i_1 = 53.9 \cdot \frac{1}{75} = 0.719 \text{ A} \quad \text{and} \quad i_2 = 915 \cdot \frac{5}{1200} = 3.813$$



The current in the star connected winding of the interposing transformer is  $i_1$

The current in the delta connected winding is:  $i_2 / \sqrt{3}$ .

The ratio of the interposing CT must be :

$$\frac{w_1}{w_2} = \frac{i_2 / \sqrt{3}}{i_1} = \frac{3.813 / \sqrt{3}}{0.719} = \frac{2.202}{0.719} = 3.06$$
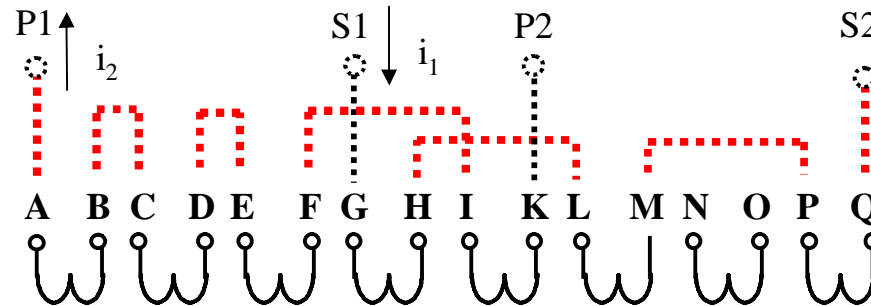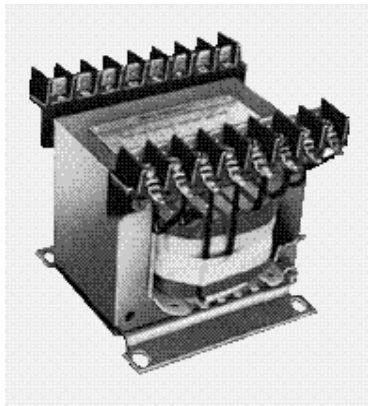
# Link selectable interposing CT 4AM5170-7AA





1	2	7	16	1	2	7	16	Windings
0,013	0,025	0,08	0,75	0,013	0,025	0,08	0,75	R in Ohm
2	4	14	32	2	4	14	32	U-max. in V
5	5	5	1	5	5	5	1	Rated current in A

$$\frac{w_1}{w_2} = \frac{i_2 / \sqrt{3}}{i_1} = \frac{3,813 / \sqrt{3}}{0,719} = \frac{2,202}{0,719} = 3.06$$

$$\text{chosen : } \frac{w_1}{w_2} = \frac{16 + 16 + 2}{7 + 2 + 1 + 1} = \frac{34}{11} = 3,09$$


Connection and links as shown.
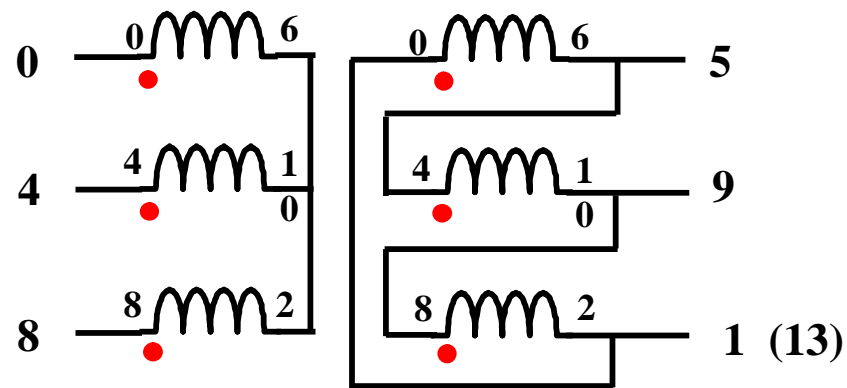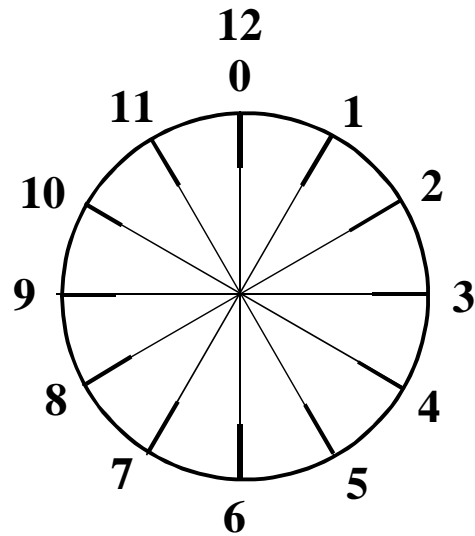
# Designation of transformer or CT vector groups (1) Clock-wise notation according to IEC 60076-1





# Designation of transformer or CT vector groups (2)
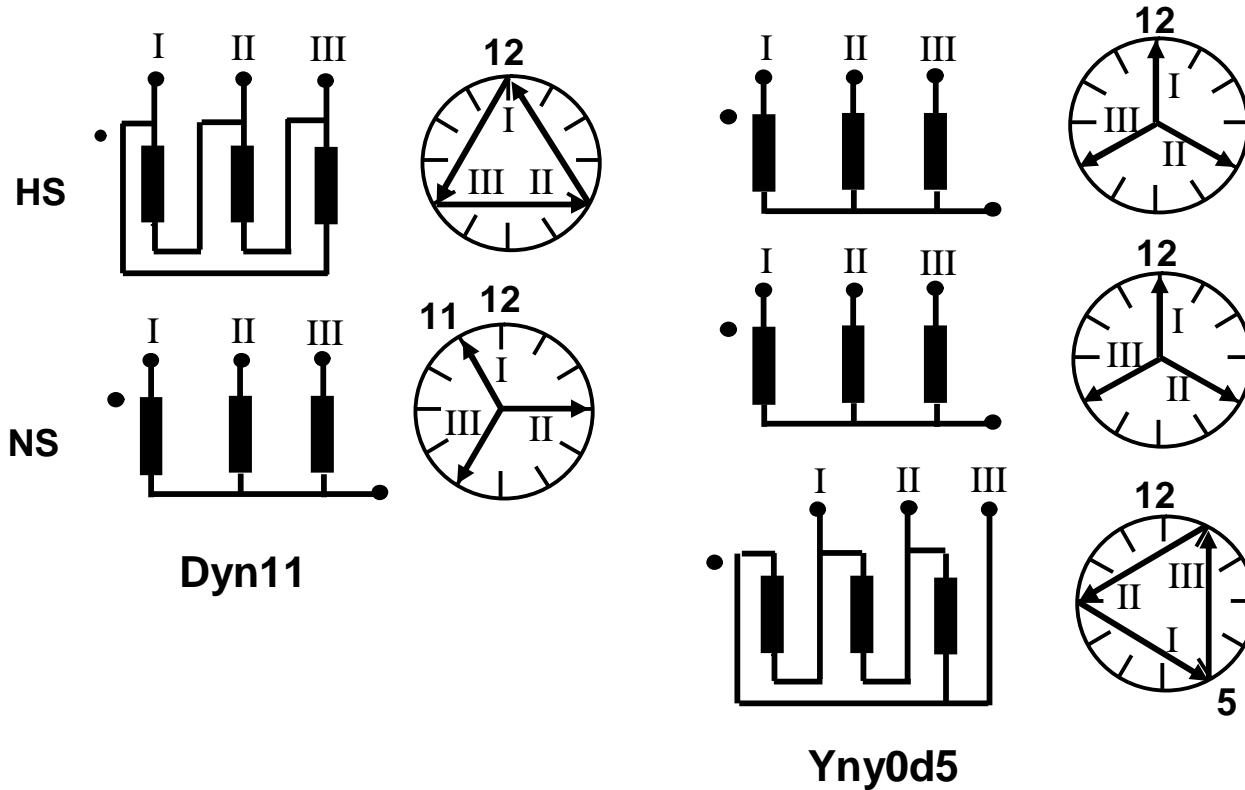
## Clock-wise notation according to IEC 60076-1, examples


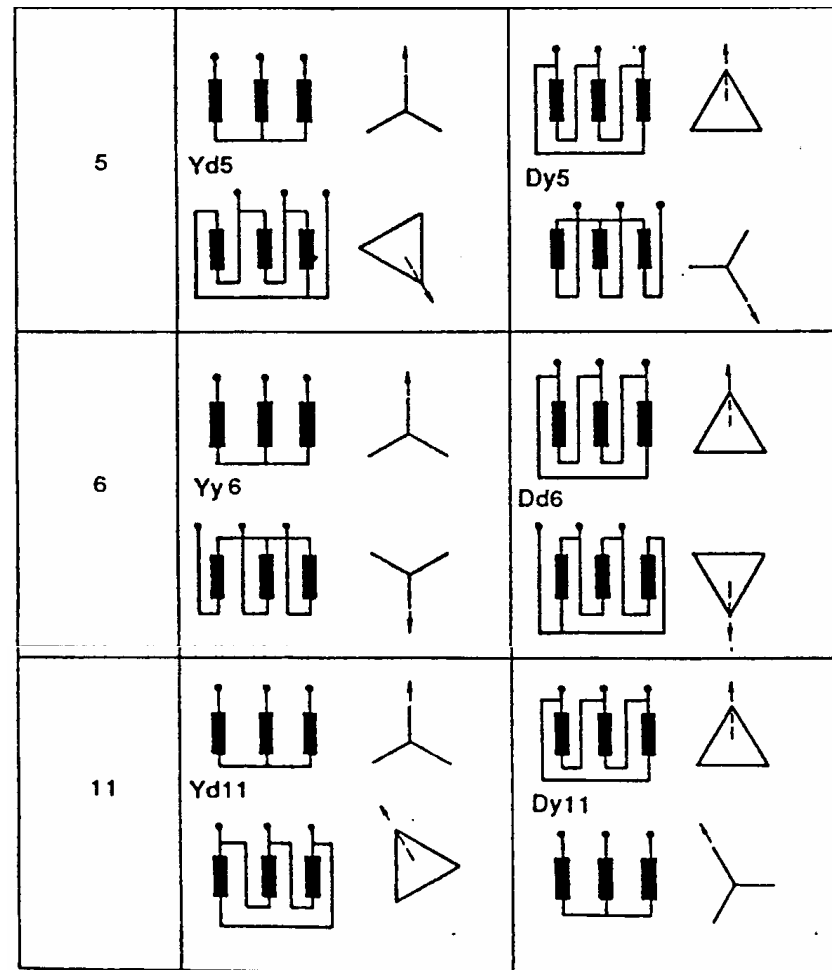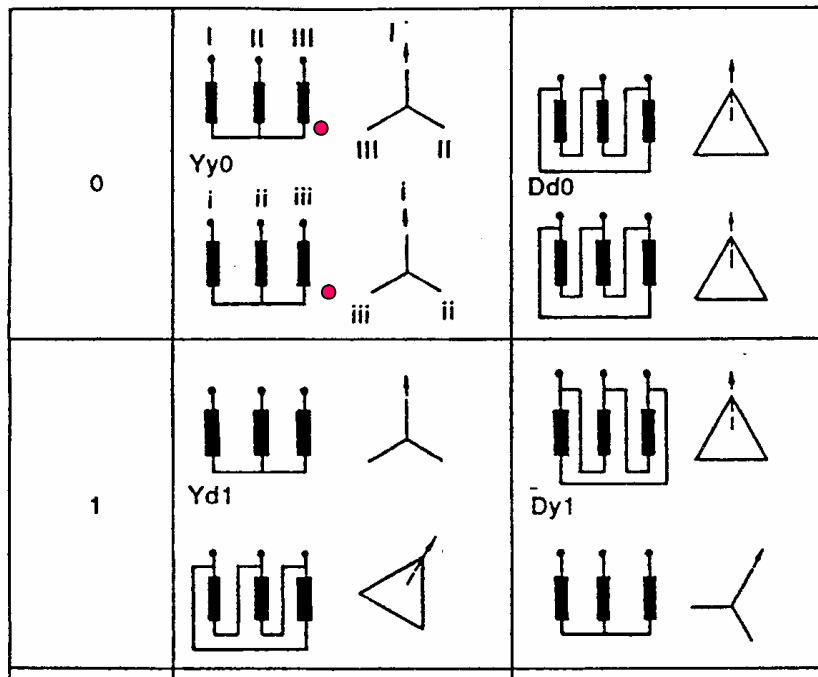
## Frequently used vector groups (IEC 60076-1)




## Finding the vector group by using the clock principle

---


Proceed in the following steps:

- 1.** Starting on the high voltage winding, the phase connection terminals are numbered with 0, 4, 8 (always  $4 \times 30^\circ = 120^\circ$  phase shift).
- 2.** The opposite end of each winding is labelled with a number incremented by +6 relative to the phase connection ( $6 \times 30^\circ = 180^\circ$ ).
- 3.** The secondary windings are numbered the same. In this context it is assumed that the polarity of the windings is the same in the diagram. (If in doubt, polarity marks may also be applied.)
- 4.** The phase connection is labelled with the average value of the corresponding terminal designations belonging to the winding terminals connected to this phase terminal, e.g.  $(6+4)/2 = 5$
- 5.** The difference between the high and low voltage side terminal numbers of same phases corresponds each with the vector group number, being Yd5 in this case.
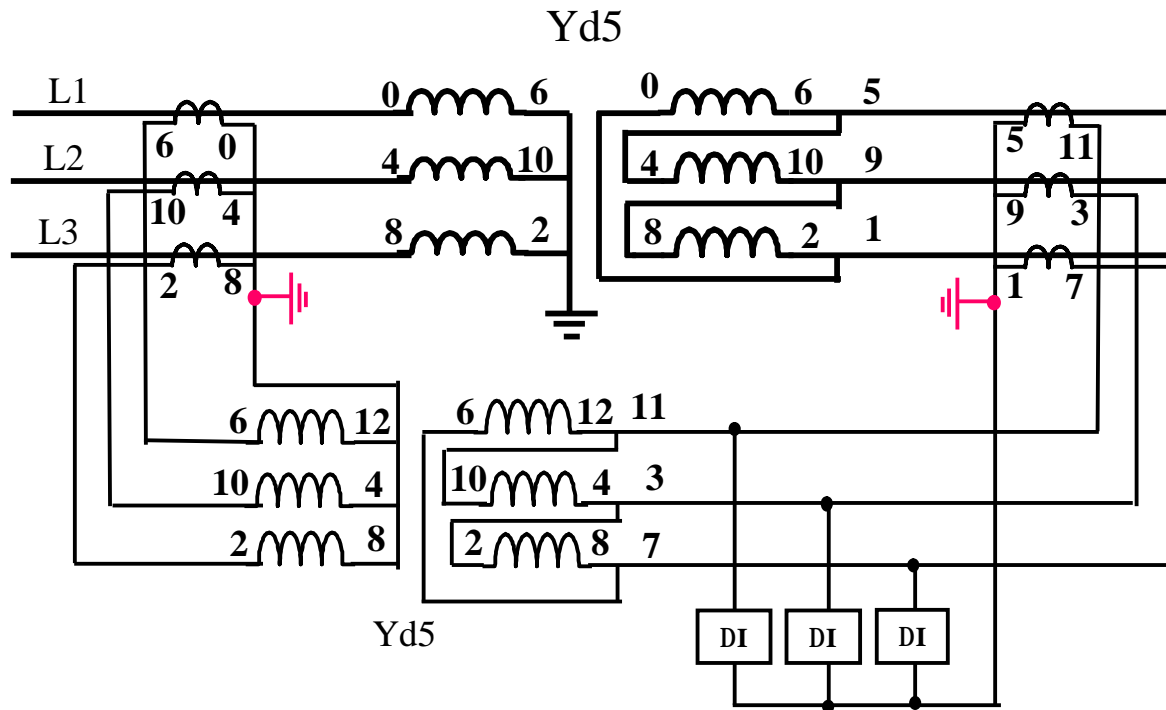
# Checking the connections of transformer differential protection using the clock-wise notation method



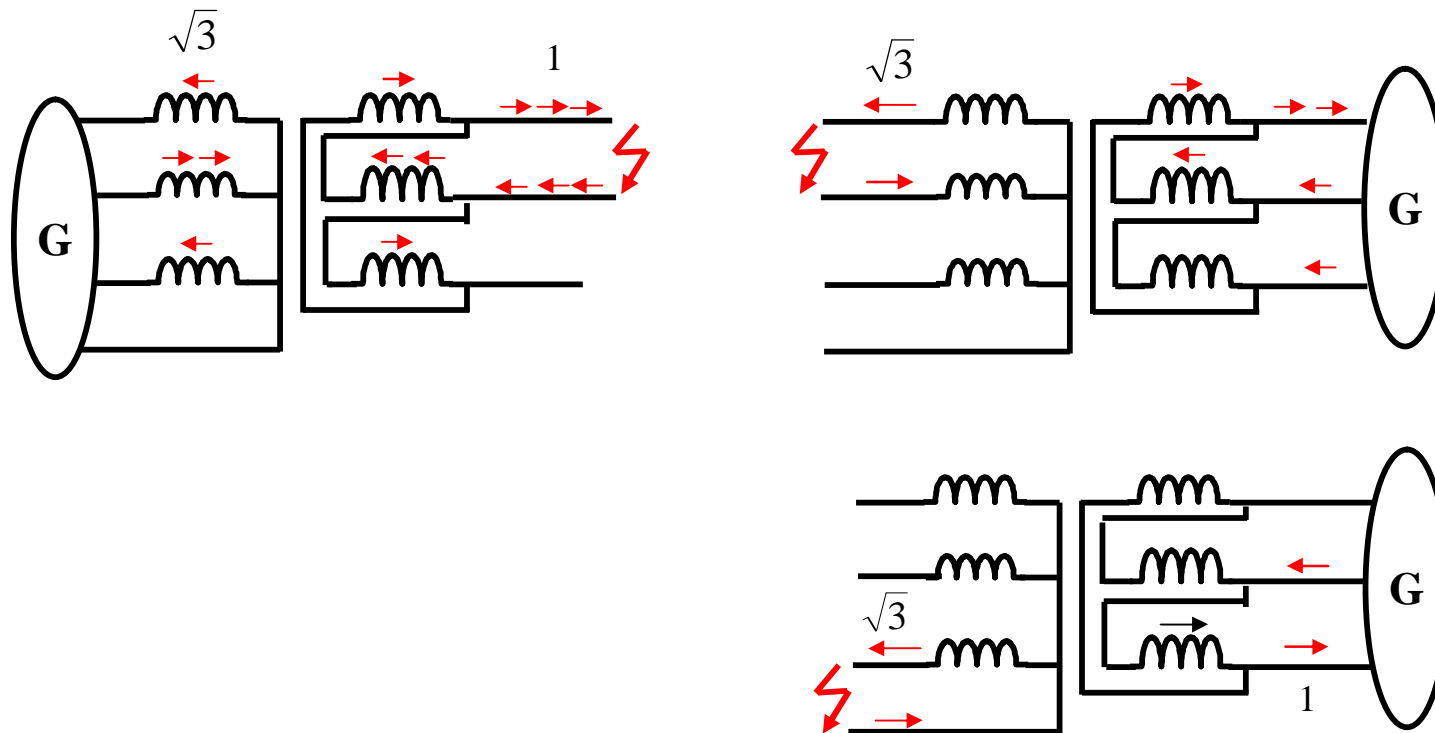
# Current distribution in Y- $\Delta$ -transformer circuits for different external fault types





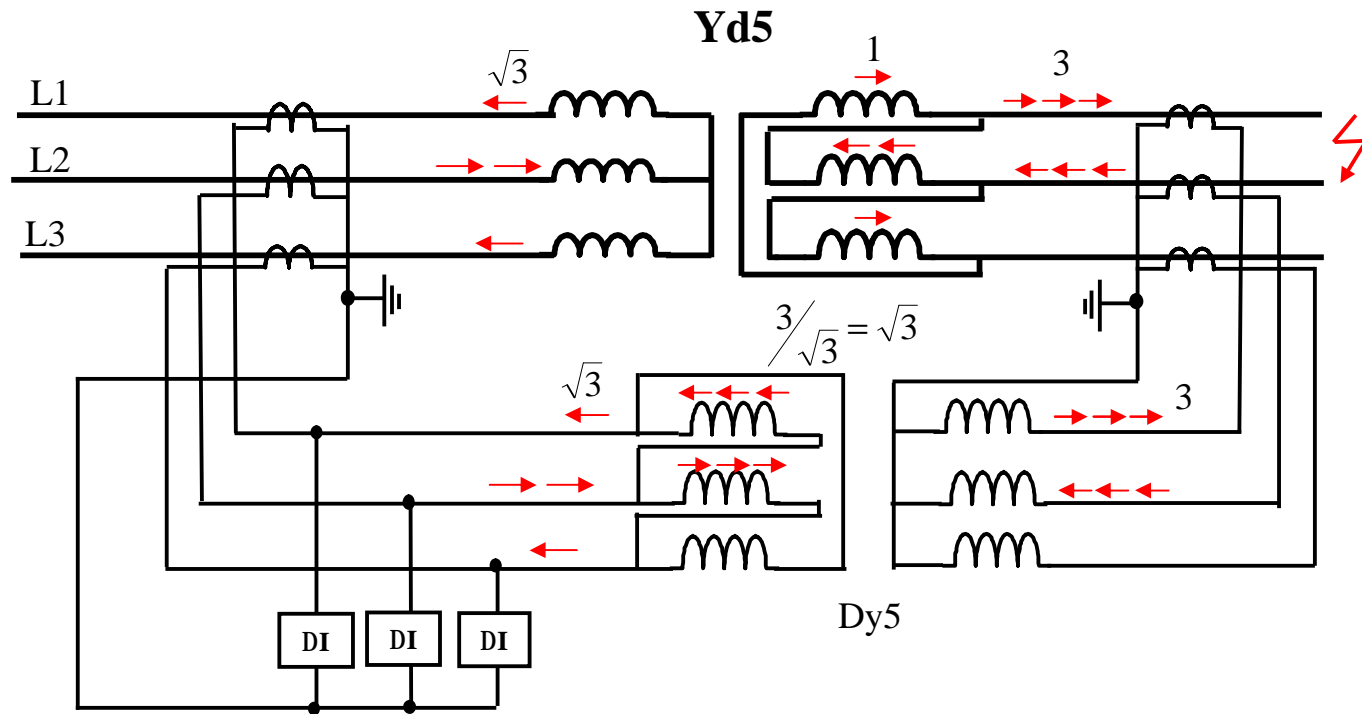
# Checking the connections of transformer differential protection using the arrow method (two-phase fault)


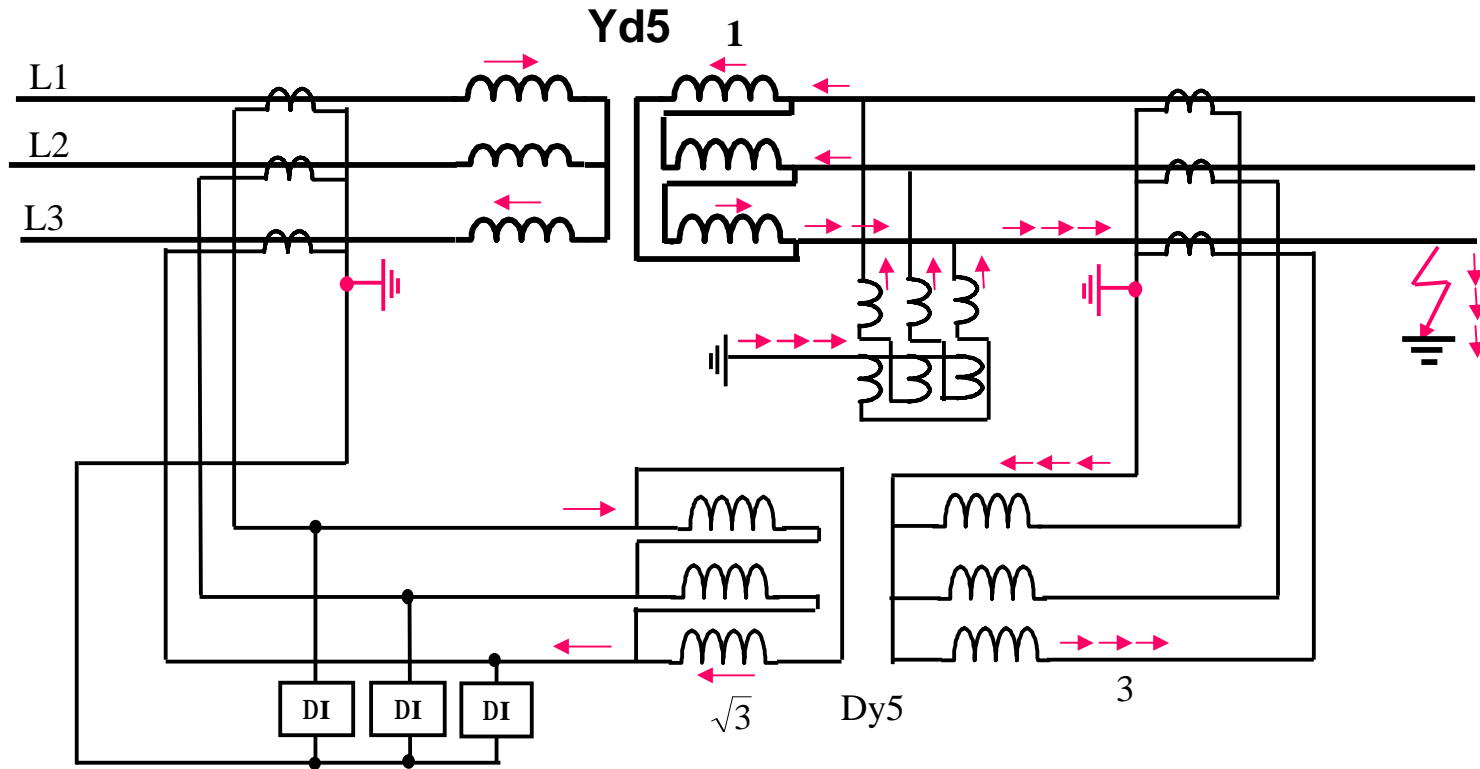
# Checking the connections of transformer differential protection using the arrow method (single-phase earth fault)






# Digital Differential Protection Communications

Gerhard Ziegler


**SIEMENS**
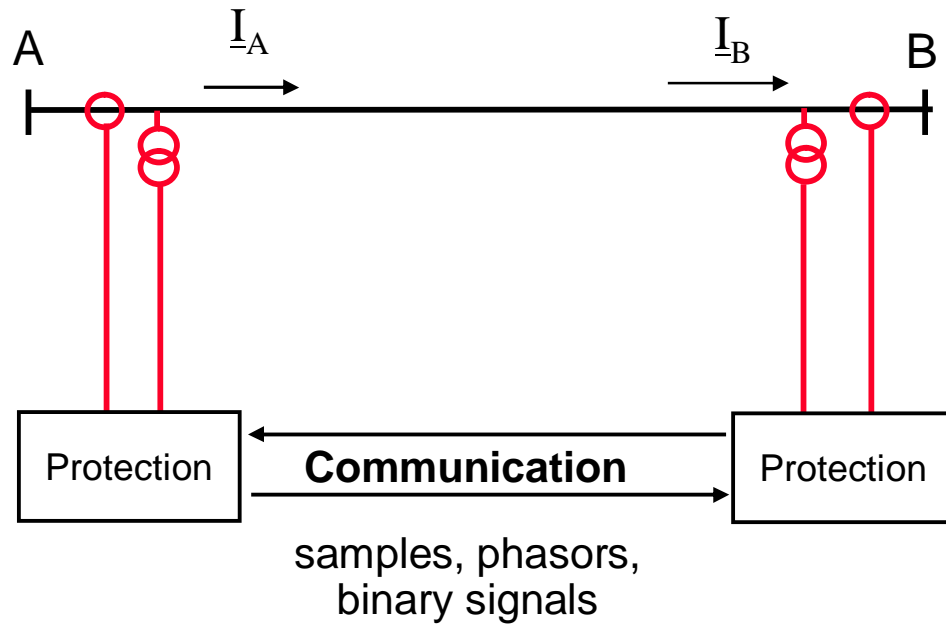
# Comparison protection

Absolute selectivity by using communication



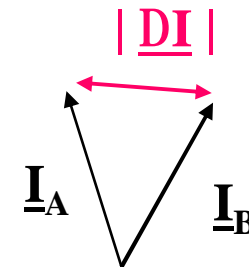- **Directial comparison**  
distance protection  
Exchange of YES/NO signals  
(e.g. fault forward / reverse)
- **Current comparison (phasors)**  
differential protection



$$|\underline{\Delta I}| = |\underline{I}_A - \underline{I}_B| > I_{pick-up}$$

## Signal transmission channels for differential relaying

---

### Pilot wires

- AC (50/60 Hz), voice frequency and digital communication (128 - kbit/s)
- for short distances (< about 20 km)
- influenced by earth short-circuit currents!


### Optical fibres

- wide-band communication (n · 64 kbit/s)
- digital signal transmission (PCM)
- up to about 150 km without repeater stations
- noise proof

### Digital microwave channels 2 - 10 GHz

- wide-band communication (n · 64 kbit/s)
- digital signal transmission (PCM)
- up to about 50 km (sight connection)
- dependent on weather conditions (fading)
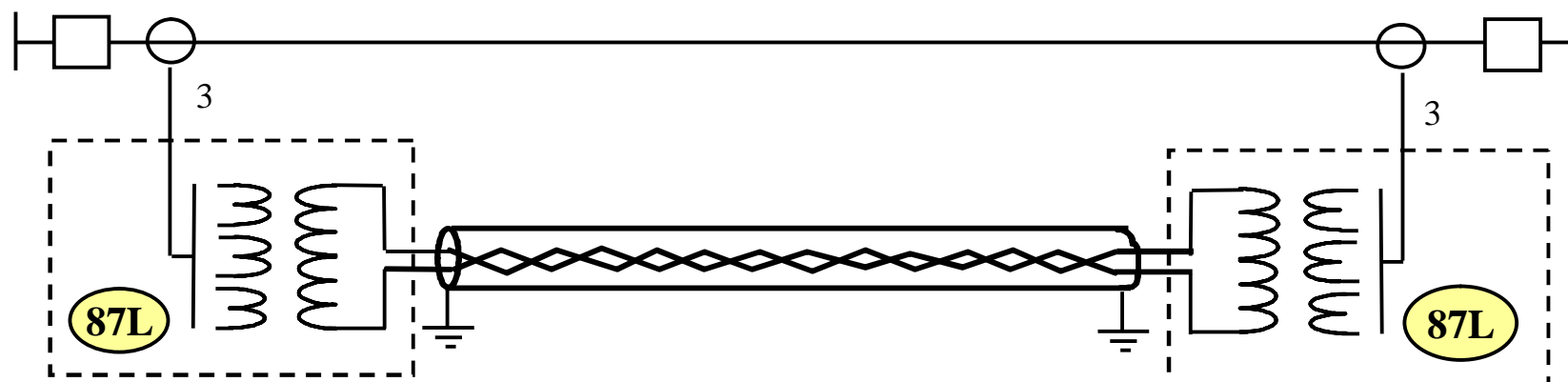
## Analog pilot wire differential relaying




- Pilot wires are normally operated insulated from earth
- Voltage limiters (glow dischargers) connected to earth, as used with telephone lines, are not allowed!


# Relay-to-Relay pilot wires communication

## New technology on existing (copper-) pilots

**Traditional:**

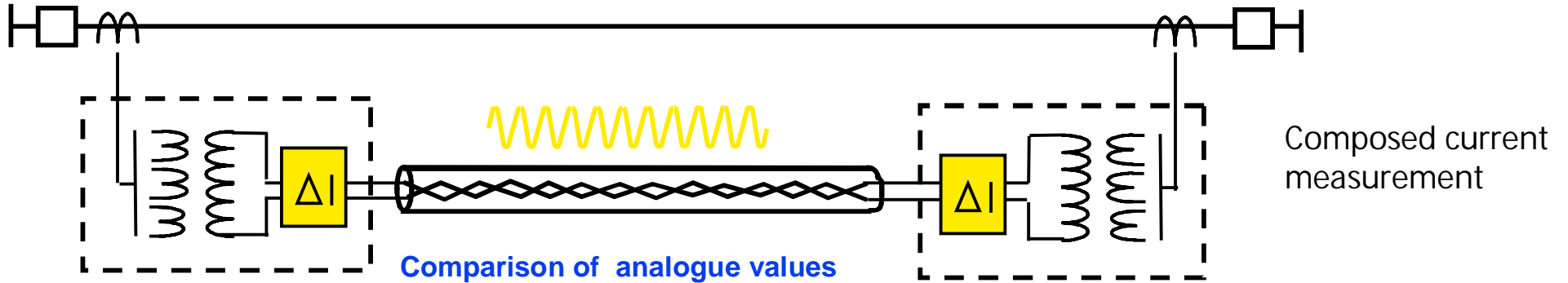


**Modern:**

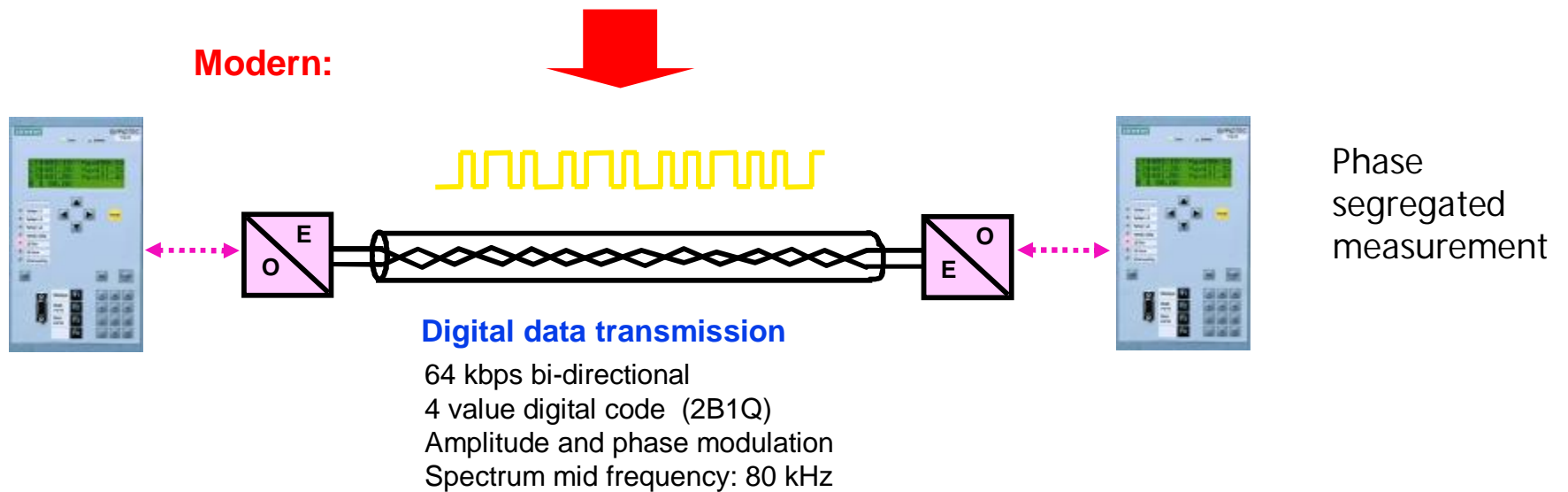


# Wire pilot cables
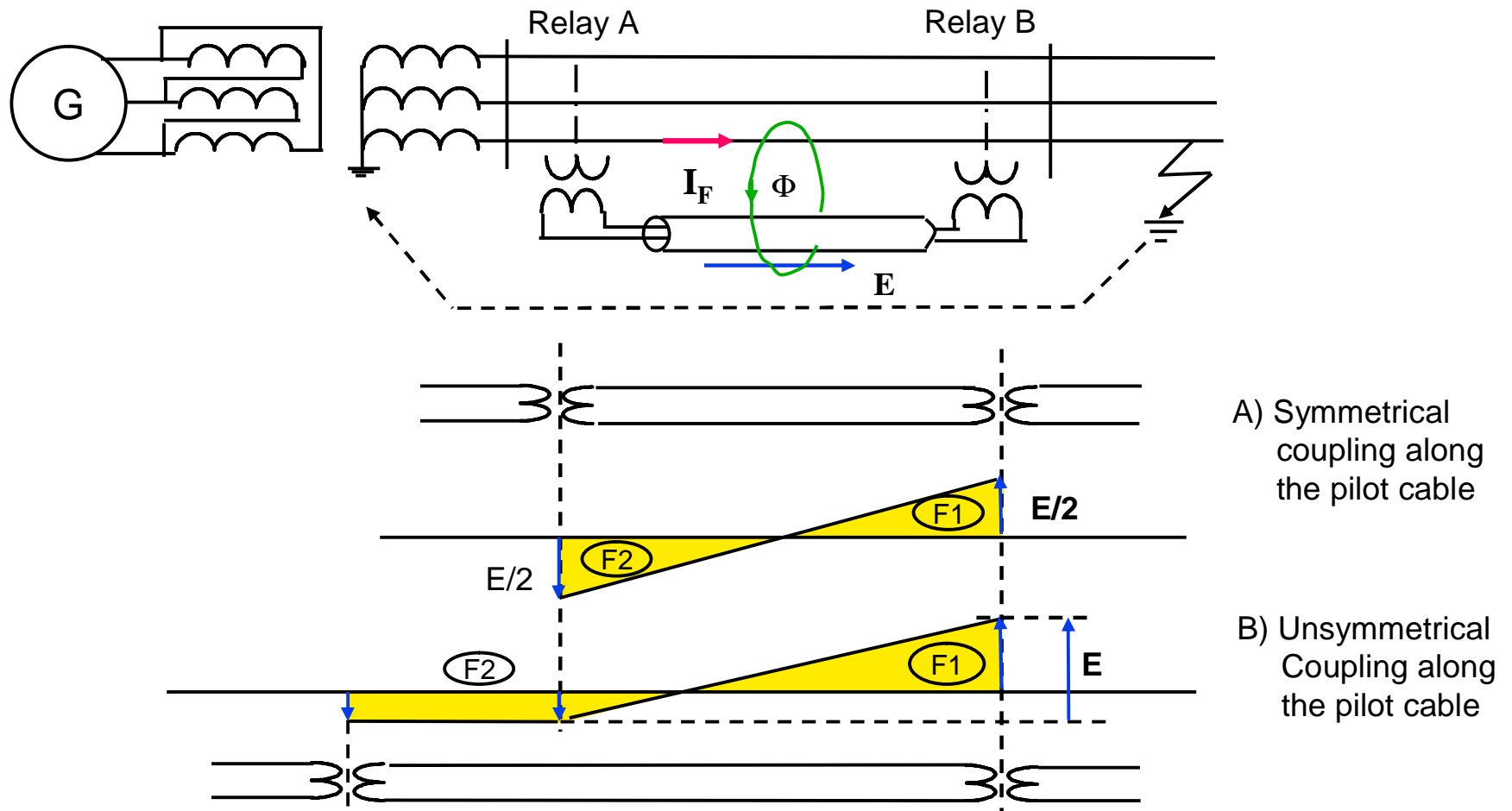
## Longitudinal voltage induced by earth currents




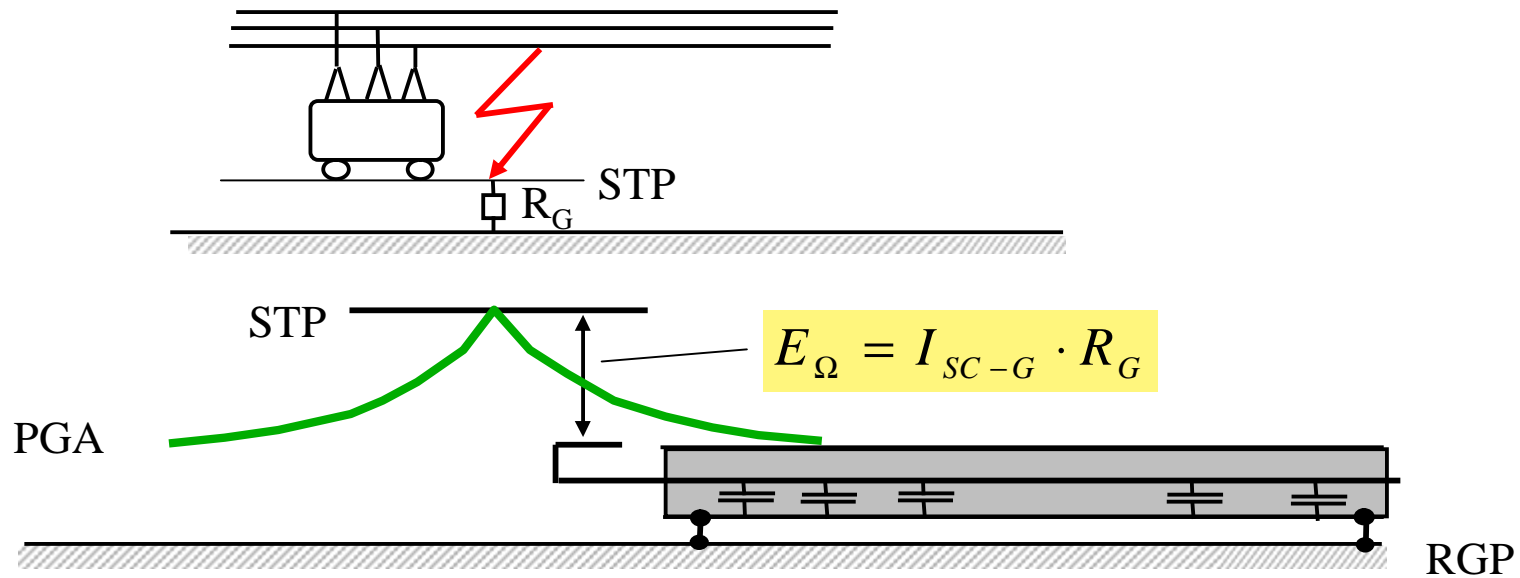
# Disturbance voltage caused by rise in station potential




Legend:

- $R_G$  station grounding resistance
- STP station potential
- PGA potential gradient area
- RGP remote ground potential
- E station potential rise against remote ground (ohmic coupled disturbance voltage)

# HV insulated protection pilot cable (example)


core diameter mm	pilot resistance		pilot capacitance nF/km	test voltage (r.m.s. value) kV				
	Core Ω/km	Loop Ω/km		core-core	core-shield	triple core to triple core	pair to pair	pair to triple core
1,4	11,9	---	---	2,5	8	8		
0,8	---	73,2	60	2	2		2	8

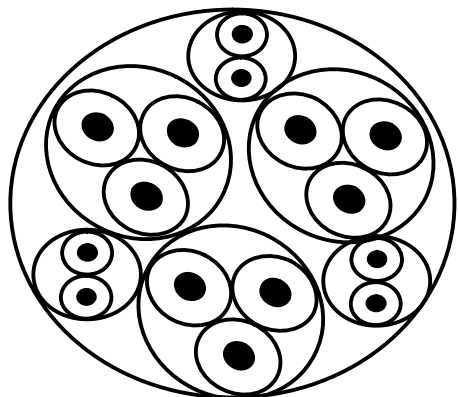

Symmetry: better  $10^{-3}$  (60 db) at 800/1000 Hz  
 better  $10^{-4}$  (80 db) at 50/60 Hz  
 $(U_q < 10^{-4} \cdot U_l)$

# American practice
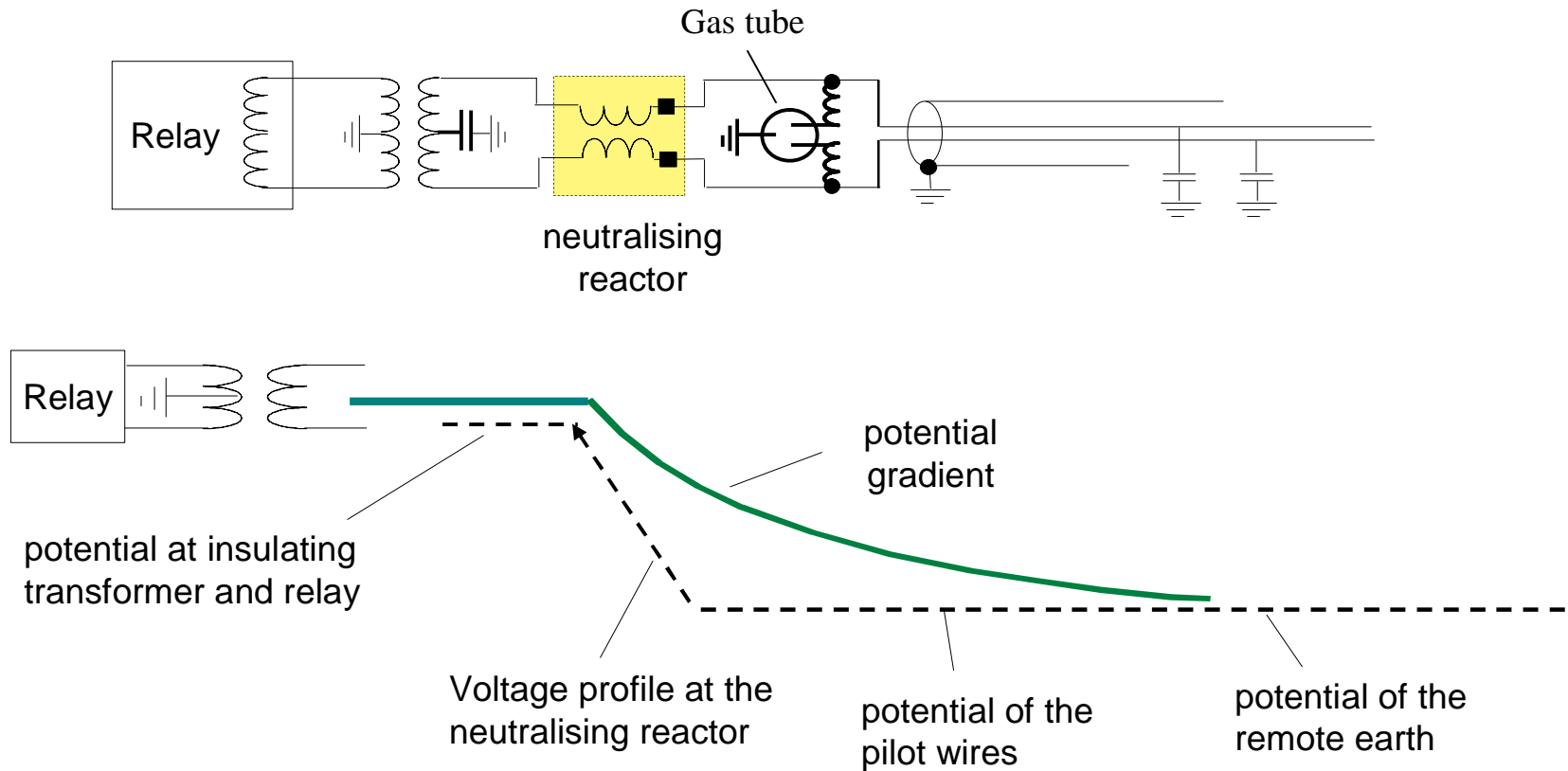
## Neutralising reactor to compensate potential rise at the station




## Optic fibre (OF) Cable

---



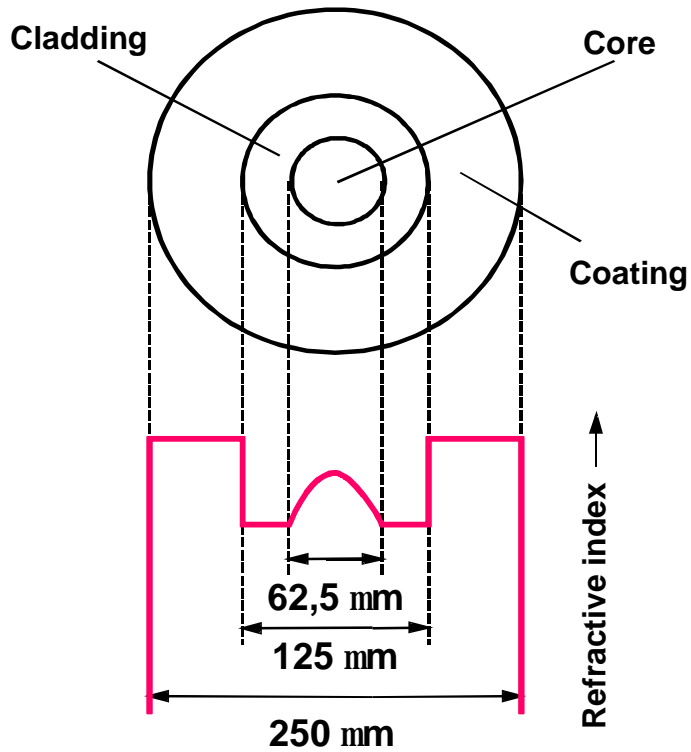
# Optic fibers and connectors

**Multi-mode fiber (IEC 793-2)  
Type 62.5 / 125 mm  
for 850 and 1300 nm**



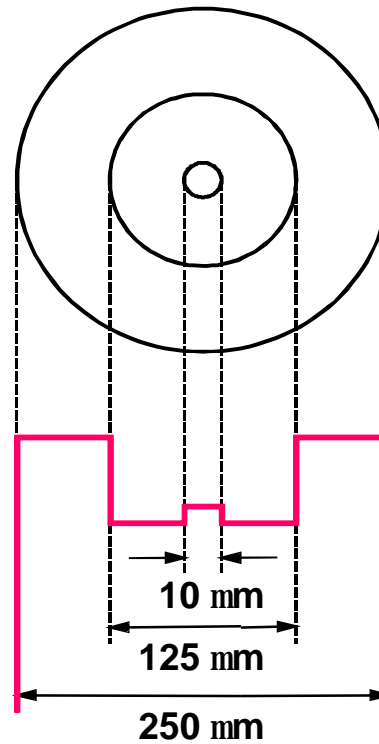**Mono-mode fiber (IEC 793-2)  
Type 10/125 mm  
for 1300 and 1550 nm**




ST connector




LC connector


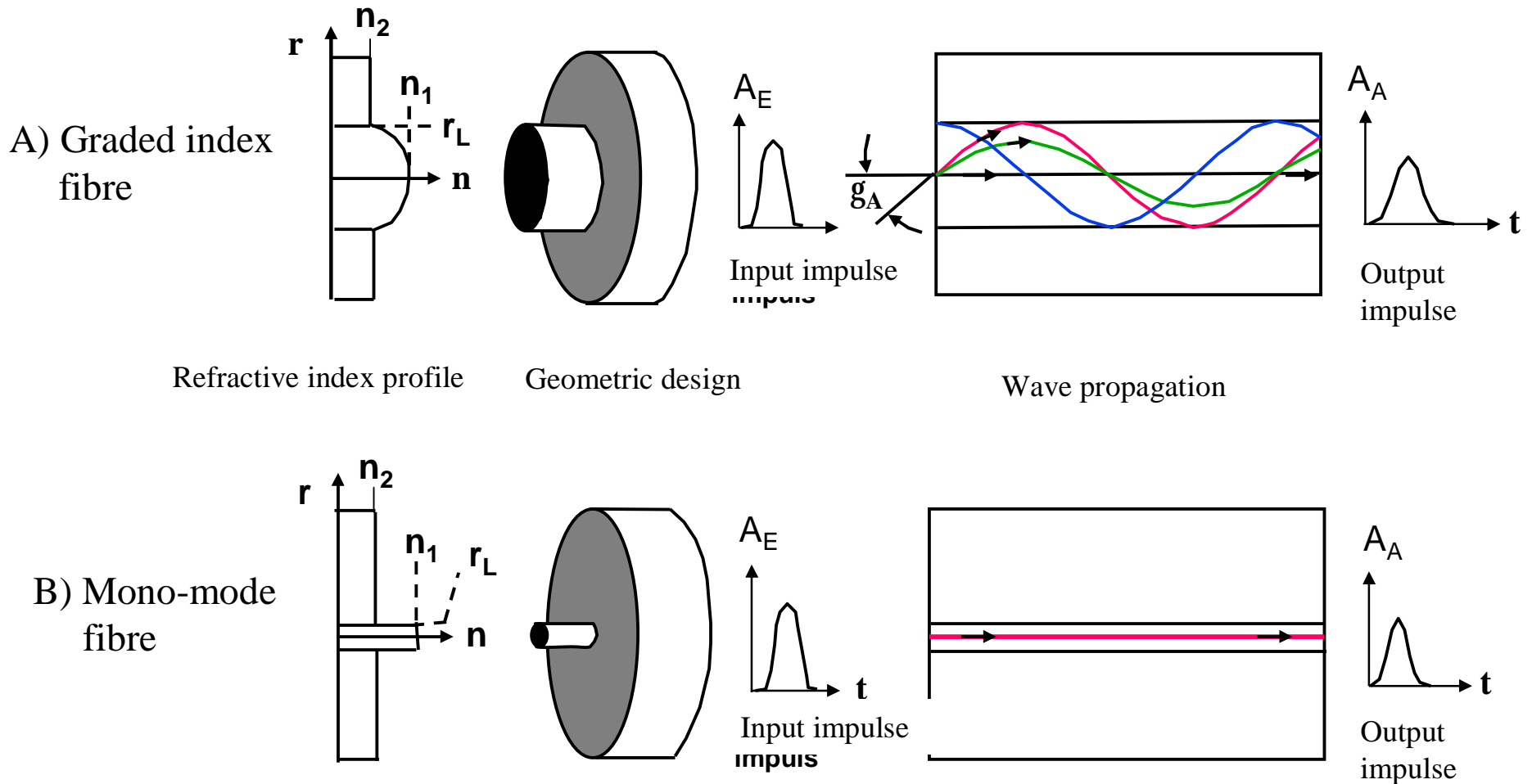
# Optic fibres: Principle of light wave propagation



# Optic attenuation of a mono-mode fibre

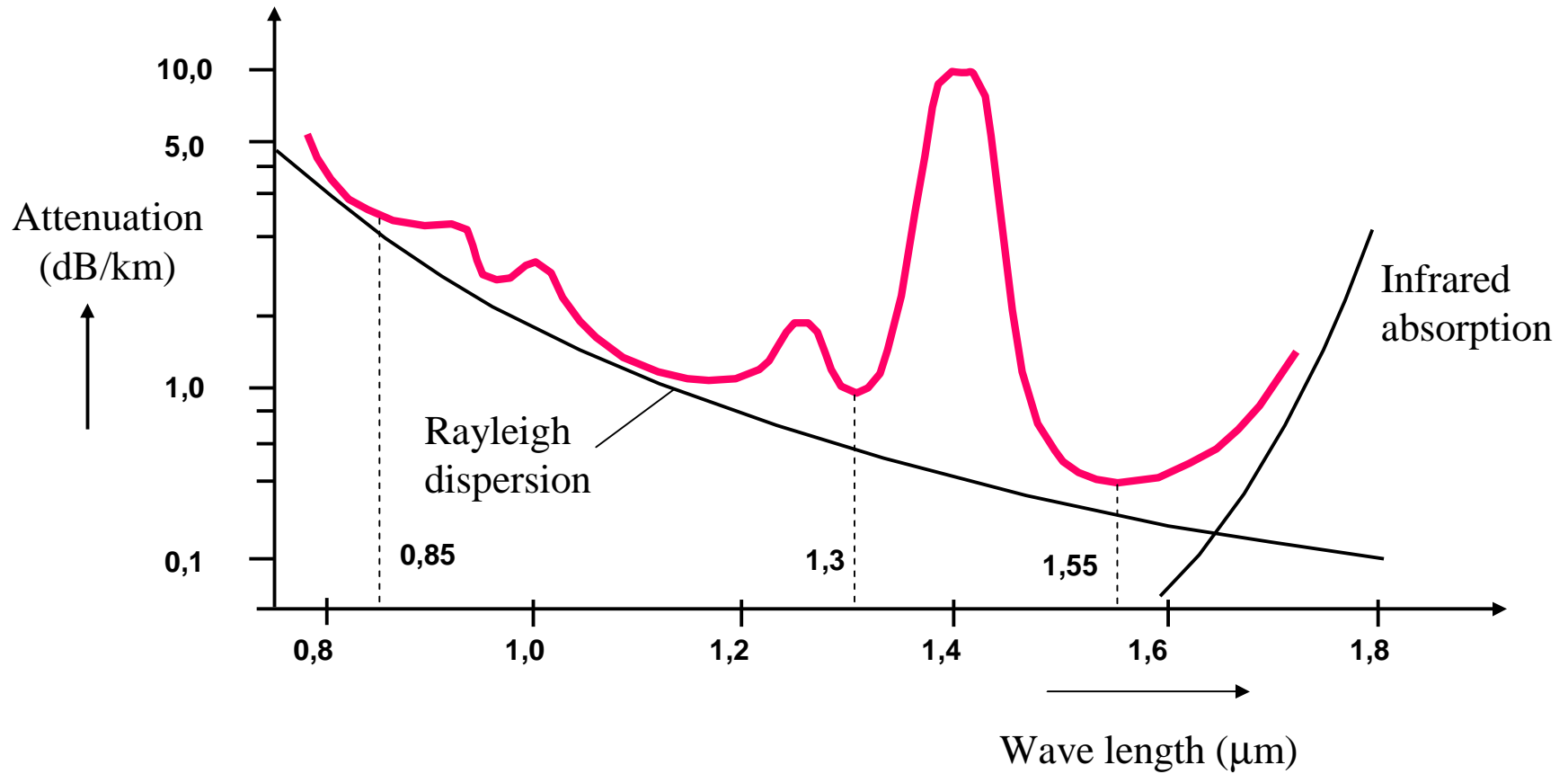

# Optic fibre connections: Coarse planning rules

Optic component:		Attenuation:
Mono-mode fibre	at 1300 nm	$\alpha_{OFC} = 0.45 \text{ dB/km}$
	at 1550 nm	$\alpha_{OFC} = 0.30 \text{ dB/km}$
Gradient fibre	at 850 nm	$\alpha_{OFC} = 2,5 \text{ to } 3,5 \text{ dB/km}$
	at 1300 nm	$\alpha_{OFC} = 0.7 \text{ to } 1.0 \text{ dB/km}$
Per splice		$\alpha_{SPL} = 0.1 \text{ dB}$
Per connector	FSMA	$\alpha_{CON} = 1.0 \text{ dB}$
	FC	$\alpha_{CON} = 0.5 \text{ dB}$
Reserve		$\alpha_{RES} = 0.1 \text{ to } 0.4 \text{ dB/km}$

Total attenuation of the OF cable system:

$$a_{TOT} = l \cdot a_{OFC} + n \cdot a_{SPL} + 2 \cdot a_{CON} + l \cdot a_{RES}$$



# Optic Fibre signal transmission system: Calculation example

---

Task: Optic fibre signal transmission device 7VR500  
Estimation of maximum reach

Given: Device data: Sending power of laser diode:  $\alpha_S = -14$  dB  
Minimum reception power:  $\alpha_E = -46$  dB  
Optic wave length: 1300 nm  
The optic fibre cable is shipped in sections of each 2 km.  
For reserve, 0.2 dB/km have been chosen.


Searched: Maximum distance that can be bridged

Solution: The cable length is:  $l = x \cdot 2$  km  
The number of splices is:  $n = x - 1$   
The admissible system attenuation:  $-14 - (-46) = 32$  dB  
Therefore:

$$32 \text{ dB} = x \cdot 2 \text{ km} \cdot 0,45 \frac{\text{dB}}{\text{km}} + (x - 1) \cdot 0,1 \text{ dB} + 2 \cdot 0,5 \text{ dB} + x \cdot 2 \text{ km} \cdot 0,2 \frac{\text{dB}}{\text{km}}$$

we get:  $x = 22$  and  $l = 44$  km

## Radio (Micro-wave) Signalling

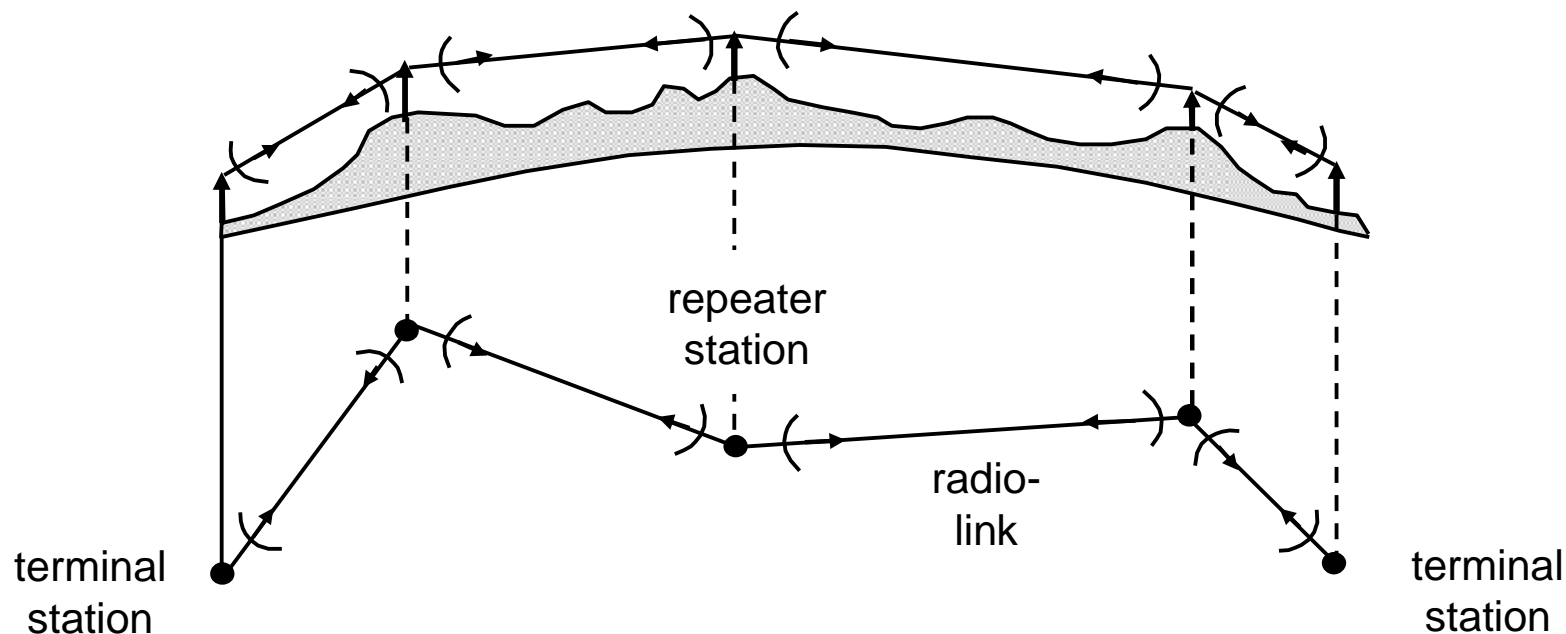

- Line-of-sight path (up to about 50 km without repeater)
- 150 MHz to 20 GHz,  $n$  times 4 kHz channels analog and  $n$  times 64 (56) kbit/s digital (PCM)
- Advantage: Independent of line short-circuit and switching disturbances
- Disadvantage: Fading and reflections during bad weather conditions  
Additional pilot links necessary to sending/receiver stations


## Digital communication

---


- u Wide-band communication via optic fibre or digital microwave
- u n times 64 (56) kbit/s channels
- u pulse code modulation (PCM)
- u transmission via dedicated channels or communication network
- u access through time division multiplexers
- u interface standard for synchronous data transmission:  
CCITT G.703 or X.21 (wired connection)
- u interface standard for asynchronous data transmission:  
V.24/V.28 to CCITT or RS485 to EIA (wired connection)

# Function sequence of message transmission

## Sending side

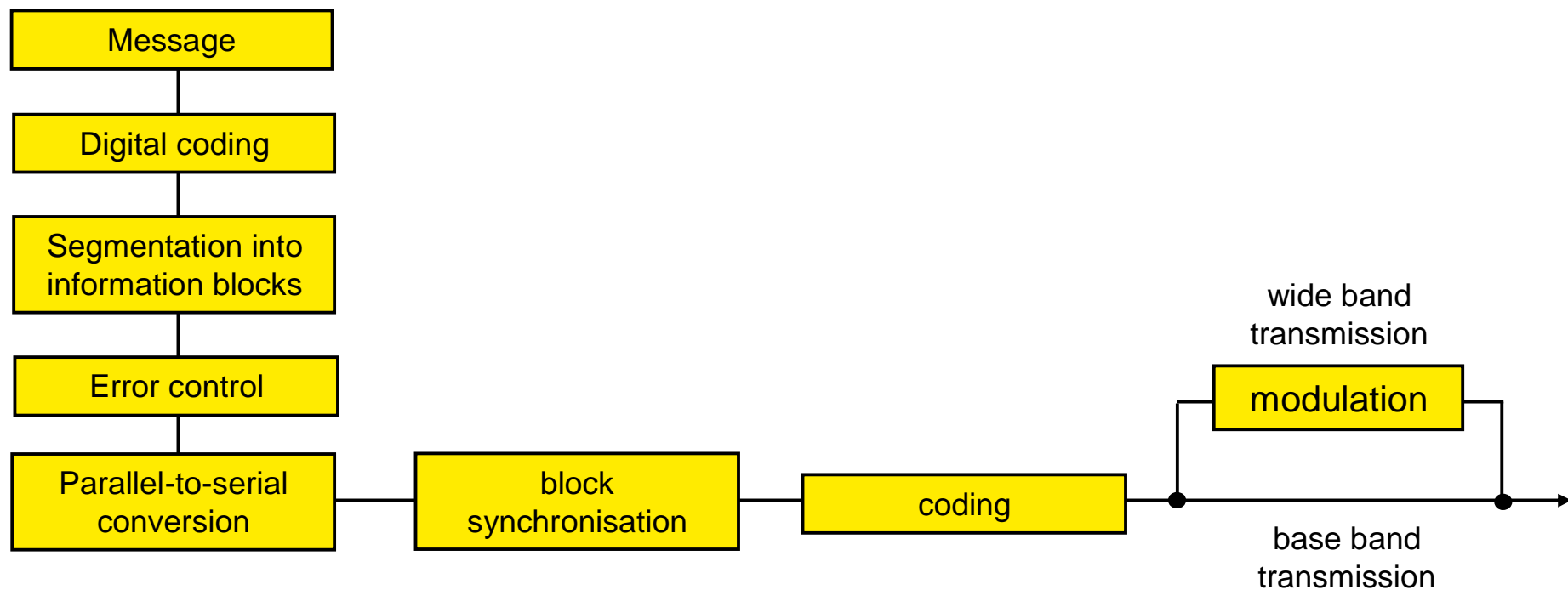
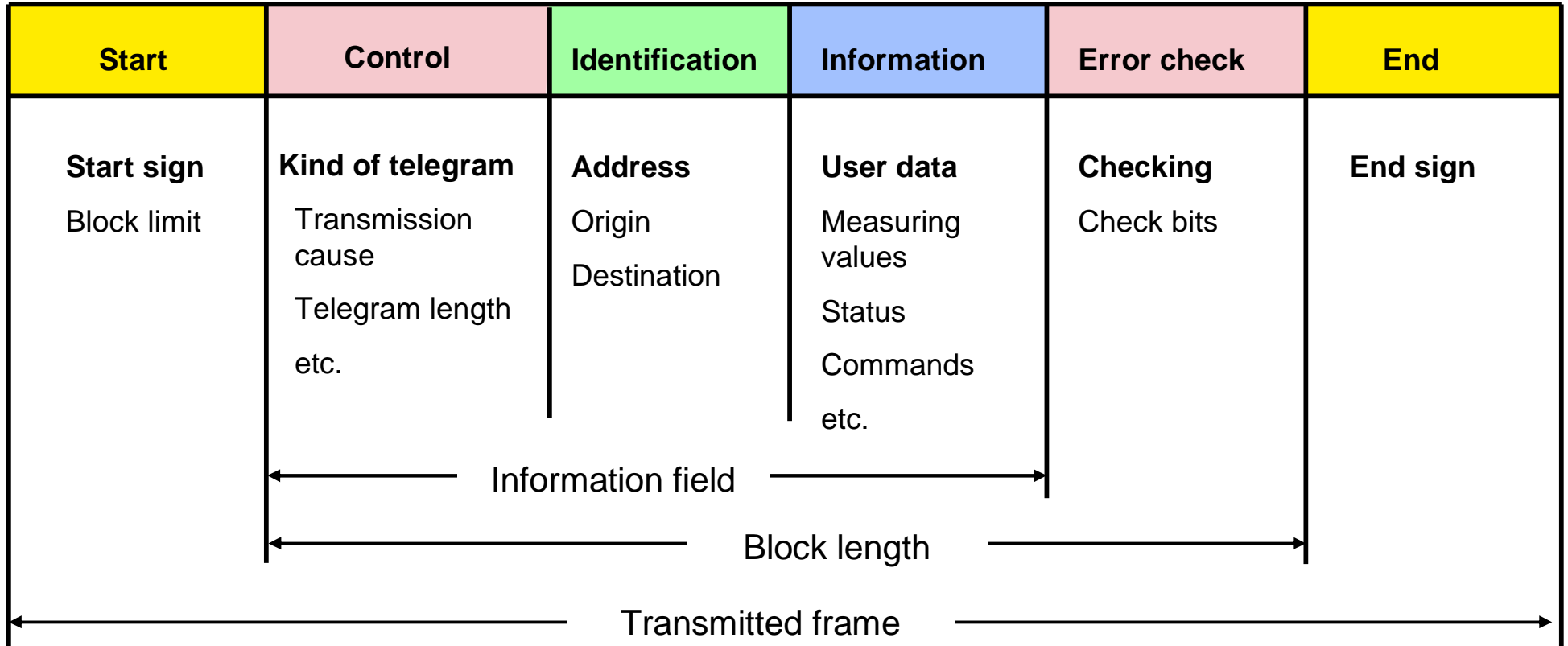
## Structure of a remote control telegram




# Digital communication

## Synchronous transmission mode

---


- all bits follow a fixed time frame
- synchronism between sending and receiving station. (separate clocking line or signal codes with clock regain)
- block (frame) synchronising by opening and closing flags
- suitable for high data rates
- used protocol: HDLC (high-level data link control)
- cyclic redundancy check (CRC) or frame check sequence (FCS) by 16 or 32 added check-bits (probability of non-detected telegram block errors:  $10^{-5}$  (CRC-16) or  $10^{-10}$  (CRC-32))
- used for high speed teleprotection

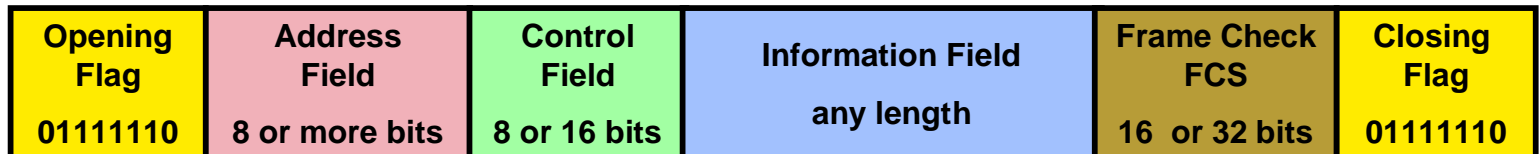HDLC telegram frame  
format  
to ISO 3309:




# Multiplexing


## Frequency Multiplexing

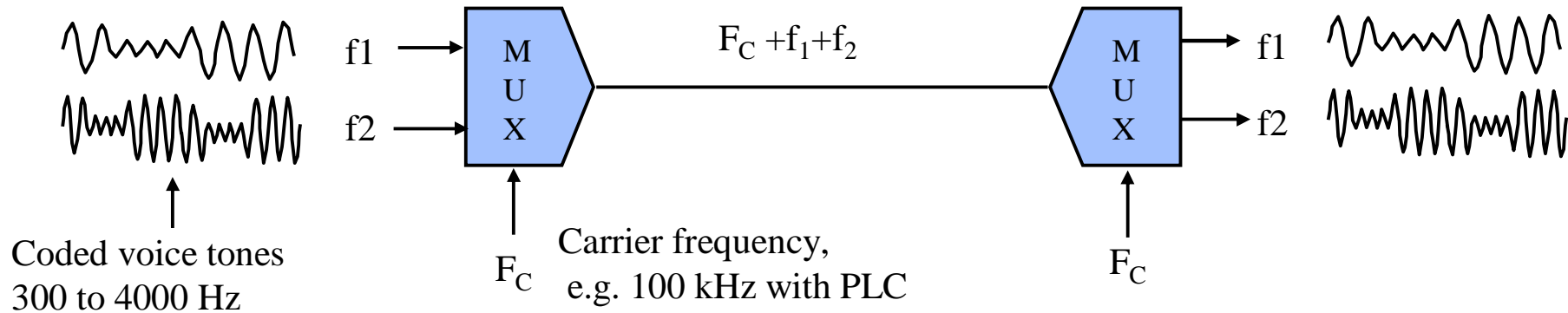

## Time Division Multiplexing (TDM)

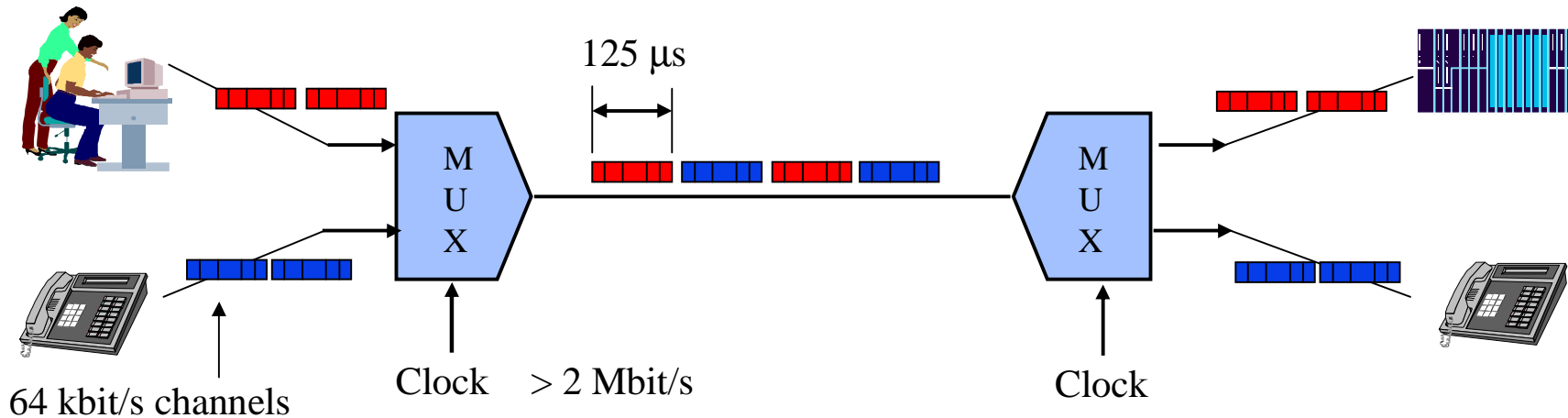

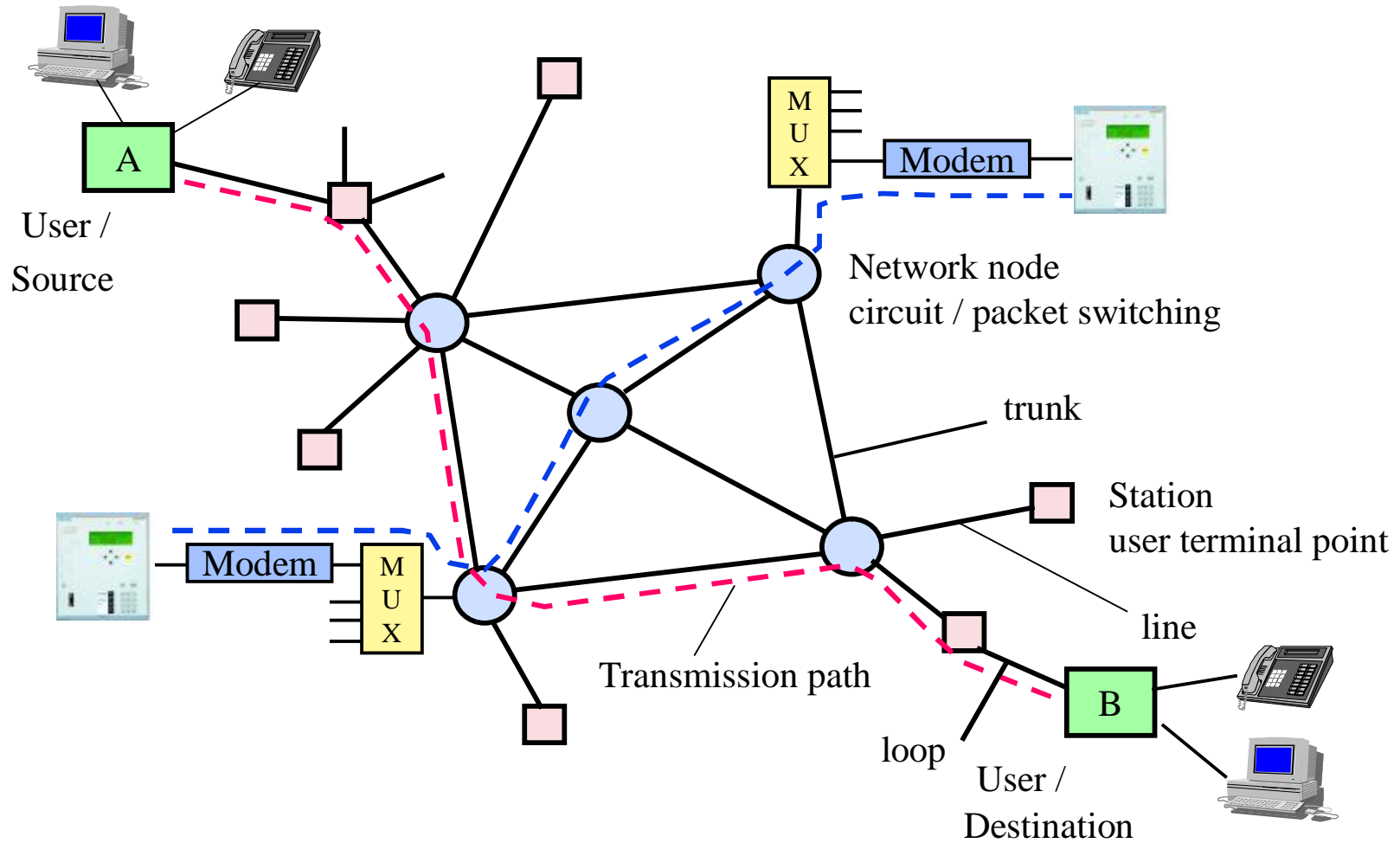
# Communication through transmission networks




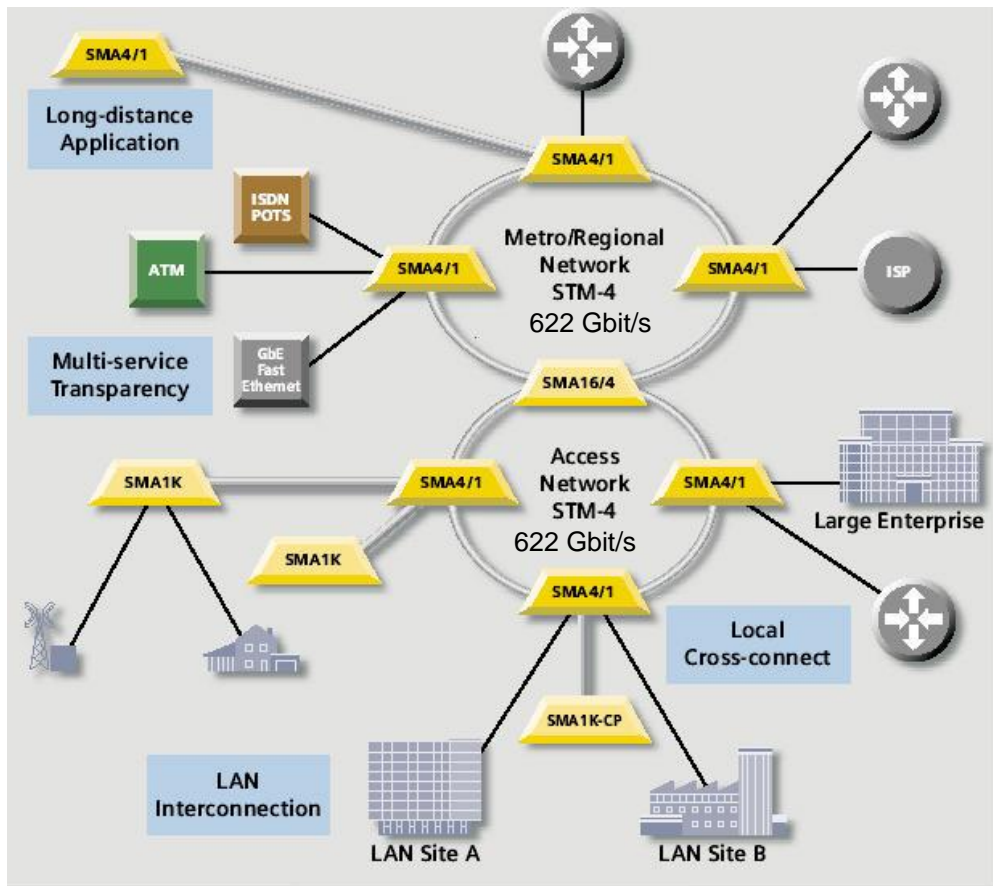
# Structure of a modern data communication network



- ∅ Networks are plesiochronous (PDH), synchronous (SDH) or asynchronous (ATM)
- ∅ Data terminal devices (e.g. relays) are synchronised through the network
- ∅ Rings guarantee redundancy.
- ∅ Data of different services (e.g. telephone and protection) are commonly transmitted (time multiplexed)
- ∅ Protection relays must be adapted to the given network conditions (e.g. changing propagation time due to path witching).

POTS: Plain Old Telephone Services

ISDN: Integrated Services Digital Network

STM-n: Synchronous Transport Module level n

SMA: Synchronous Module Access

ATM: Asynchronous Transmission Mode

ISP: Internet Service Provider

## Comparison of Switching Methods

---

### Circuit Switching

The physically assigned channel is established before and disconnected after communication

POT (Plain old telephony), ISDN

Digital networks on basis of PCM with plesiochronous digital hierarchy (PDH)

Reliable and fast transmission possible when connection is established.

Circuit establishment requires a free channel from A to B

Connection occupies channel also when no data is exchanged

Deterministic data transmission (fixed data transmission time per channel)

### Packet switching

Data stream is segmented to packets

Transmission runs connection-oriented or connection-less


Synchronous digital hierarchy (SDH), ATM Backbone

Channel not occupied during whole connection time

Channels can be used quasi-simultaneously

Data transmission by principle time is random. SDH and ATM can provide virtual circuit-switched channels. However, **split path** signal routing may however result in unsymmetrical signal transmission times.


# SDH network: Split path routing

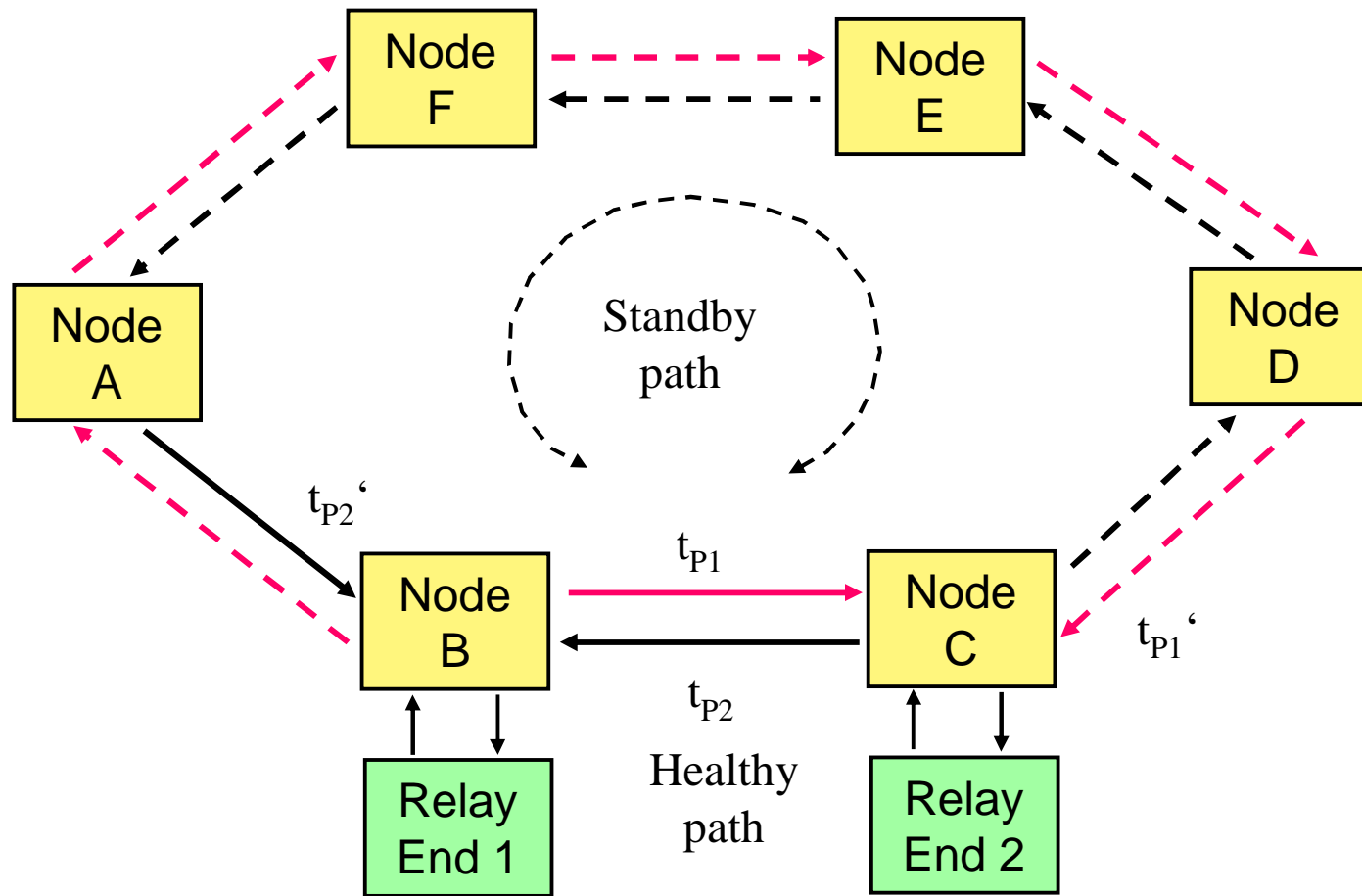

# Digital Transport Systems: Bundling of channels


## PDH Hierarchy

Plesiochronous (almost synchronous)

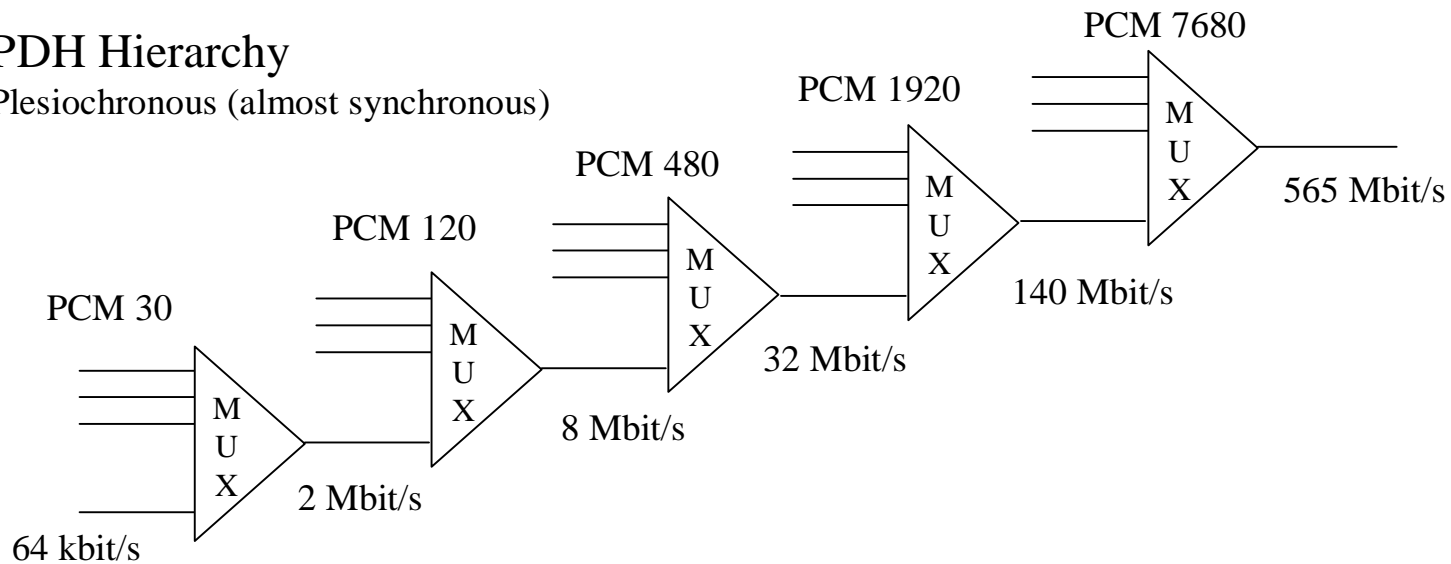

## SDH Hierarchy

Synchronous

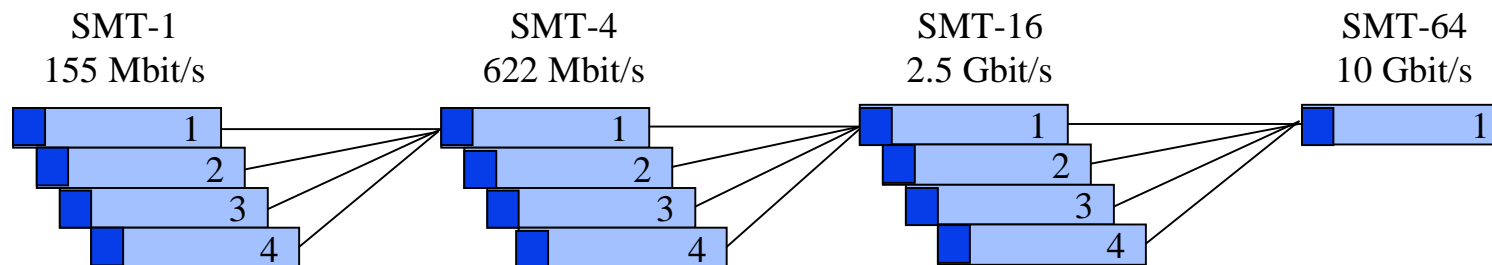

## PDH (Plesiochronous Digital Hierarchy)

---

### Multiplexing structure:

- ∅ Base rate 64 kbit/s (digital equivalent of analogue telephone channel)
- ∅ Equipments may generate slightly different bit rates due to independent internal clocks
- ∅ Bit stuffing is used to bring individual signals up to the same rate prior to multiplexing (Dummy bits are inserted at the sending side and removed at the receiving side)
- ∅ Intermediate inserting and extracting of individual channels is not possible, but the full multiplexing range has always to be run through.

Hierarchical level	Europe	USA
0	64 kbit/s	56 kbit/s
1	2'048 Mbit/s	1'544 Mbit/s
2	8'448 Mbit/s	6'312 Mbit/s
3	34'368 Mbit/s	44'736 Mbit/s
4	139'264 Mbit/s	139'264 Mbit/s

## SDH (Synchronous Digital Hierarchy)

### Multiplexing structure


- ∅ SONET (Synchronous Optical Network) first appeared in USA (1985)
- ∅ ITU-T (formerly CCITT) issued B-ISDN as world wide standard (1988)
- ∅ All multiplexing functions operate synchronously using clocks derived from a common source
- ∅ Designed to carry also future ATM

SDH		SONET		
STM level	Aggregate Rate	OC level	STS level	Aggregate Rate
STM-1	155,520 Mbit/s	OC-1	STS-1	51,840 Mbit/s
STM-4	622,080 Mbit/s	OC-3	STS-3	155,520 Mbit/s
SZM-16	2'488,320 Mbit/s	OC-12	STS-12	622,080 Mbit/s
STM-64	9'953,280 Mbit/s	OC-48	STS-48	2'488,320 Mbit/s
		OC-192	STS-192	9'953,280 Mbit/s


## ATM (Asynchronous Transfer Mode) and Broadband B-ISDN
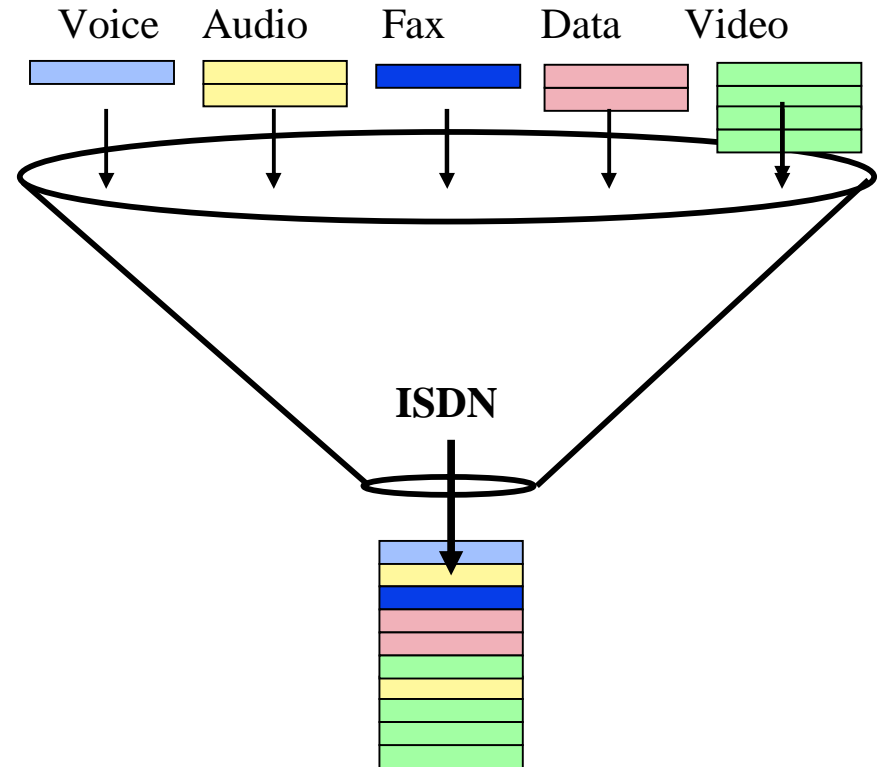
### Features of ATM:

- ∅ Synchronisation individually per packet
- ∅ Packets carry each complete address of destination so that each can be separately delivered (Datagrams, here called Cells)
- ∅ Information stream is segmented into cells that are 53 octets long
- ∅ ATM sets up a virtual switched connection and sends data along a switched path from source to destination
- ∅ Requirements on bandwidth, bounded delay and delay variation can be set by the user
- ∅ Single cells can be inserted or removed at the nodes, as required
- ∅ The predominant use is for net backbones



# TDM over optical fiber

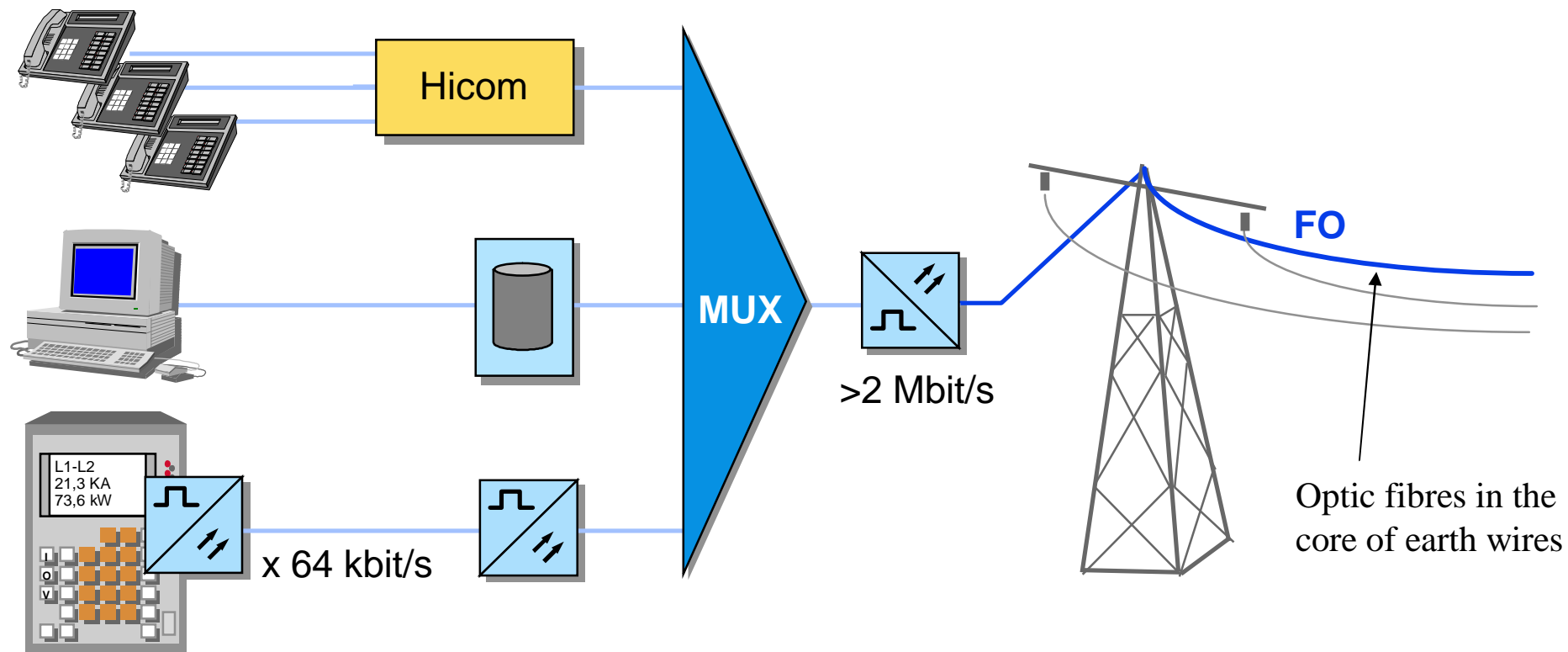



## Bit error rate (of data channels)

---

Bit error rate:

$$p = \frac{\text{number of faulty bits}}{\text{total number of sent bits}}$$

### Typical bit error rates of public services:

Telephone circuits	ca. $10^{-5}$
Digital data networks (Germany)	ca. $10^{-6}$ to $10^{-7}$
Coaxial cables (LAN)	ca. $10^{-9}$
Fiber optic communication	ca. $10^{-12}$



### Utility conditions (CIGRE SC34 Report 2001):

Fiber optic communication	ca. $10^{-6}$
Data networks (PDH, SDH, ATM)	ca. $10^{-6}$
Microwave	ca. $10^{-3}$

### Requirements acc. to CIGRE report:

Protection and control	
in general:	$< 10^{-6}$
Function guaranteed up to	$< 10^{-3}$ however downgraded (reduced operating speed)
Line differential protection	$< 10^{-6}$ and $< 10^{-5}$ during power system faults


# Error detection methods: Cyclic redundancy check

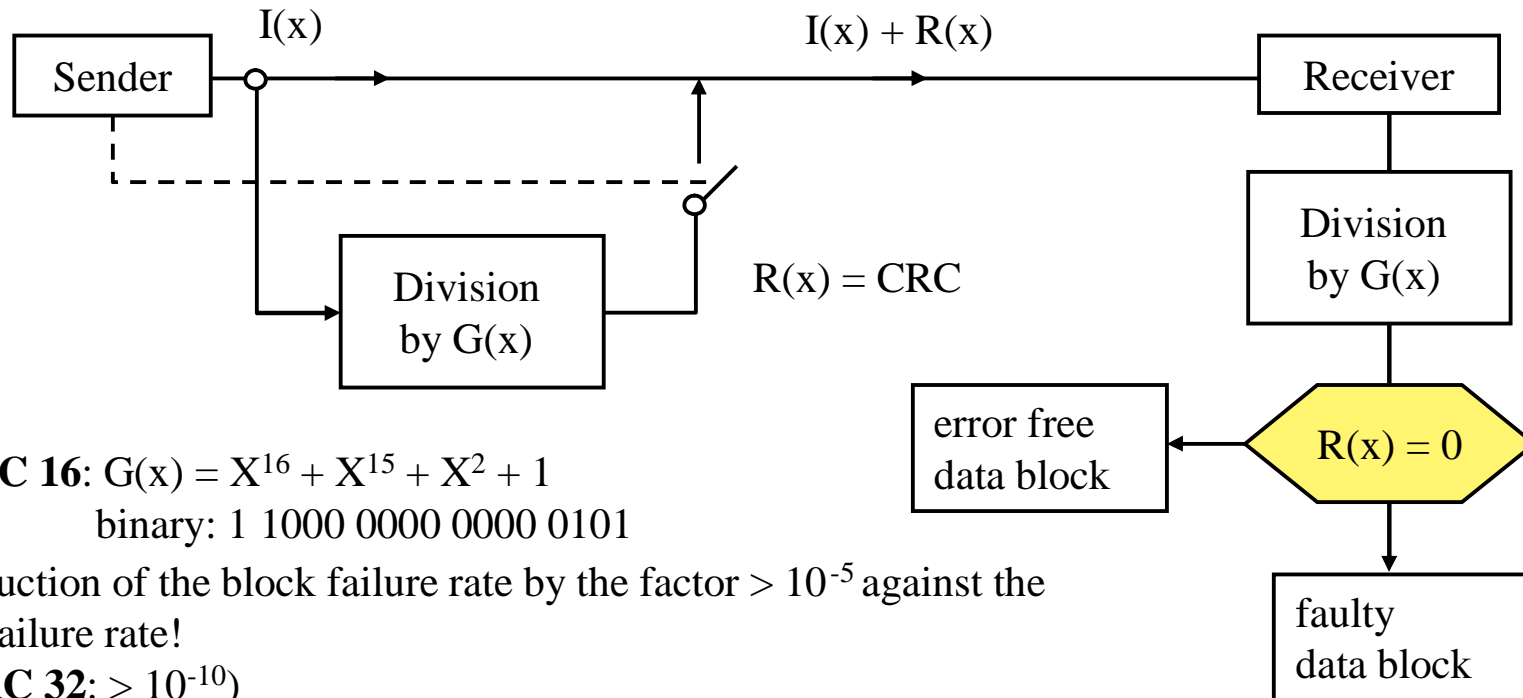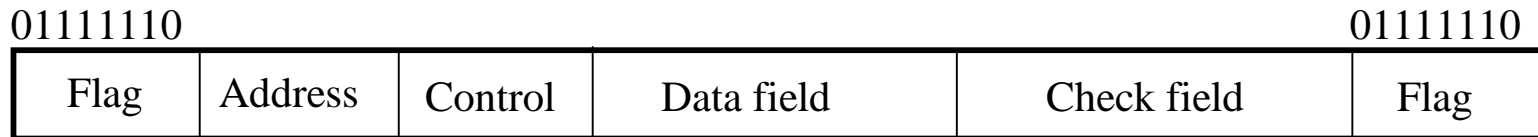

**CRC 16:**  $G(x) = X^{16} + X^{15} + X^2 + 1$   
 binary: 1 1000 0000 0000 0101

Reduction of the block failure rate by the factor  $> 10^{-5}$  against the bit failure rate!  
 (CRC 32:  $> 10^{-10}$ )
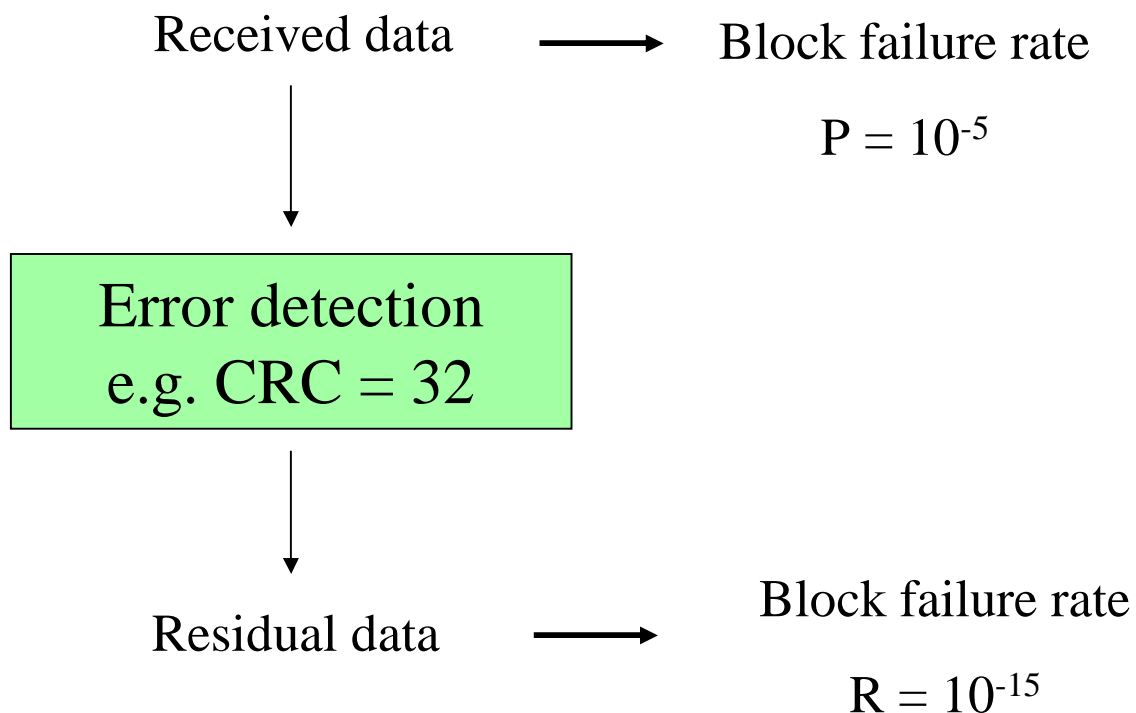
## Data integrity (line differential protection 7SD52/61)



## Residual error rate

---

Residual error rate: 
$$R = \frac{\text{number of not detected faulty telegrams (data blocks)}}{\text{total number of sent telegrams (data blocks)}}$$

Practical range of protection and control systems:  $R < 10^{-10}$  to  $10^{-15}$

Time between 2 **not** detected errors: 
$$T = \frac{n}{v \cdot R}$$

n= length of telegram (data block)  
v= transmission speed in bit/s


### Example:

Telegrams of n =200 bit are continuously transmitted at 64 kbit/s.

R	T	typical application
$10^{-7}$	20 hours	cyclic transmission (metering)
$10^{-10}$	2.3 years	
$10^{-15}$	230000 years	remote control and <b>protection</b>

# Protection of a short line lines
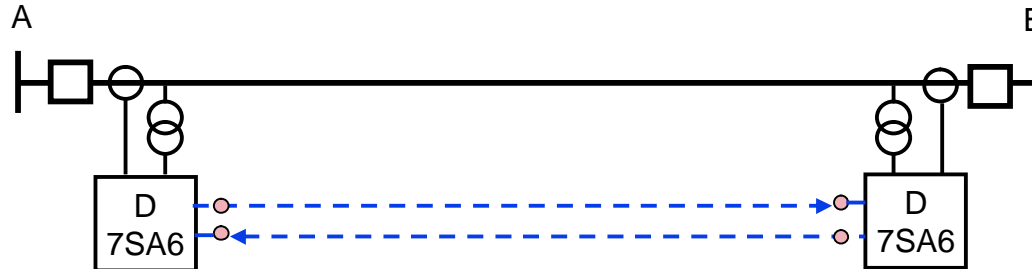
## Differential relay using direct digital relay-to-relay communication




### Communication via direct relay-relay connection

Fibre type	optical wave length	maximum attenuation	permissible distance
Multi-mode 62.5/125 $\mu\text{m}$	820 nm	16 dB	ca. 3.5 km
Monomode 9/ 125 $\mu\text{m}$	1300 nm	29 dB	ca. 60 km
9/ 125 $\mu\text{m}$	1500 nm	29 dB	ca. 100 km
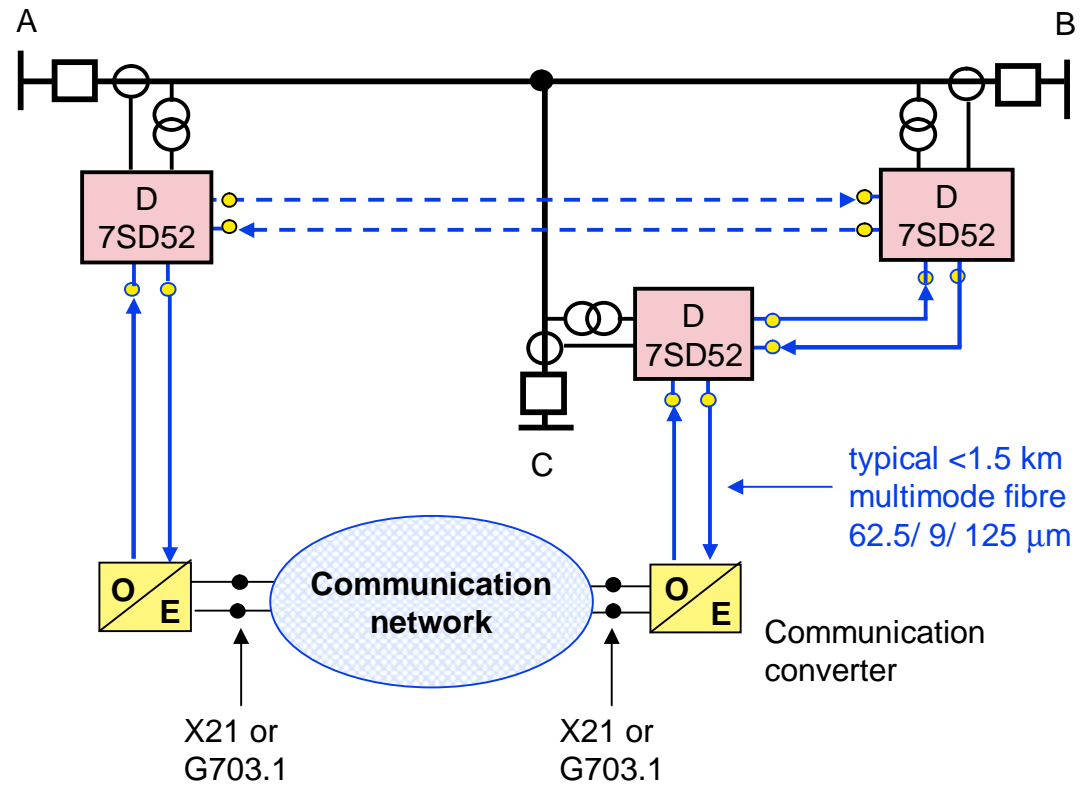
# Line differential relaying using digital communication

Chain topology or  
redundant ring topology



# Differential protection with communication through data net

---

## I **Microsecond exact time keeping in the relays**

- n Each relay has its individual time keeping
- n Sent and received telegrams get microsecond accurate time stamps

## I **Special relay properties for network communication**

- Measurement of propagation times and automatic correction 0 - 30 ms
- Detection of channel switching in the network
- Unique address for each relay (1 - 65525)  
to detect signal misdirection (channel cross-over of loop-back)
- Measurement of channel quality (availability, error rate)

## I **Change of the network path -> Adaptive add-on stabilisation**

Settable time difference to consider given data transmission asymmetry


## I **Adaptive topology recognition**

- Automatic recognition of connections and remote end devices
  - Automatic re-routing from ring to chain topology if one data connection fails
- In case of multi-terminal protection, remaining relay system continues operation if one line end is switched off and the relay is logged out for maintenance

# Individual time references by synchro-phasors


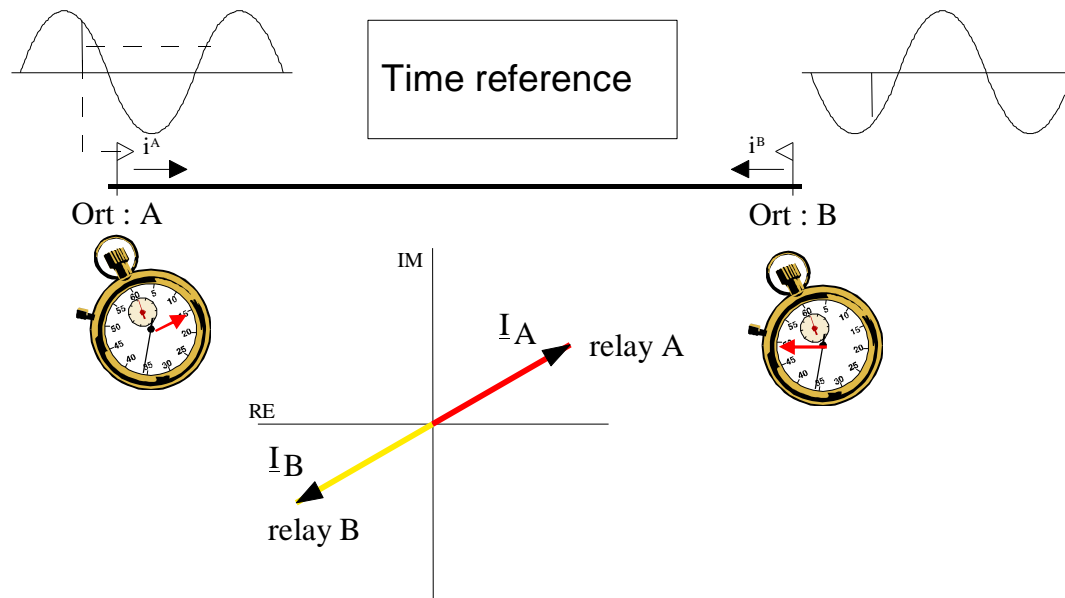
## Definition of a synchro-phasor:

Synchro-phasors, are phasors, which are measured at different network locations by independent devices and referred to a common time basis




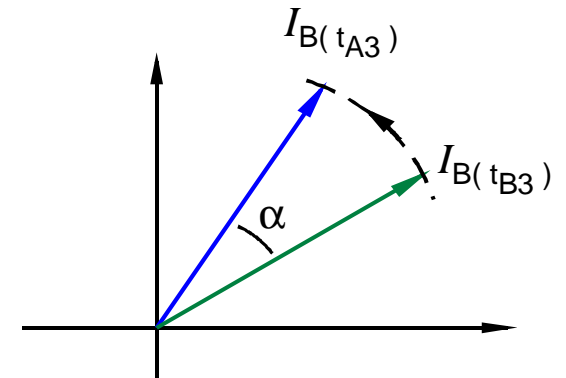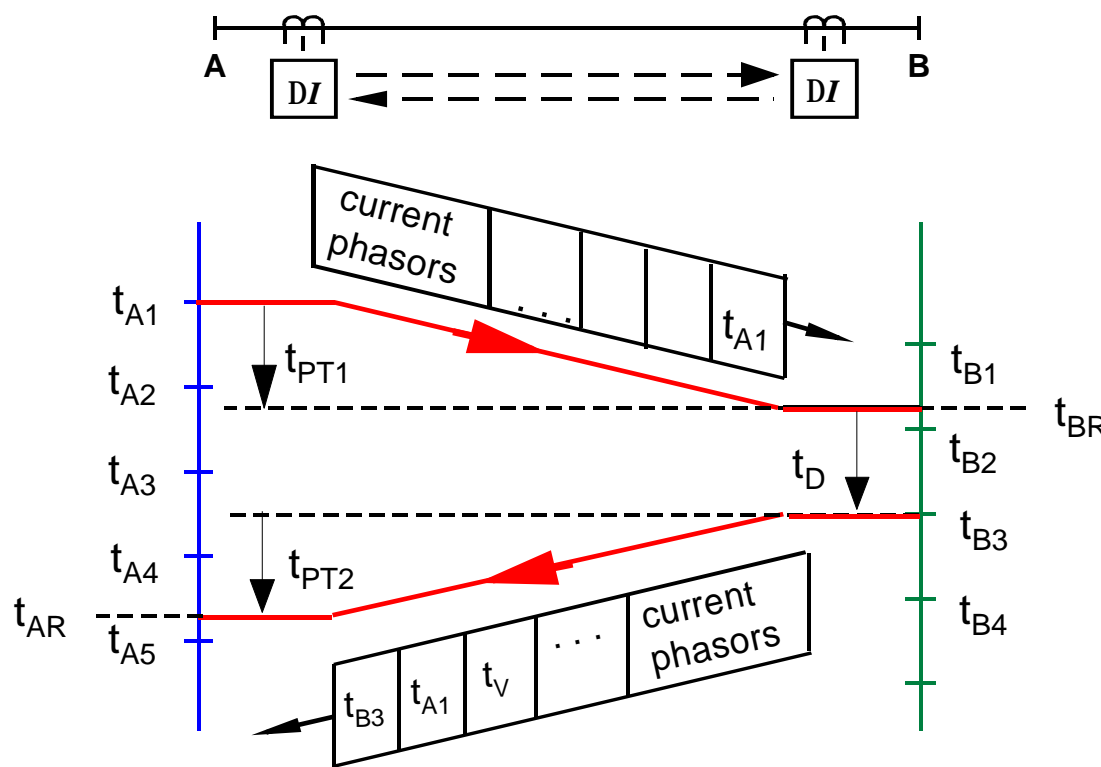
# Phasor synchronisation between line ends



$$\alpha = \frac{t_{B3} - t_{A3}}{T_P} \cdot 360^\circ$$

Signal transmission time:  $t_{PT1} = t_{PT2} = \frac{1}{2}(t_{A1} - t_{AR} - t_D)$

Sampling instant:  $t_{B3} = t_{AR} - t_{TP2}$

Specification of data channel for line differential protection  
based on Cigre Report: Protection using Telecommunication \*)

---

Data rate	64 kbit/s (min.)
Channel delay time:	< 5 ms
Channel delay time unsymmetry:	< 0.2 ms
Bit error rate normal:	< $10^{-6}$
during power system fault	< $10^{-5}$ *)
Availability:	> 99.99 %

\*) Report of WG34/35.11, Brochure REF. 192, Cigre Central Office, Paris, 2001,

\*) It is suggested that for a BER of less than  $10^{-6}$  the dependability shall not suffer a noticeable deterioration . For a BER of  $10^{-6}$  to  $10^{-3}$  the teleprotection may still able to perform its function although a loss in dependability is to be expected.




# Digital Protection of Generators and Motors


Gerhard Ziegler

**SIEMENS**

# Generator differential protection

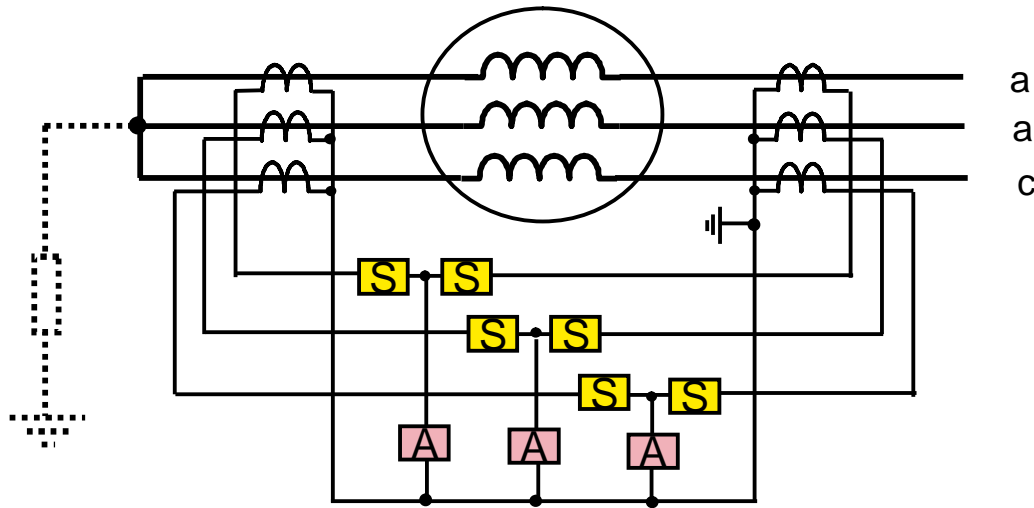


Connection circuit

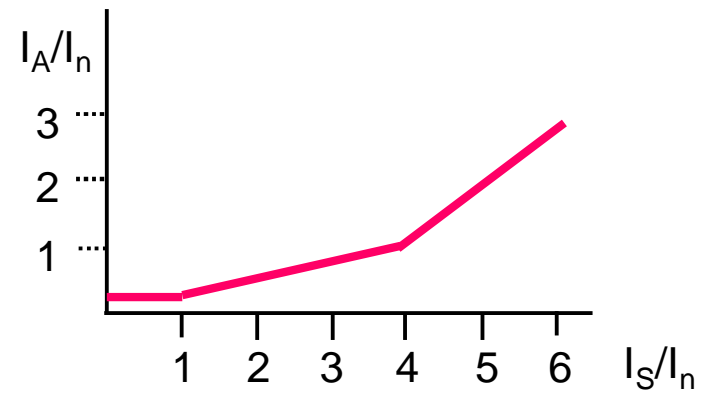


Operating characteristic


# Generator HI differential protection

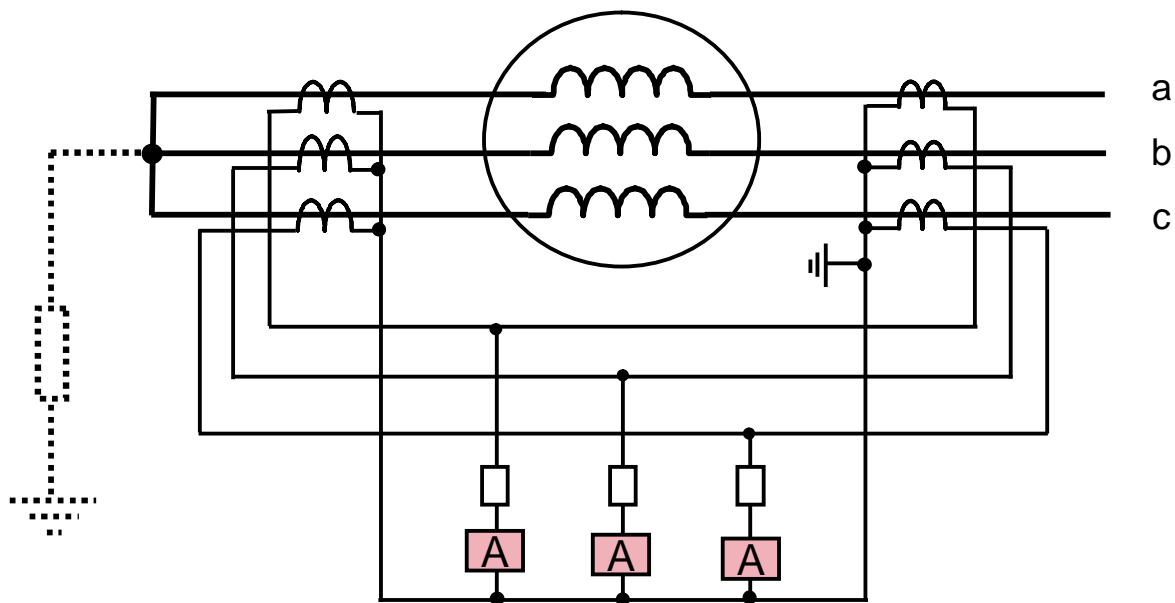


# Transverse differential protection

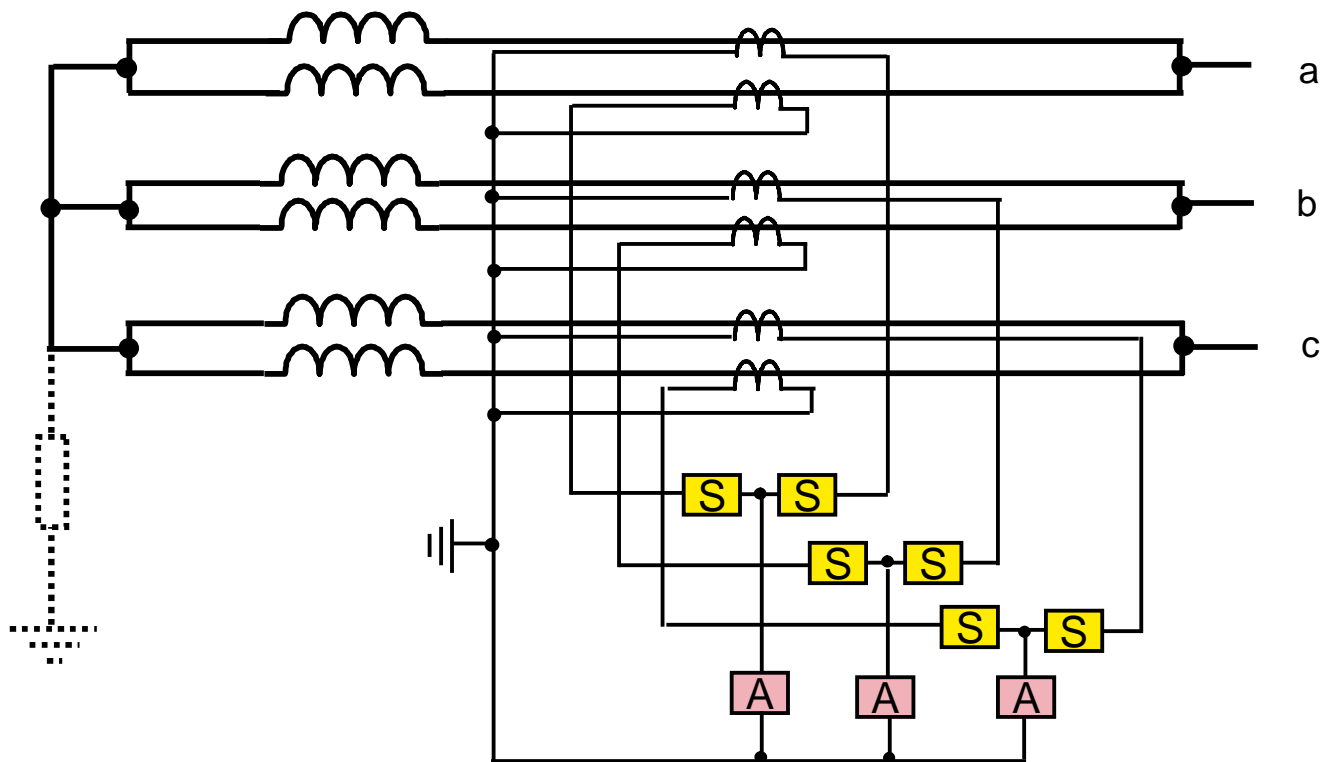
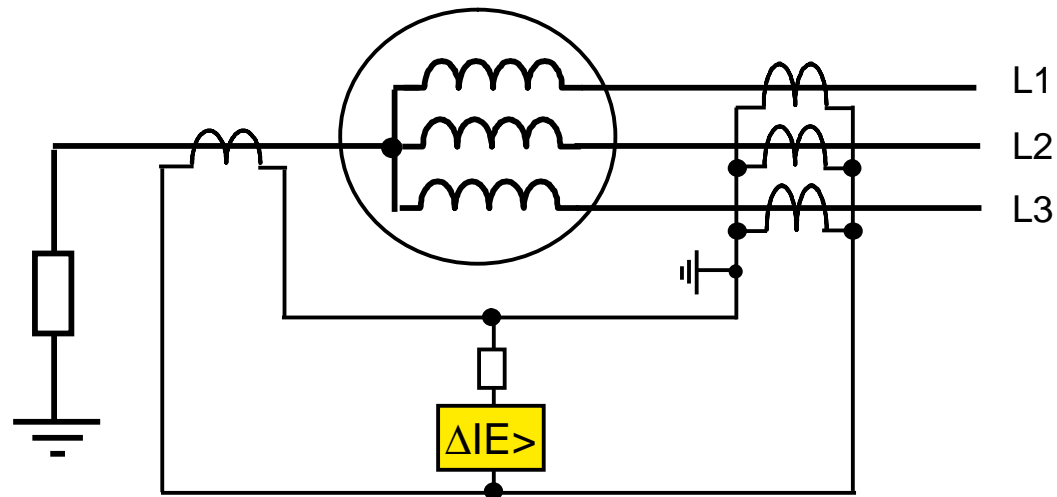
# HI earth current differential protection



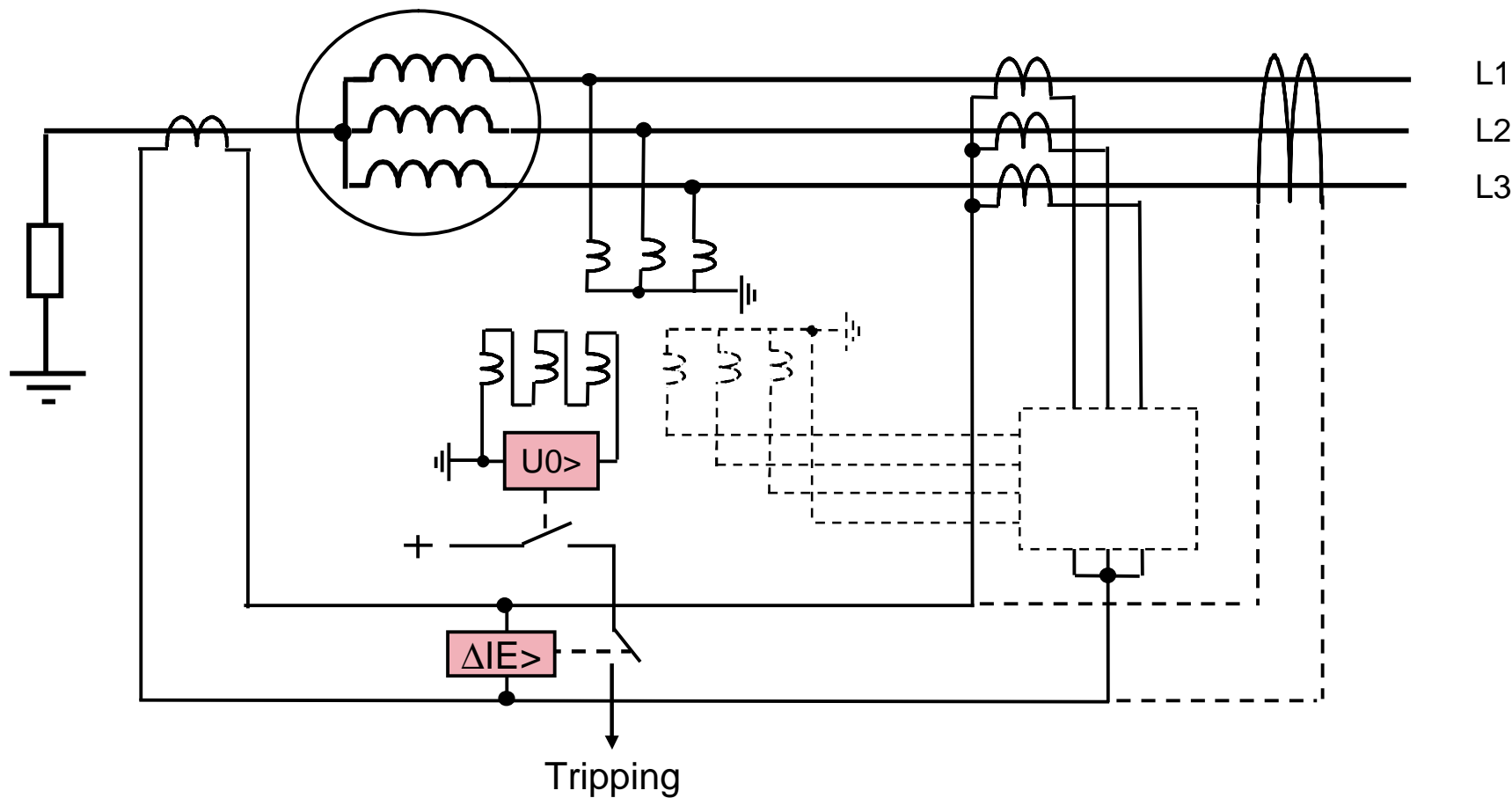
# Earth current differential protection for generators





# Motor starting current

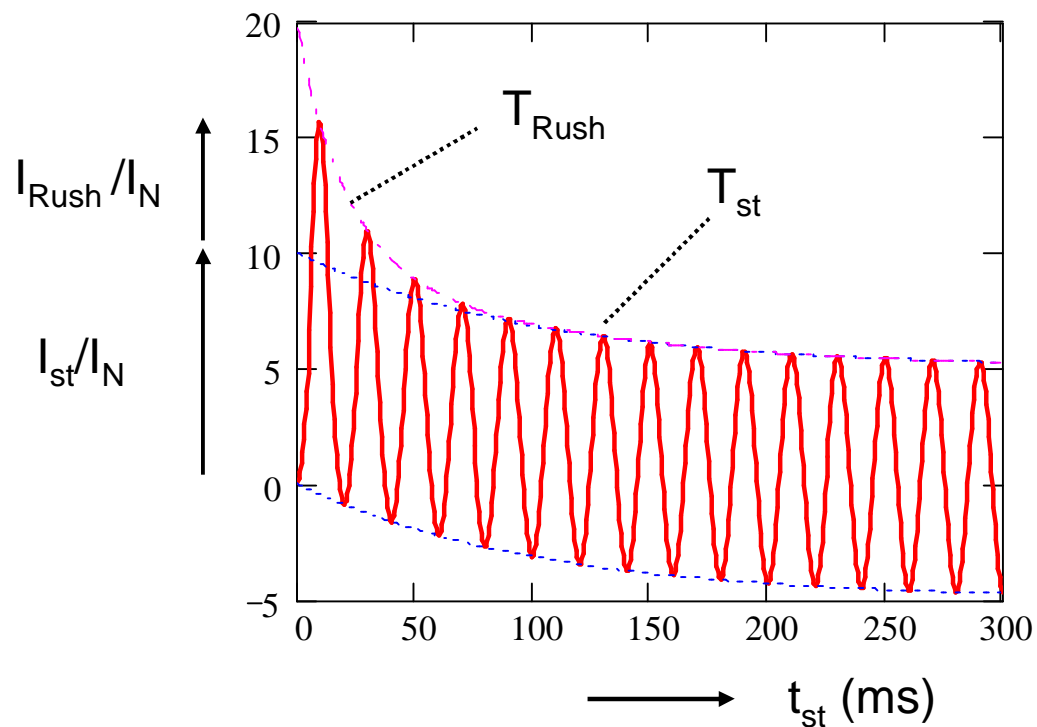




# Transformer Differential Protection


Gerhard Ziegler

**SIEMENS**
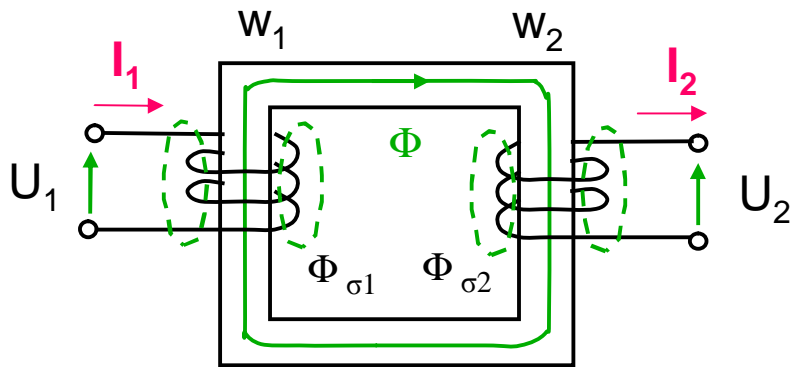
# Transformer: Function principle and equivalent circuits




Equivalent electromagnetic circuit

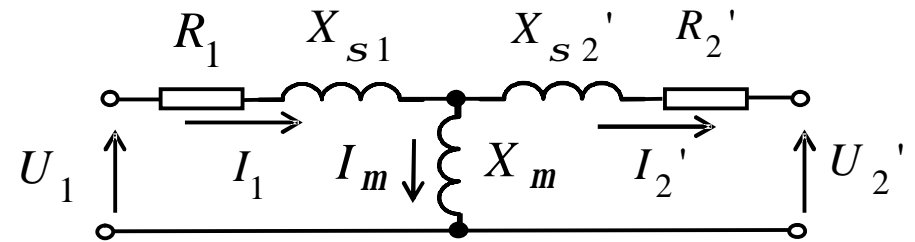

Equivalent electric circuit

$$I_1 \cdot w_1 + I_2 \cdot w_2 = I_m \cdot w_1$$

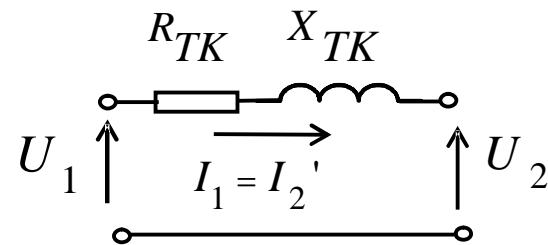At load and short-circuit:  $I_m \ll I_{1,2'}$



$$I_1 \cdot w_1 = I_2 \cdot w_2$$

$$X_{TK} = X_{s1} + X_{s2'}$$

$$R_{TK} = R_1 + R_2'$$


## Typical Transformer data

---

Rated power	Ratio	Short-circuit voltage % UN	No-load magnetizing current % I <sub>n</sub>
MVA	kV/kV		
850	850/21	17	0.2
600	400/230	18.5	0.25
300	400/120	19	0.1
300	230/120	24	0.1
40	110/11	17	0.1
16	30/10.5	8.0	0.2
6.3	30/10.5	7.5	0.2
0.63	10/0.4	4.0	0.15



---

# Transformer Inrush current

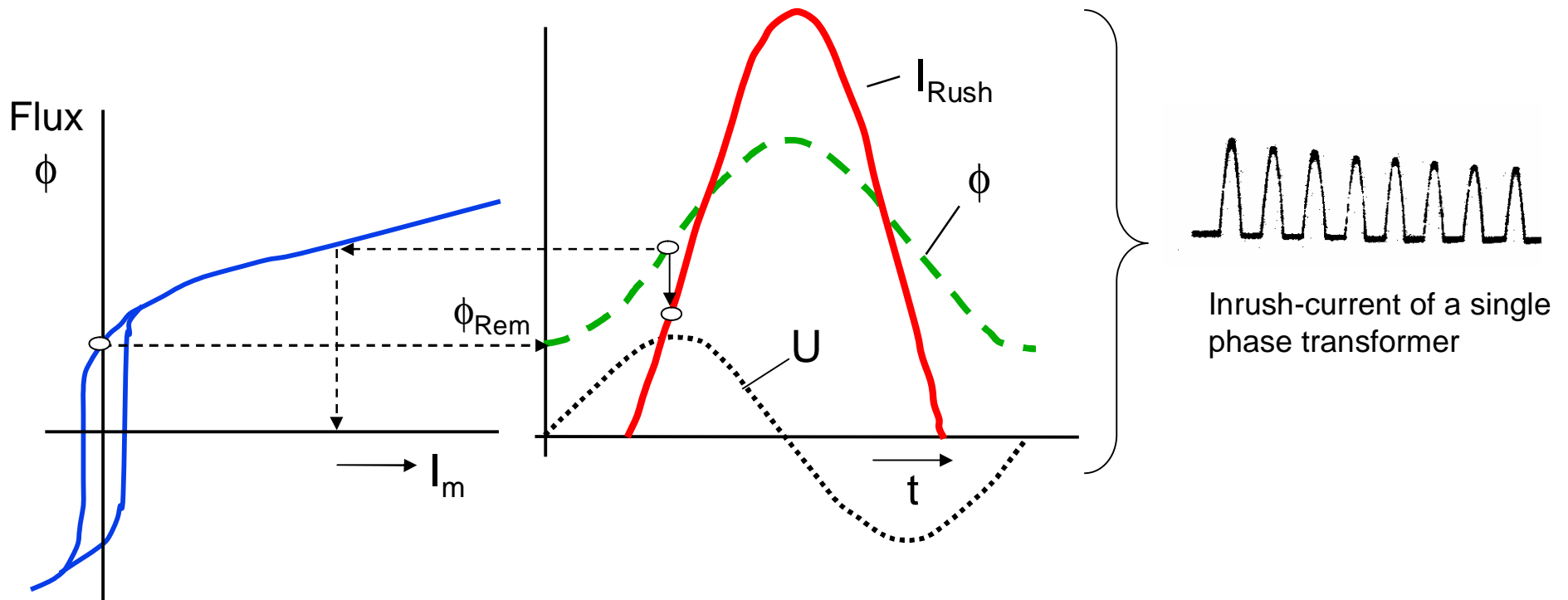


Source: Sonnemann, et al.: Magnetizing Inrush phenomena in transformer banks, AIEE Trans., 77, P. III, 1958, pp. 884-892
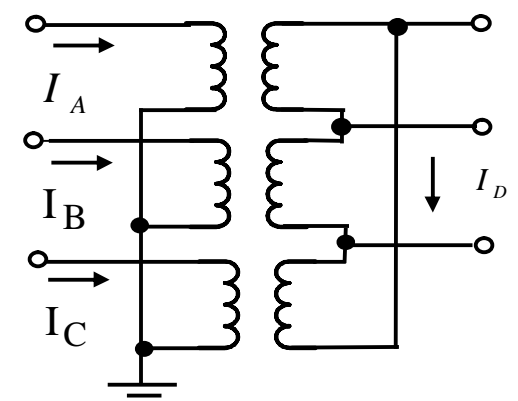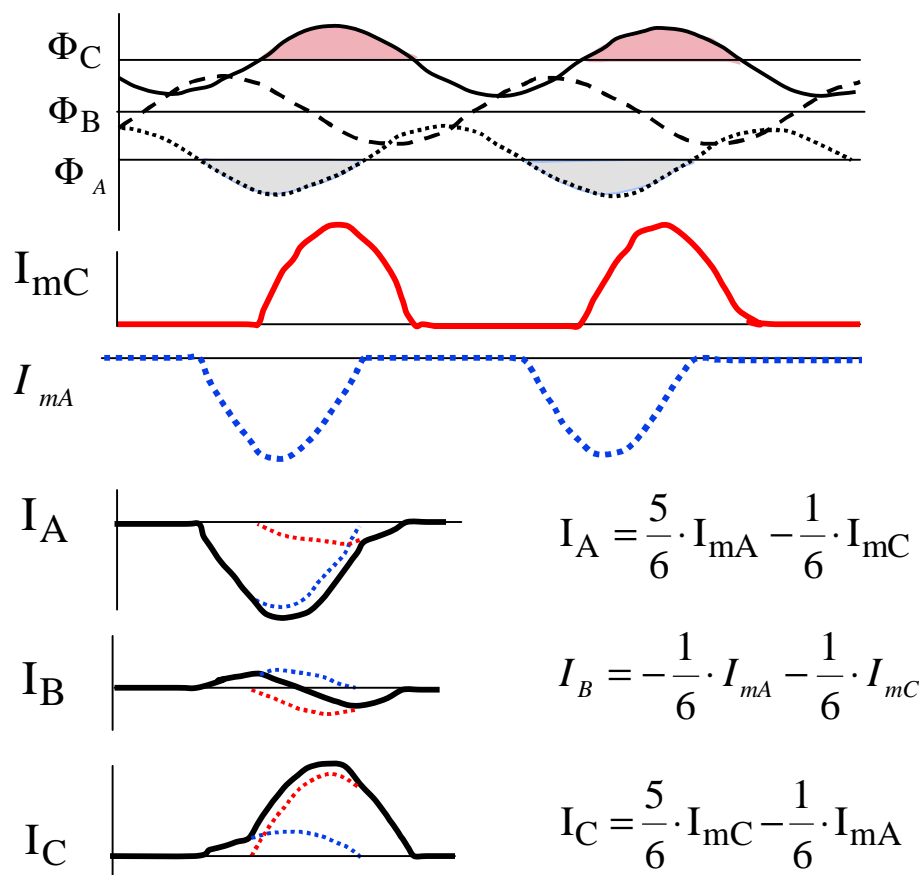
# Inrush currents of a Y-Δ-transformer Neutral of Y-winding earthed




Oscillogram:

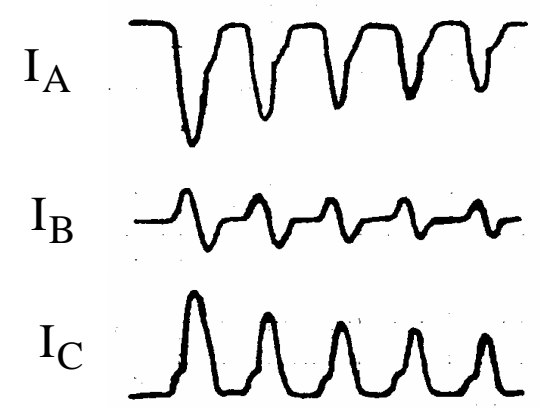


Source: Sonnemann et al. : Magnetizing Inrush phenomena in transformer banks, AIEE Trans., 77, P. III, 1958, pp. 884-892
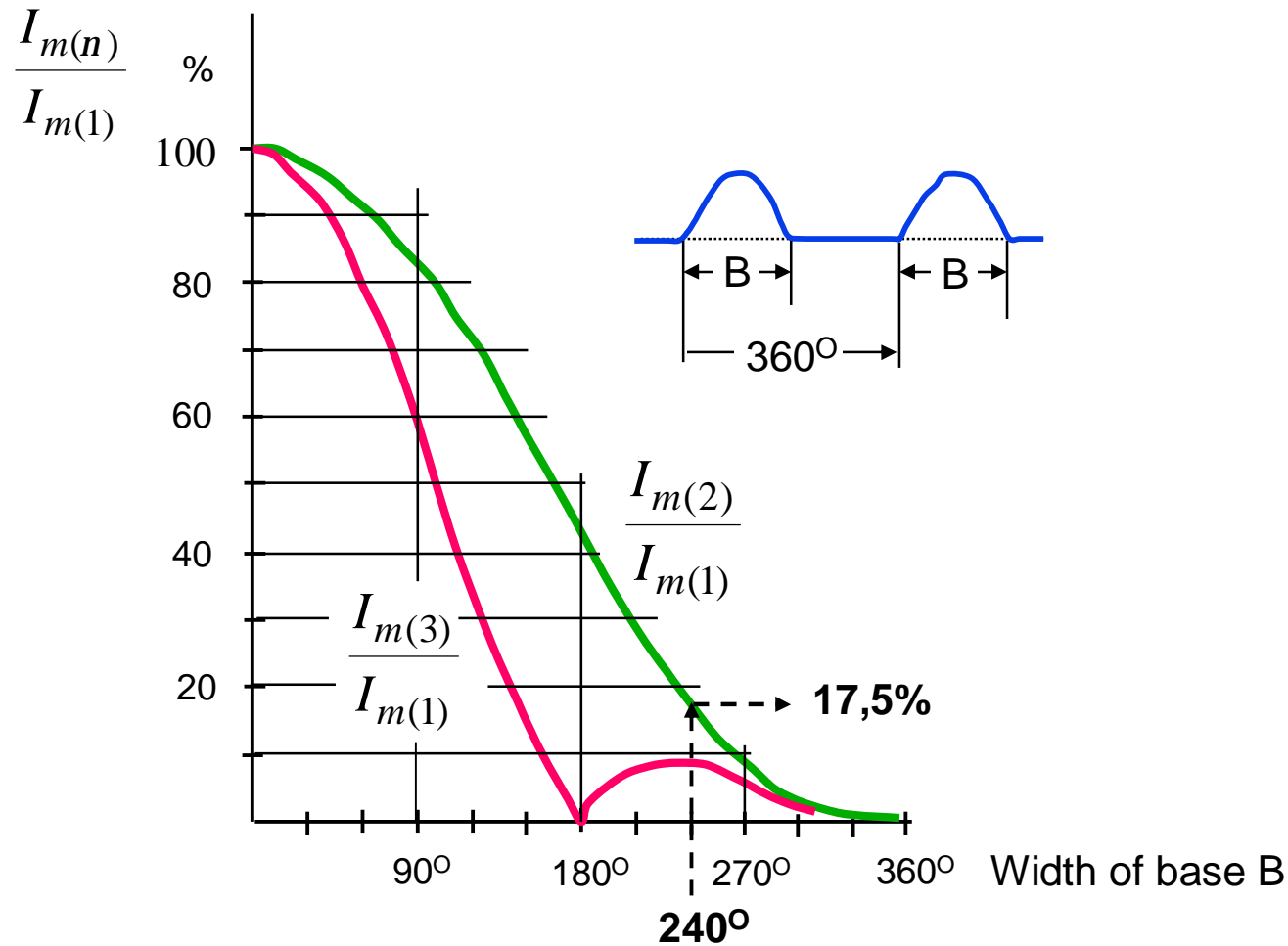
# Inrush current : Content of 2nd und 3rd harmonic



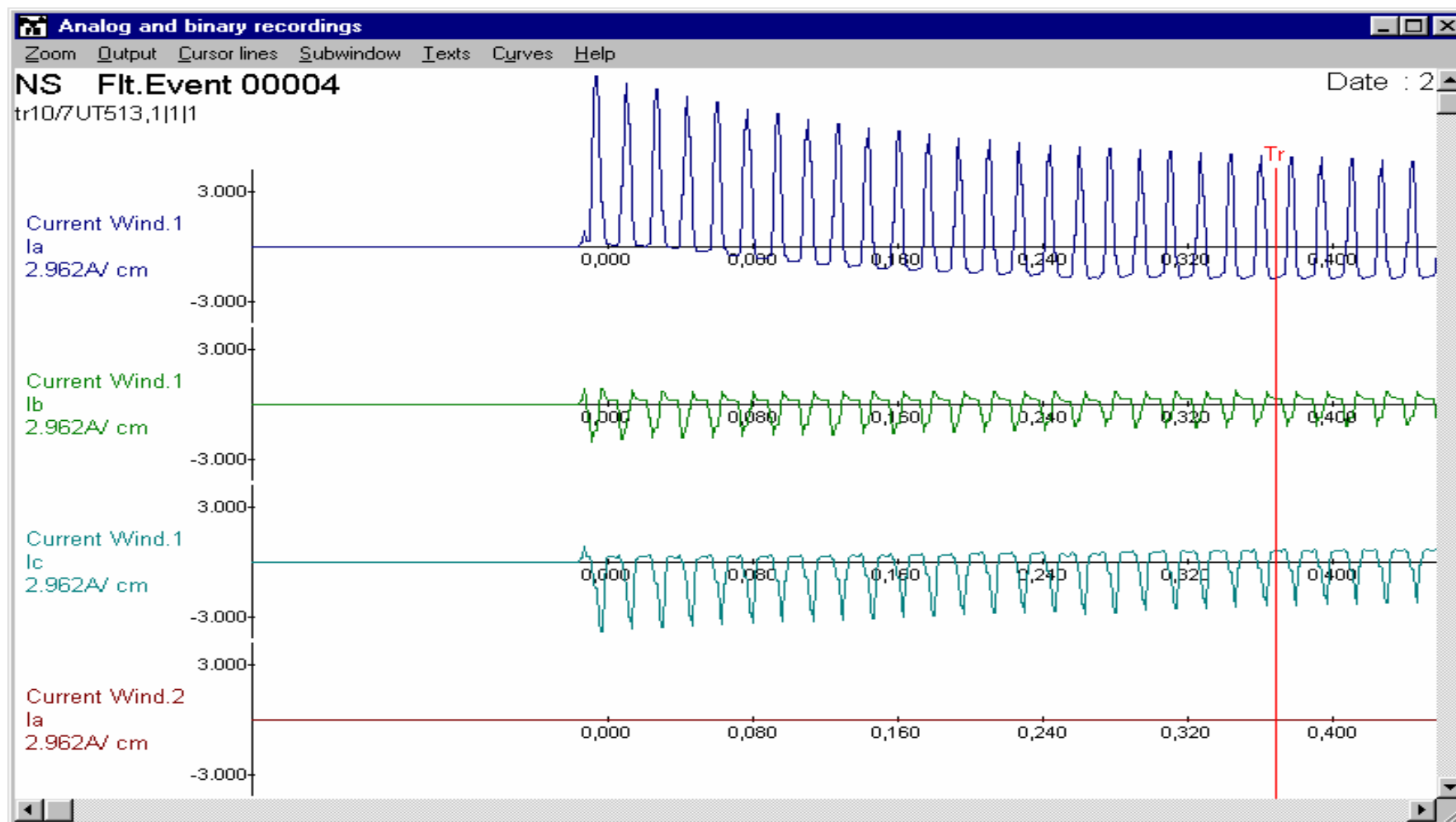
# Inrush currents of a three-phase transformer recorded with relay 7UT51





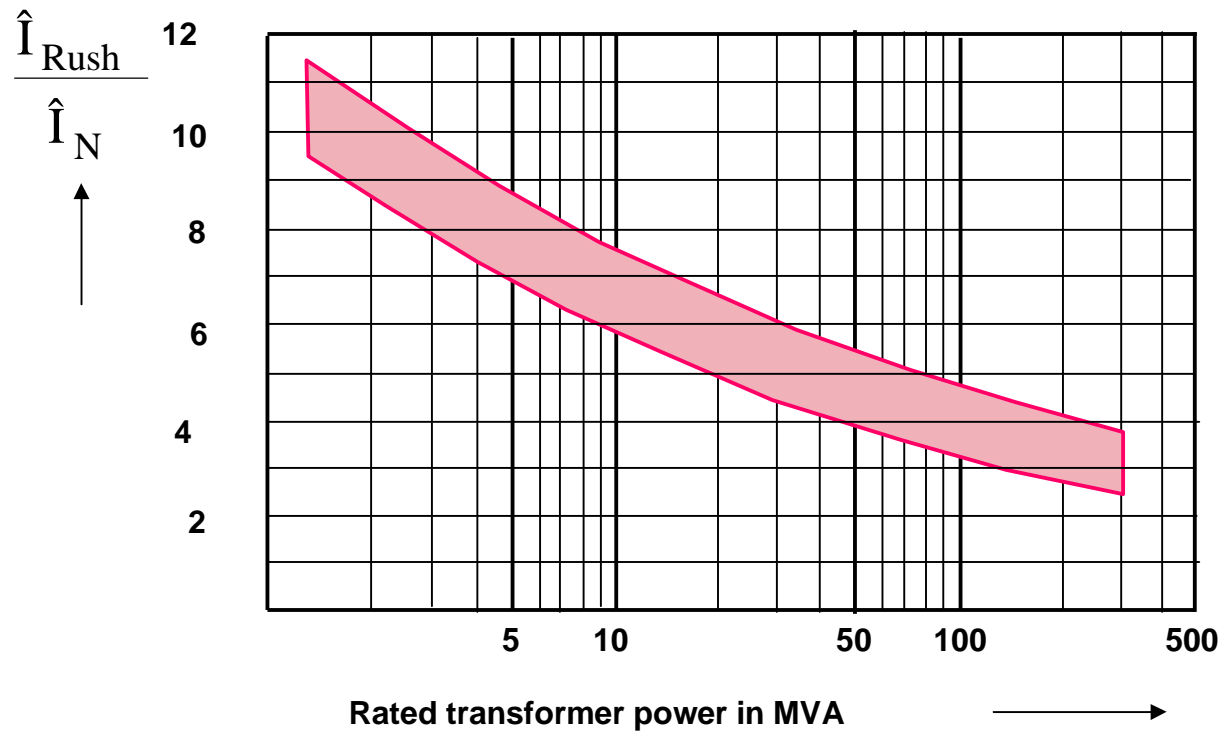
# Transformer Inrush current: Amplitude and time constant



Rated power in MVA	time constant in seconds
0,5....1,0	0,16....0,2
1,0 10	0,2 .....1,2
>10	1,2 ....720

# Sympathetic Inrush

Wave form:



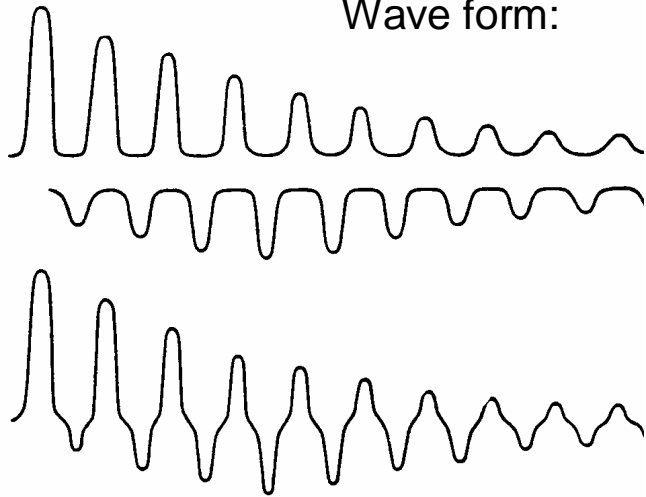


$I_1$

$I_2$


$I_T$

Transient currents:

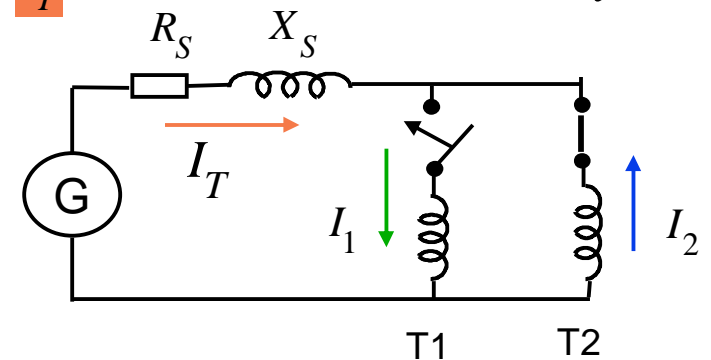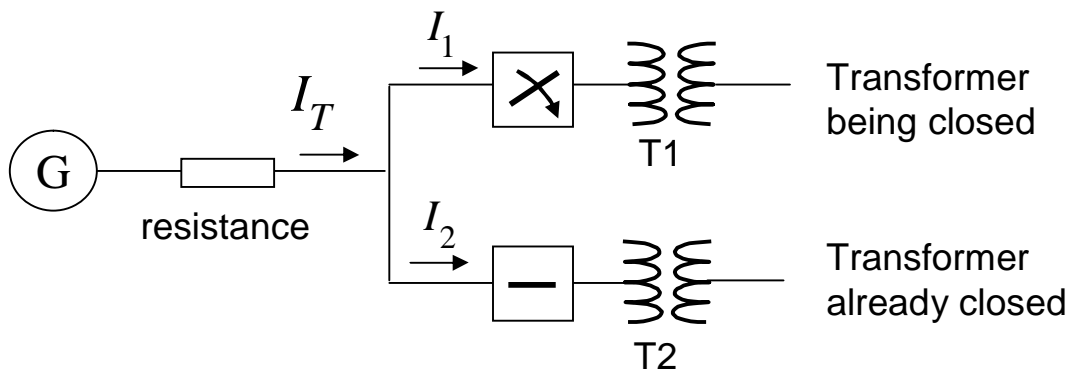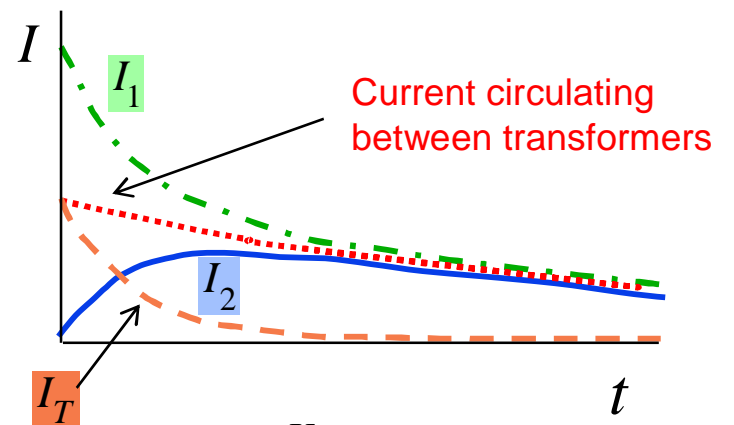


# Transformer overfluxing


Deduction of wave form

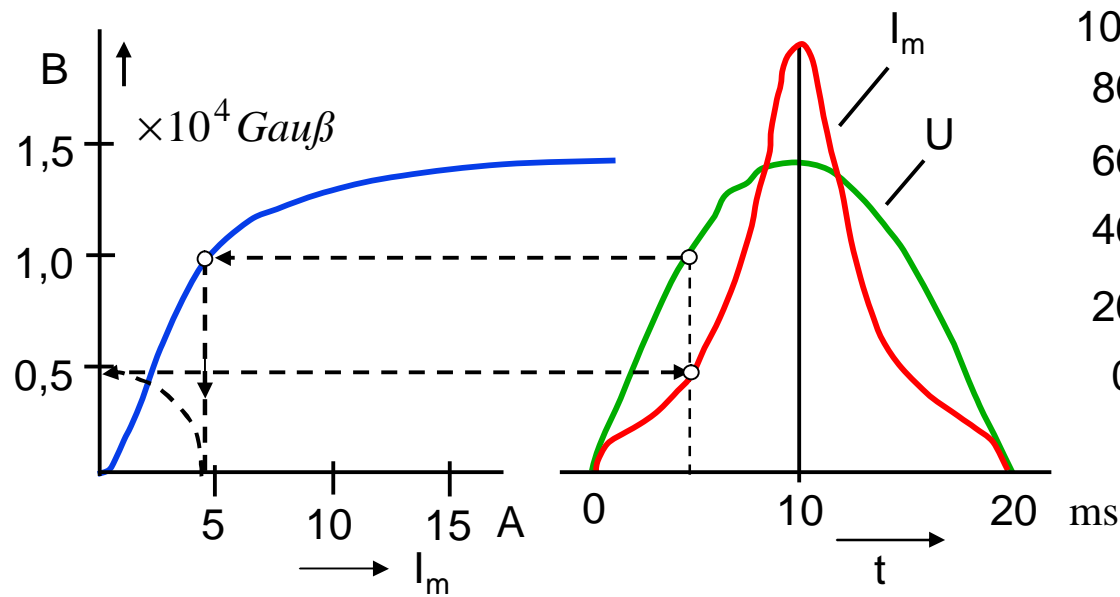

Harmonic content


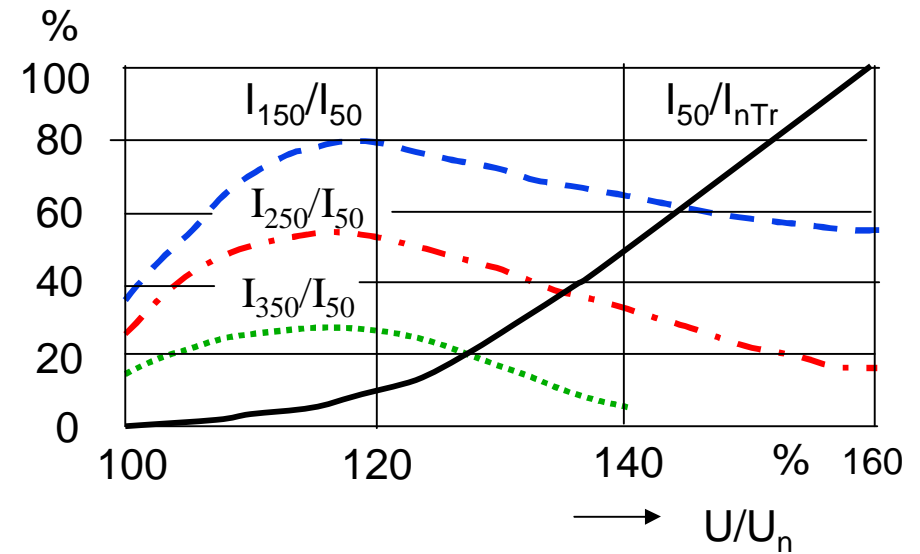

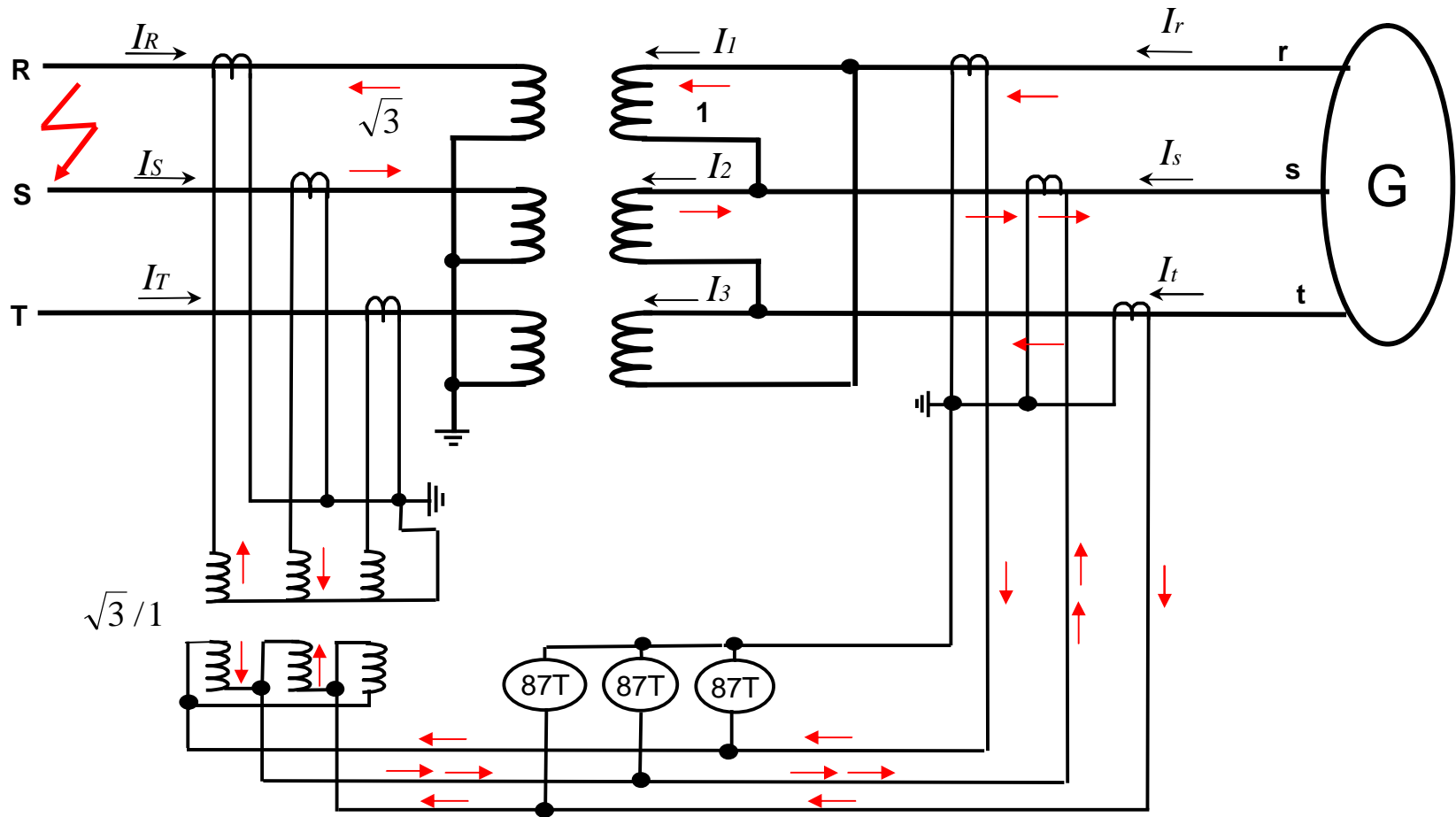
# Vector group adaptation with matching CTs Current distribution with external ph-ph fault




# Vector group adaptation and $I_0$ -elimination with matching CTs
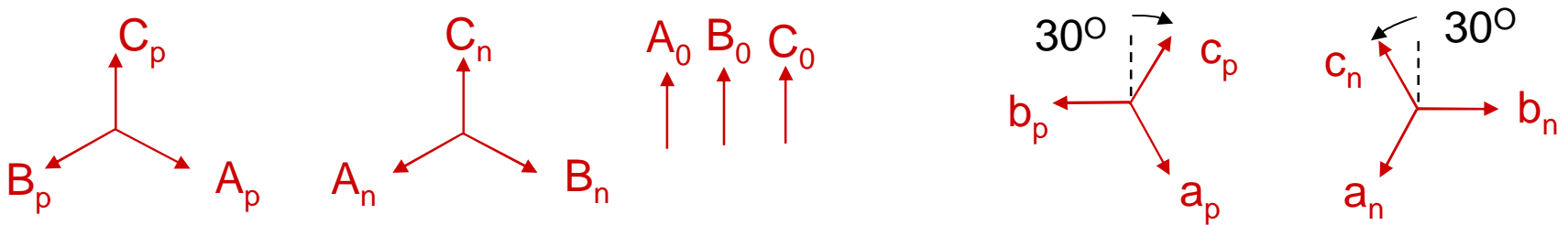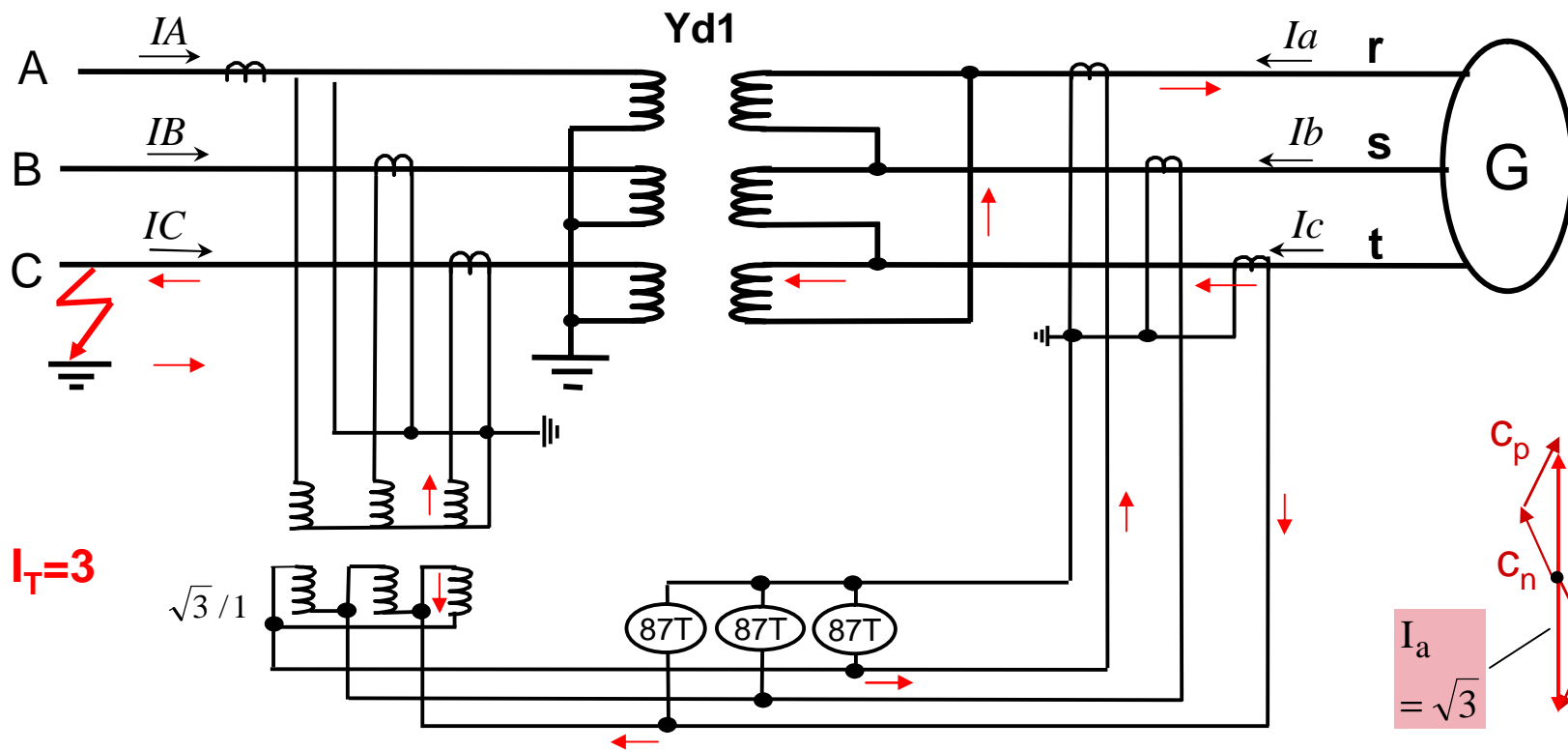
## Current distribution with external ph-E fault




# Traditional $I_0$ -elimination with matching CTs
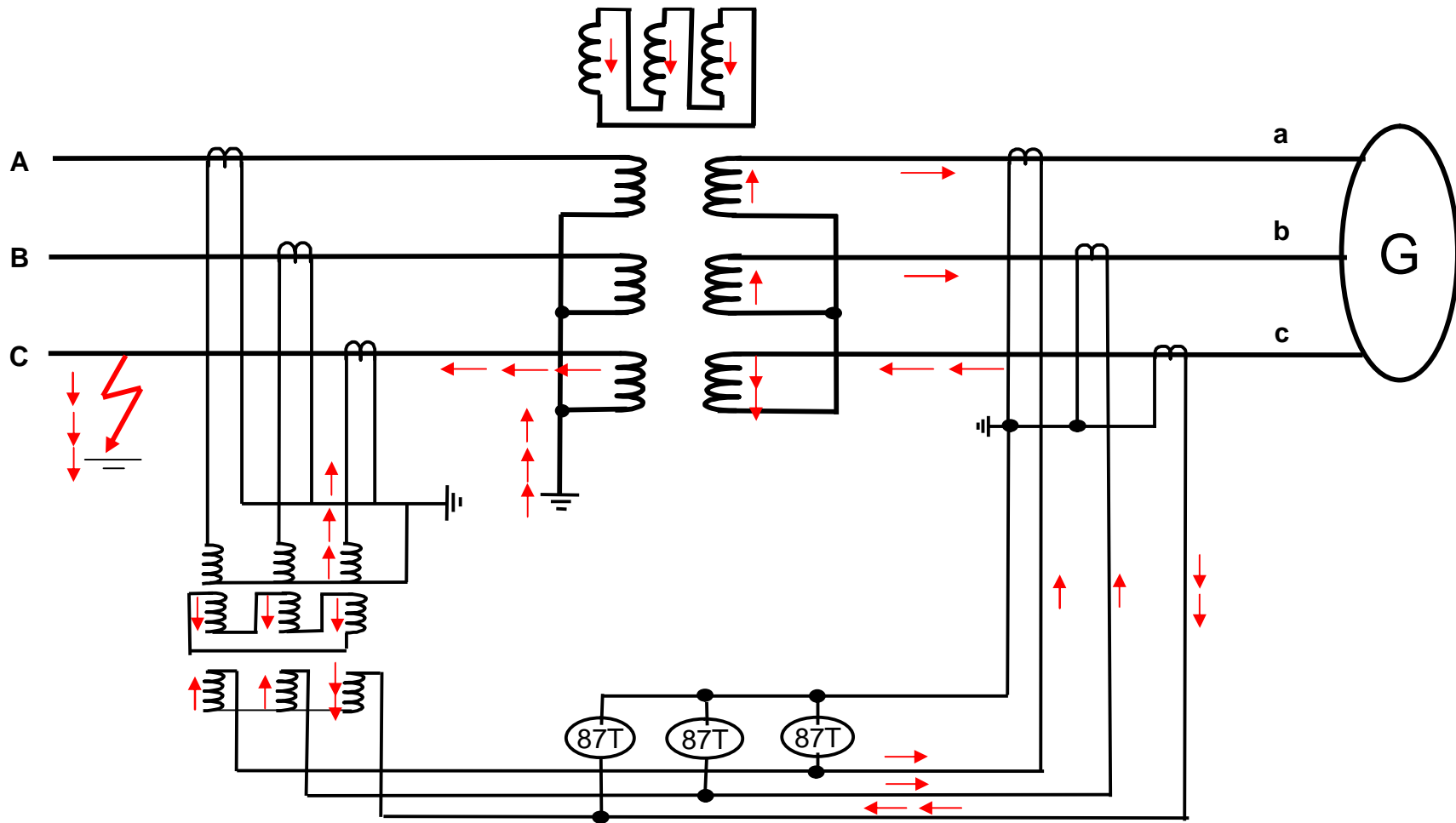
## Current distribution in case of an external earth fault




# Traditional $I_0$ -elimination with matching CTs
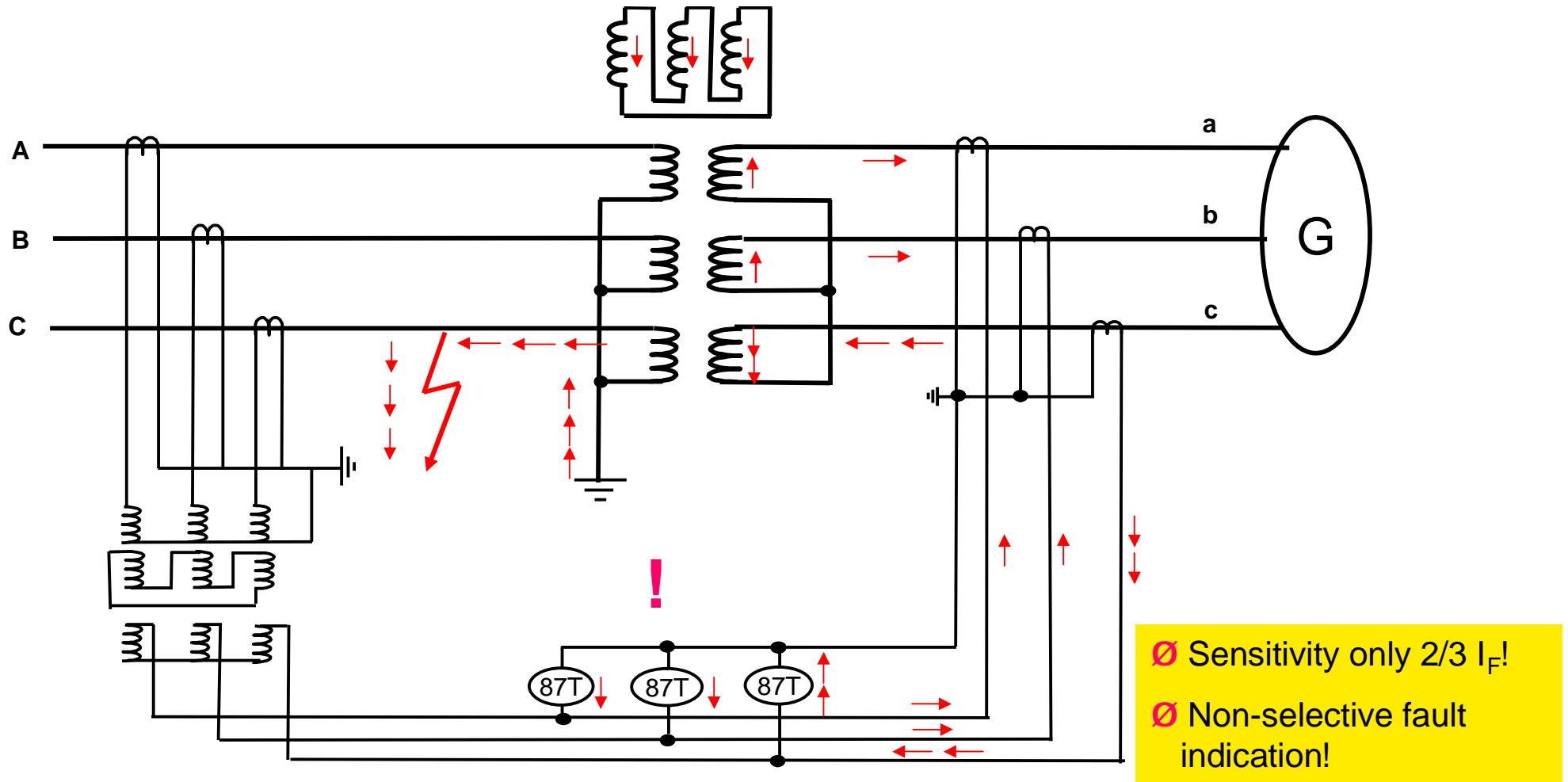
## Current distribution in case of an internal earth fault



# Traditional $I_0$ -correction with matching CTs

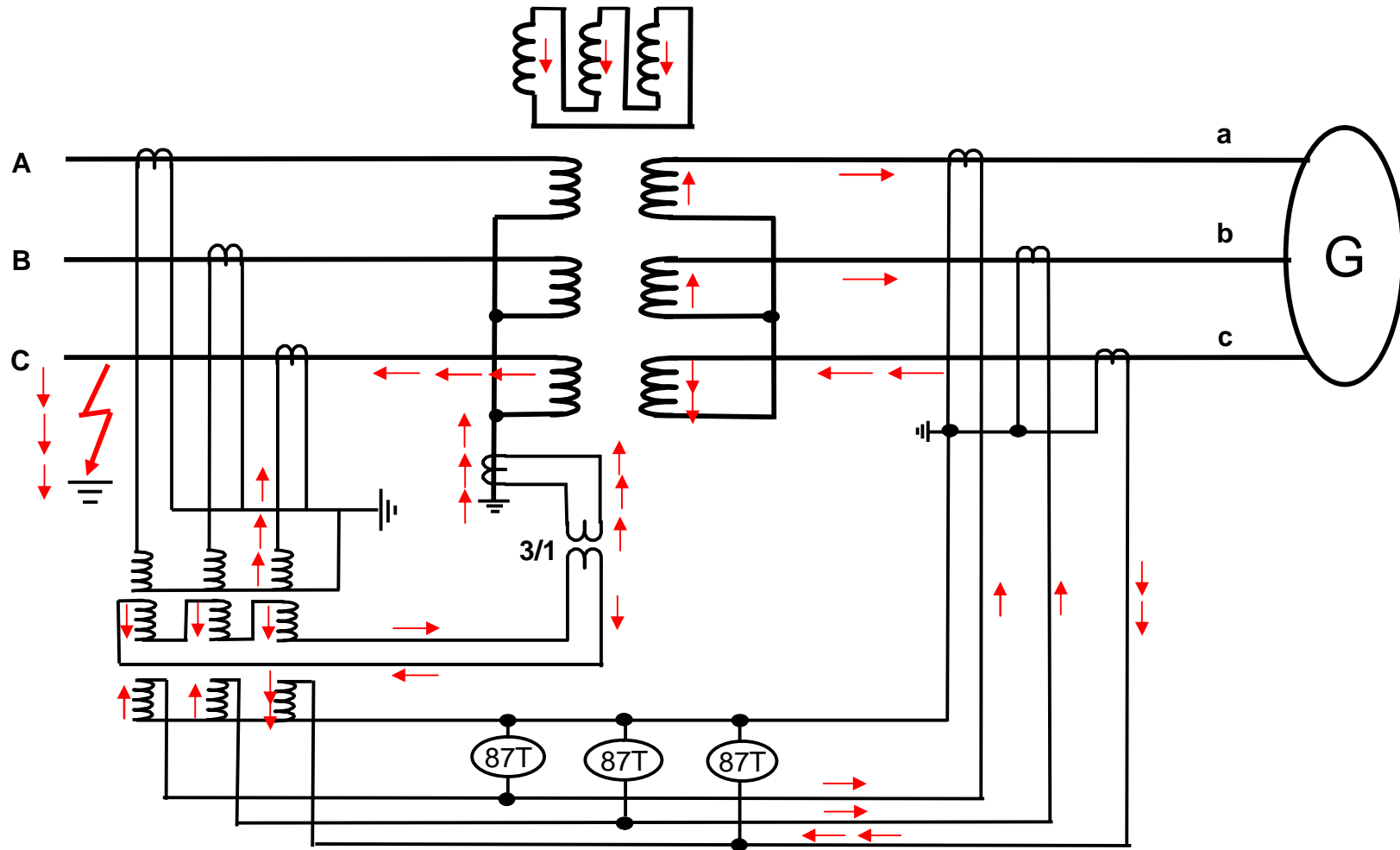
## Current distribution with external ph-E fault






# Traditional $I_0$ -correction with matching CTs
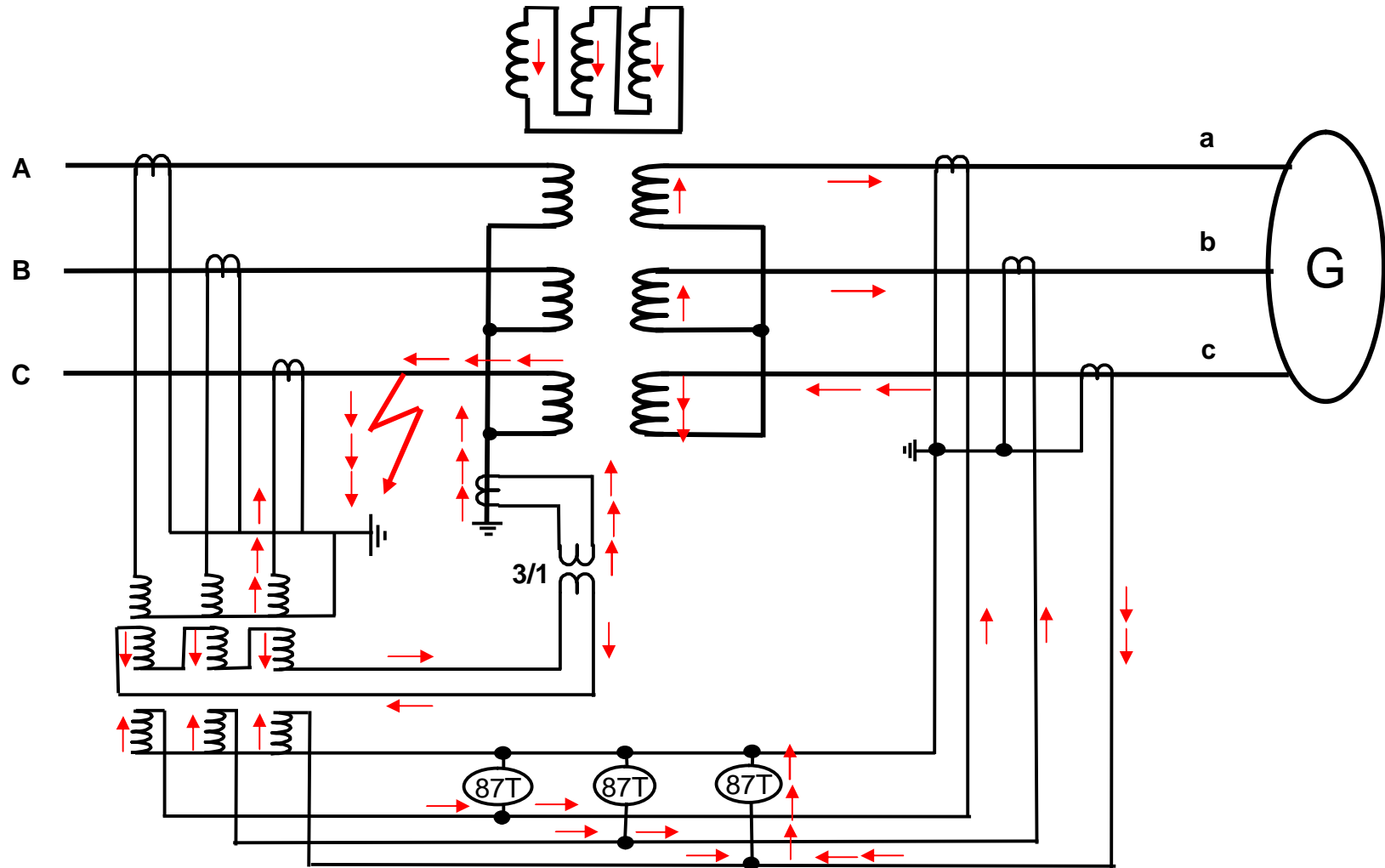
## Current distribution with internal ph-E fault


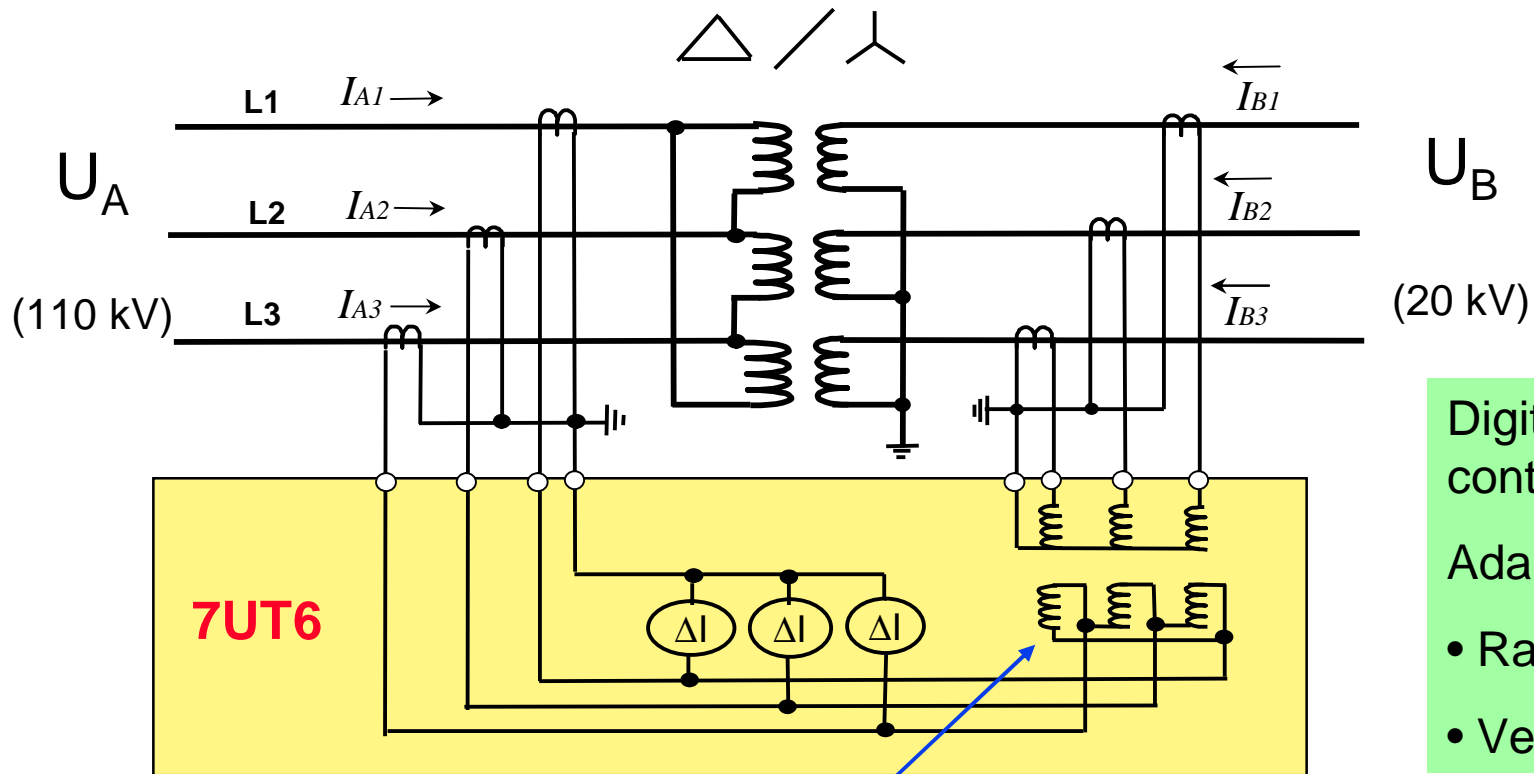
# Transformer differential protection, connection




Digital protection contains:  
 Adaptation to

- Ratio  $U_A / U_B$
- Vector group

# Digital transformer protection
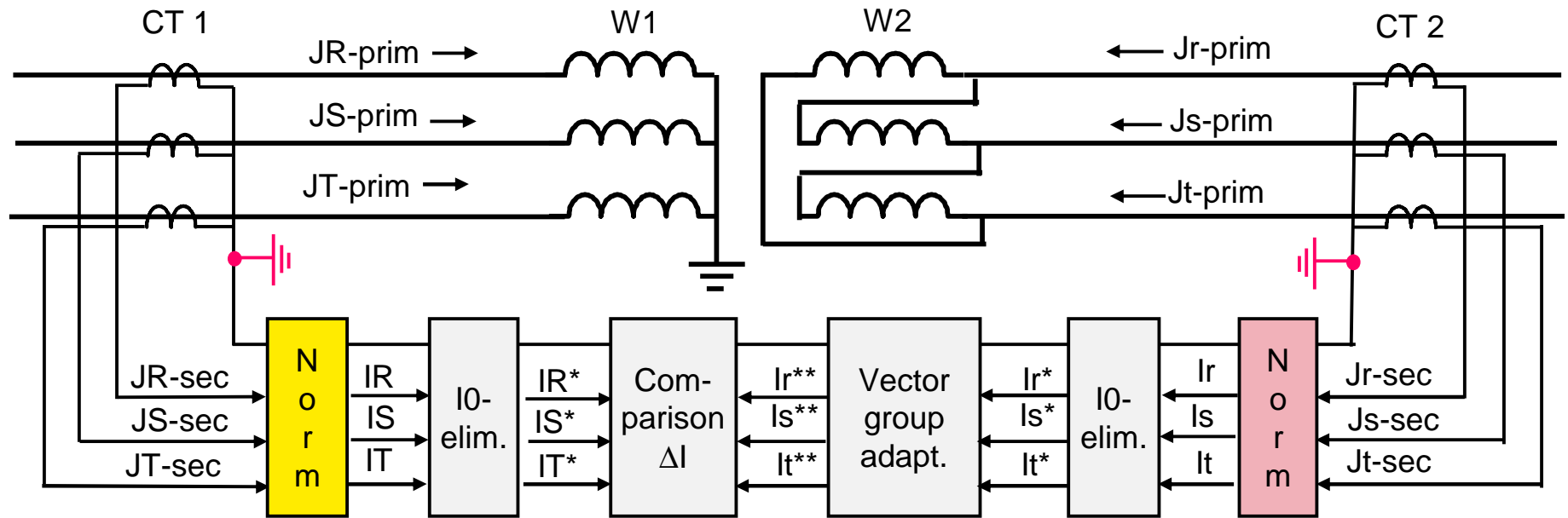
## Adaptation of currents for comparison (1)



$$I_{N-Transf-W1} = \frac{S_N}{\sqrt{3} \cdot U_{N-1}}$$


$$I_{N-Transf-W2} = \frac{S_N}{\sqrt{3} \cdot U_{N-2}}$$

$$\begin{vmatrix} I_R \\ I_S \\ I_T \end{vmatrix} = \frac{I_{N-Prim-CT1}}{I_{N-Transf-W1}} \cdot \begin{vmatrix} J_{R-sec} \\ J_{S-sec} \\ J_{T-sec} \end{vmatrix} = k_{CT-1} \cdot \begin{vmatrix} J_{R-sec} \\ J_{S-sec} \\ J_{T-sec} \end{vmatrix}$$

$$\begin{vmatrix} I_r \\ I_s \\ I_t \end{vmatrix} = \frac{I_{N-Prim-CT2}}{I_{N-Transf-W2}} \cdot \begin{vmatrix} J_{r-sec} \\ J_{s-sec} \\ J_{t-sec} \end{vmatrix} = k_{CT-2} \cdot \begin{vmatrix} J_{r-sec} \\ J_{s-sec} \\ J_{t-sec} \end{vmatrix}$$

# Digital transformer protection
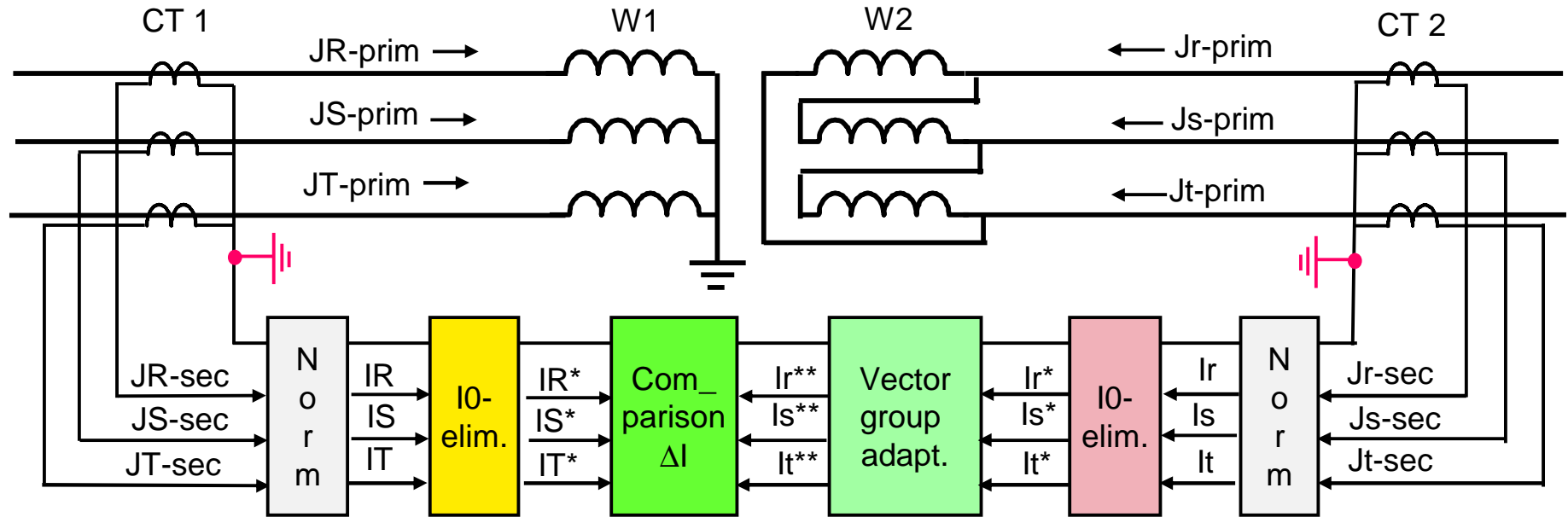
## Adaptation of currents for comparison (2)



$$I_0 = \frac{1}{3} \cdot (I_R + I_S + I_T)$$

$$I_R^* = I_R - I_0$$

$$I_S^* = I_S - I_0$$

$$I_T^* = I_T - I_0$$

$$\begin{bmatrix} I_{\Delta-R} \\ I_{\Delta-S} \\ I_{\Delta-T} \end{bmatrix} = \begin{bmatrix} I_R^* \\ I_S^* \\ I_T^* \end{bmatrix} + \begin{bmatrix} I_r^{**} \\ I_s^{**} \\ I_t^{**} \end{bmatrix}$$

Example Yd5:

$$\begin{bmatrix} I_r^{**} \\ I_s^{**} \\ I_t^{**} \end{bmatrix} = \frac{1}{\sqrt{3}} \begin{bmatrix} -1 & 0 & 1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \end{bmatrix} \cdot \begin{bmatrix} I_r^* \\ I_s^* \\ I_t^* \end{bmatrix}$$

$$I_0 = \frac{1}{3} \cdot (I_r + I_s + I_t)$$

$$I_r^* = I_r - I_0$$

$$I_s^* = I_s - I_0$$

$$I_t^* = I_t - I_0$$

# Adaptation of currents for comparison

## Relay input data

---

### Input data:

- n times 30<sup>0</sup>      vector group number  
(only for 2nd and 3rd winding,  
1st winding is reference)
- UN (kV)      Rated winding voltage
- SN (MVA)      rated winding power
- INW (A)      Primary rated CT current
- Line or BB      direction of CT neutral
- Elimination /  
Correction /  
without      I<sub>0</sub>-treatment
- Side XX      Assignment input for REF
- INW S (A)      Primary rated current of neutral CT
- Neutral CT      Earth side connection to relay: Q7 or Q8?

Winding 1 (reference) is normally:


- High voltage side

At windings with tap  
changer:

$$U_N = 2 \cdot \frac{U_{max} \cdot U_{min}}{U_{max} + U_{min}}$$

# Digital transformer protection

## Current adaptation, Example (1)

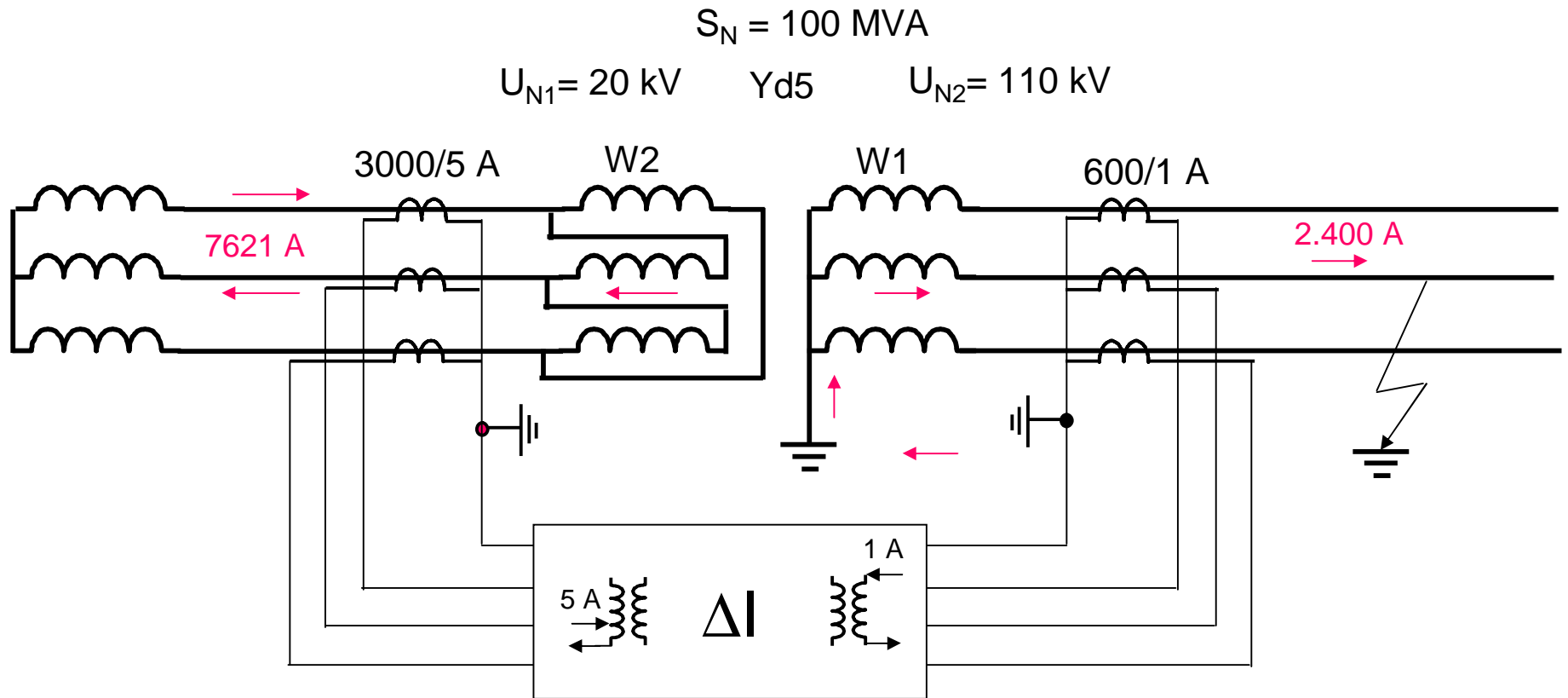

# Digital transformer protection

## Current adaptation, Example (2)

20-kV-side

$$I_{N-Trafo-W2} = \frac{100\text{MVA}}{\sqrt{3} \cdot 20\text{kV}} = 2887\text{A}$$

$$J_{R,S,t\text{-sek}} = \frac{1}{3000} \cdot 13200 / \sqrt{3} = 4,4 / \sqrt{3} \text{ A}$$

$$I_{\text{Norm}} = \frac{3000}{2887} \cdot 4,4 / \sqrt{3} = 4,57 / \sqrt{3} \text{ A}$$

I0-elimination:

$$\begin{pmatrix} I_r^{**} \\ I_s^{**} \\ I_t^{**} \end{pmatrix} = \frac{1}{\sqrt{3}} \begin{vmatrix} -1 & 0 & 1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \end{vmatrix} \cdot \begin{vmatrix} 4,57 / \sqrt{3} \\ -4,57 / \sqrt{3} \\ 0 \end{vmatrix} = \begin{vmatrix} -4,57 / 3 \\ 2 \cdot 4,57 / 3 \\ -4,57 / 3 \end{vmatrix}$$

$$I_{A-R} = I_R^* + I_r^{**} = 4,57 / \sqrt{3} - 4,57 / \sqrt{3} = 0$$

$$I_{A-S} = I_S^* + I_s^{**} = -2 \cdot 4,57 / \sqrt{3} + 2 \cdot 4,57 / \sqrt{3} = 0$$

$$I_{A-T} = I_T^* + I_t^{**} = 4,57 / \sqrt{3} - 4,57 / \sqrt{3} = 0$$

110-kV-side

$$I_{N-Trafo-W1} = \frac{100\text{MVA}}{\sqrt{3} \cdot 110\text{kV}} = 525\text{A}$$

$$J_{R,S,T\text{-sek}} = \frac{1}{600} \cdot 2400 = 4,0 \text{ A}$$

$$I_{\text{Norm}} = \frac{600}{525} \cdot 4 = 4,57\text{A}$$

Vector group adaptation: Yd5


$$\begin{pmatrix} I_r^* \\ I_s^* \\ I_t^* \end{pmatrix} = \frac{1}{3} \begin{vmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{vmatrix} \cdot \begin{vmatrix} 0 \\ -4,57 \\ 0 \end{vmatrix} = \begin{vmatrix} 4,57 / 3 \\ -2 \cdot 4,57 / 3 \\ 4,57 / 3 \end{vmatrix}$$

# Current adaptation (1)
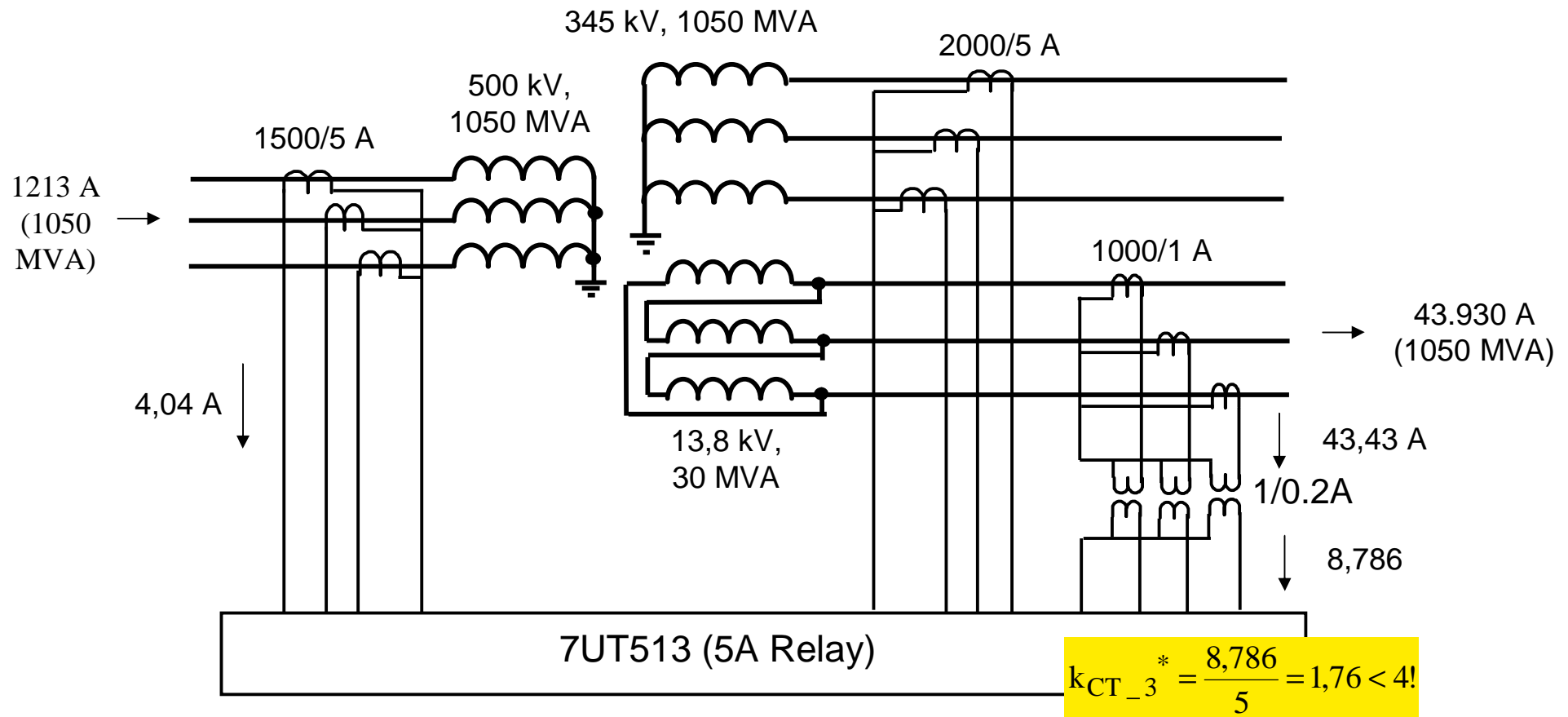
## Practical example for the need of matching CTs

Matching CTs recommended, if  $k_{Wan\_n} > 4$  or  $k_{Wan\_n} < 1/4$ : \*)

\*) To keep the specified measuring accuracy of 7UT51. For protection only necessary if  $8 < k_{Wan\_n} < 1/8$





# Current adaptation (2)

Practical example for the need of matching CTs

$$I_{n-Tr-W1} = \frac{1050 \cdot 10^3}{\sqrt{3} \cdot 500} = 1213A$$

$$I_{n-Tr-W1-sec} = \frac{1213A}{1500/5} = 4,04A$$

$$k_{CT-1} = \frac{4.04}{5} = 0,809$$

$$I_{n-Tr-W2} = \frac{1050 \cdot 10^3}{\sqrt{3} \cdot 345} = 1757A$$

$$I_{n-Tr-W2-sec} = \frac{1757A}{2000/5} = 4,39A$$

$$k_{CT-2} = \frac{4,39}{5} = 0,878$$


$$I_{n-Tr-W3} = \frac{1050 \cdot 10^3}{\sqrt{3} \cdot 13,8} = 43.930A$$

$$I_{n-Tr-W3-sec} = \frac{43.930A}{1000/1} = 43,93A$$

$$k_{CT-3} = \frac{43,93}{5} = 8,786 > 4!$$

Relay	Transformer winding 1	Transformer winding 3
40·In = 15 Bit +sign = 2 <sup>15</sup> = 32.768		
32.768	32.36	351,44
15		
40·In		
1	0,099%	1,072%
0,122%In		

# 7UT6 Operating characteristic

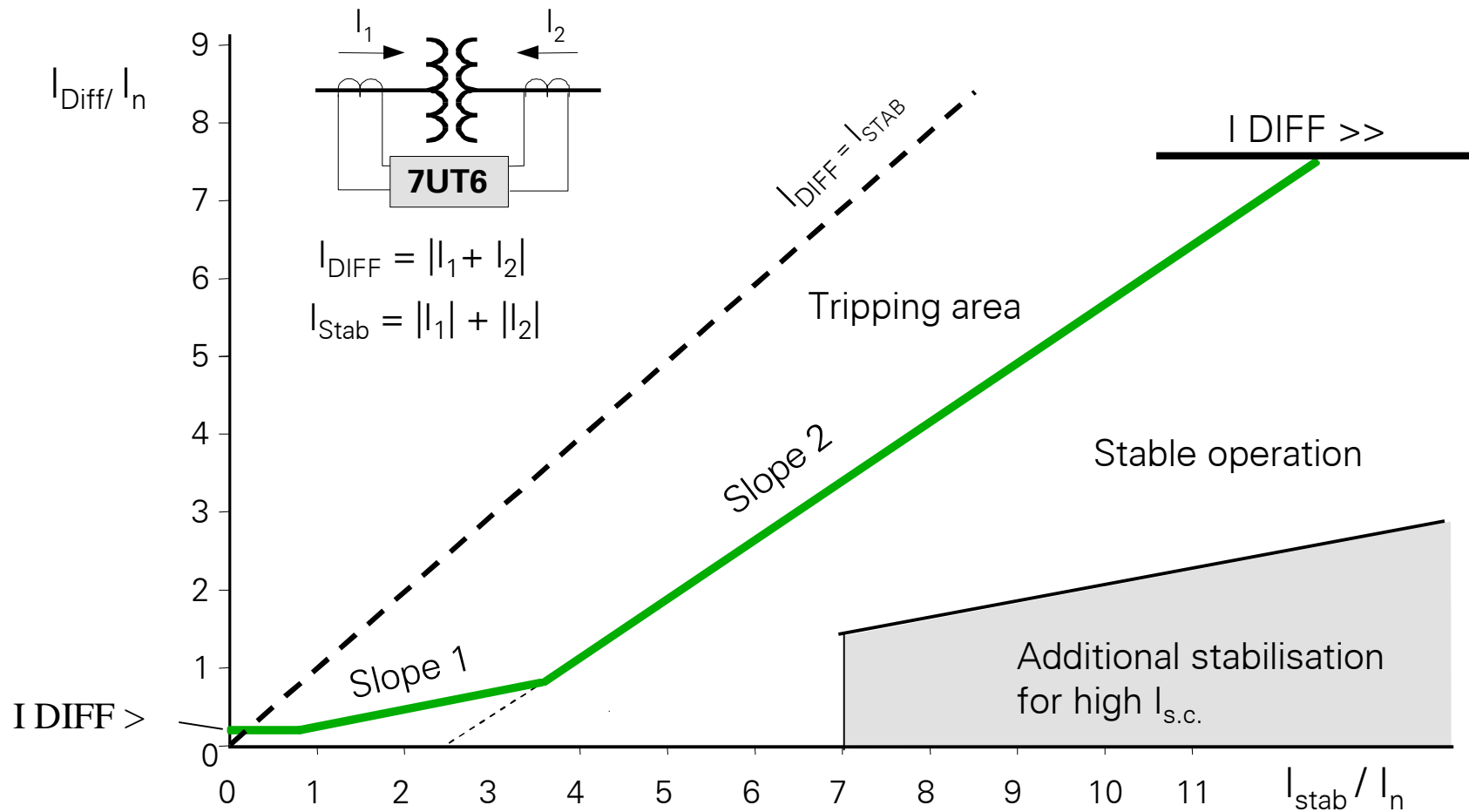



## $I_0$ -elimination / correction: Summary

---

- è  **$I_0$ - elimination** necessary at all windings with earthed neutral or with grounding transformer in the protection range  
Earth fault sensitivity reduced to 2/3 !  
Incorrect fault type indication!
- è  **$I_0$ - correction** provides full earth current sensitivity and correct phase selective fault type indication, however requires CT in the neutral-to-earth connection of the transformer.
- è As an alternative, earth differential protection can be used to enhance earth fault sensitivity.

# Transformer winding to earth fault



## Solid earthed neutral

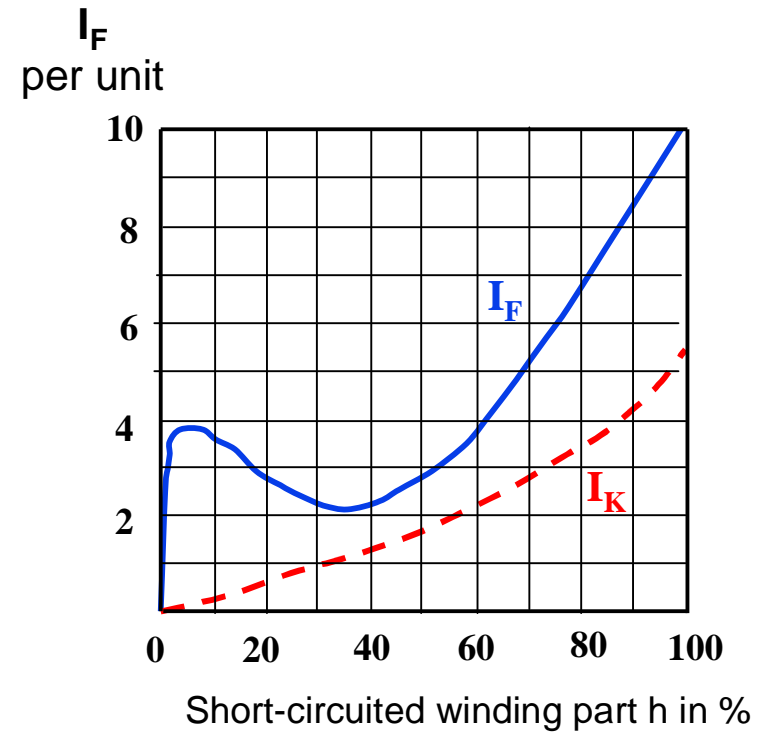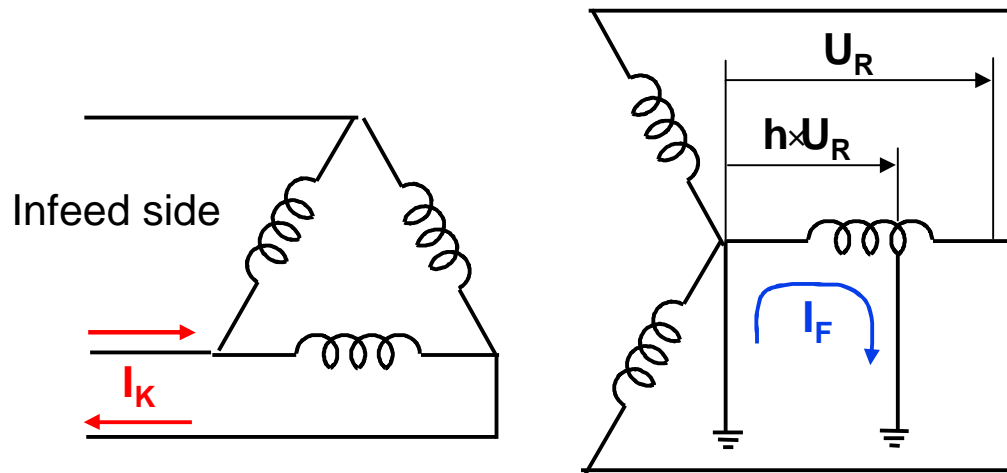

Source: P.M. Anderson: Power System Protection, McGraw-Hill and IEEE Press (Book)

# Transformer winding to earth fault
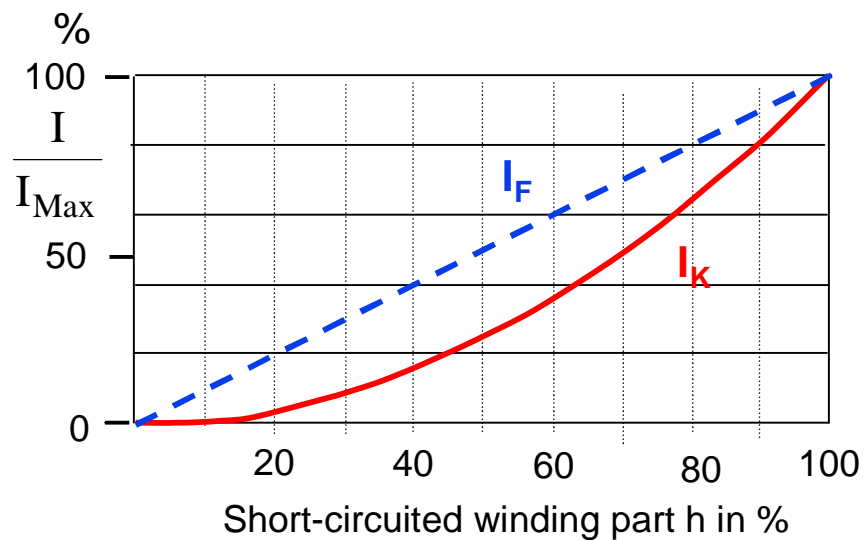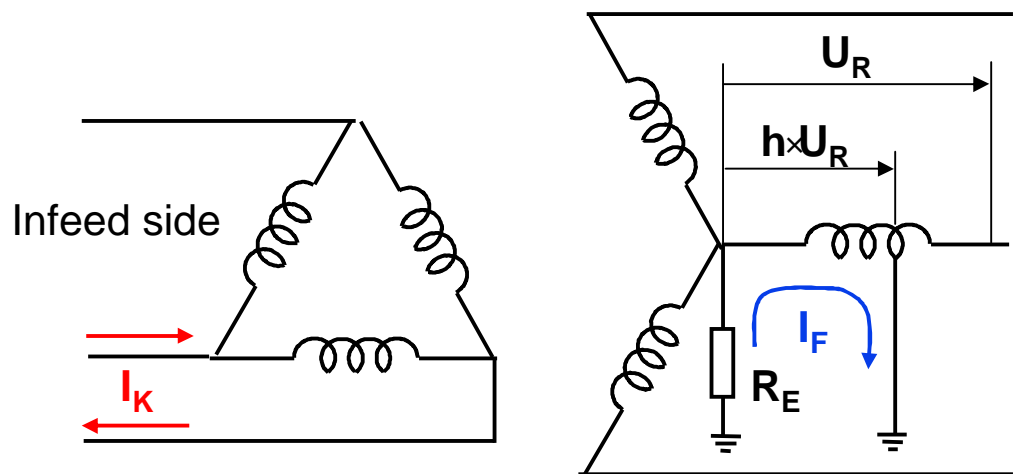
## Resistance or reactance earthed neutral





$$I_F = \frac{h \cdot U_R}{R_E}$$

$$I_K = \frac{h \cdot w_2}{w_1} \cdot I_F = h \cdot \frac{U_{2n}}{U_{1n} \cdot \sqrt{3}} \cdot I_F$$

$$I_K = h^2 \cdot \frac{1}{\sqrt{3}} \cdot \frac{U_{2n}}{U_{1n}} \cdot \frac{U_R}{R_E}$$


Source: P.M. Anderson: Power System Protection, McGraw-Hill and IEEE Press (Book)

# Transformer winding short-circuit

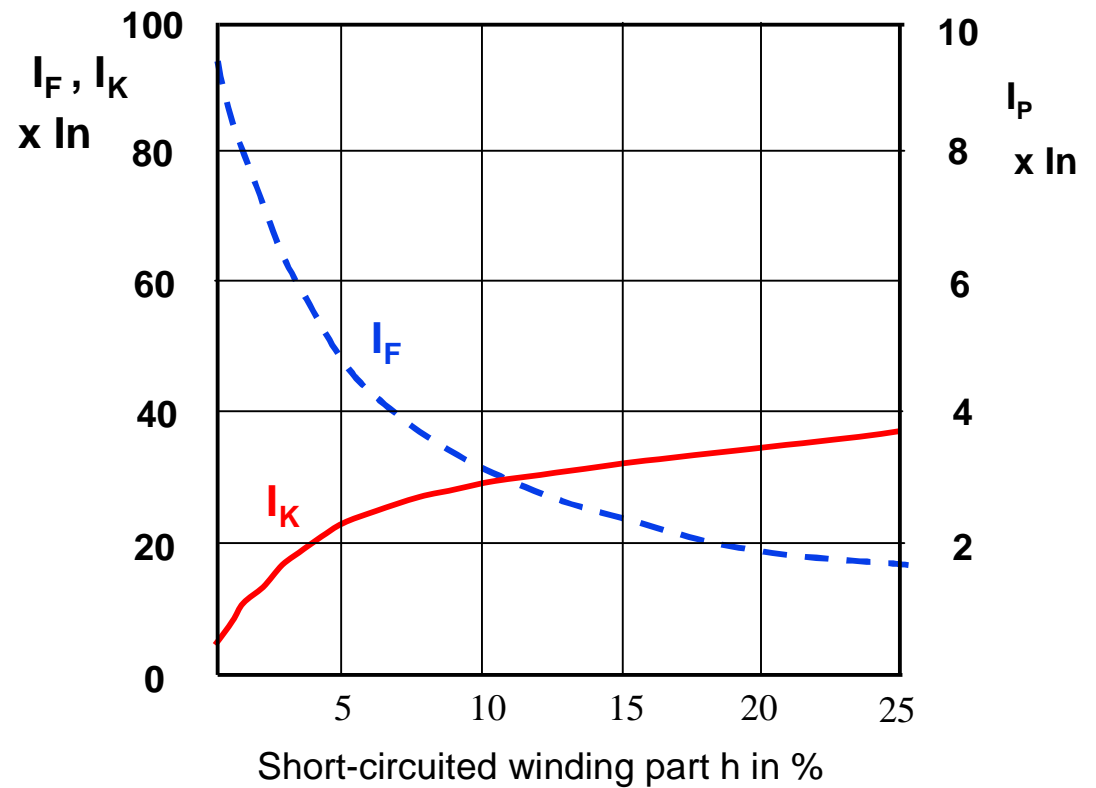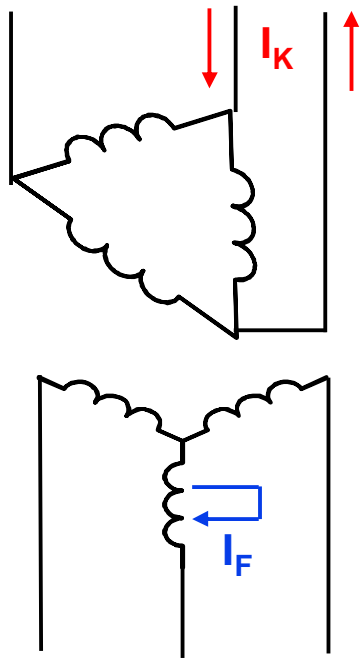

Source: Protective Relays, Application Guide, GEC Alstom T&D, 1995
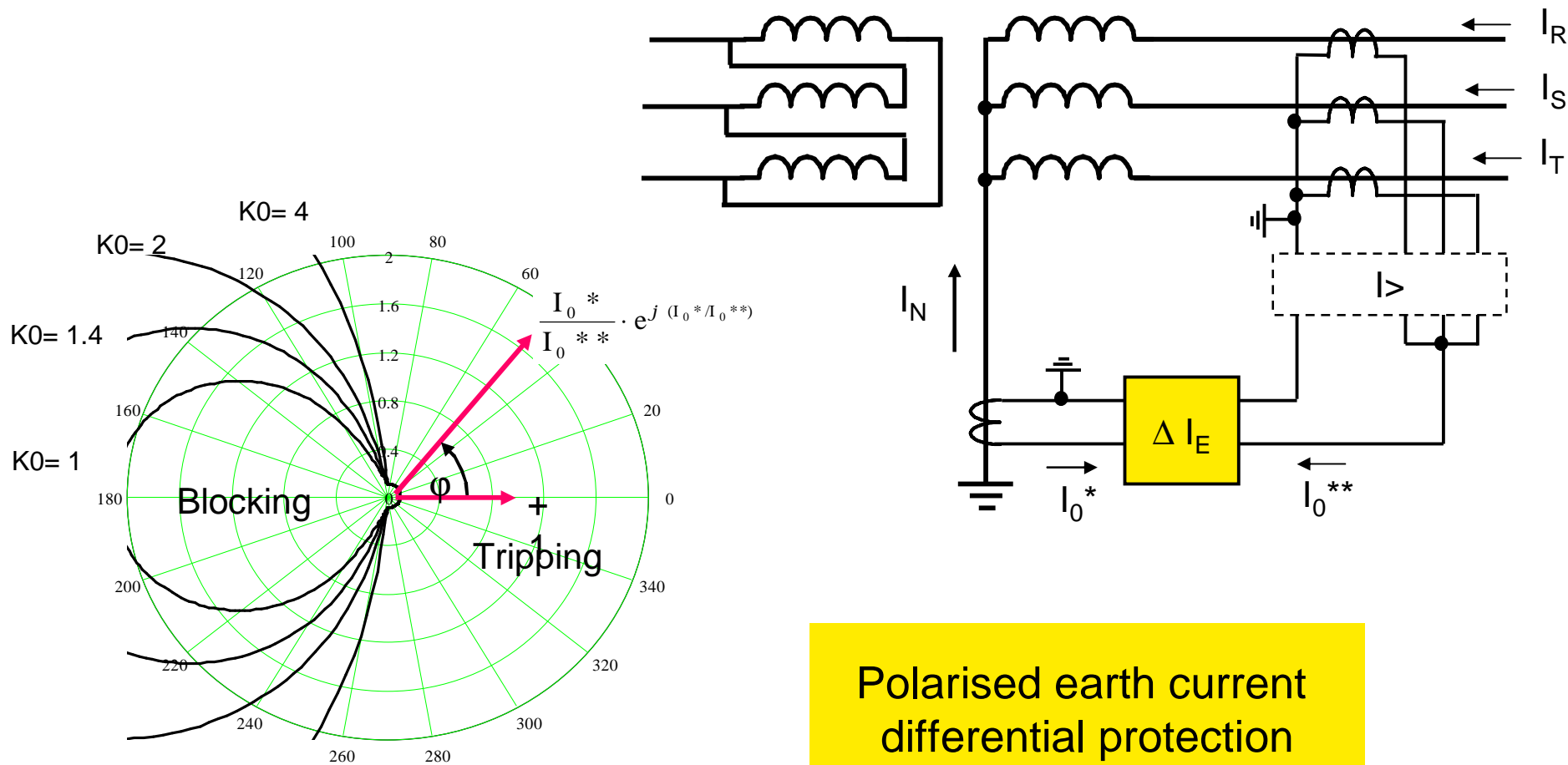
# Restricted earth fault protection of relay 7UT6



Polarised earth current differential protection

## Restricted earth fault protection 87N (7UT6)


### Application aspects

---


- n Increased sensitivity with earth faults near winding neutral  
Preferably used in case of resistance or reactance neutral earthing
- n Sensitive to turns short-circuit
- n  $I_0 / I_N$  amplitude and angle comparison
- n 2nd harmonic stabilised
- n Can protect a separate shunt reactor or neutral earthing transformer in addition to the two winding transformer differential protection
- n **Not applicable with autotransformers!** (as only one stabilising input at transformer terminal side, -- high impedance principle to be used in this case.)




# Transformer HI-earth fault protection

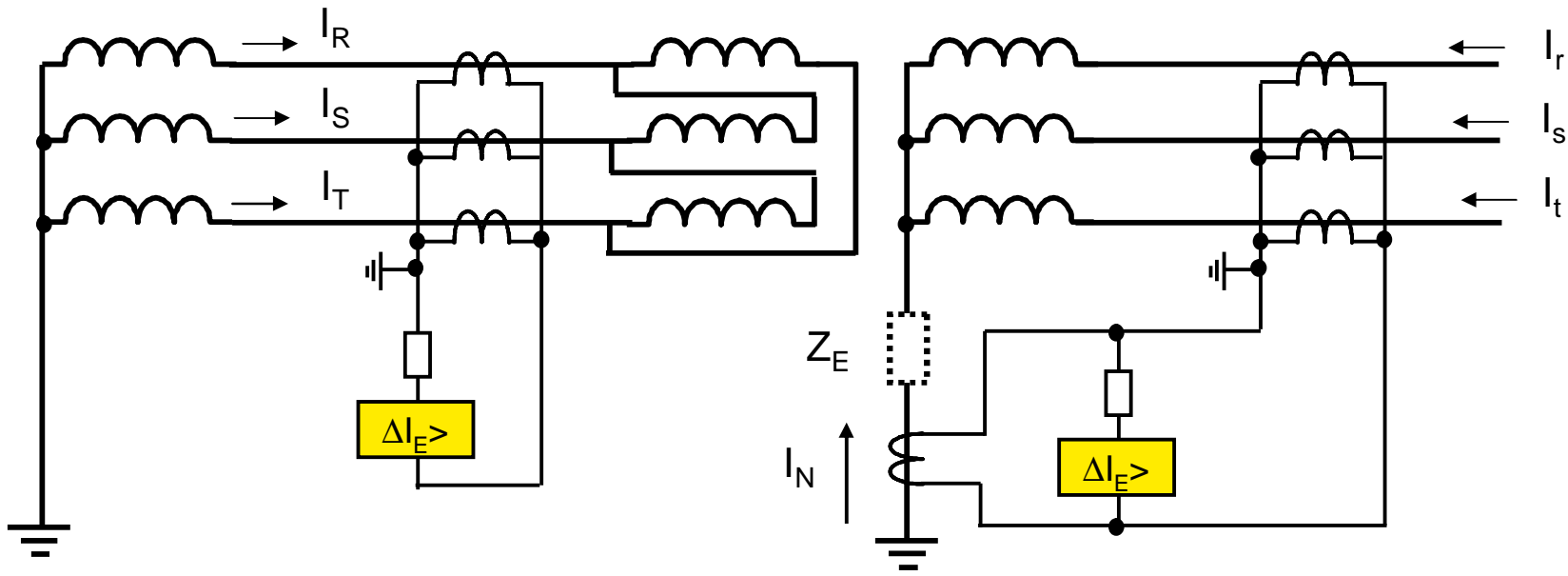

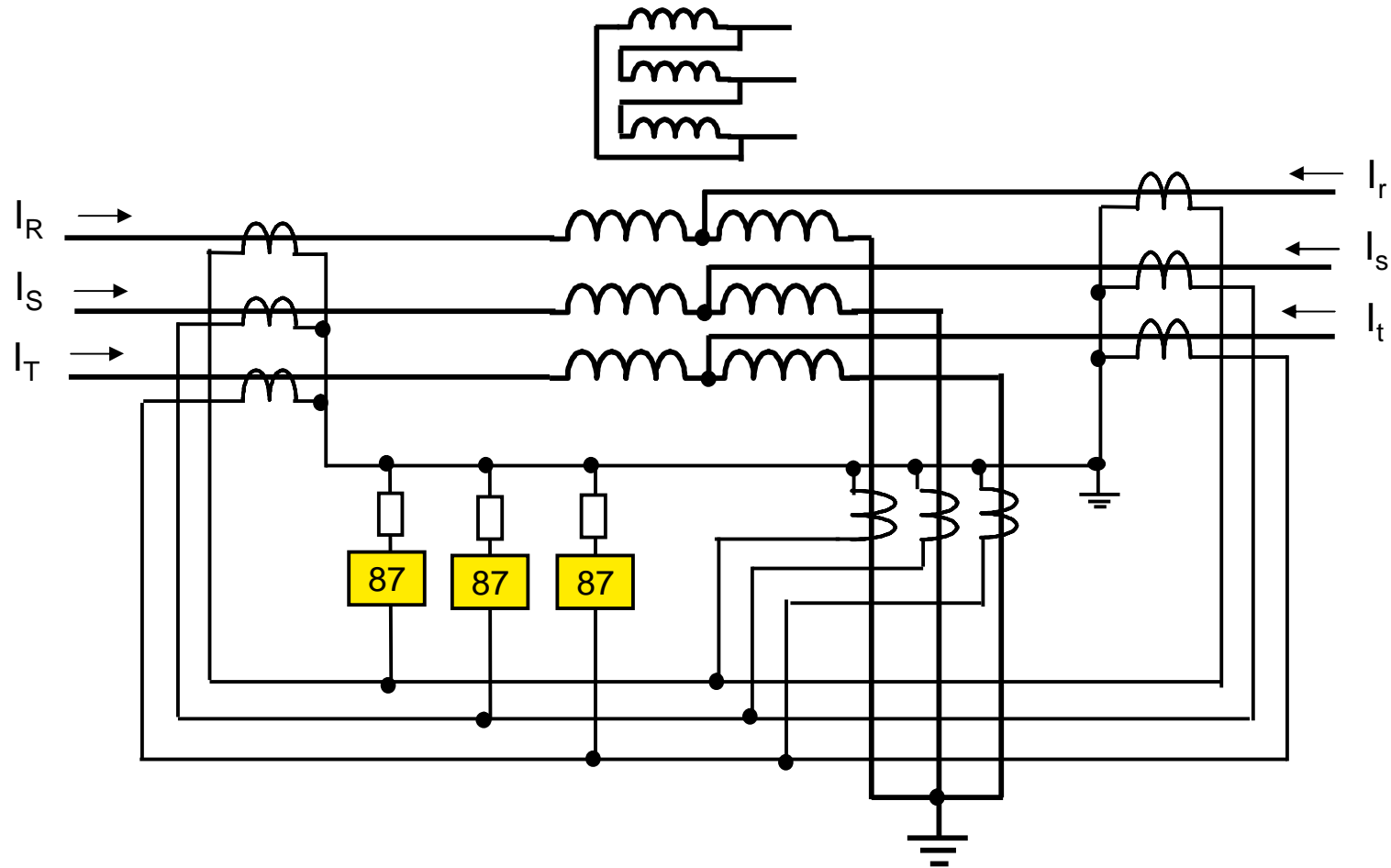
# HI differential protection of an autotransformer



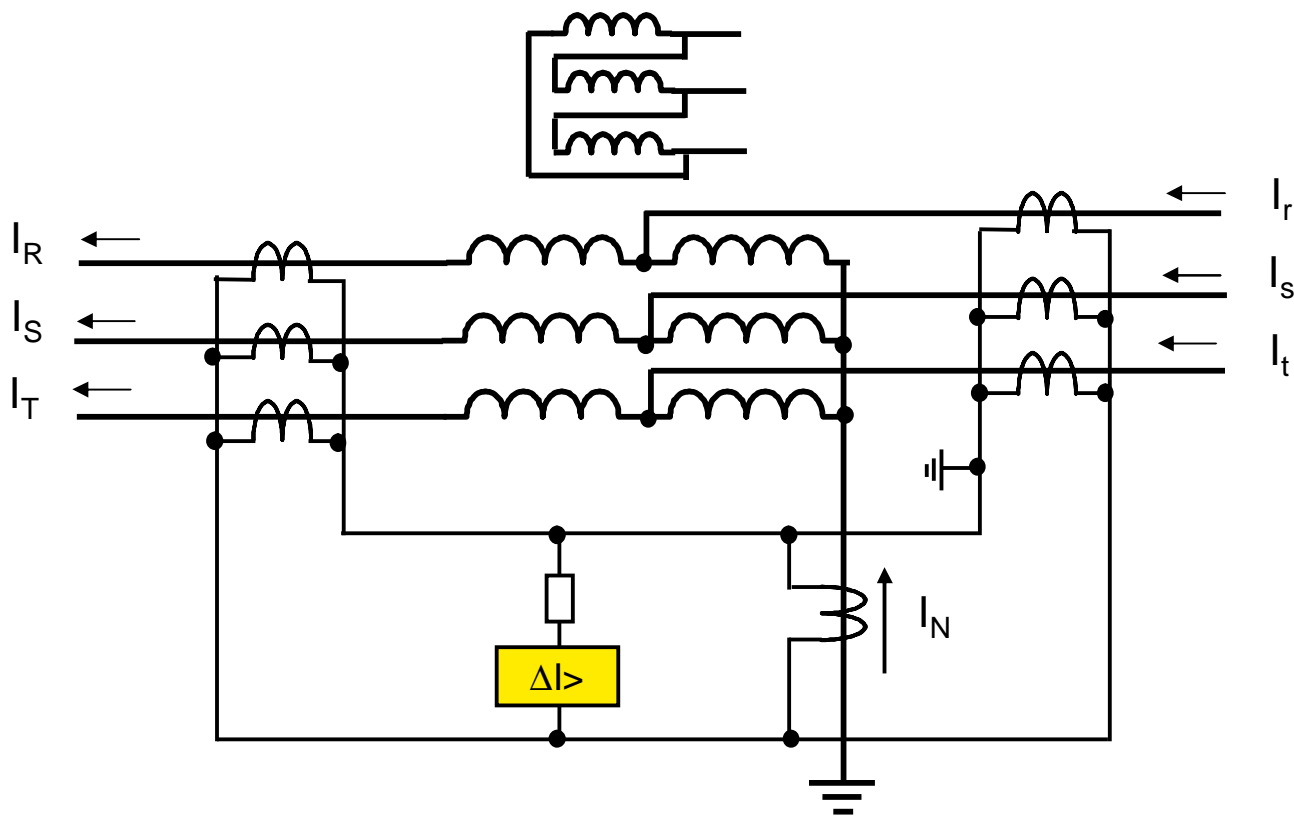
# HI earth fault protection of an autotransformer


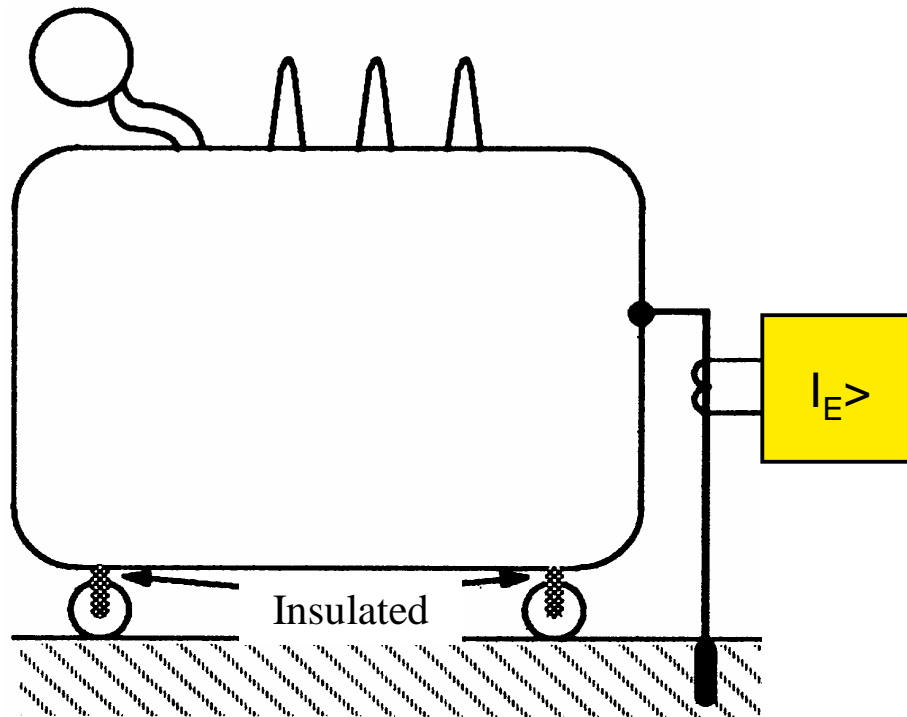
# Transformer tank protection 64T: Principle



# Transformer protection, Relay design

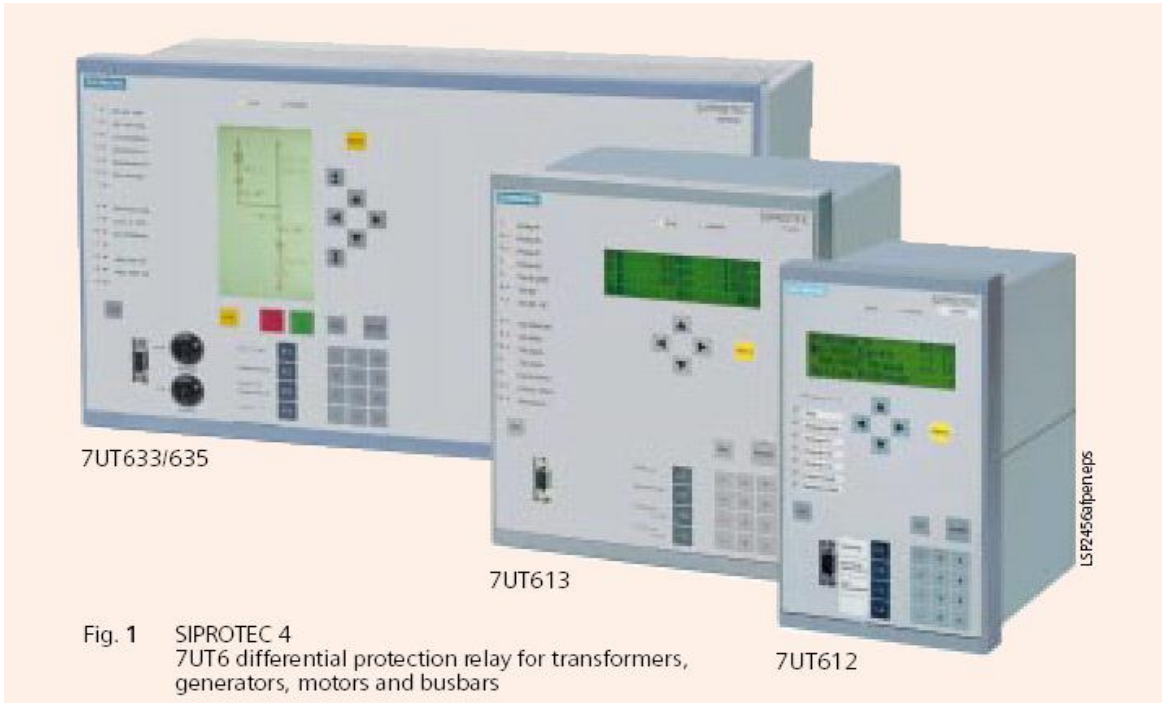

**7UT6** differential protection for

- Transformers
- Generators
- Motors
- Busbars

Fig. 1 SIPROTEC 4  
7UT6 differential protection relay for transformers, generators, motors and busbars

- 7UT612: for protection objects with **2 ends** (1/3 x 19" case 7XP20)
- 7UT613: for protection objects with **3 ends** (1/2 x 19" case 7XP20)
- 7UT633: for protection objects with **3 ends** (1/1 x 19" case 7XP20)
- 7UT635: for protection objects with **5 ends** (1/1 x 19" case 7XP20)


# 7UT6

## Integrated protection functions


---

Function	ANSI No.	Function	ANSI No.
Differential	87T	Overfluxing V/Hz	24
Earth differential	87 N	Breaker failure	50BF
Phase overcurrent,	50/51	Temperature monitoring	38
Neutral overcurrent $I_N >, t$	50N/51N	Hand reset trip	86
Ground overcurrent ( $I_E, t$ )	50G/51G	Trip circuit supervision	74TC
Unbalanced current $I_2 >, t$	46	Binary inputs for tripping commands	
Thermal overload IEC 60255-8	49		
Therm. OL IEC 60354 (hot spot)	49		


# Application range (7UT6)

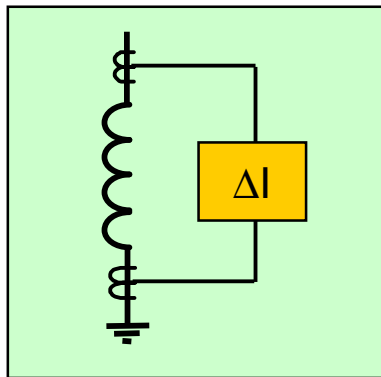


*Shunt Reactor*

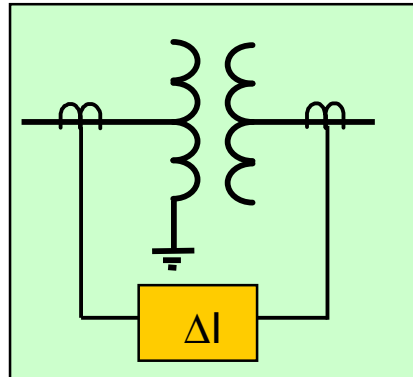


*Two winding transformer*

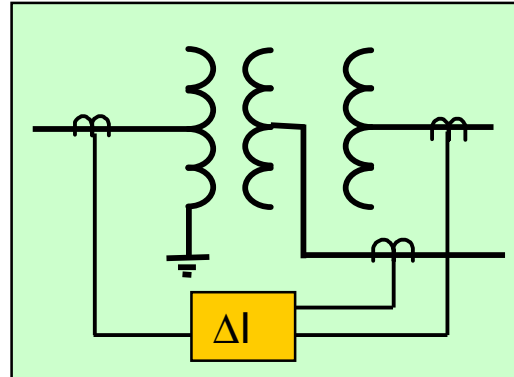


*Three winding transformer*

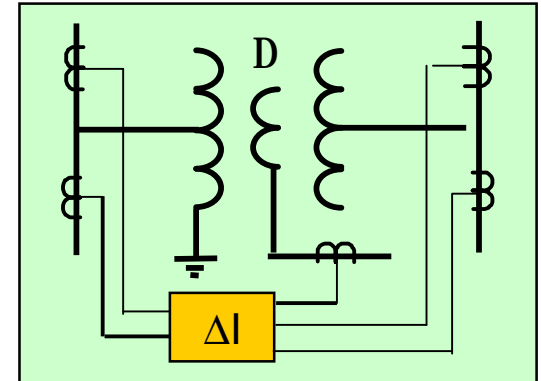

*Transformer bank (1-1/2-LS)*

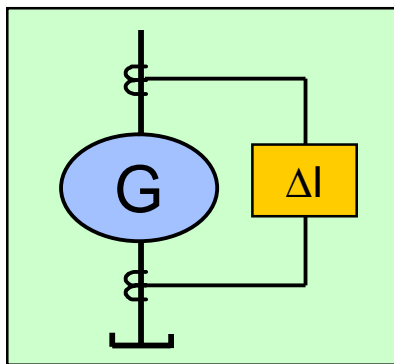


*Generator / Motor*

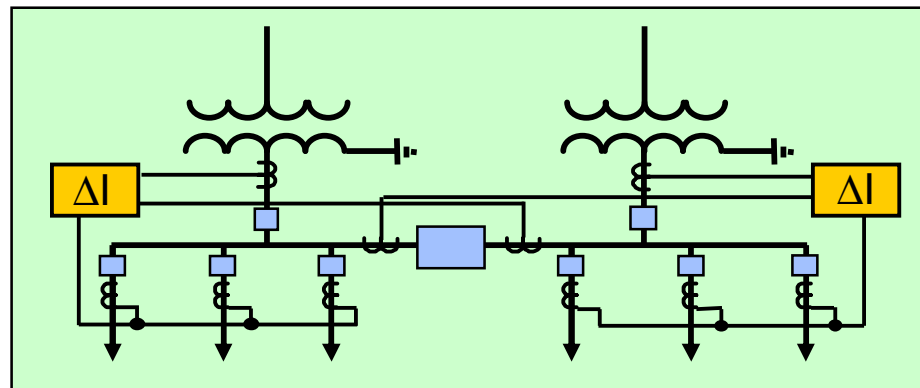


*Busbars*
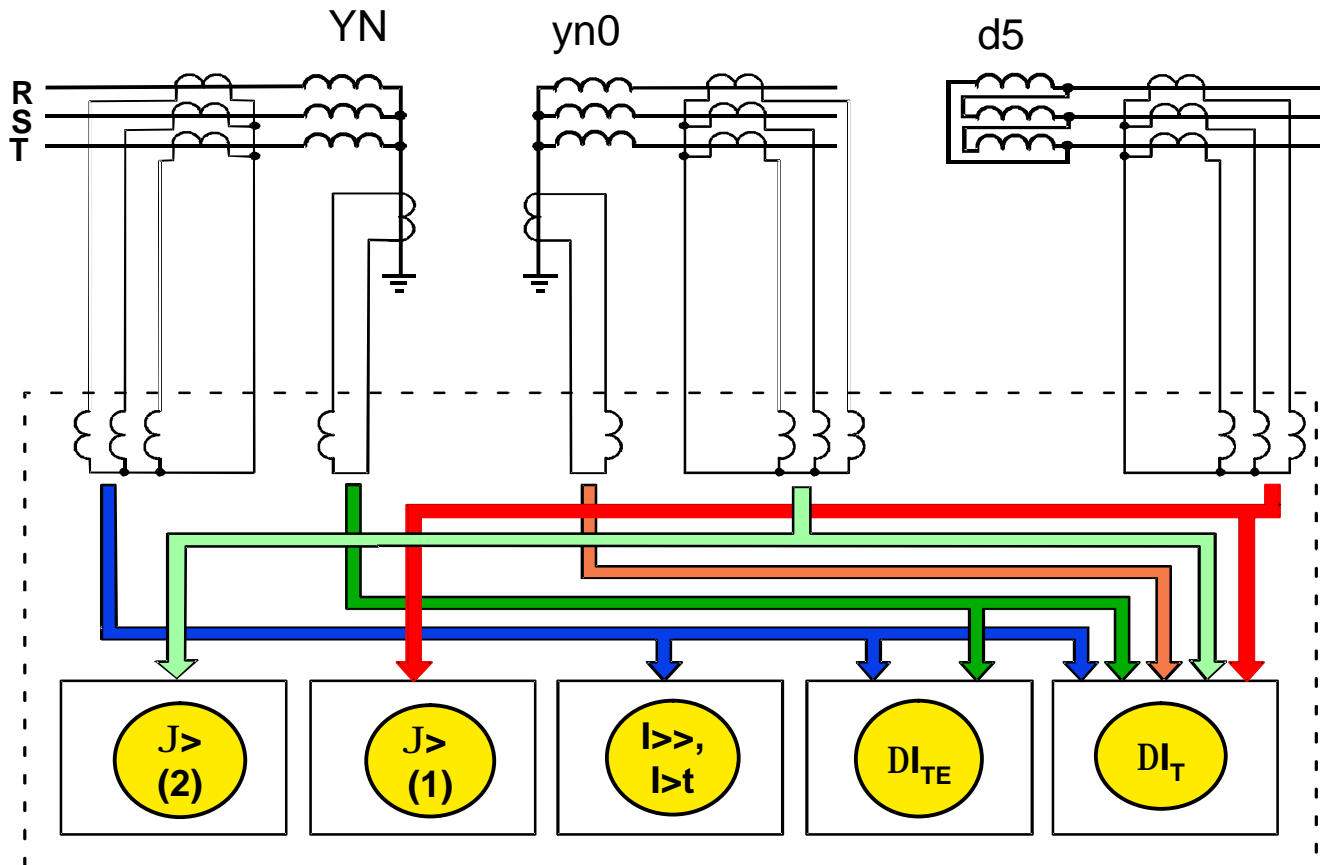
# Digital transformer protection relay 7UT613: Current inputs and integrated protective functions






# Operating characteristic (7UT6)

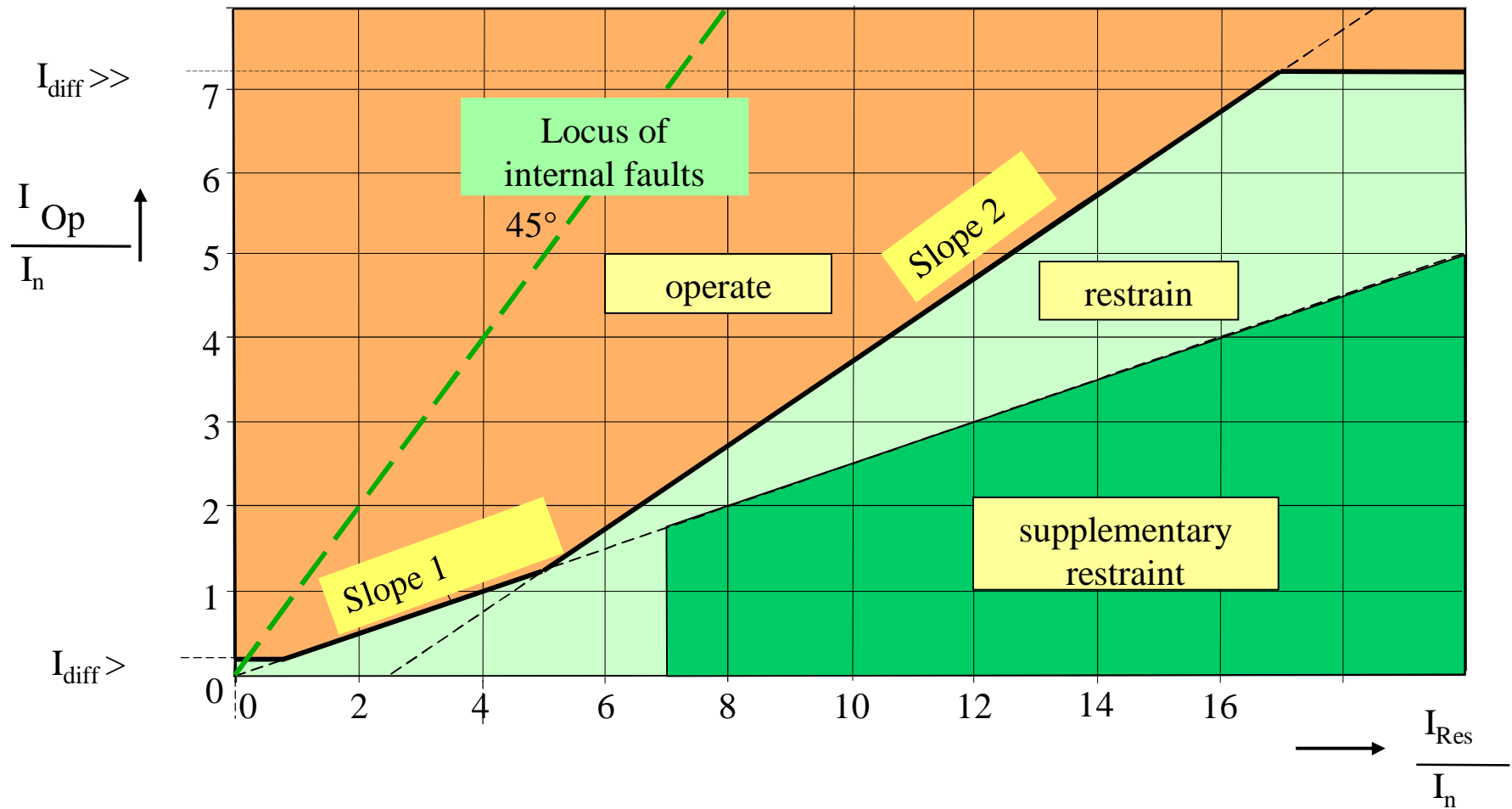


## 7SA6: Temperature monitoring

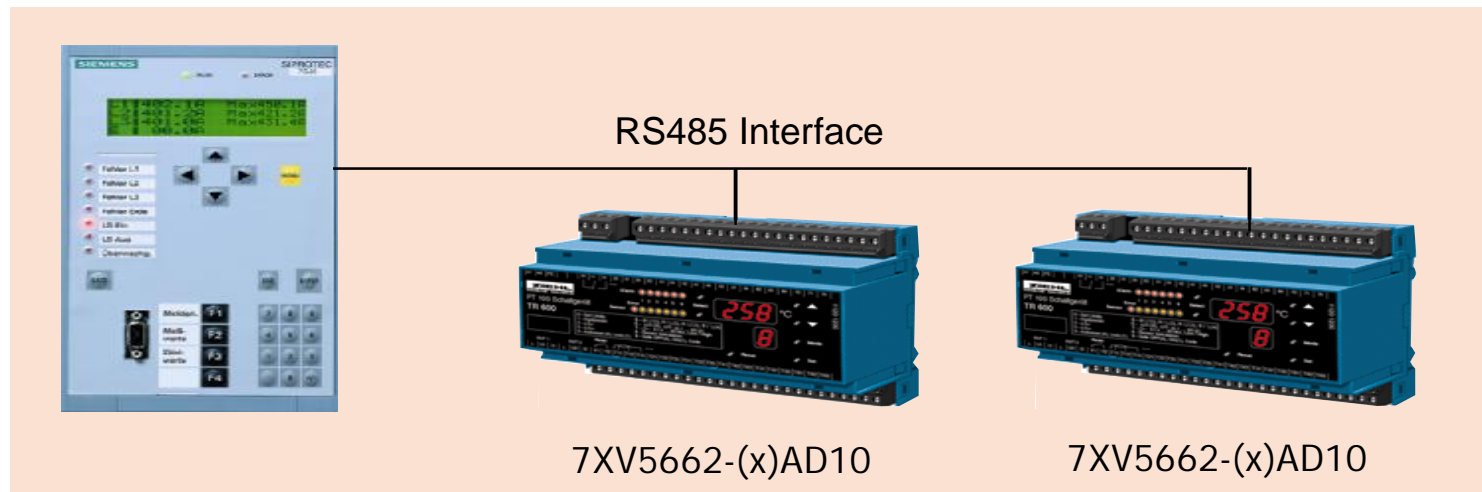

- Two thermo-devices can be connected to the serial service interface (RS485)
- Monitoring of up to 12 measuring points (6 per thermo-device)
  - each with two pick-up levels
- Display of the measured temperatures
  - directly at the thermo-device (which can also be used stand alone)
  - at the relay
- One input is reserved for hot spot monitoring (measurement of oil temperature)
- Thermistors: Pt100, Ni100 or Ni120

# 7UT6: Temperature monitoring with hot spot calculation (1)

Example: Natural cooling

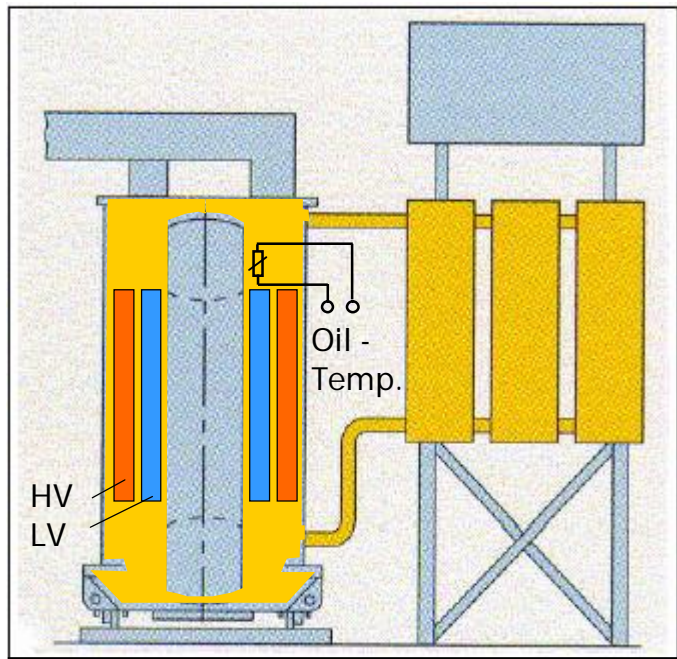

$$\Theta_h = \Theta_o + H_{gr} \cdot k^Y$$

$\Theta_h$ = hot spot temperature

$\Theta_o$ = oil temperature

$H_{gr}$ =hot-spot-to-oil temperature gradient

$k$ = load factor  $I/I_n$

$Y$ = winding exponent

Aging rate:

$$V = \frac{\text{Aging at } \Theta_h}{\text{Aging at } 98^\circ\text{C}} = 2^{(\Theta_h - 98)/6}$$

98° is reference for the aging of Cellulose insulation

Mean value of aging during a fixed time interval:

$$L = \frac{1}{T_2 - T_1} \cdot \int_{T_1}^{T_2} V \cdot dt$$


# 7UT6: Temperature monitoring with hot spot calculation (2)

Number	Measured value	Value
01060	Hot spot temperature of leg 1	102 °C
01061	Hot spot temperature of leg 2	102 °C
01062	Hot spot temperature of leg 3	102 °C
01063	Aging Rate (L)	1.6
01066	Load Reserve to warning level	-10 %
01067	Load Reserve to alarm level	5 %

Number	Measured value	Value
01068	Temperature of RTD 1	73 °C


$$\Theta_h = \Theta_o + H_{gr} \cdot k^Y \approx 73 + 23 \cdot 1.15^{1.6} = 102^\circ\text{C}$$
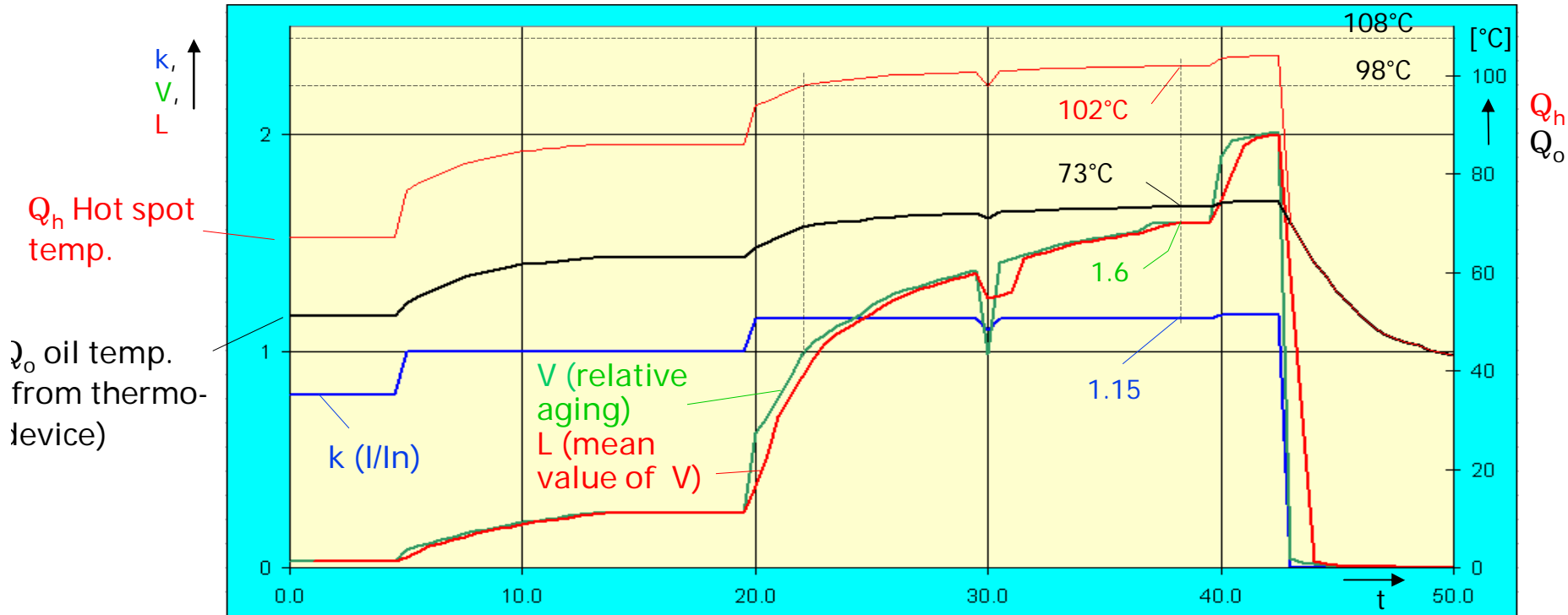
$$V = 2^{(\Theta_h - 98)/6} = 2^{(102 - 98)/6} \approx 1.6$$




# 7UT6: Commissioning und service tool (1)

## WEB-Technology

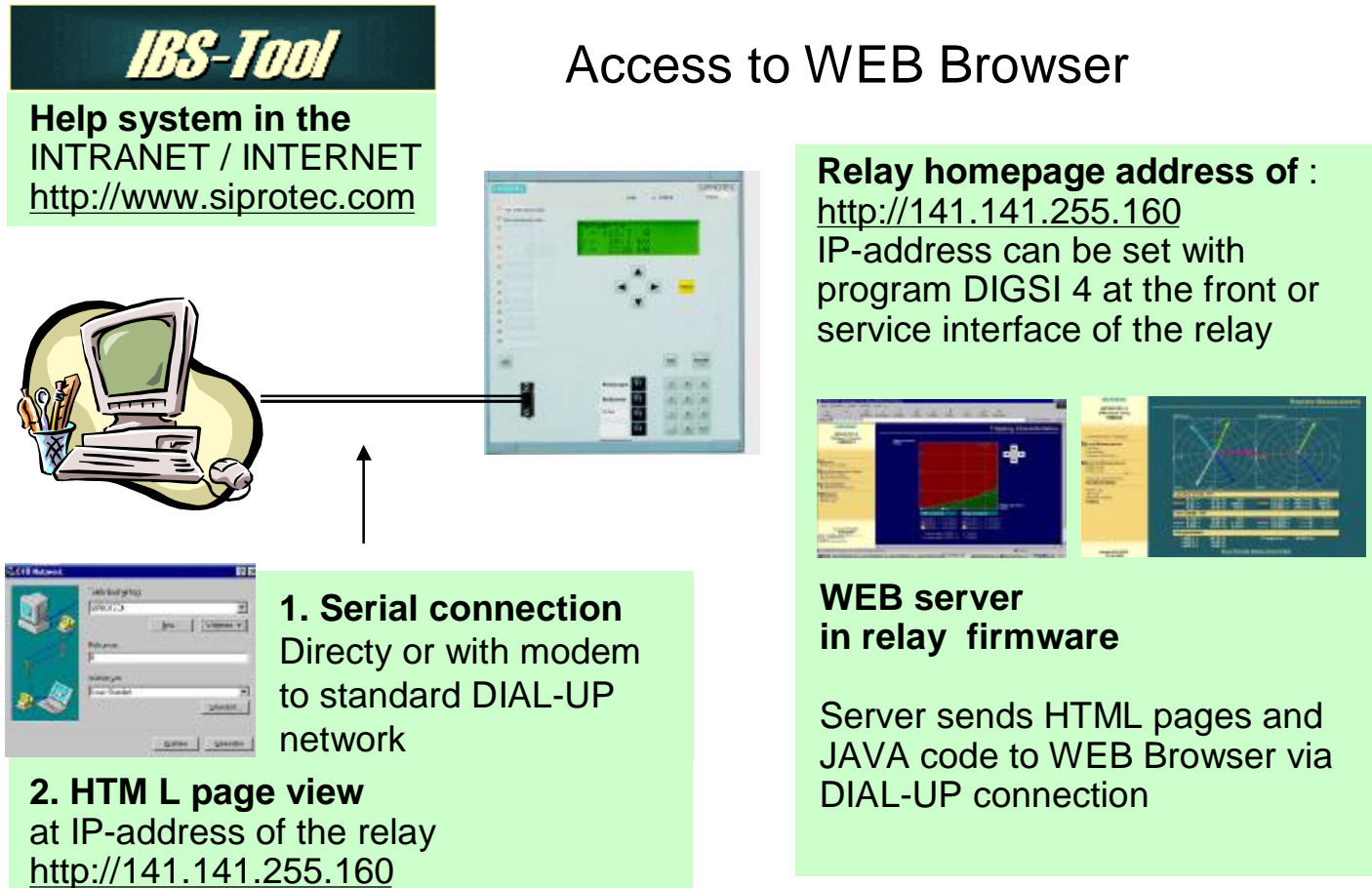


# 7UT6: Commissioning and service tool (2)
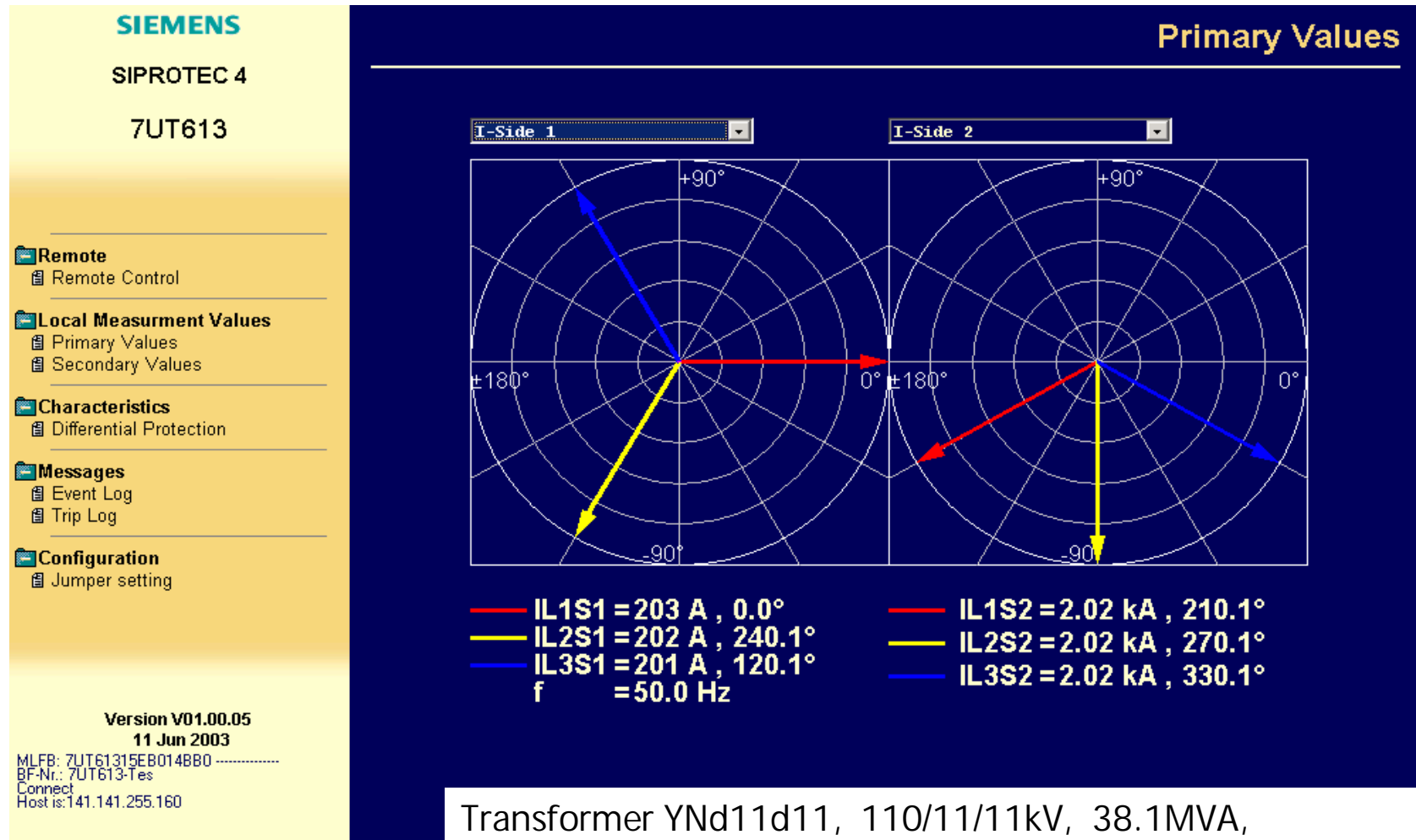
## Display of current phasors of all terminals



# 7UT6: Commissioning and service tool (3)

## Display of operating/restraint state

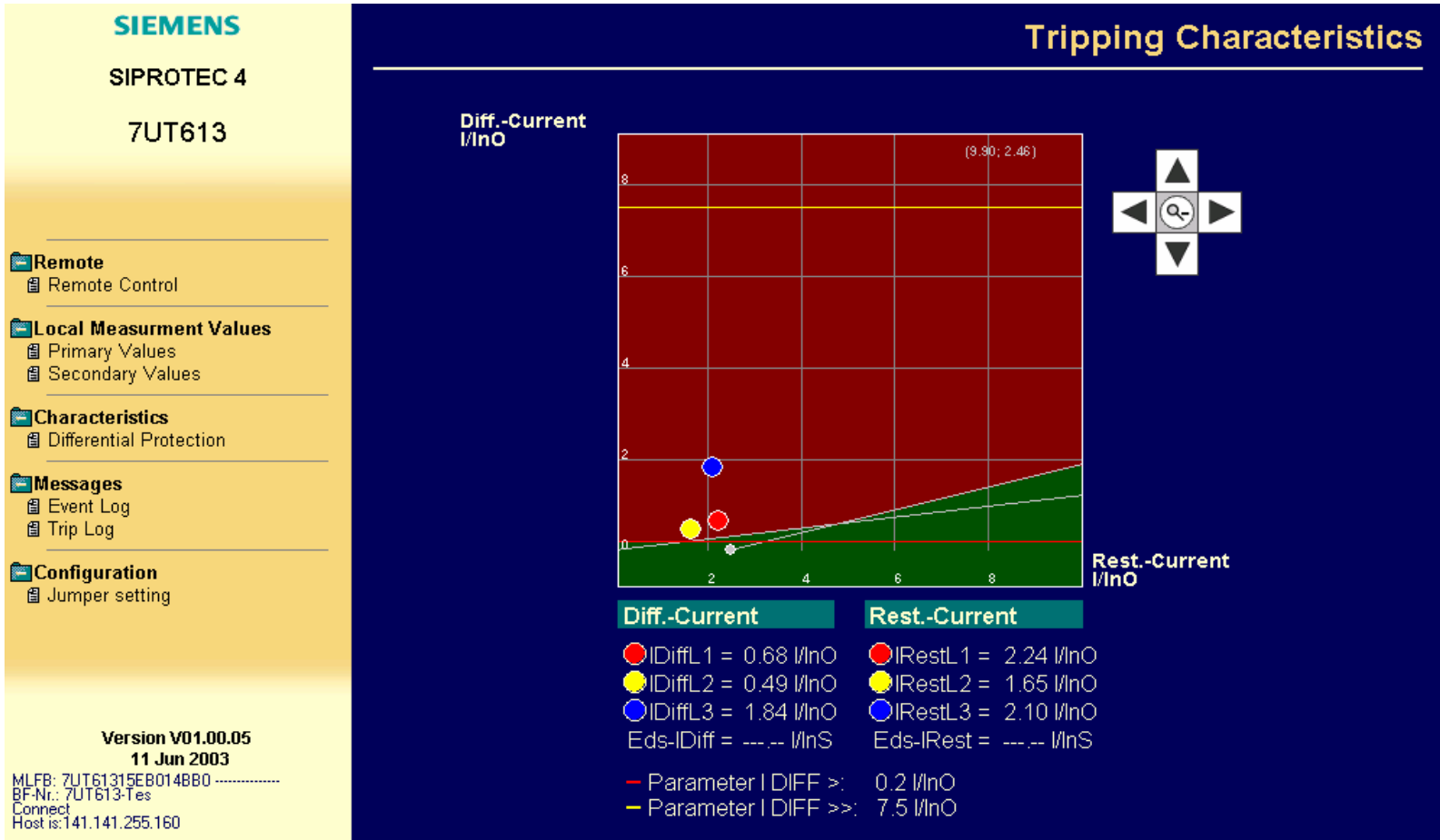


Transformer YNd11d11, 110/11/11kV, 38.1MVA, IL2S2à wrong polarity


# Application examples



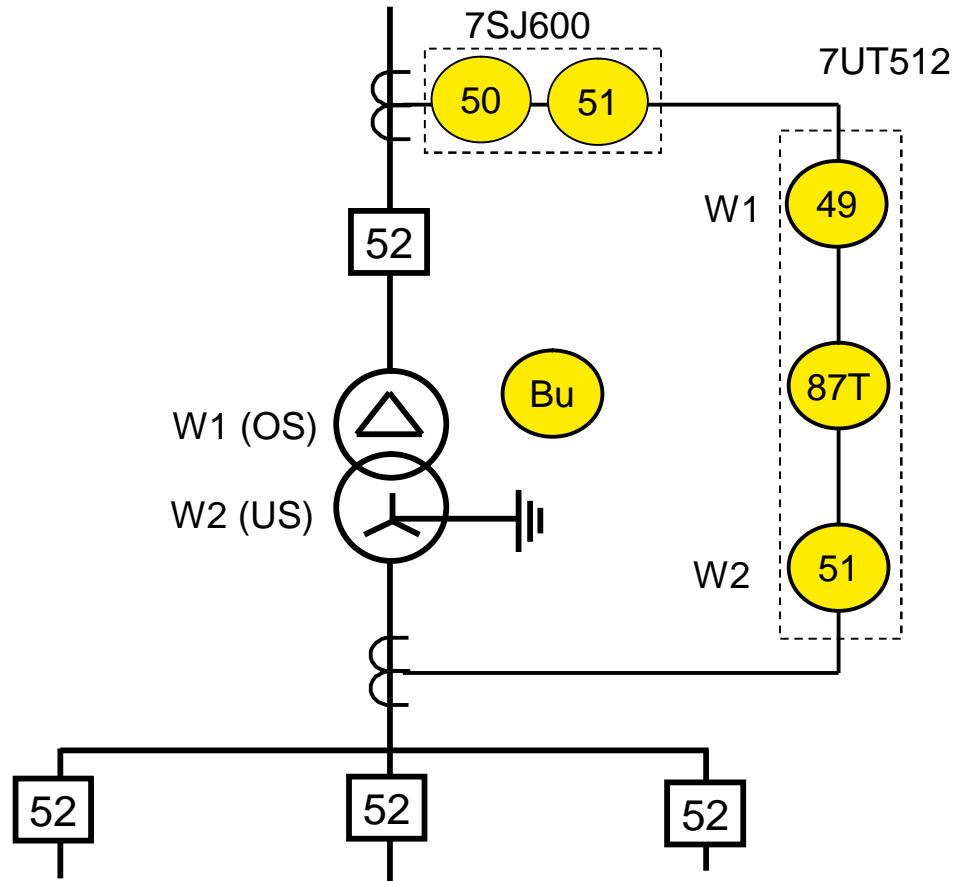
# Protection of a two winding transformer



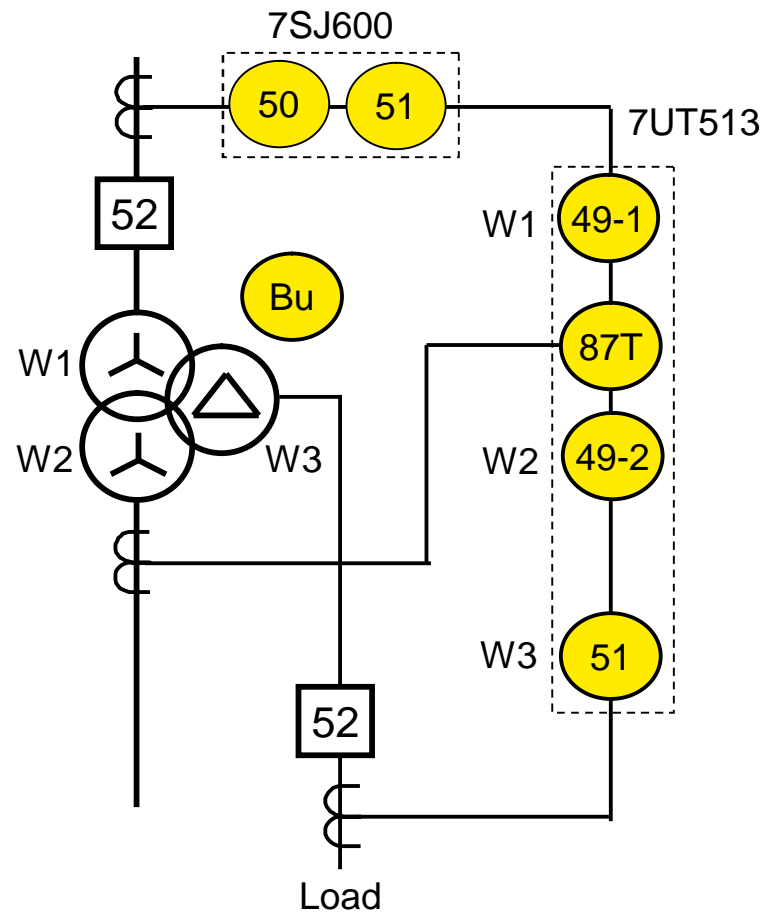
# Protection of a three winding transformer



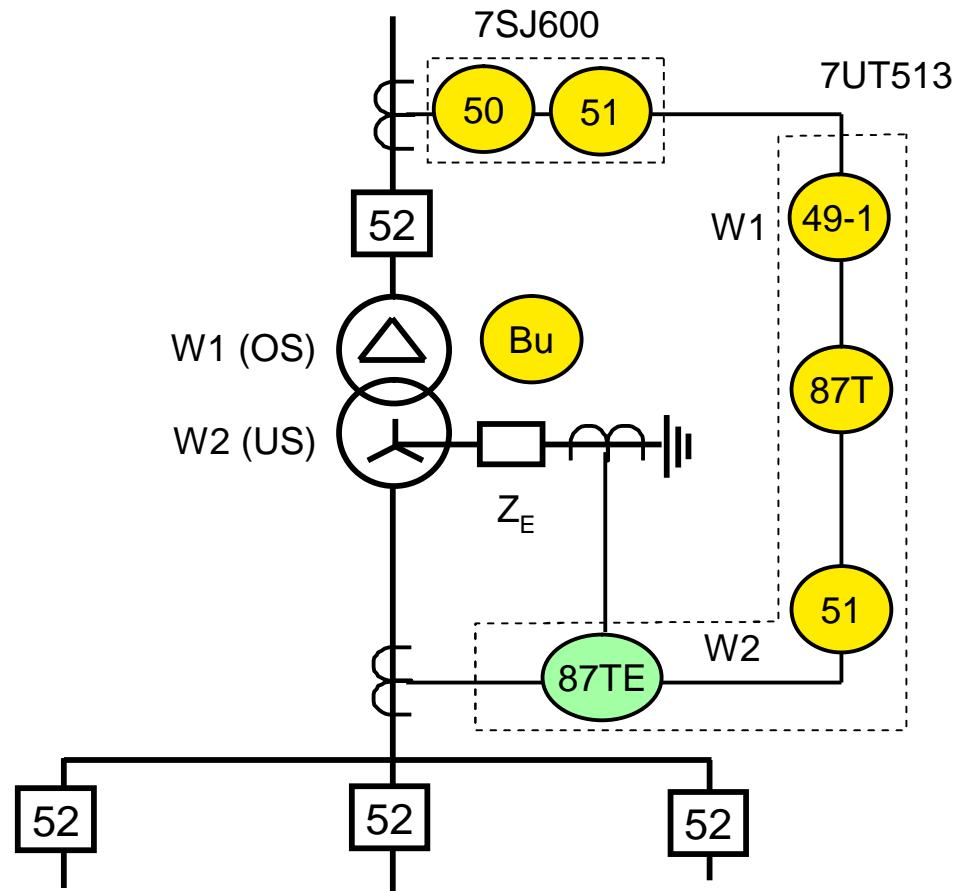
# Restricted earth fault protection for a two winding transformer




# Protection of an autotransformer

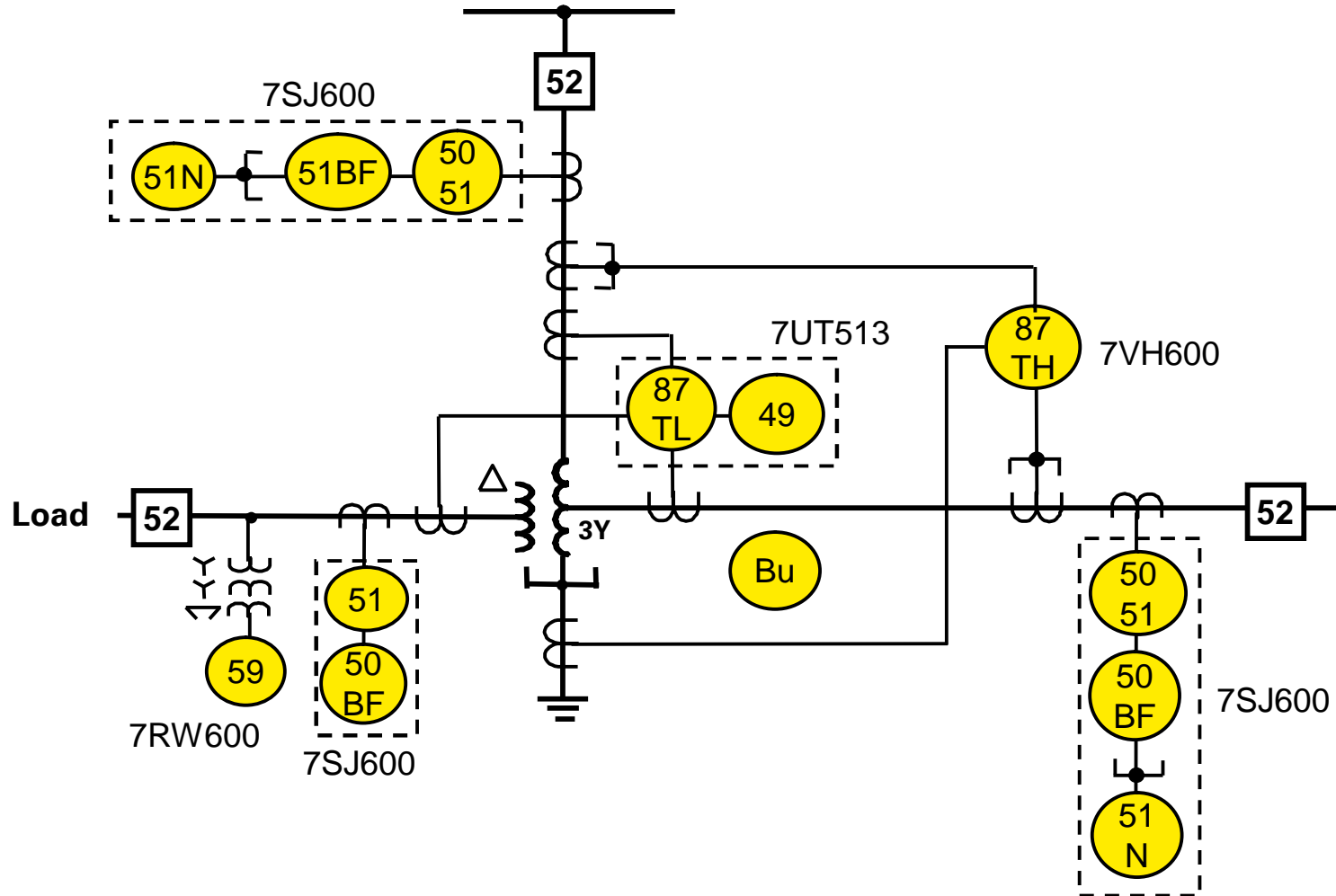

# Protection of a large transformer bank

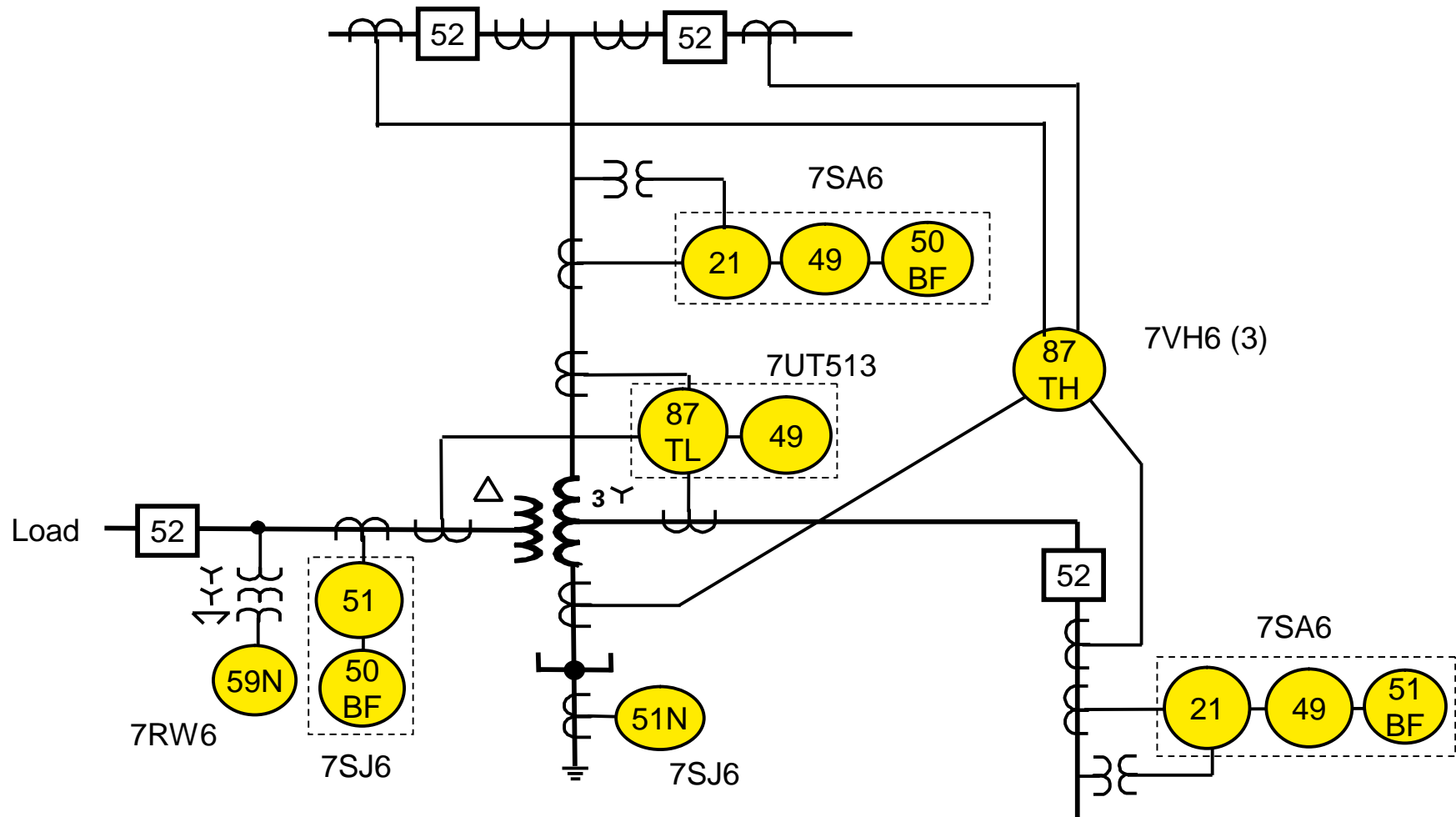

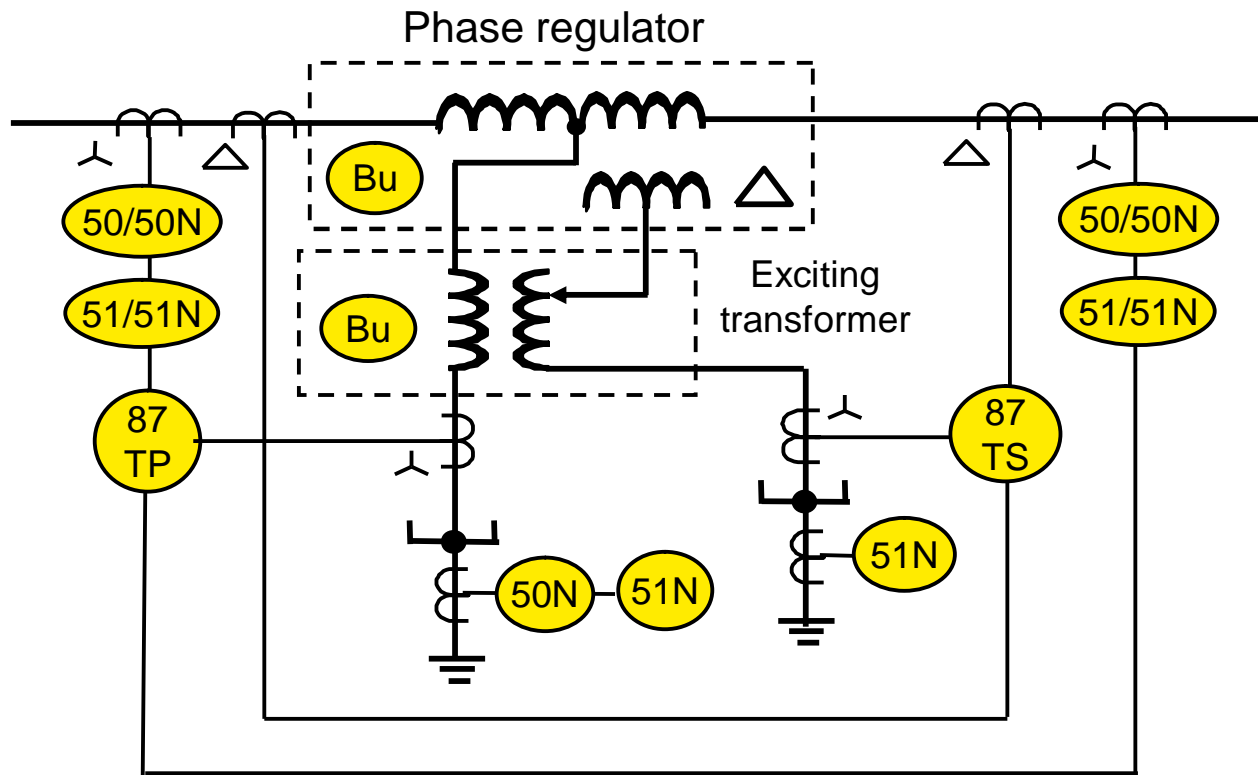
# Protection of a phase regulating transformers




# Protection of a compensation reactor

## No phase CTs at neutral side

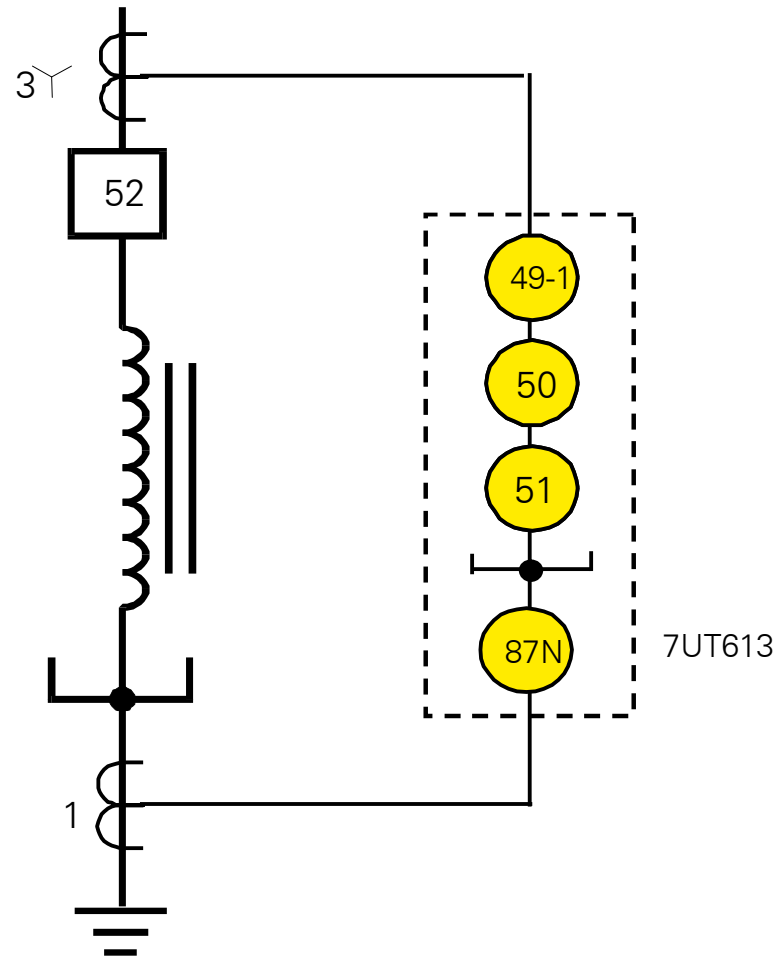

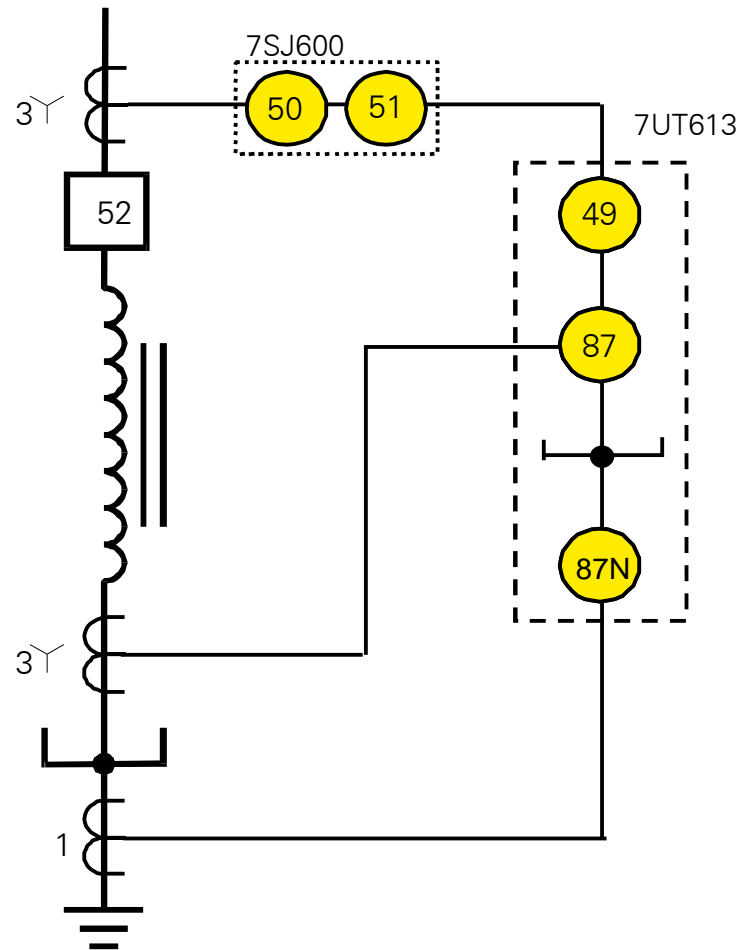
# Protection of a compensation reactor with phase CTs at neutral side






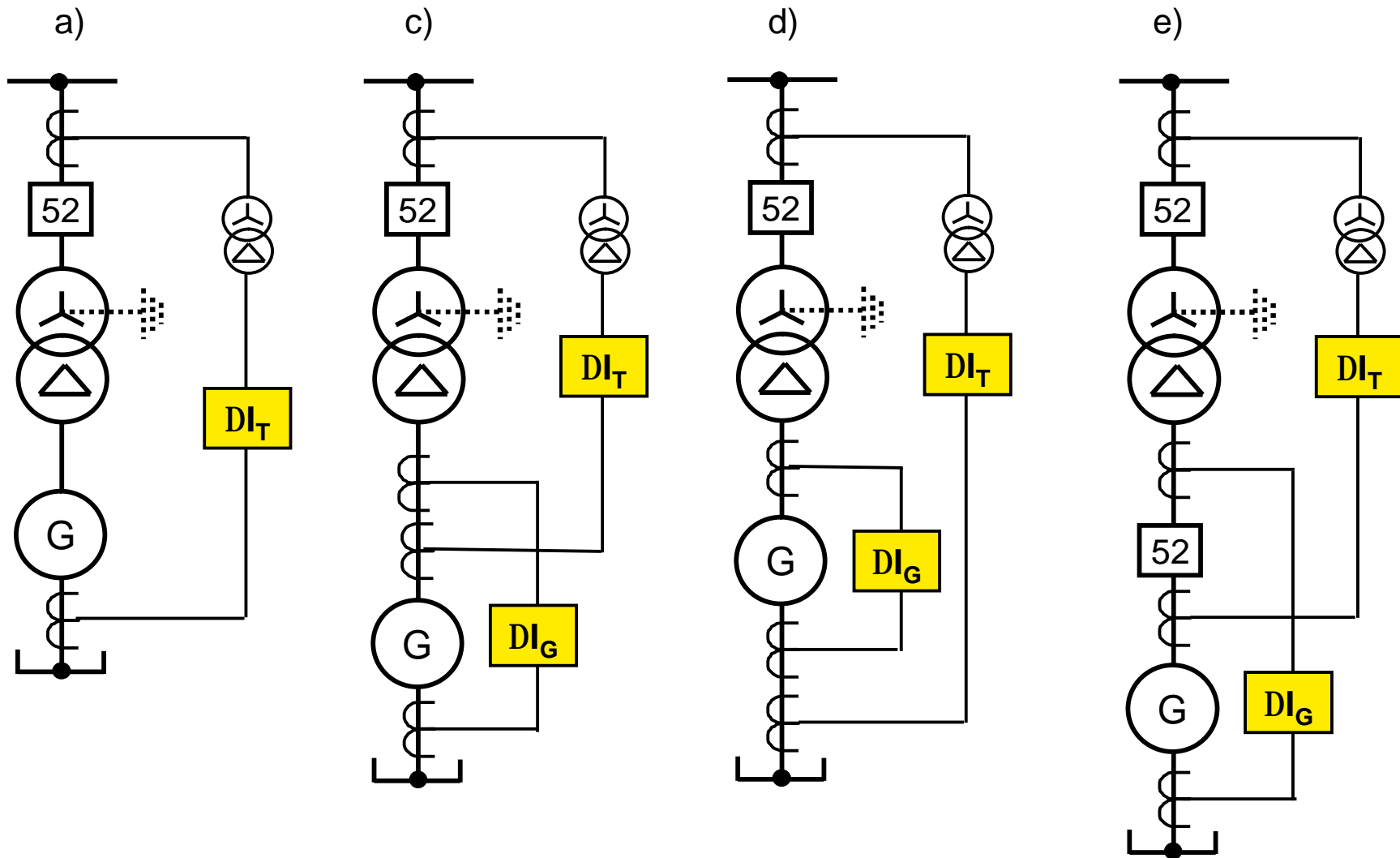
# Differential protection of generation units (1)


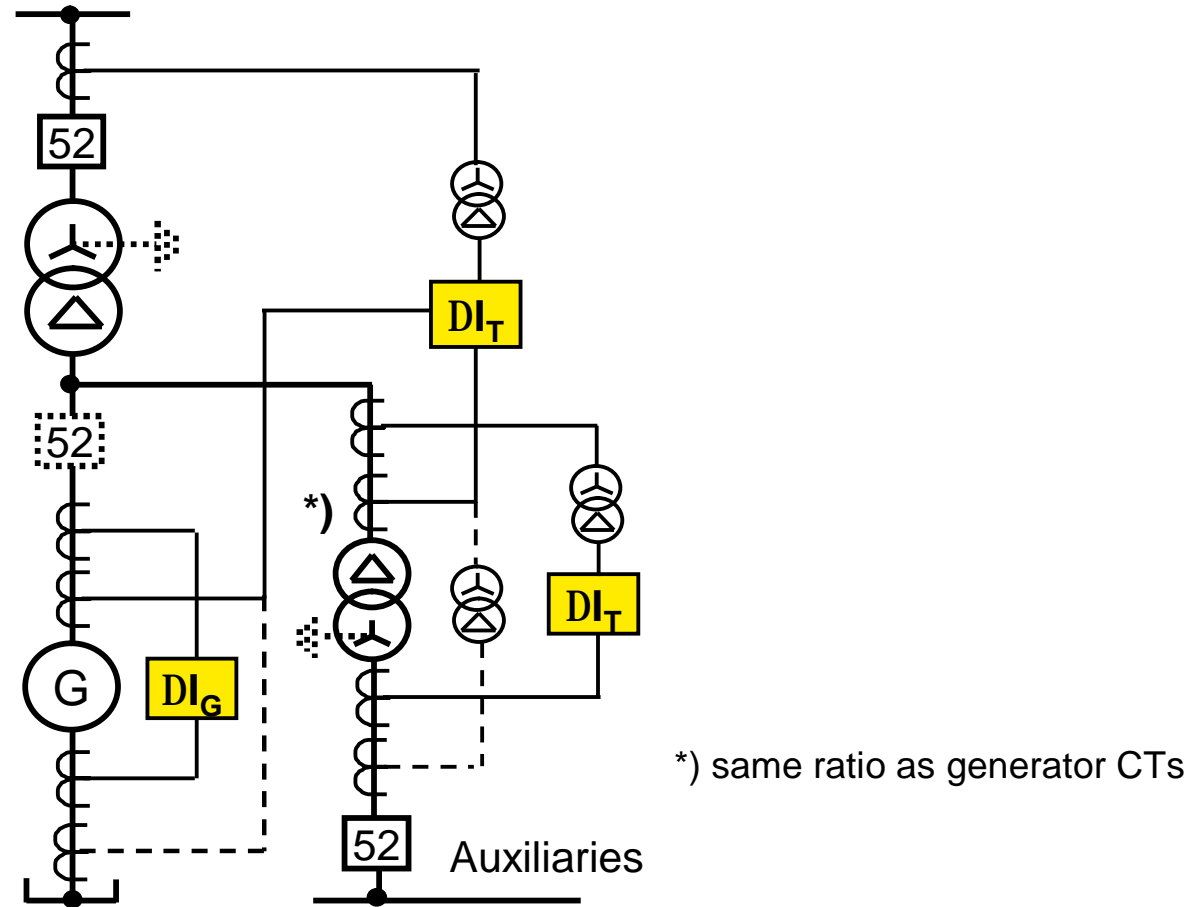
## Differential protection of generation units (2)


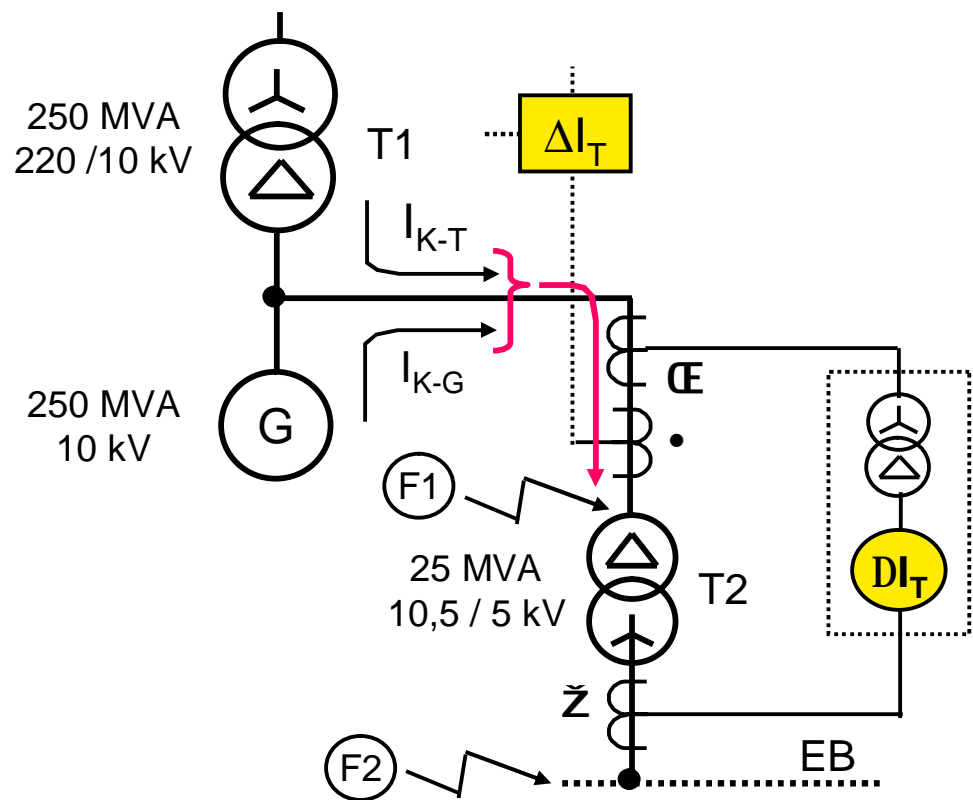
# Dimensioning of CTs at the station service transformer



Fault F1:  
 High fault currents in relation to the rated current of the station-service transformer T2 ( $>100 \times I_N$ ) and long DC time constants ( $>100$  ms) require considerable over-dimensioning of CT cores CE and • .

Fault F2:  
 uncritical as current is limited by short-circuit impedance of station-service transformer T2. CT Z can have normal dimensions




# Digital Transformer Differential Protection


## I0-correction + vector group adaptation

**SIEMENS**
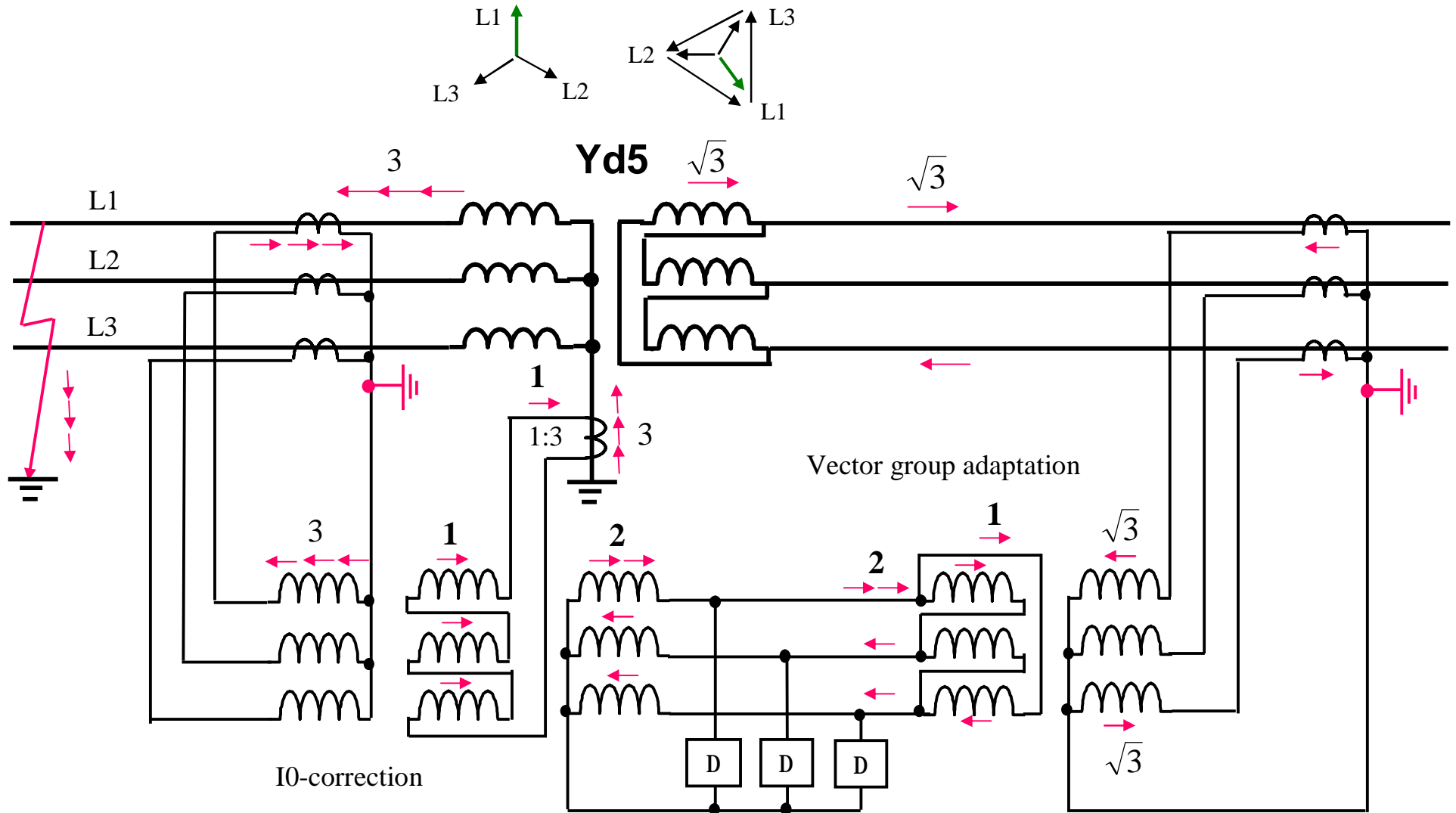
# Transformer differential protection with I<sub>0</sub>-correction External fault



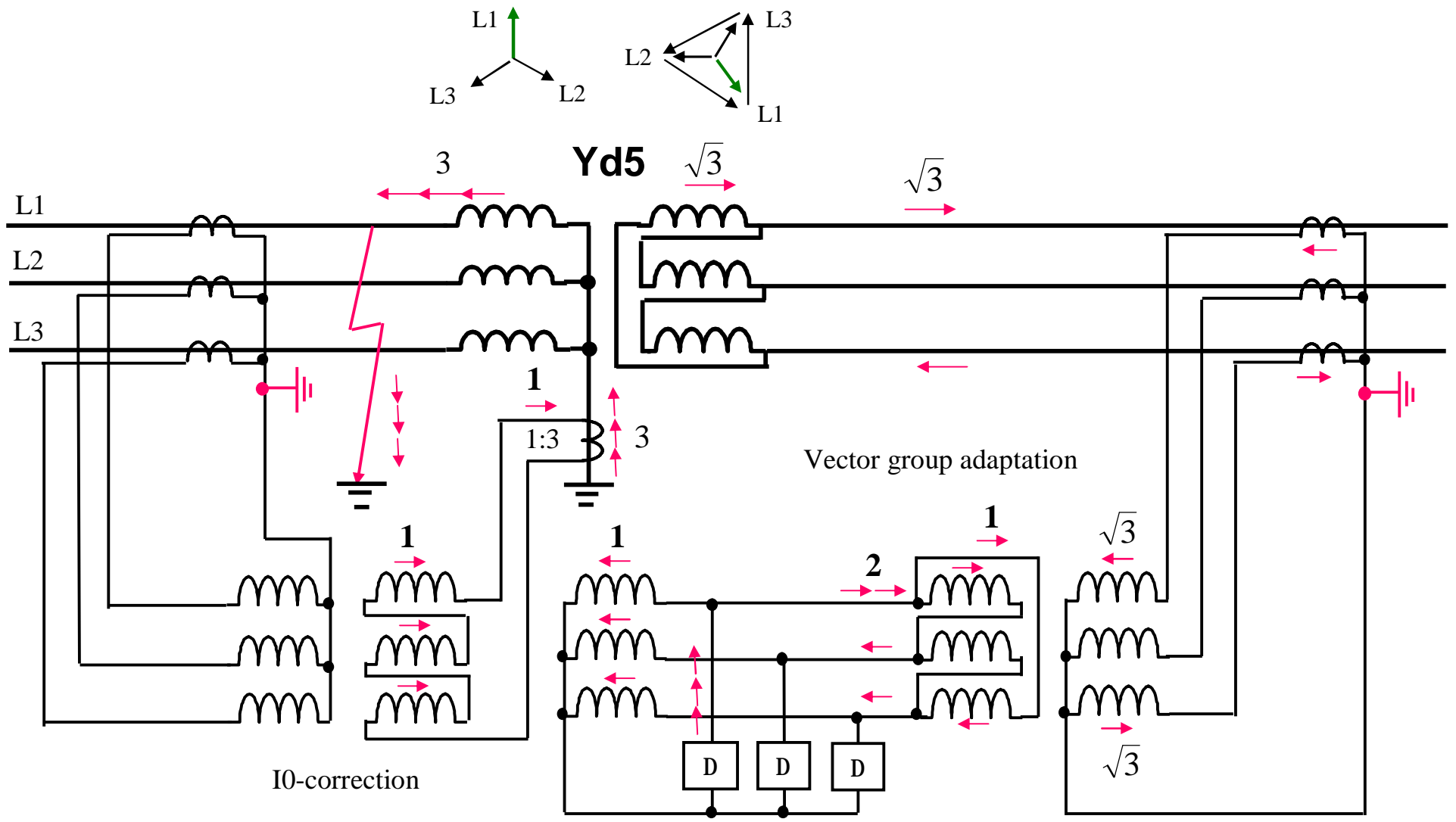Transformer differential protection with I<sub>0</sub>-correction  
Internal fault







# Digital Line Differential Protection

Gerhard Ziegler



**SIEMENS**

# Line differential protection, Versions
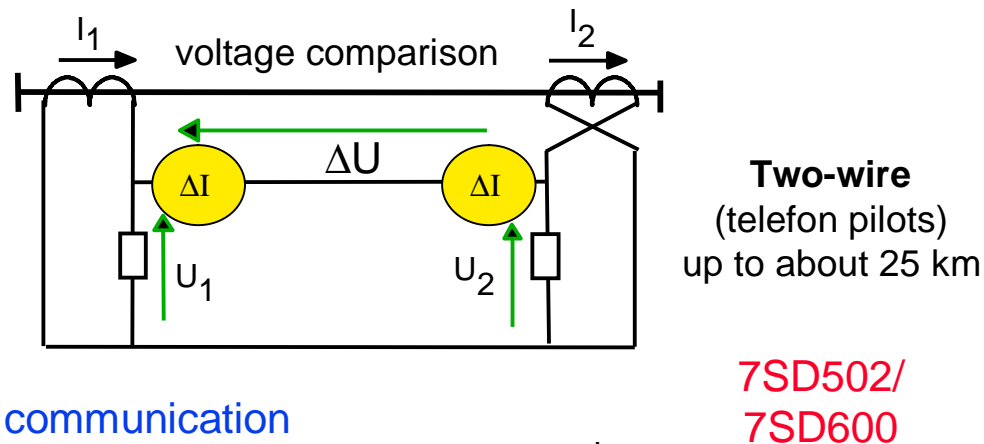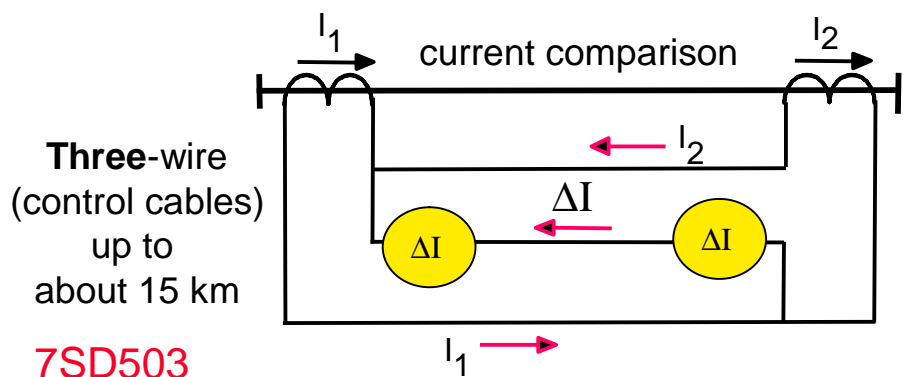
## Line differential protection with wire connection



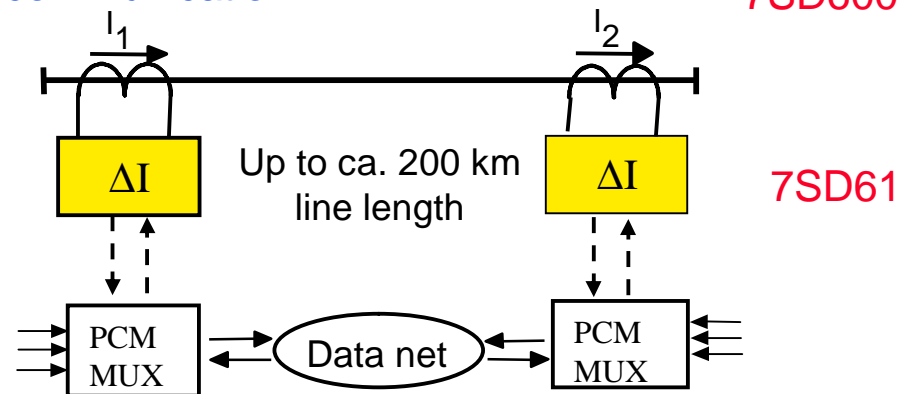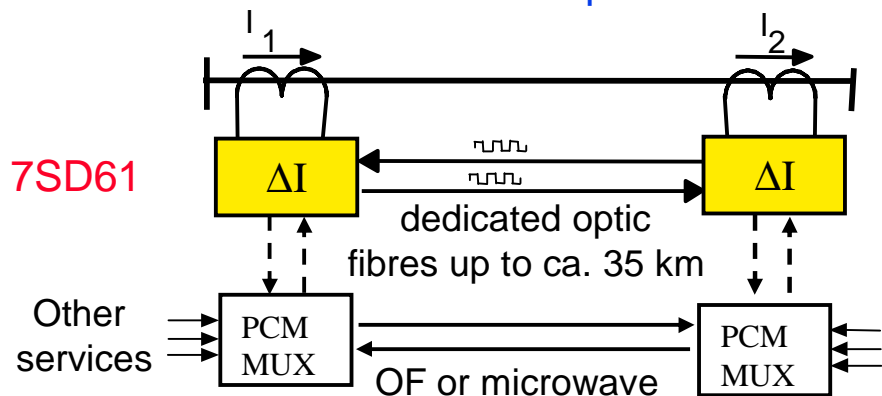
## Line differential protection with digital communication





# Digital pilot wire relay 7SD600

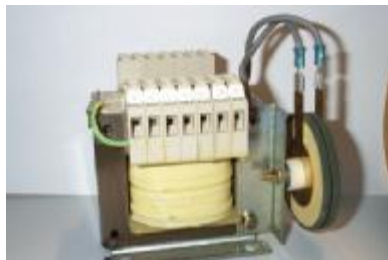

Combines

∅ Traditional pilot wire protection principle

with

∅ Modern digital relay technology

Novel features:

§ Self-monitoring and pilot wire supervision


§ Saturation detector

§ Measurement of pilot loop resistance


§ Add-on functions

# Relay to Relay pilot wires communication New technology on existing (copper-) pilots


**Traditional:**

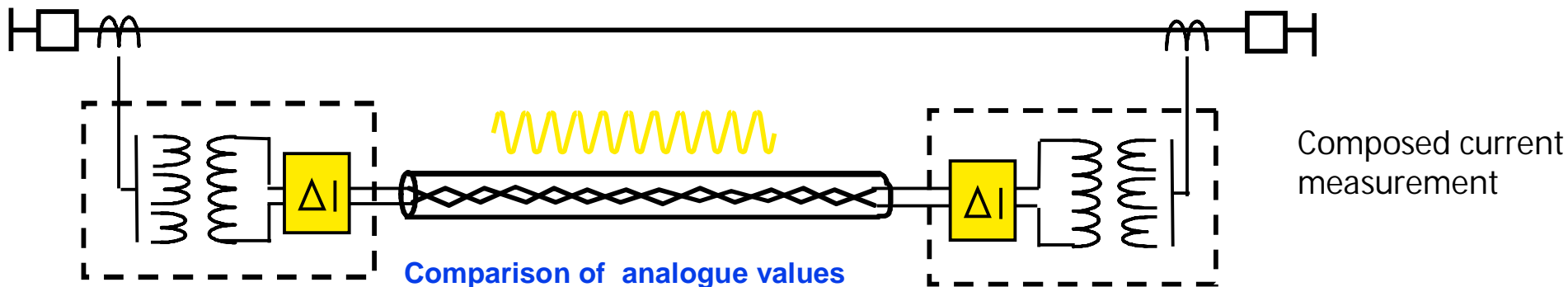


**Modern:**

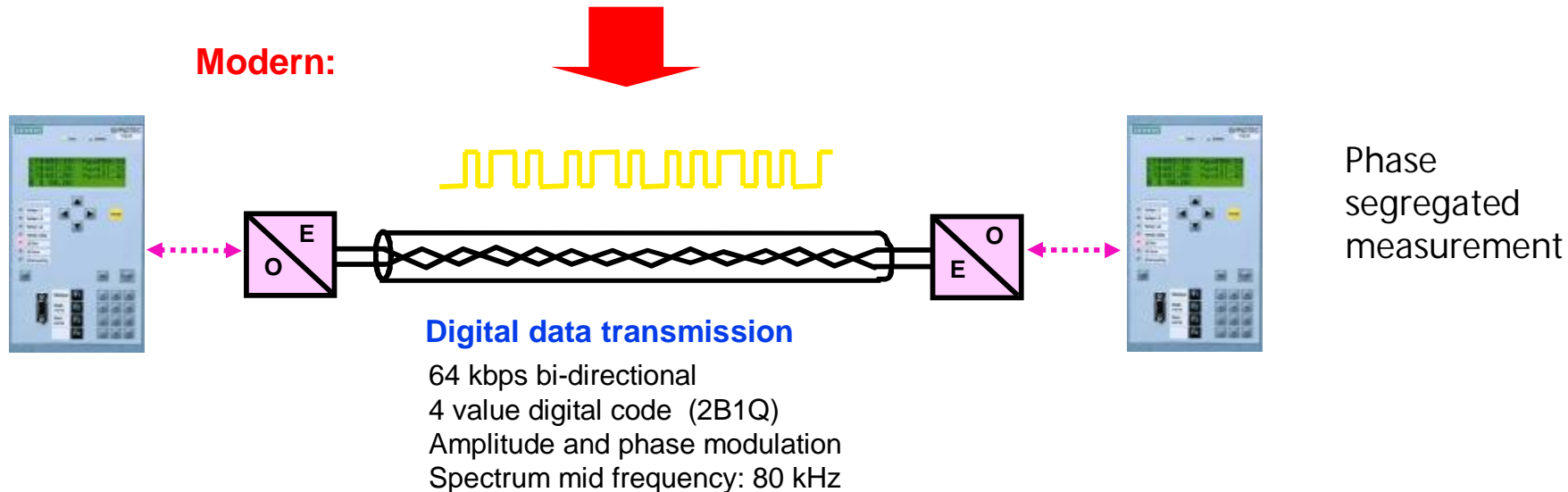
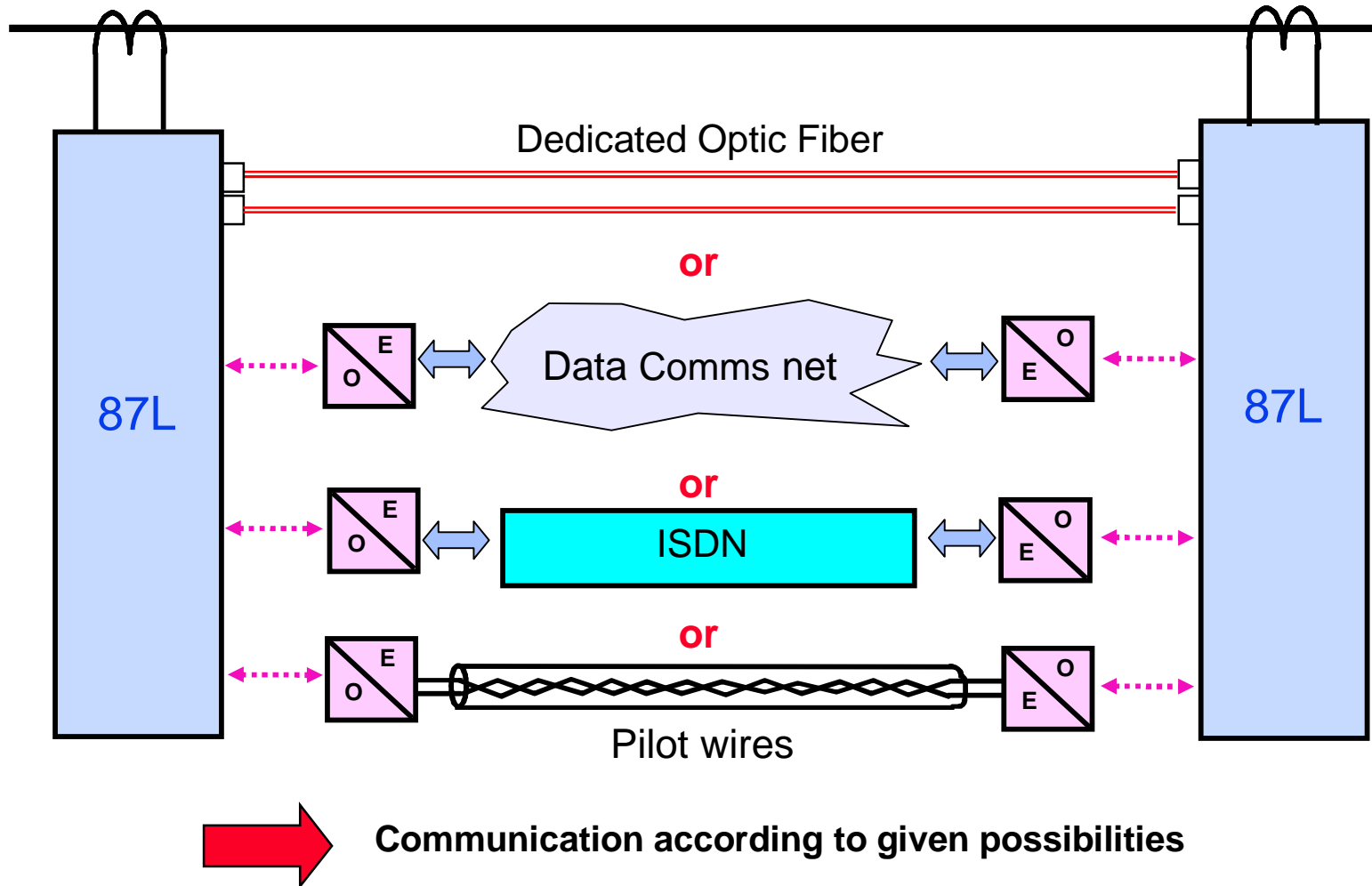
# Digital Relay to Relay Communication (Overview)


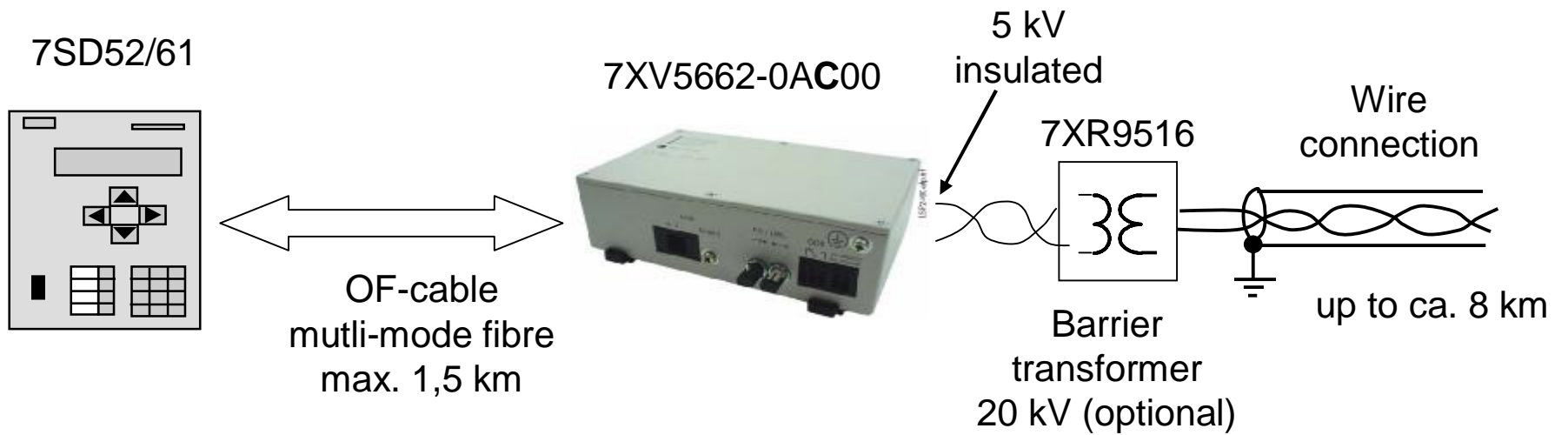
# Converter for digital communication via pilot wire




# Line differential protection with converter for digital communication


7SD52/61



7XV56

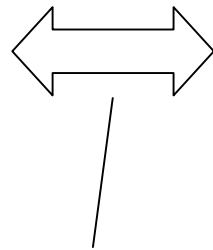


OF  
Multi-mode fibre  
max. 1.5 km

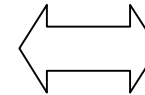


Digital  
data  
network

Interface to data network:  
X.21 or G.703.1  
(wired connection)
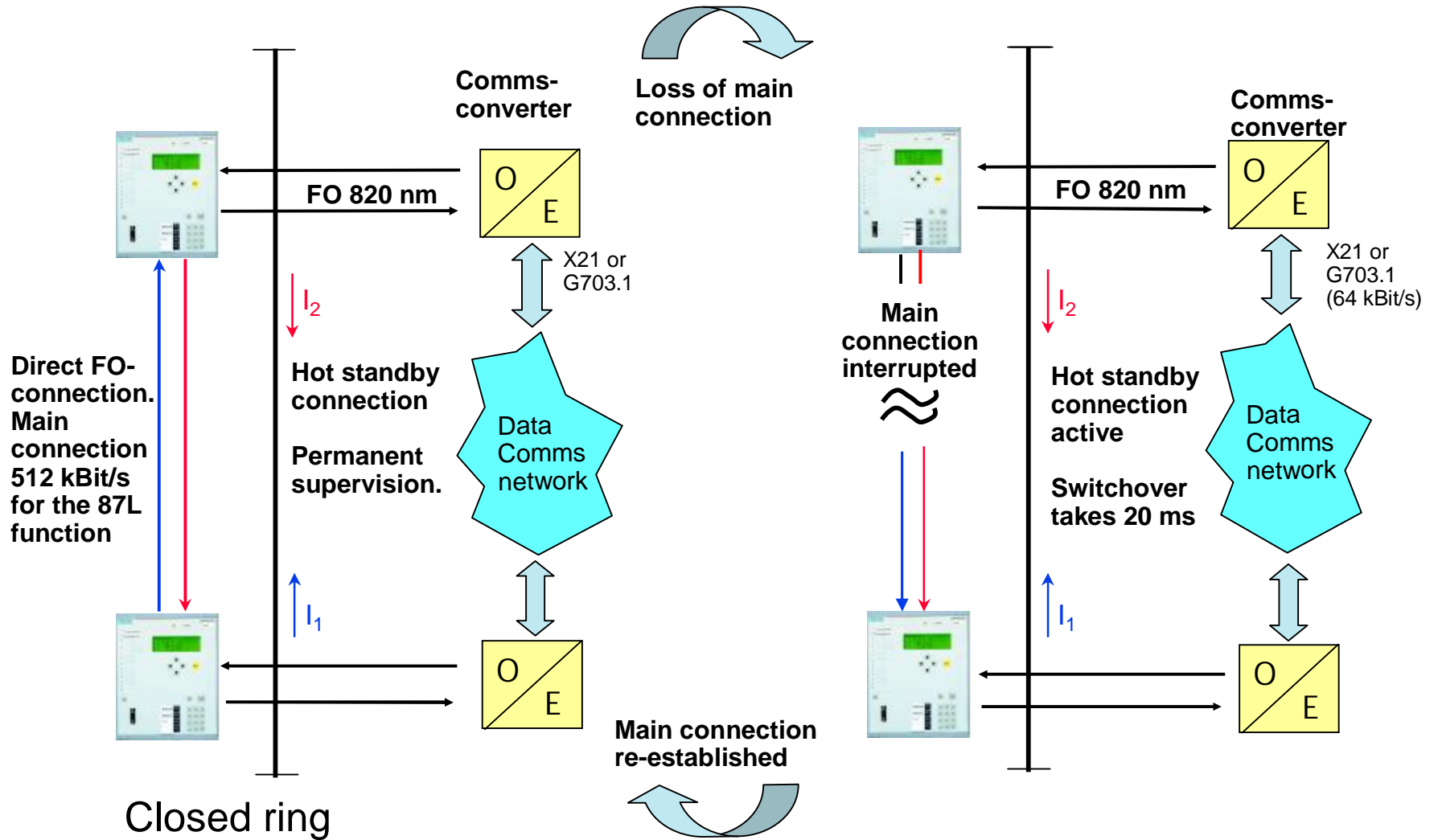
## Relay to Relay Communication: Two terminal configuration with hot standby connection



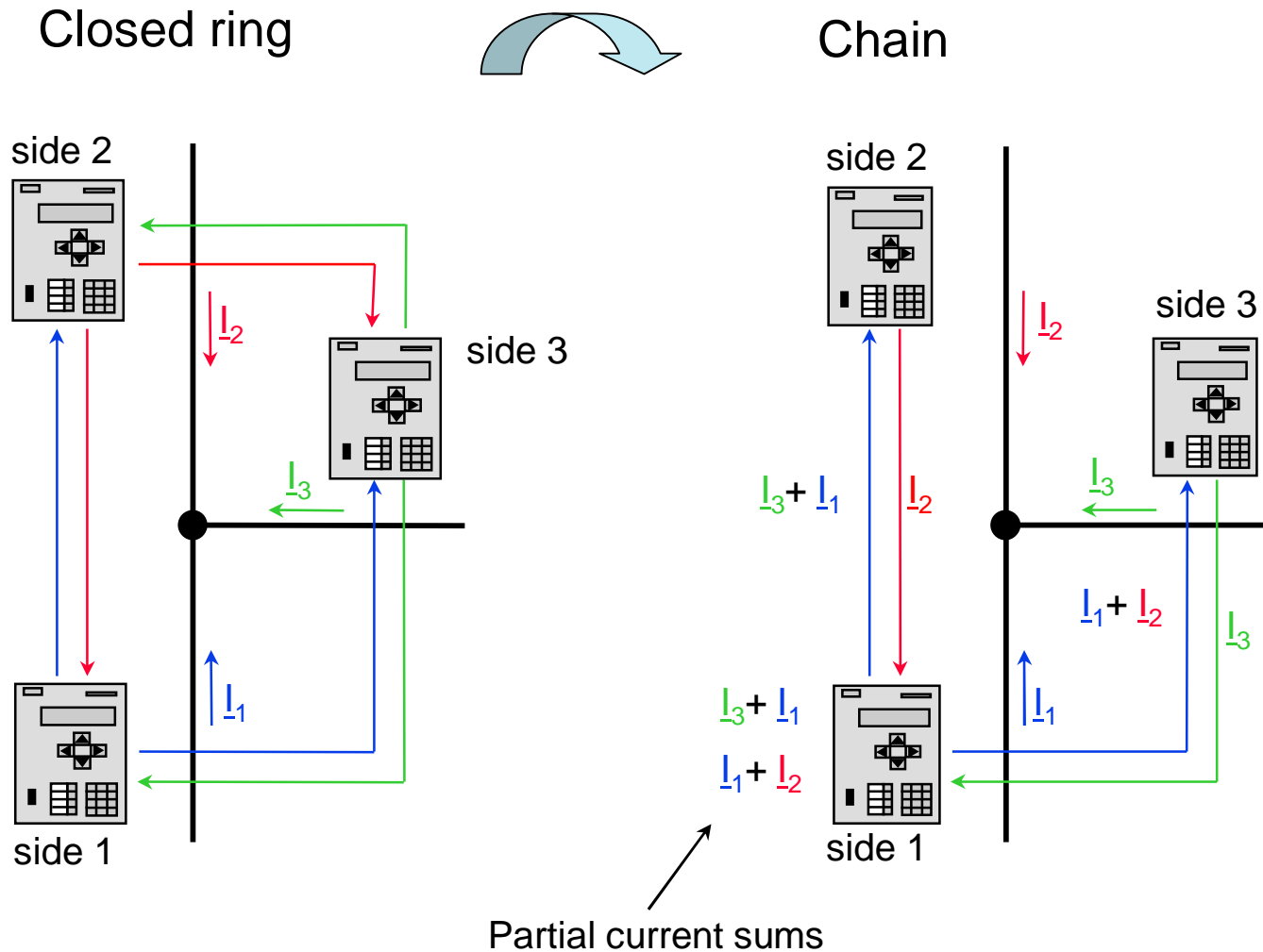
# Relay to Relay Communication: Ring- and Chain topology, loss of one data connection tolerated




# Line differential relay with digital communication (7SD52)

## Application to 3-terminal line

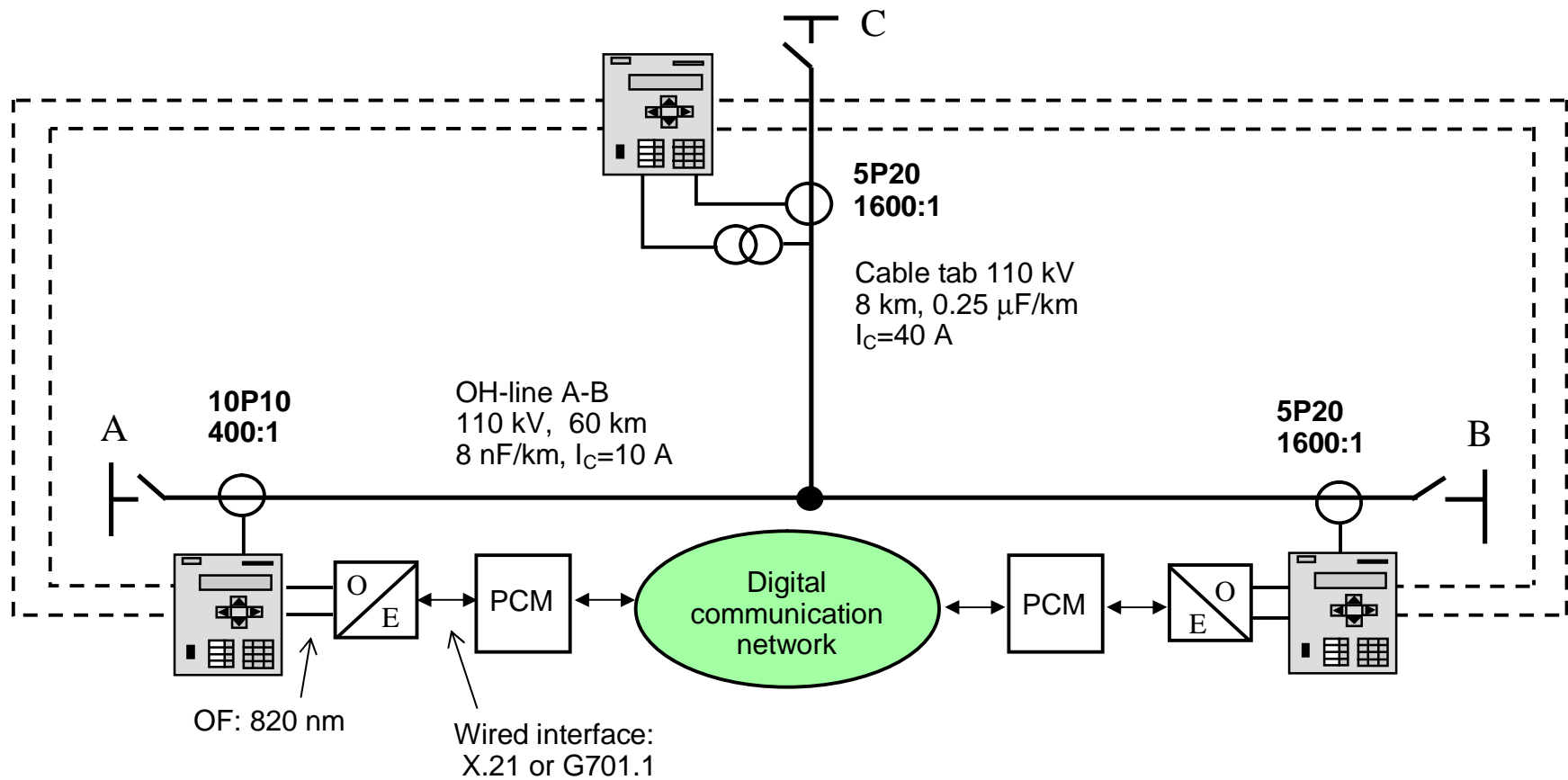




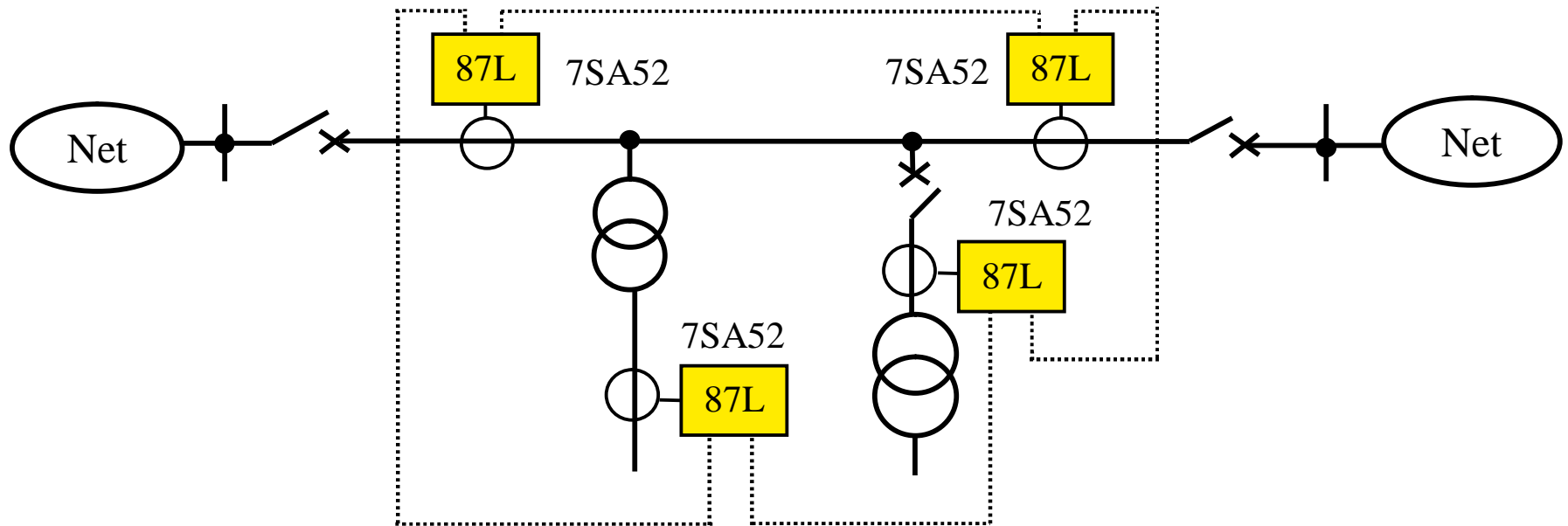
# Line differential relay with digital communication (7SD52) Application to tapped line


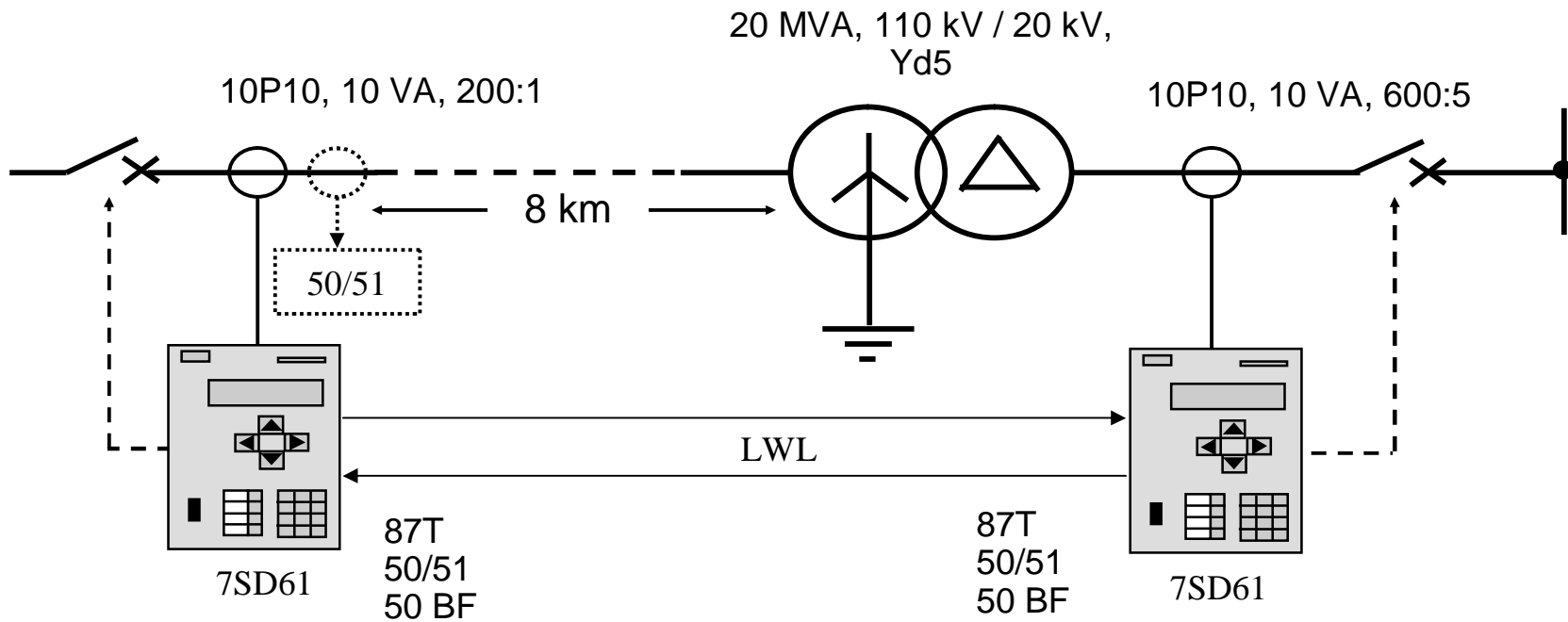
# Line differential relay with digital communication (7SD61) Transformer-line protection





# 7SD52/61: Bias for CT errors

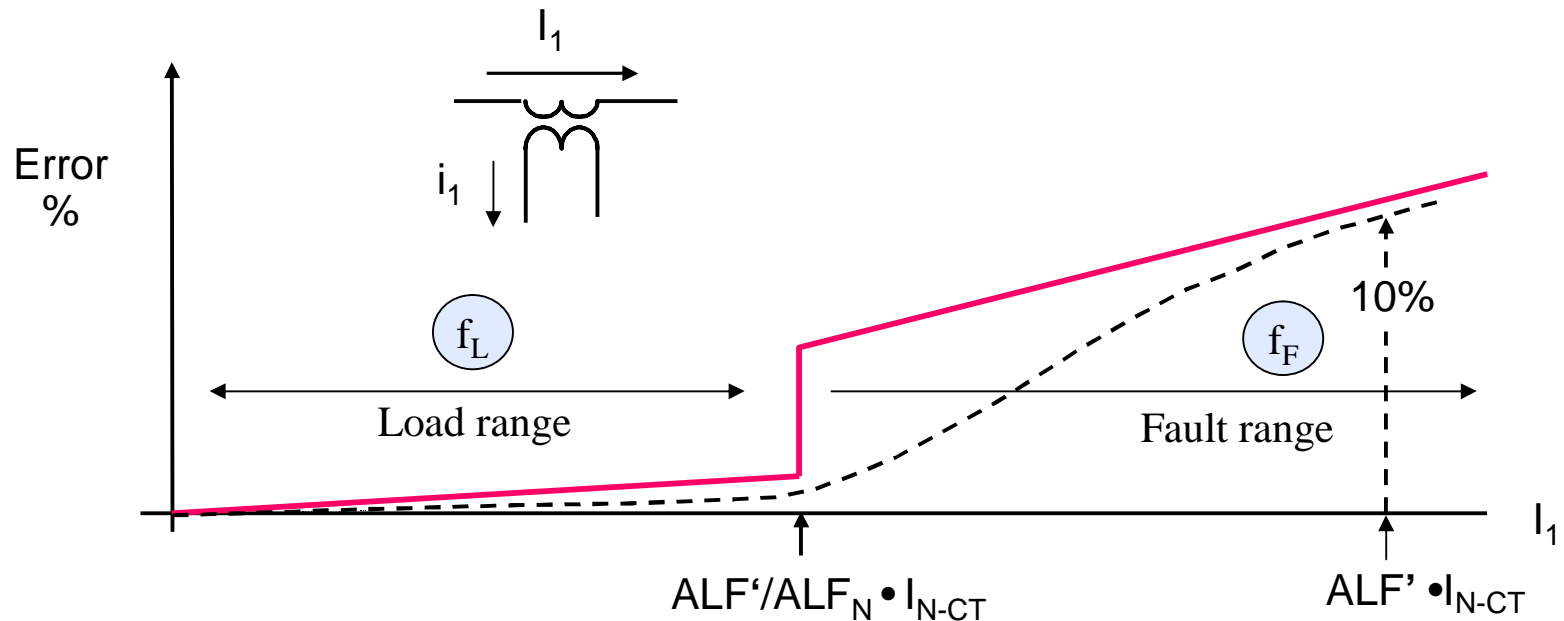

$f$  : relay setting parameters

Example: 10P10,  $f_L < 3\%$ ,  $f_F = 10\%$  at  $ALF' \cdot I_{N-CT}$

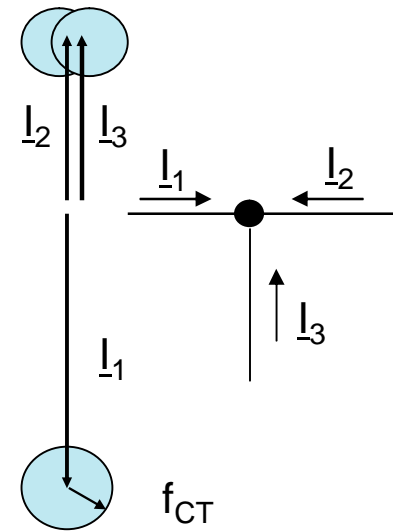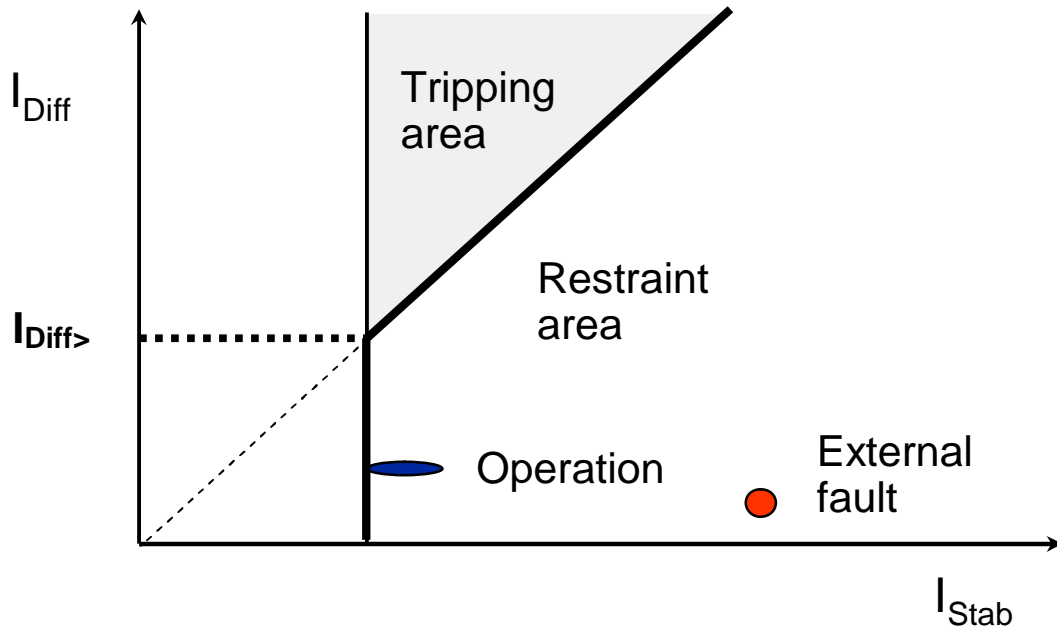
# Relays 7SD52/61: Operating characteristic



$$I_{Diff} = I_1 + I_2 + I_3 \quad (\text{Calculated differential current})$$

$$I_{Stab} = I_{Diff>} + \Sigma \text{ Sync.error} + |I_1| \cdot f_{CT1} + |I_2| \cdot f_{CT2} + |I_3| \cdot f_{CT3}$$
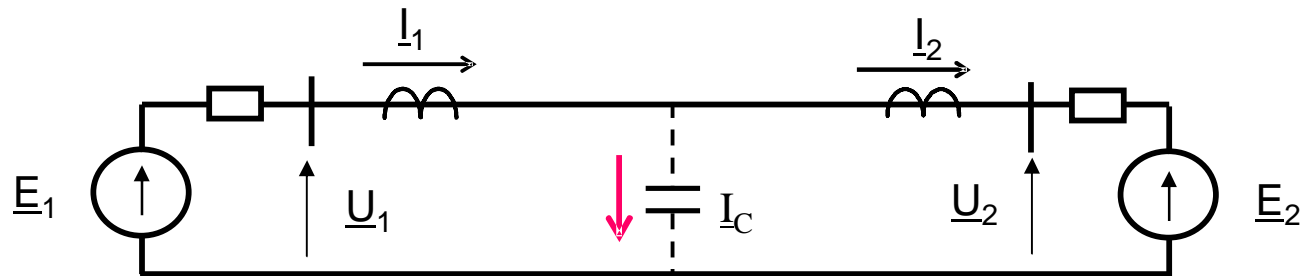
## 7SD52/61: Impact of line charging current



$$I_{\text{Diff}} = I_1 + I_2 + I_C \quad (\text{currents } I_1 \text{ and } I_2 \text{ counted positive in line direction!})$$


### Without charge current compensation:

Pick-up value:  $I_{\text{Diff}} > 2,5.. 4 \cdot I_C$       è Sensitive setting only for short cables or lines

### With charge current compensation:

Pick-up value:  $I_{\text{Diff}} > 0,2 \cdot I_N$
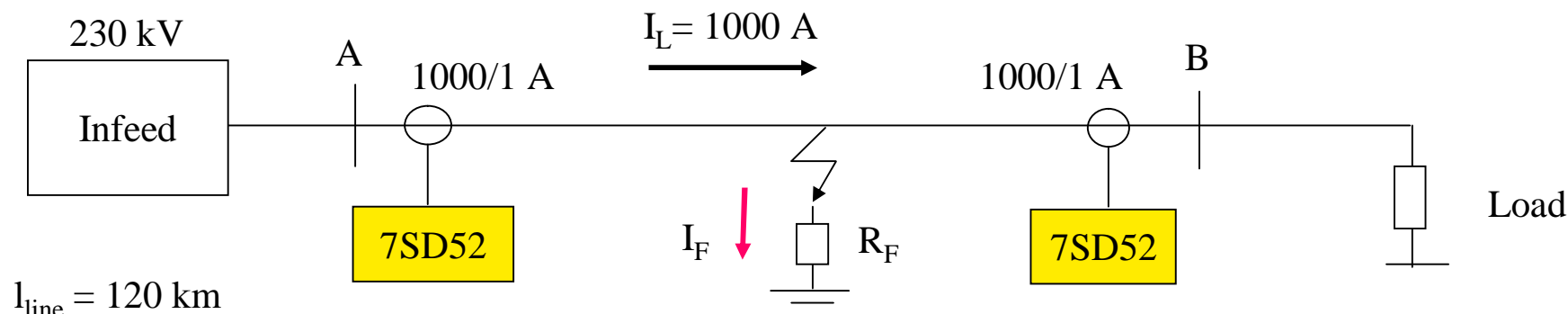
## 7SD52/61: High resistance fault sensitivity



$l_{\text{line}} = 120 \text{ km}$   
 $I_c = 72 \text{ A}$

Channel unsymmetry:  $0.2 \text{ ms} = 4.32^\circ \approx 5^\circ$  (60 Hz)

5P type CT, i.e. 1% error in the load area, set:  $f_{\text{CD}} = 2\%$

Relay pick-up setting about  $4 \times I_c$ :  $I_{\text{Diff} >} = 30\% I_n = 300 \text{ A}$




$$I_{\text{Op}} = I_A + I_B = 1000 \text{ A} + I_F - 1000 \text{ A} = I_F$$

$$I_{\text{Res}} = I_{\text{Diff} >} + F_{\text{sync}} + f_{\text{CTA}} \cdot I_A + f_{\text{CTB}} \cdot I_B = I_{\text{Diff} >} + (I_L + I_F) \cdot \sin \frac{\Delta\phi}{2} + I_L \cdot \sin \frac{\Delta\phi}{2} + f_{\text{CTA}} \cdot (I_L + I_F) + f_{\text{CTB}} \cdot I_L$$

$$I_F > \frac{I_{\text{Diff} >} + (2 \cdot \sin(\Delta\phi/2) + f_{\text{CTA}} + f_{\text{CTB}}) \cdot I_L}{1 - (\sin(\Delta\phi/2) + f_{\text{CTA}})} = \frac{300 \text{ A} + (2 \cdot \sin 5^\circ / 2 + 0.02 + 0.02) \cdot 1000 \text{ A}}{1 - (\sin(5^\circ / 2) + 0.02)} = 457 \text{ A}$$

$$R_{\text{F-max.}} = \frac{230 \text{ kV}}{\sqrt{3} \cdot I_{\text{F-min.}}} = \frac{230 \text{ kV}}{\sqrt{3} \cdot 457 \text{ A}} = 290 \text{ Ohm}$$

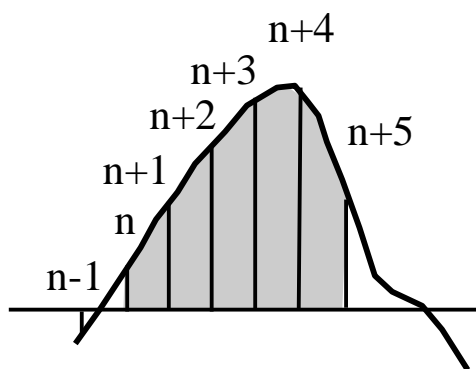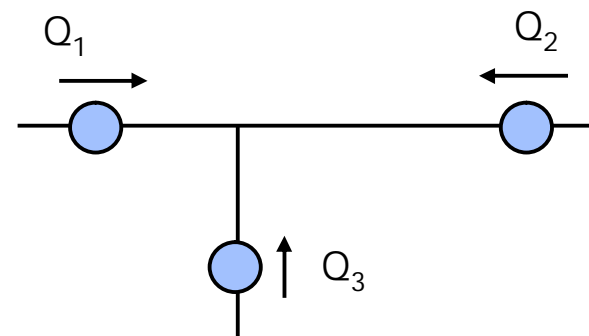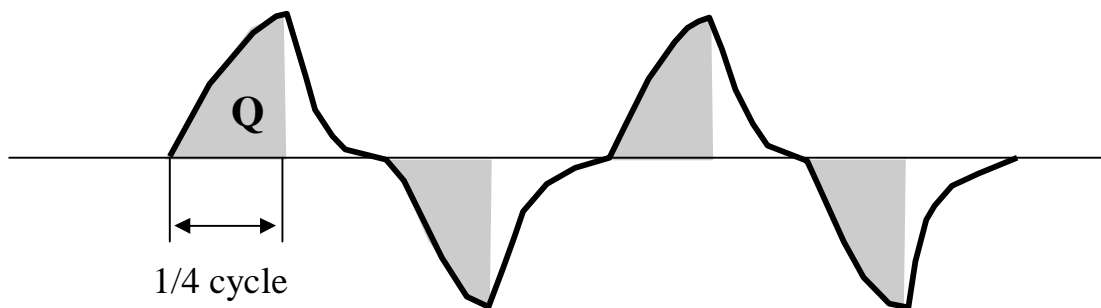
# 7SD52/7SD61: Charge comparison protection supplement



Calculation of the charge

$$Q = \int_t^{t+T/4} I(t) \cdot dt \approx \left( \frac{i_n}{2} + \frac{i_{n+5}}{2} + \sum_{n+1}^{n+4} I_n \right) \cdot \Delta T$$

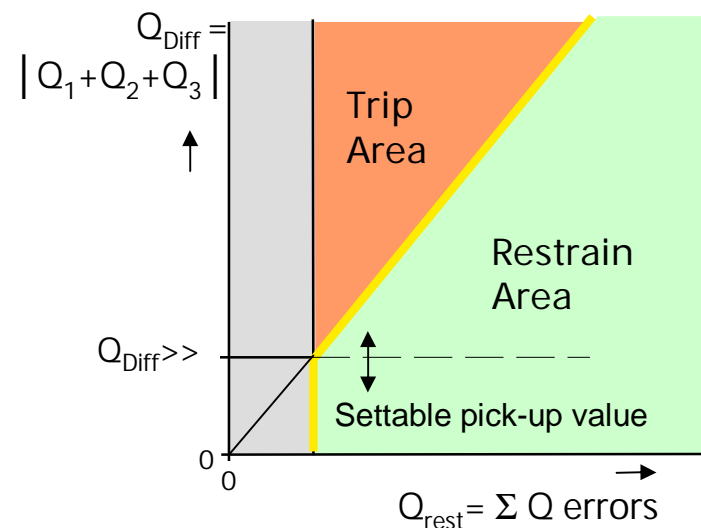with  $\Delta T = 1 \text{ ms (18}^\circ \text{ el.)}$



speed	2 relays	3 relays	6 relays
64 kbit/s	21 ms	21 ms	41 ms
128 kbit/s	16 ms	16 ms	24 ms
512 kbit/s (FO)	14 ms	14 ms	17 ms


## Development of IED processing and communication power

Year	Memory	Processing power	Bus width	Communication
1986	192 kB	0.5 MIPS	16 bit	19.2 kbps
1992	768 kB	1.0 MIPS	16 bit	115.2 kbps
1998	8.5 MB	35 MIPS	32 bit	1.5 Mbps (LAN)
2004	28 MB	80 MIPS	32 bit	100 Mbps (LAN)



# 21 & 87 Relay
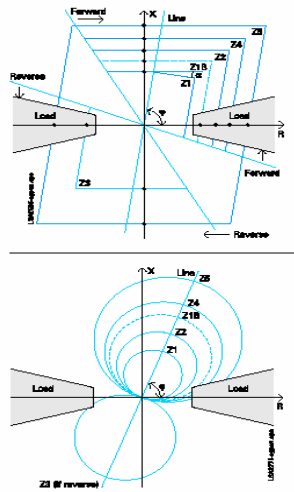
## United full scheme distance and differential protection



21



Copy of well proven features


21, 21N	85 - 21
67N	85 - 67N
68, 68T	27 WI

79	25
59	27
49	81
51/51N	50 BF

21 & 87




87

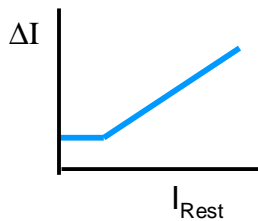

87

# Universal line protection relay

---

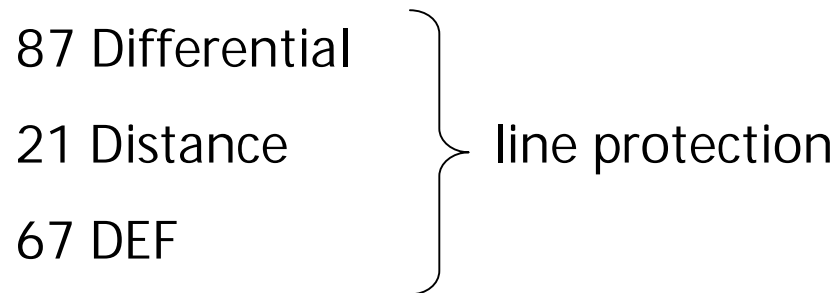

## For all kind of lines

Short to long lines

Parallel lines

Multi-terminal lines

Tapped lines

Transformer lines

Series comp. lines

## For all kind of communication:

Traditional : PLC, Pilot wires, Microwave

Dedicated OF

Digital microwave


Comms networks

## For all kind of operation


Single and/or three-pole ARC

# Line with larger transformer taps
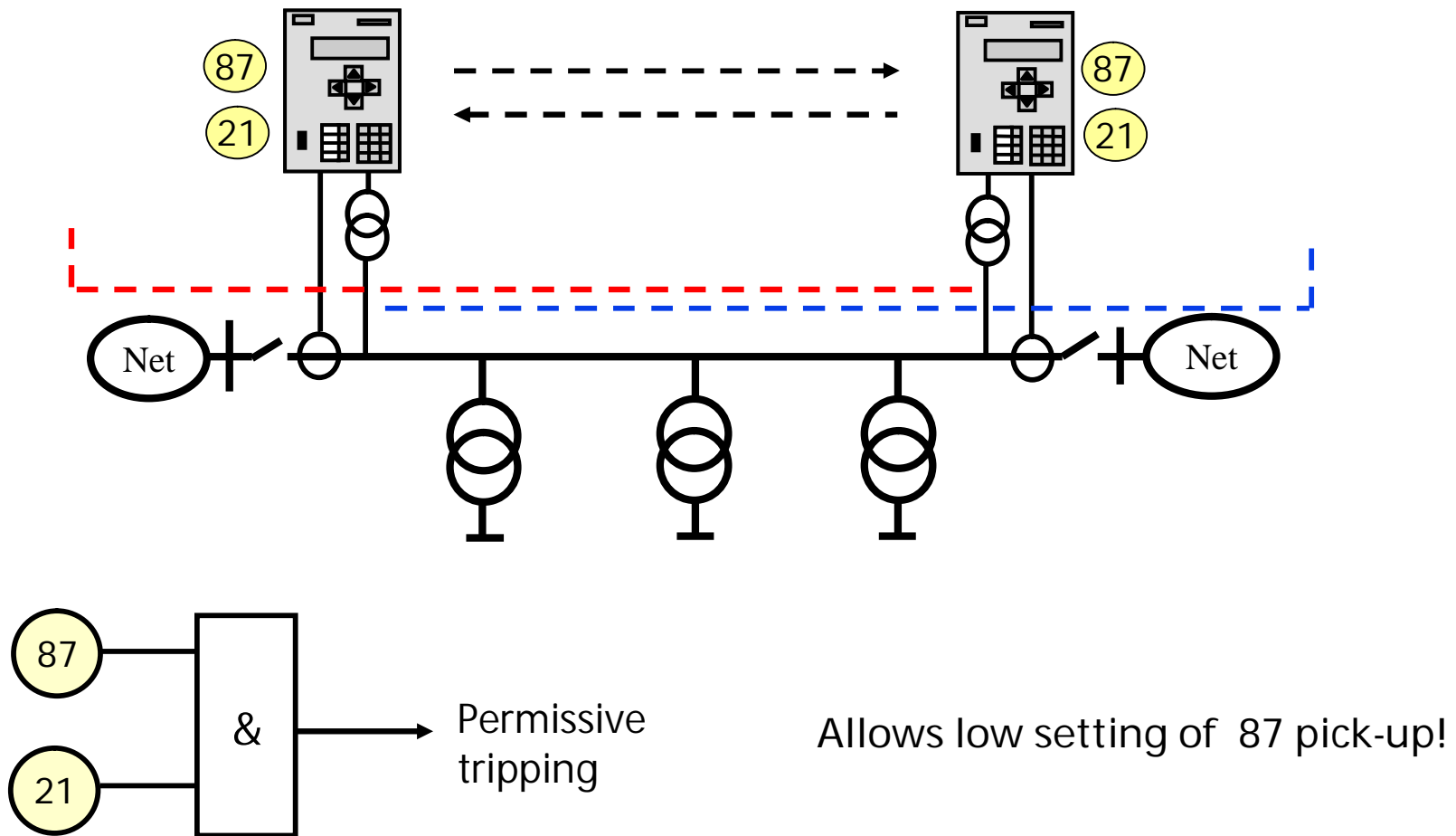
## Release of 87 by 21 distance overreaching zone


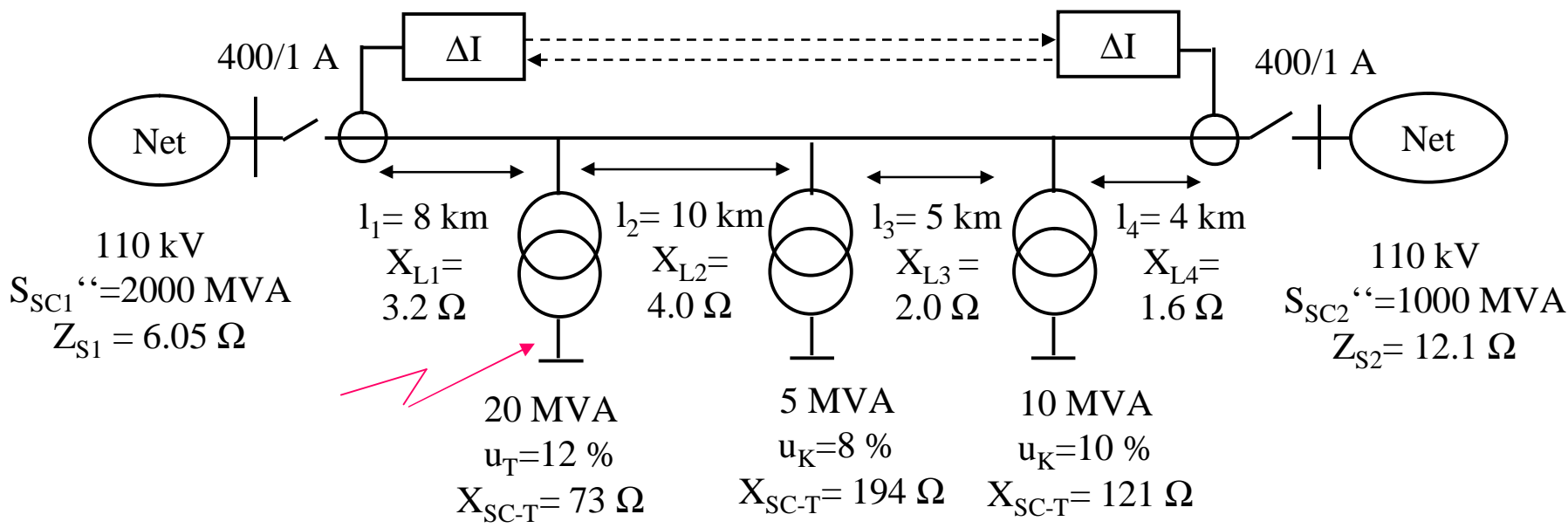
# Line differential relay with digital communication (7SD61) Application to tapped line, Example




$$I_{SC} \approx \frac{1.1 \cdot U_N / \sqrt{3}}{X_{SC-T}} = \frac{1.1 \cdot 110 / \sqrt{3} \text{ kV}}{73 \Omega} = 957 \text{ A}$$

$$\Sigma I_{Rush} \approx 5 \cdot \frac{\sum S_{N-T}}{\sqrt{3} \cdot U_N} = 5 \cdot \frac{35 \text{ MVA}}{\sqrt{3} \cdot 110 \text{ kV}} = 918 \text{ A}$$


- ➔
- u Setting pick-up value  $\Delta I > 1.3 \cdot 957 \text{ A}$
  - u or blocking  $\Delta I$  via remote signalling when tap protection operates
  - u or release of  $\Delta I$  by an overreaching distance zone
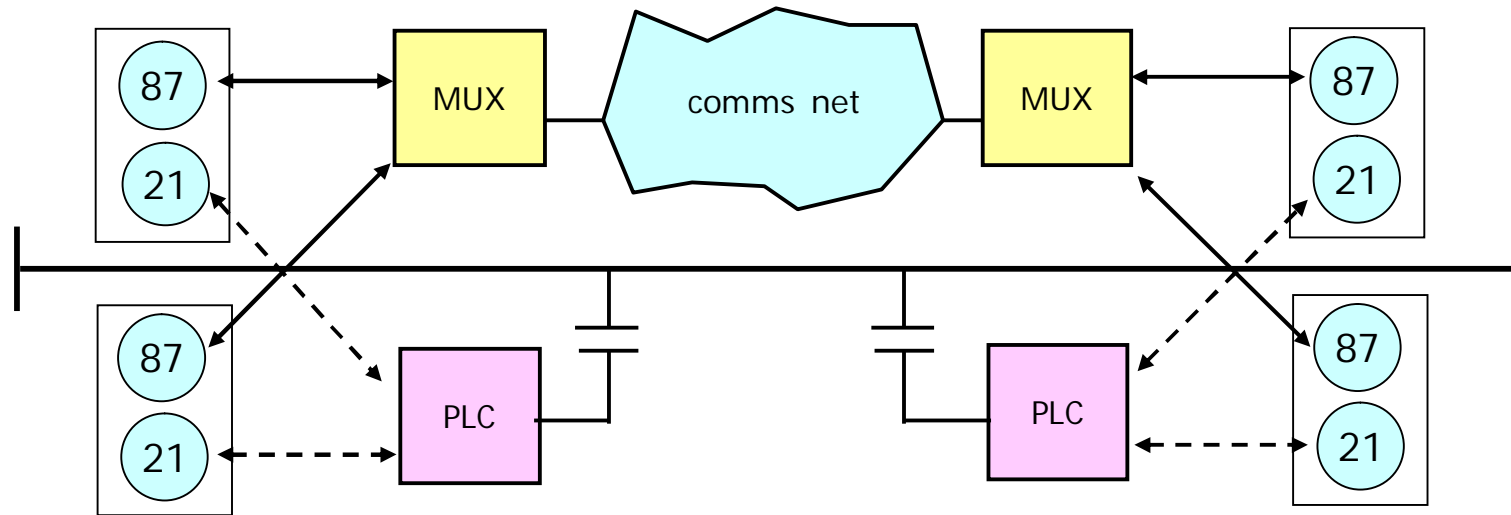
# Fully redundant line protection using dissimilar protection and comms principles




Fully redundant 87 and 21 teleprotection remains in operation  
in each combination of relay and communication failure!

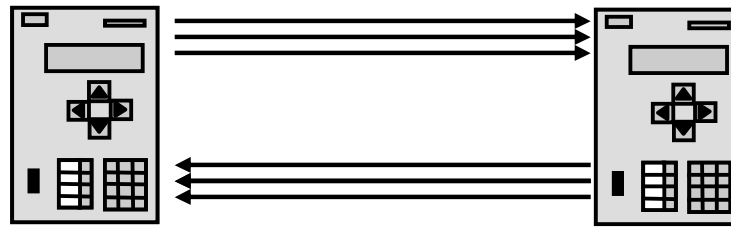Phase segregated 87 differential and 21 distance pilot protection:  
Enhanced selectivity with multiple faults




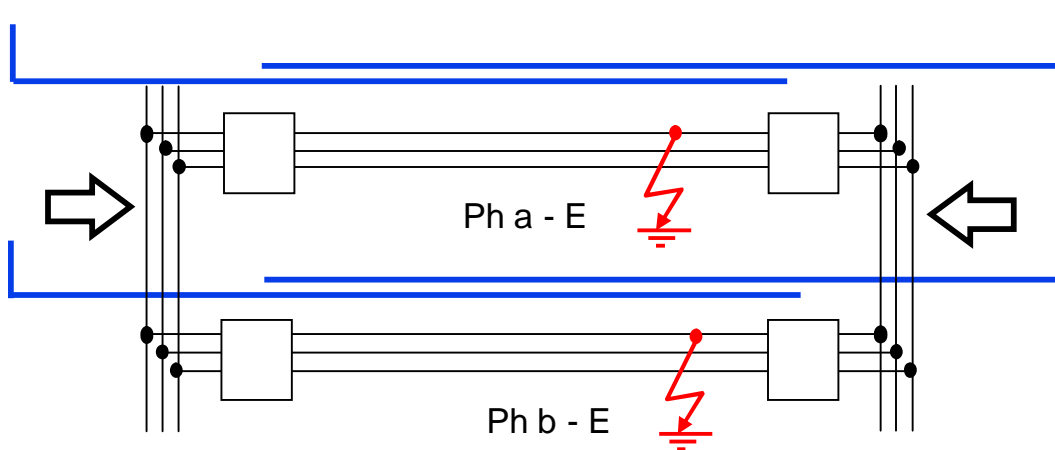87 differential  
and  
21 pilot protection




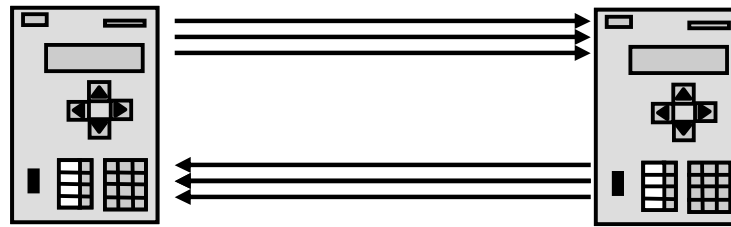**Phase selective fault clearance and auto-reclosing also with multiple-faults**

Phase segregated 87 differential and 21 distance pilot protection:  
Enhanced selectivity with multiple faults





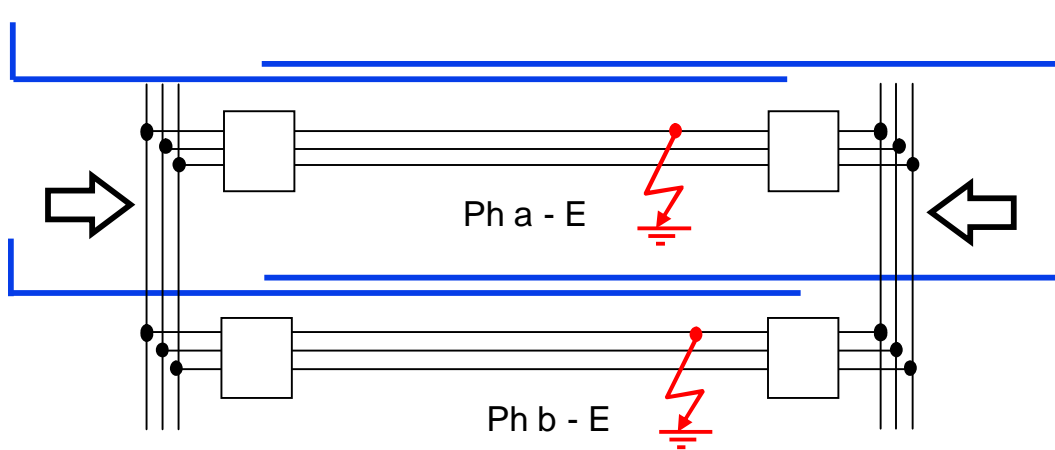87 differential  
and  
21 pilot protection



**Phase selective fault clearance and auto-reclosing also with multiple-faults**

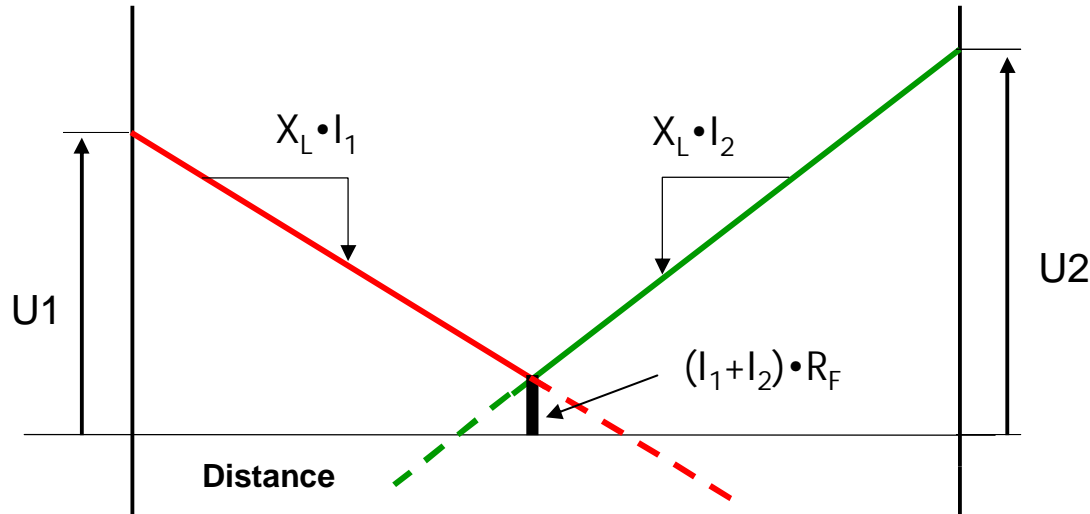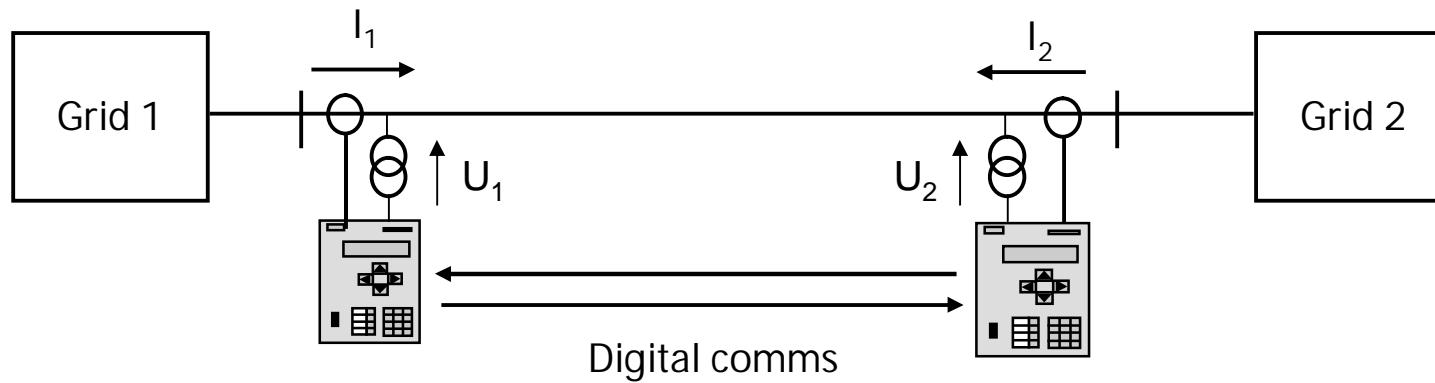
# Two-sided fault locator using 87&21 relay communication






- ü Combined distance and differential protection relays , together with modern comms, allow to enhance line protection in a cost saving way.
- ü The dissimilar protection principles complement each other perfectly.
- ü Distance and differential protection can both be configured as phase segregated teleprotection schemes allowing absolute phase selective fault clearance and autoreclosure even with complex cross county and inter-circuit faults.
- ü Digital relay to relay comms allows to exchange data for upgraded two sided fault locating.
- ü Using a single relay type for distance and/or differential protection also saves on cost in investment and operation.


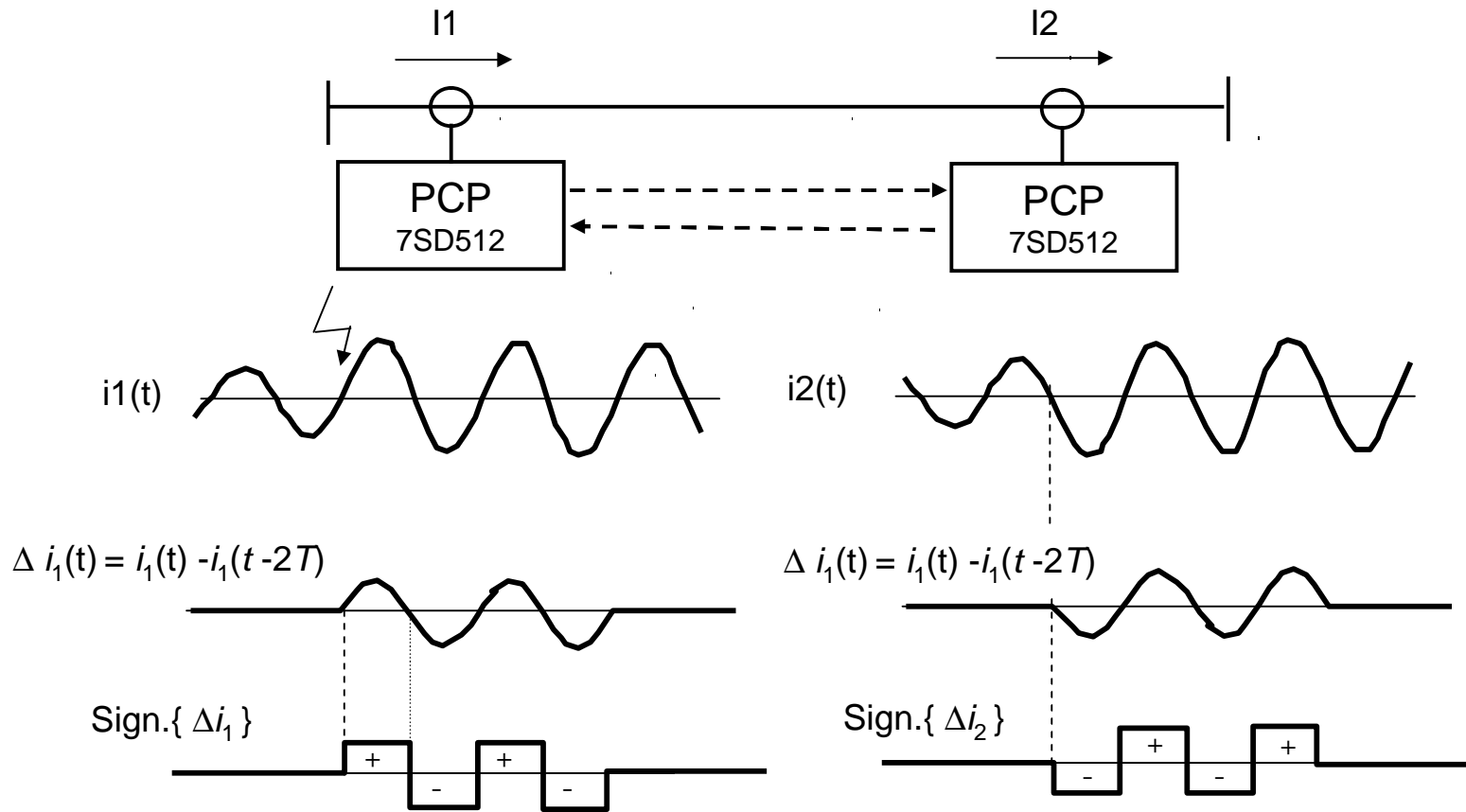
# 7SD51: Phase comparison, Dynamic supplement based on delta-quantities




# 7SD51: Phase comparison

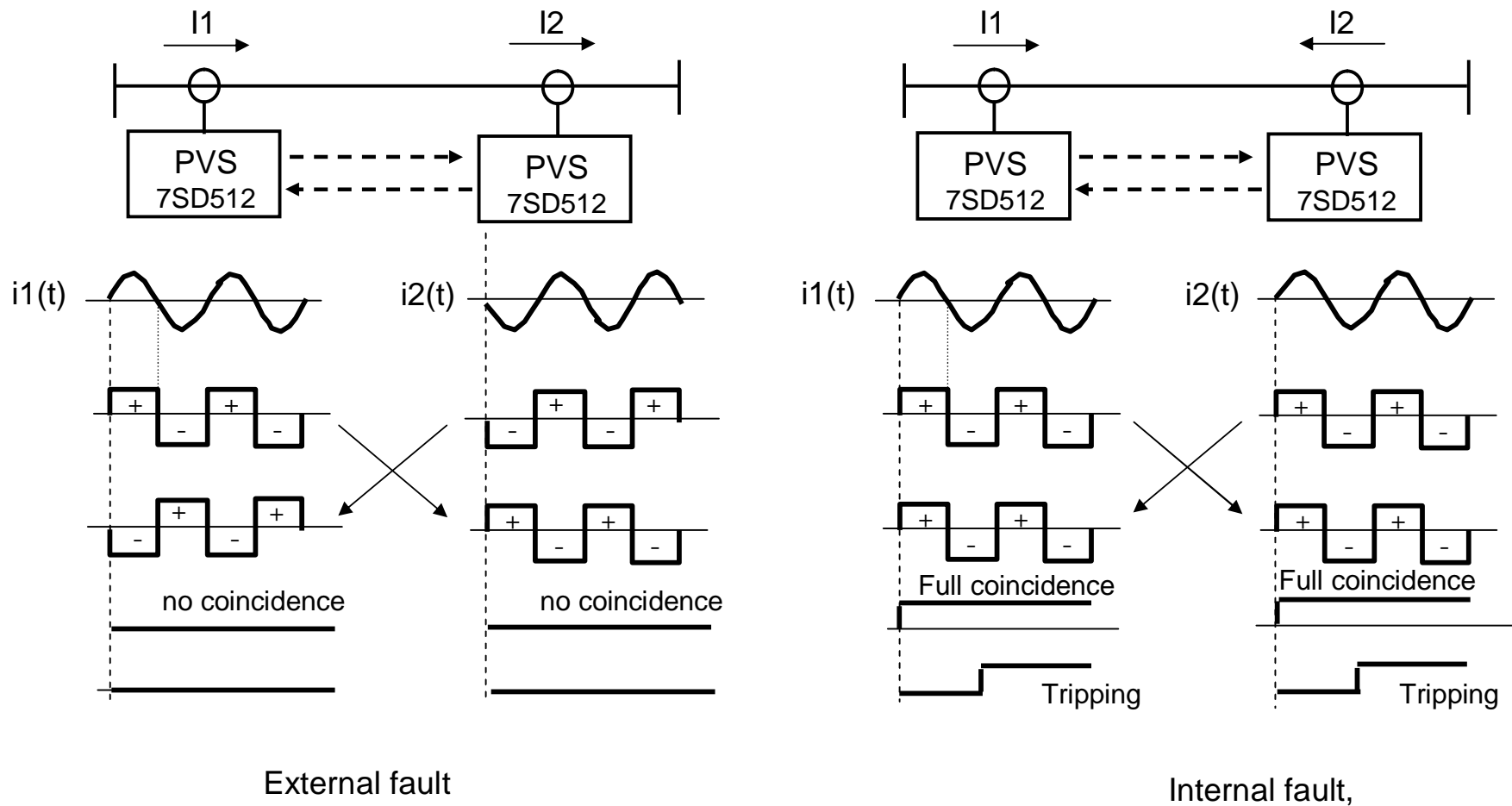
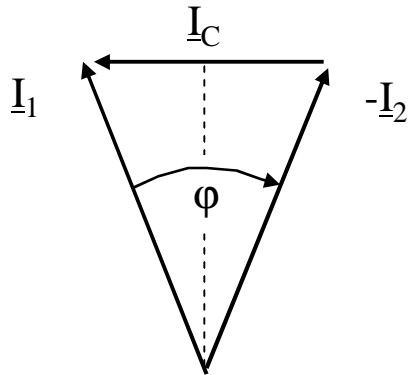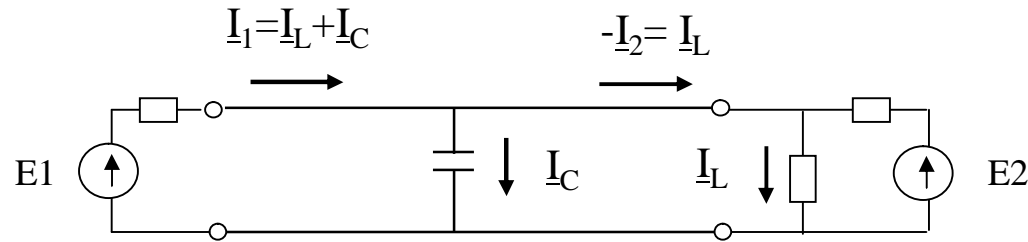
## 7SD51: Phase comparison: Impact of charging current



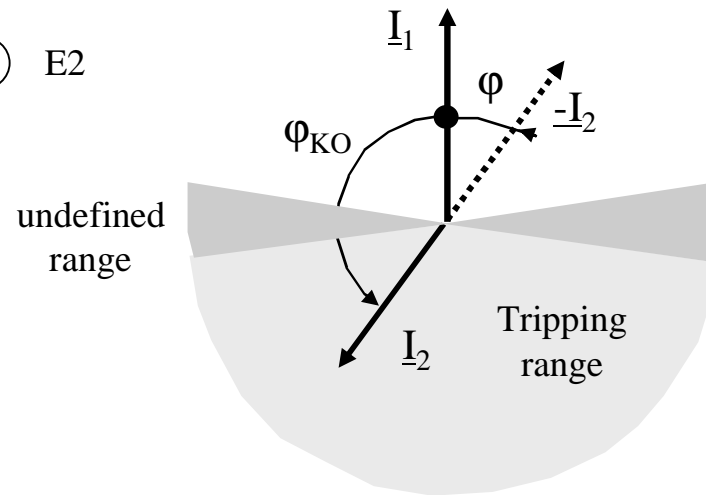
Phase shift  $\phi$  caused by charging current  $I_C$



undefined range due to discrete sampling :  
 $\pm 1/2\Delta T = \pm 1,66/2 \text{ ms} = \pm 15^\circ$

# Phase comparison protection 7SD51:
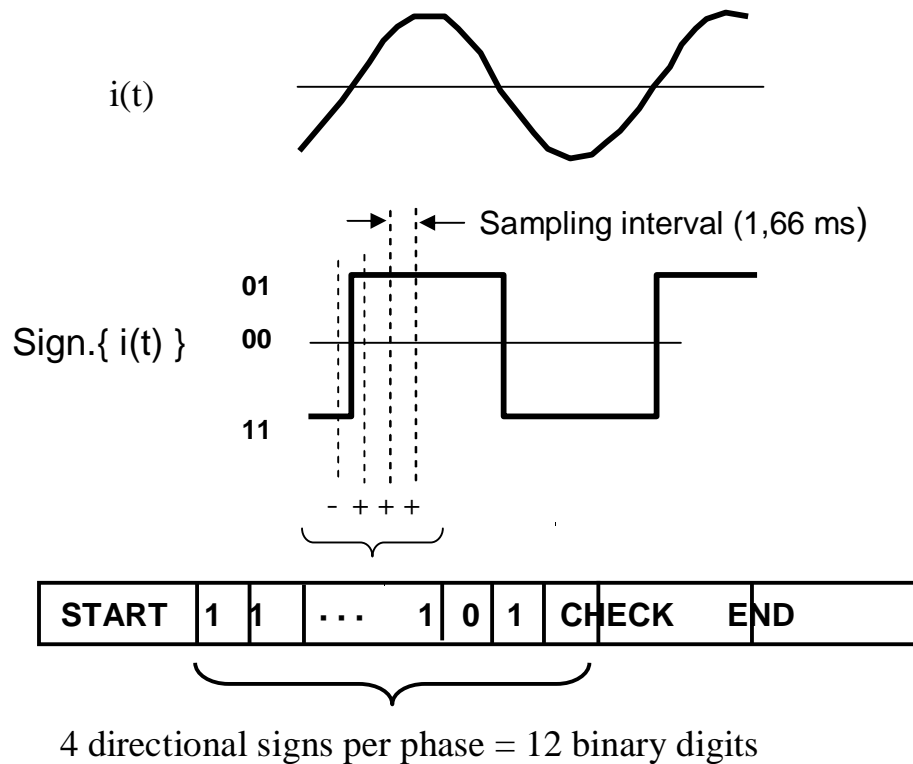
## Sampling of the rectangular sign wave and data transmission telegram




Telegram acc. to IEC 60870-5  
Hamming distance  $d=4$

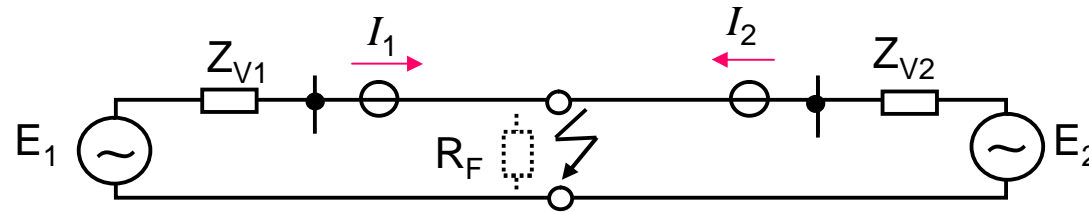
# Measurement based on delta quantities, Principle

Total situation after fault inception:


$\Delta I_1, \Delta I_2$ : DELTA-quantities



⊖ Load before fault inception:

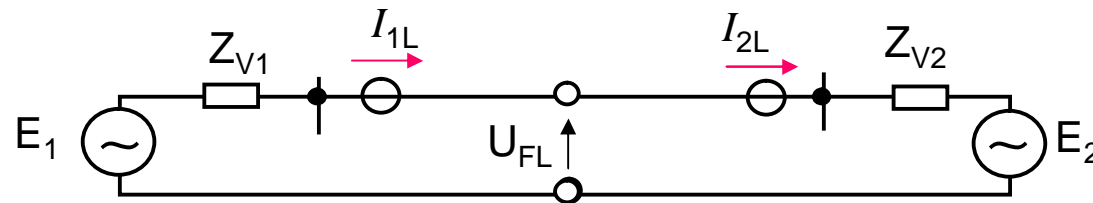

⊕ Pure fault part :

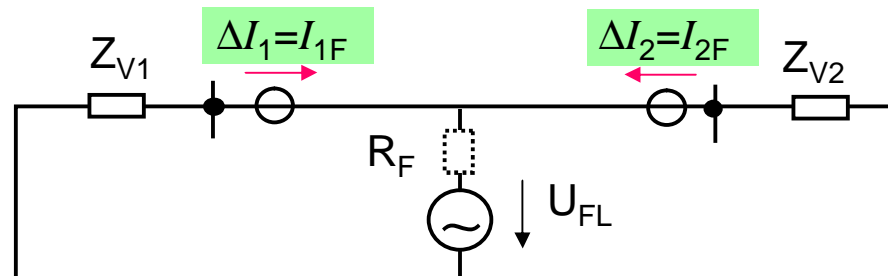





# Digital Busbar Protection

Gerhard Ziegler


**SIEMENS**
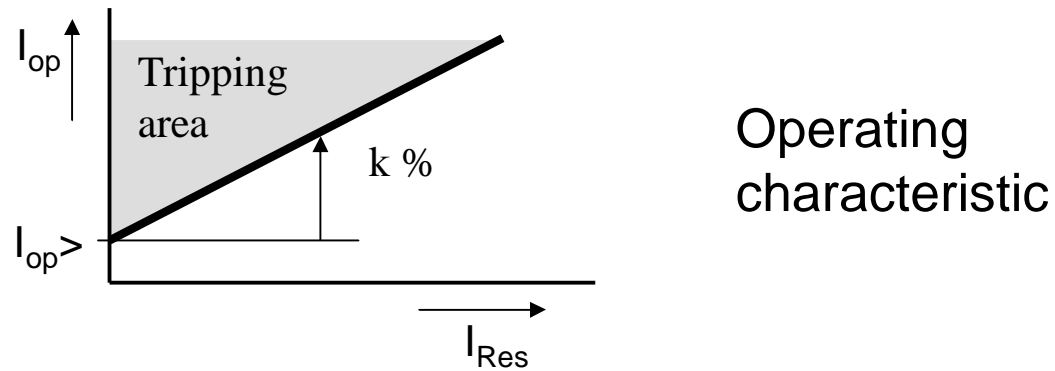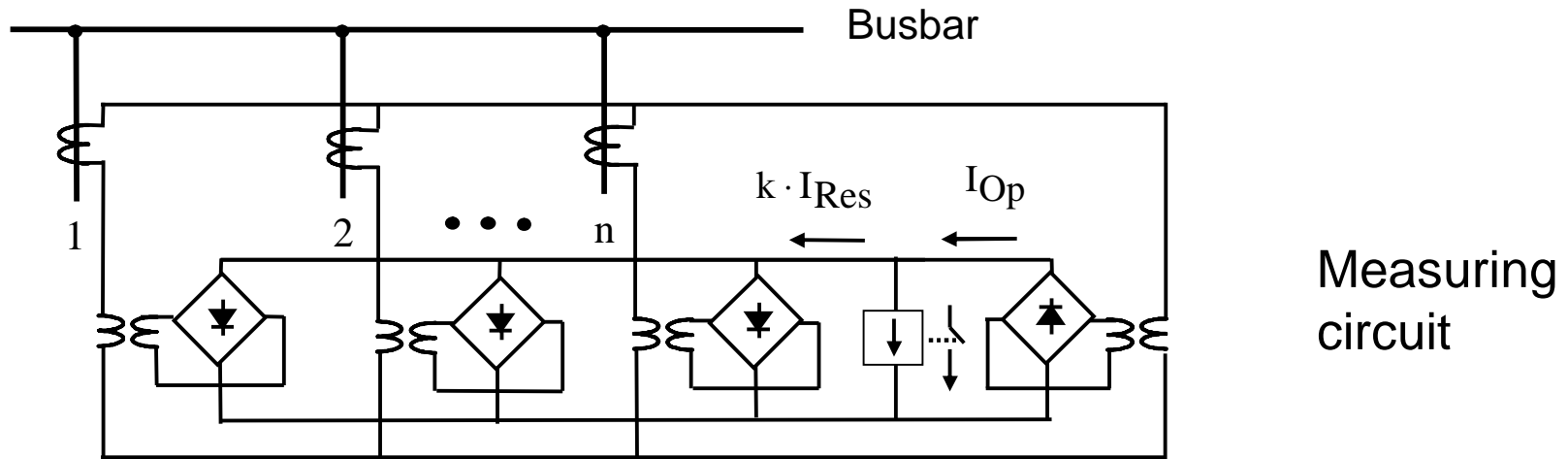
# Busbar differential protection, Principle (Analog technique)







# Part-digital Busbar protection 7SS6

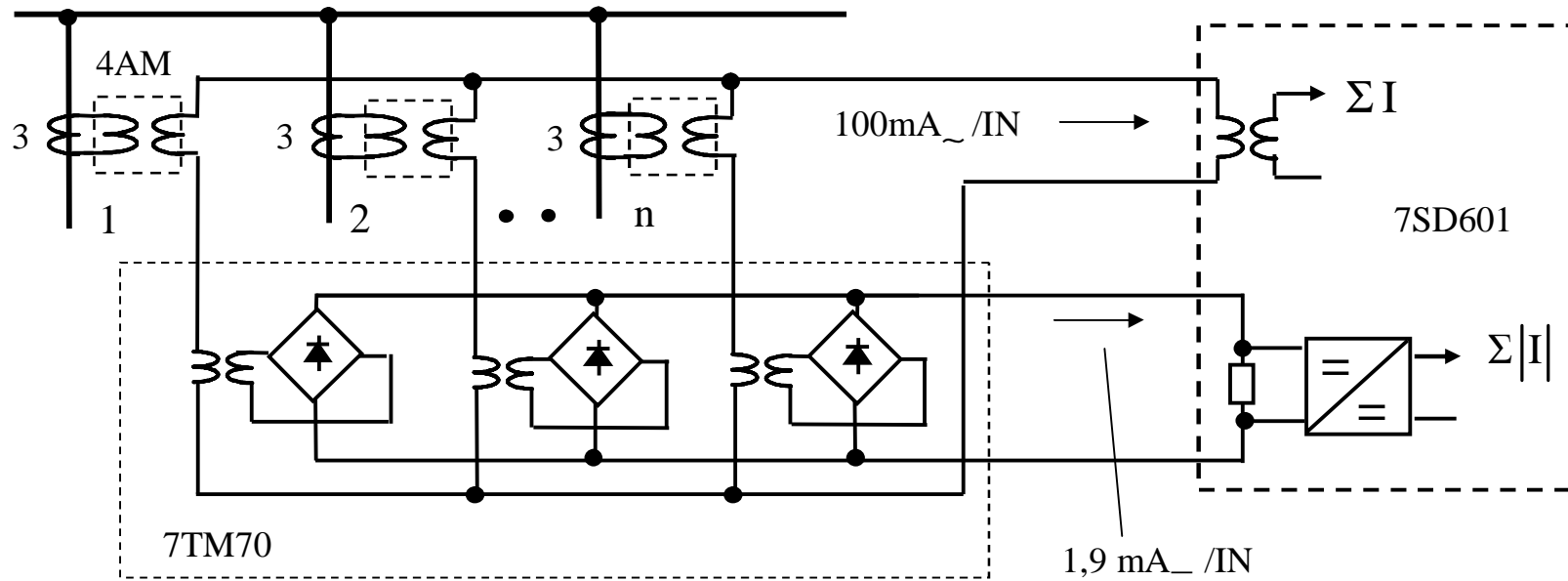


# 7SS6: Operating characteristic

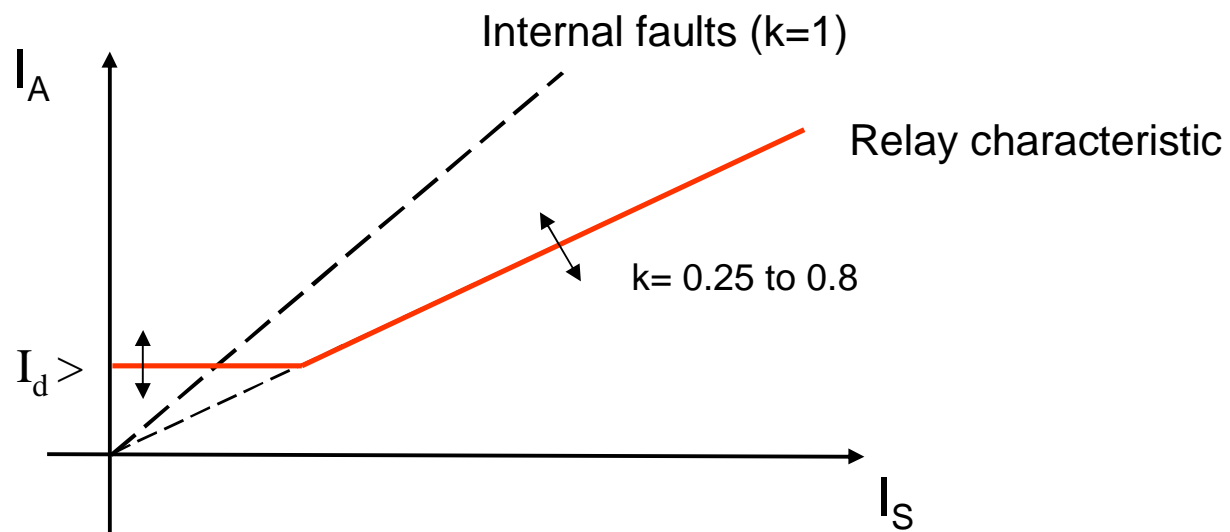

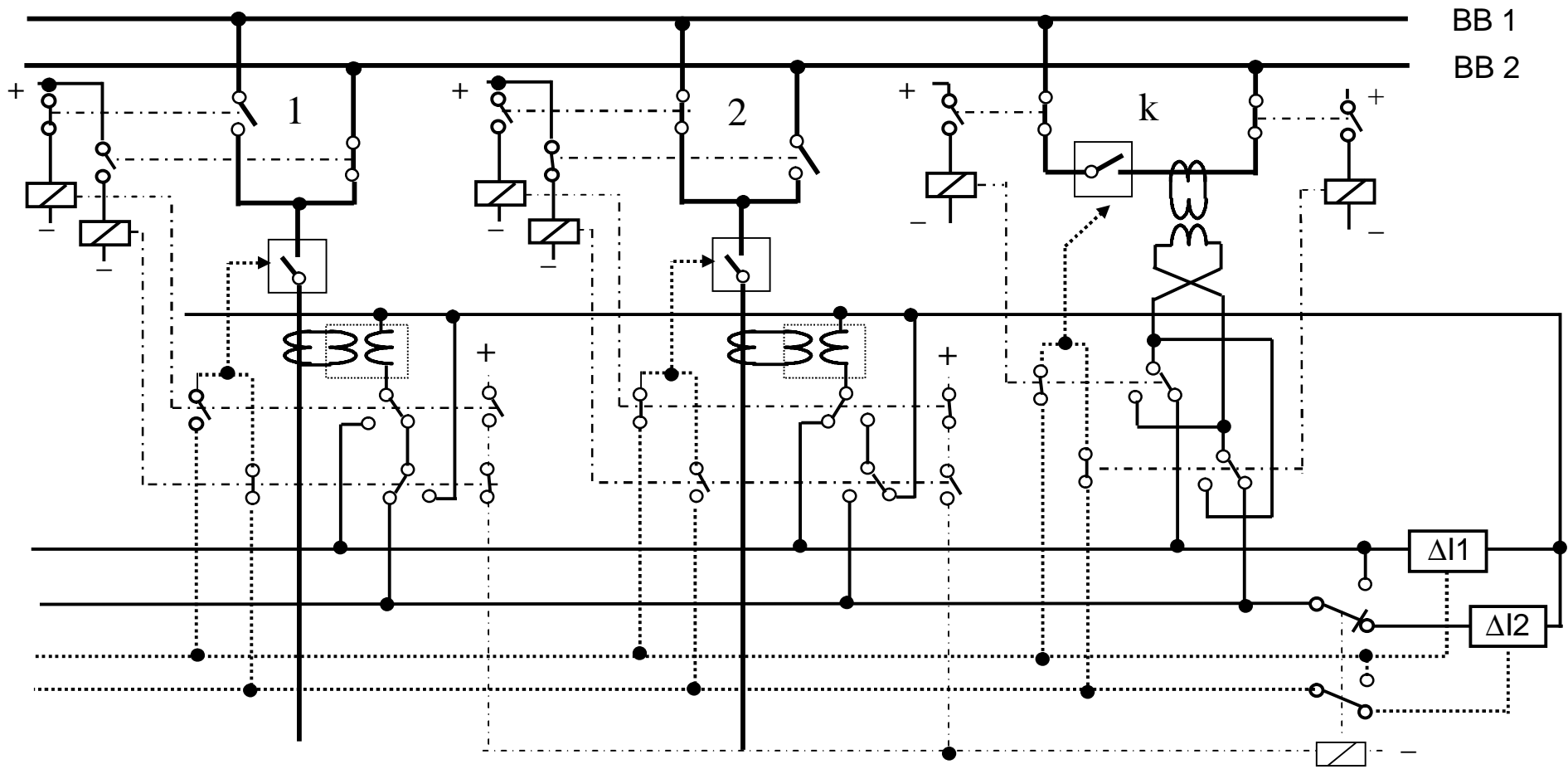
# Isolator replica, Principle, (stabilising circuit not shown)


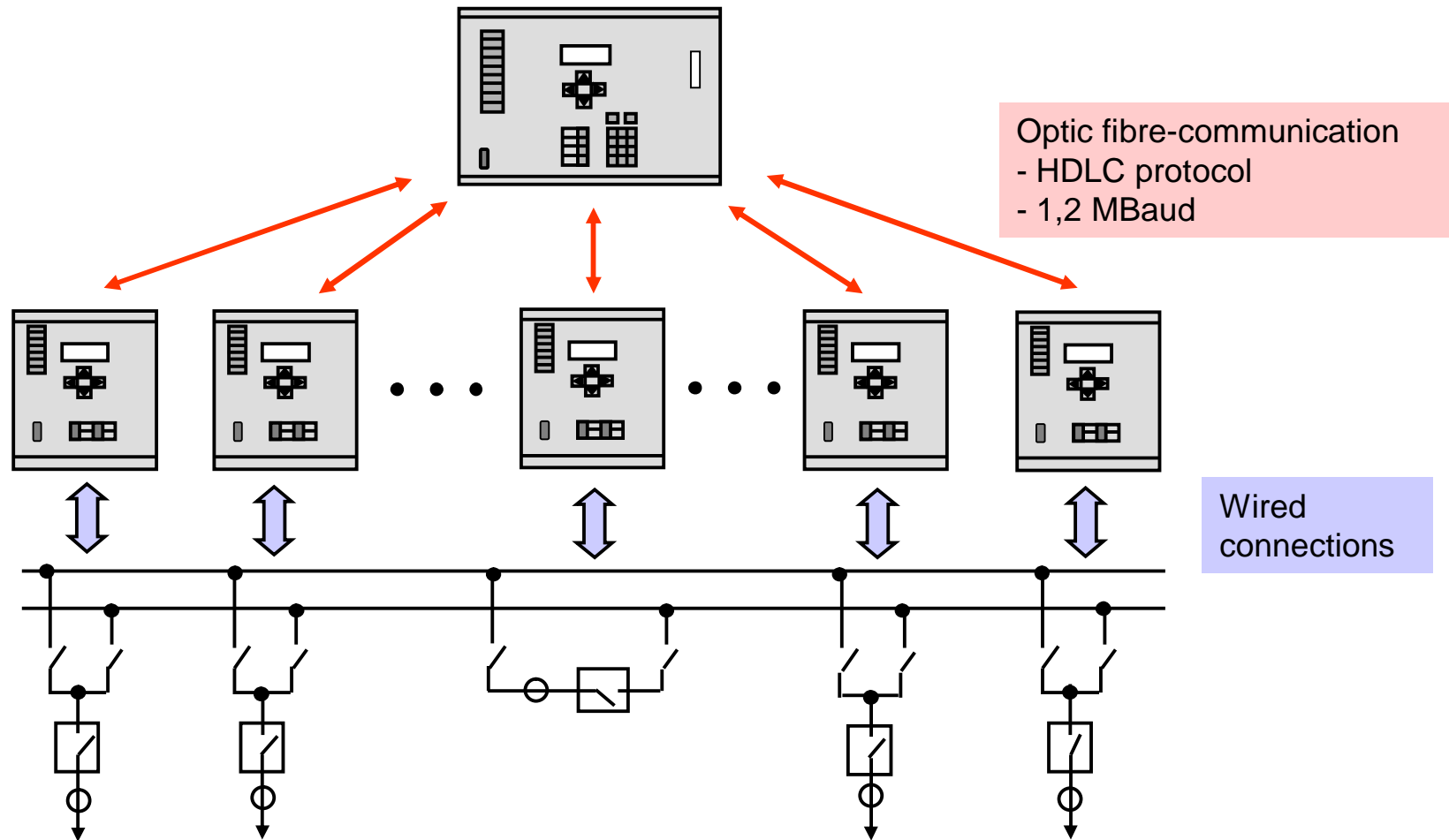
# Decentralised BB-protection 7SS52, Structure




## 7SS50/52: Maximum configuration

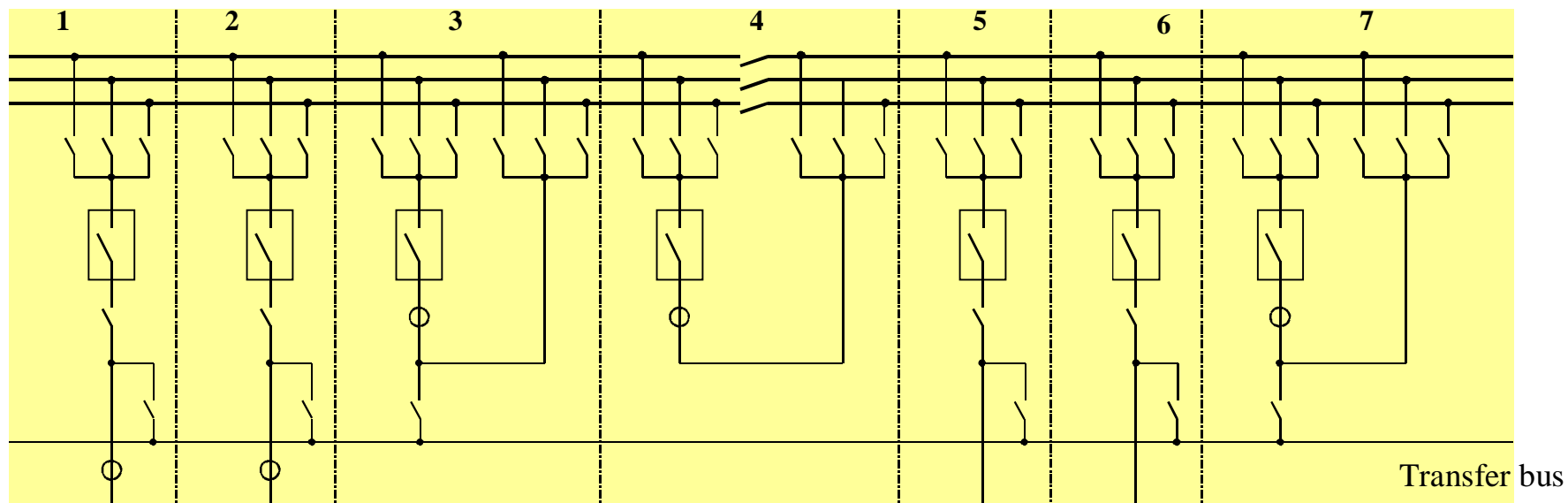


	<b>7SS50 centralised</b>	<b>7SS52 decentralised</b>
<b>Bays</b>	<b>32</b>	<b>48</b>
<b>BB-zones</b>	<b>8</b>	<b>12</b>
<b>couplings</b>	<b>4</b>	<b>16</b>
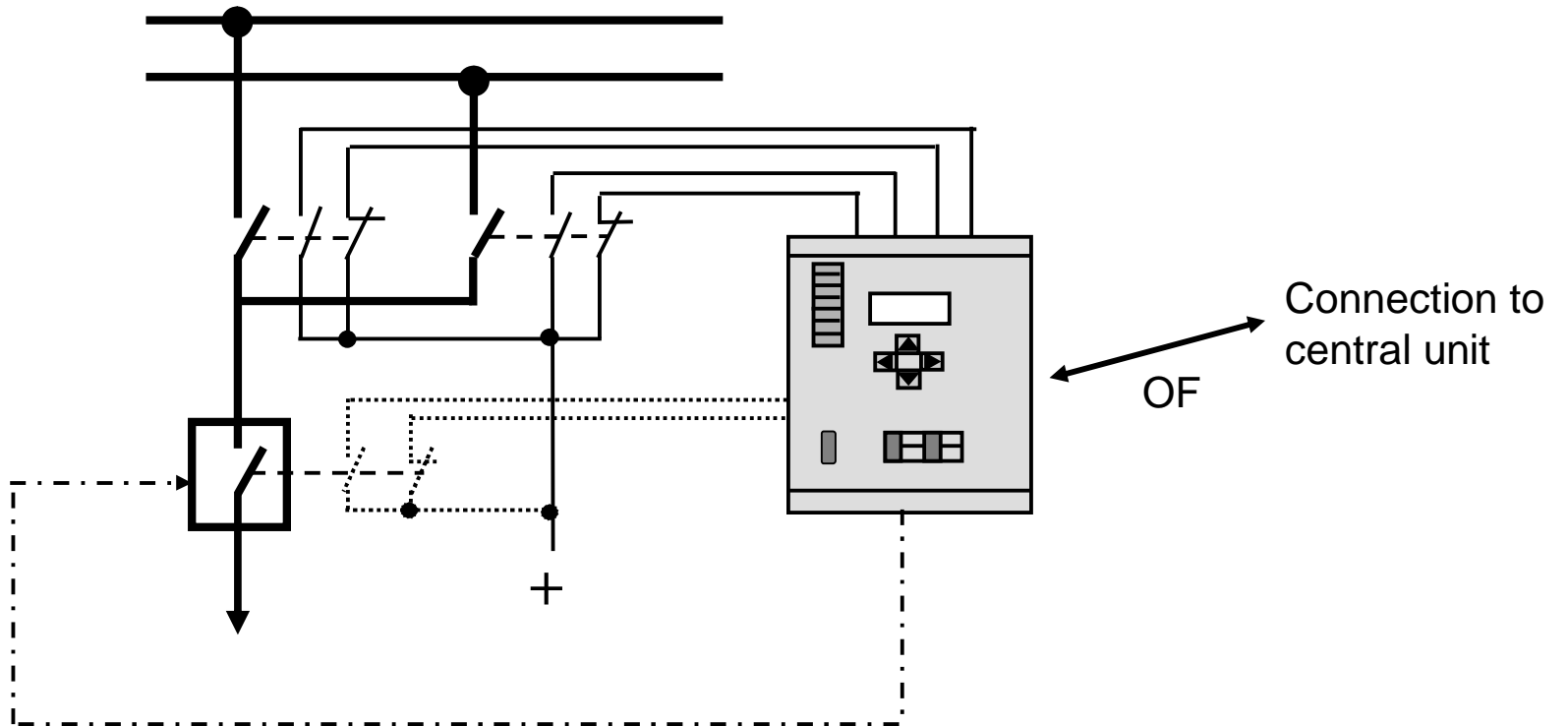
# 7SS50/52: Acquisition and supervision of isolator positions



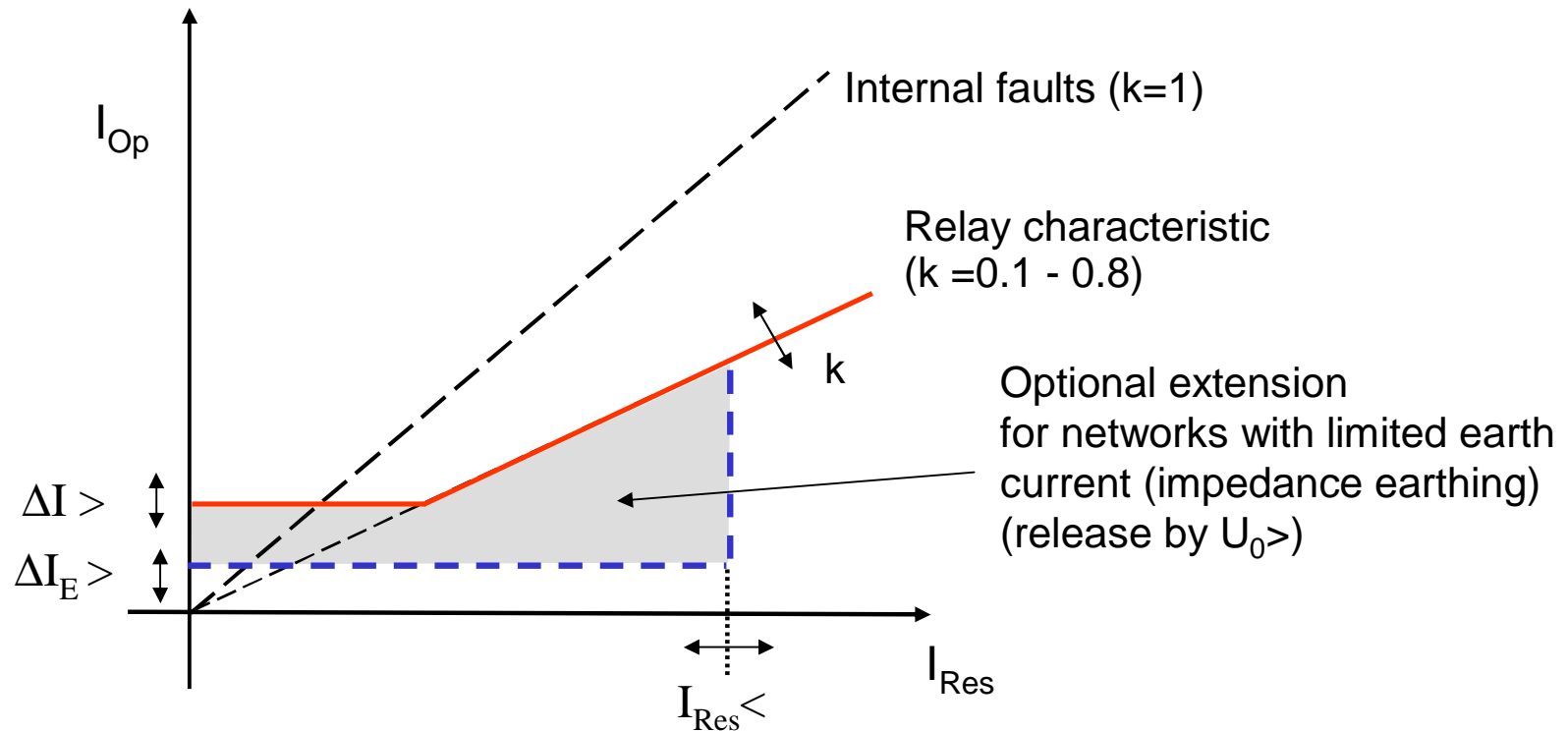
# Operating characteristic of BB protection 7SS52



# BB-Protection 7SS52
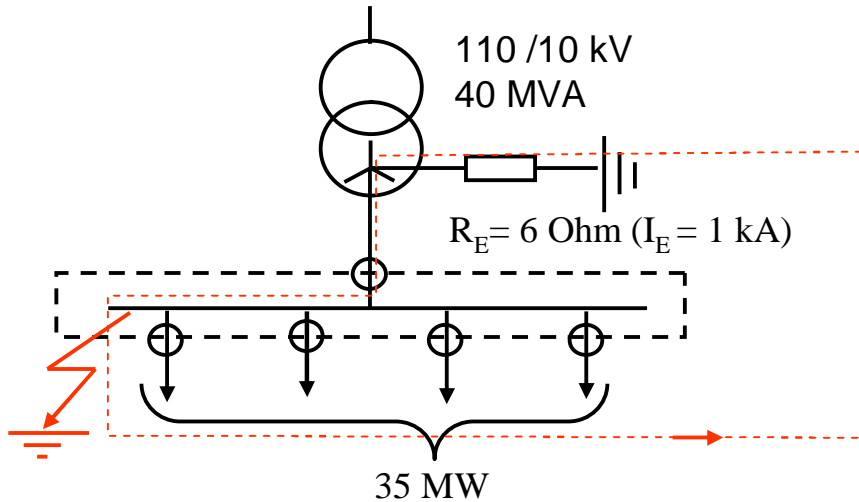
## Performance in networks with earth current limitation




$$I_L = \frac{35 \text{ MVA}}{10 \text{ kV} \cdot \sqrt{3}} = 2 \text{ kA}$$

$$I_F = I_E = 10 / \sqrt{3} \text{ kV} / 6 \Omega \approx 1 \text{ kA}$$

Restraint current:  $I_{Res} = \Sigma |I| = (2 + 1) + 2 \text{ kA}$


Operating current:  $I_{Op} = |\Sigma I| = I_E = 1 \text{ kA}$
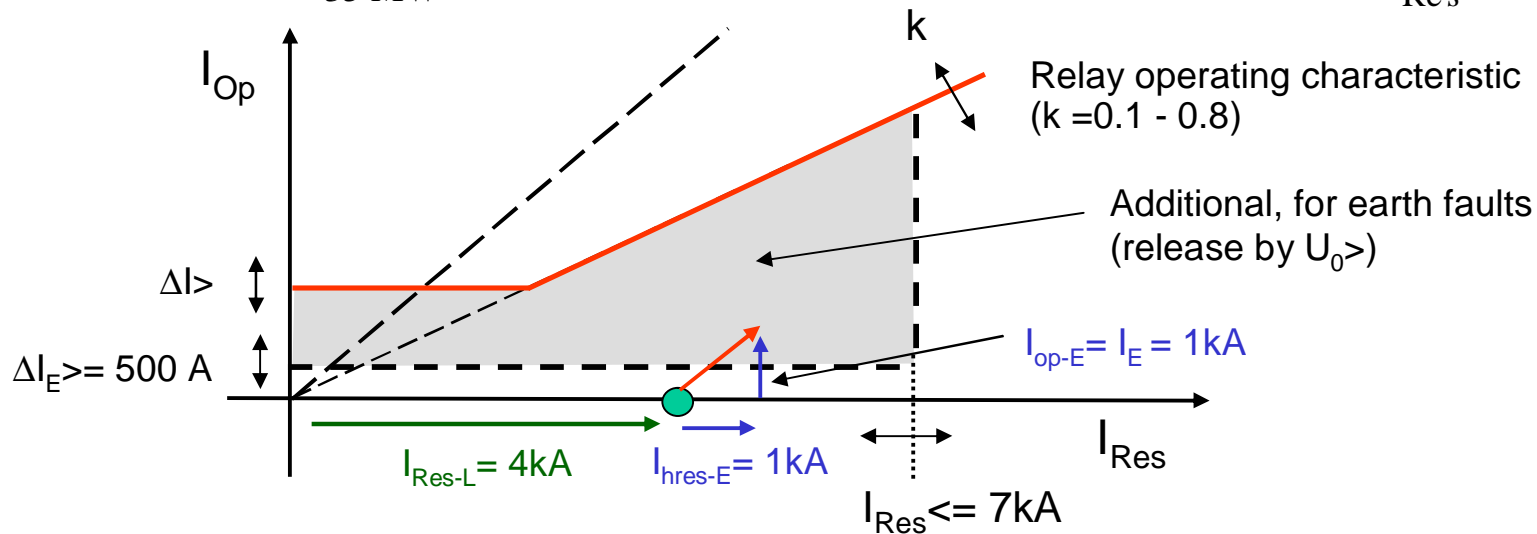
$$k = \frac{I_{Op}}{I_{Res}} = \frac{1}{5} = 0.2$$







## Check zone of busbar protection

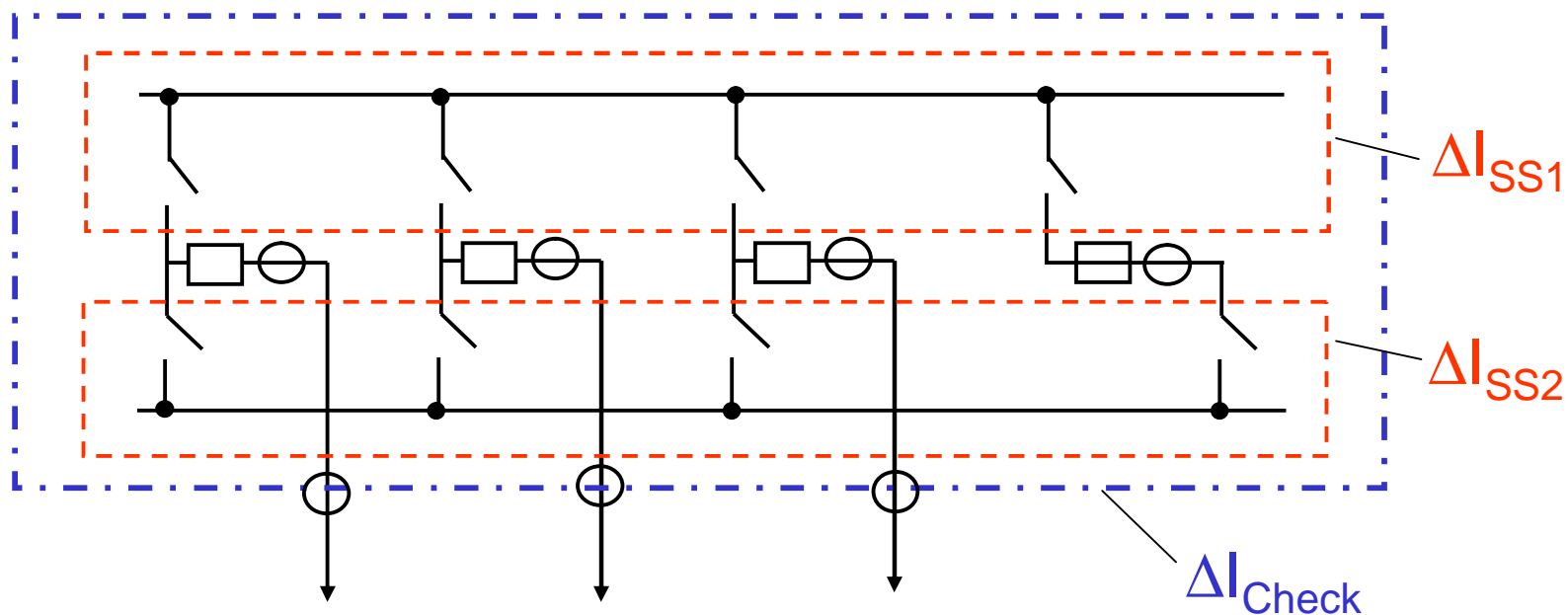

### Check zone:


- ∅ in the past used with HI protection on EHV level (needs separate CT cores)
- ∅ in general not used with traditional low impedance busbar protection (too expensive)
- ∅ However, now integrated as software function in full scheme versions 7SS51 and 7SS52
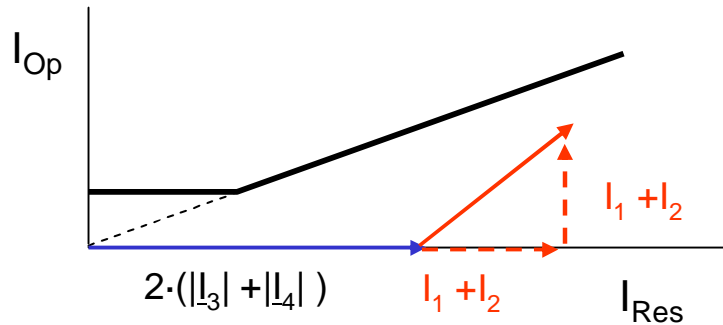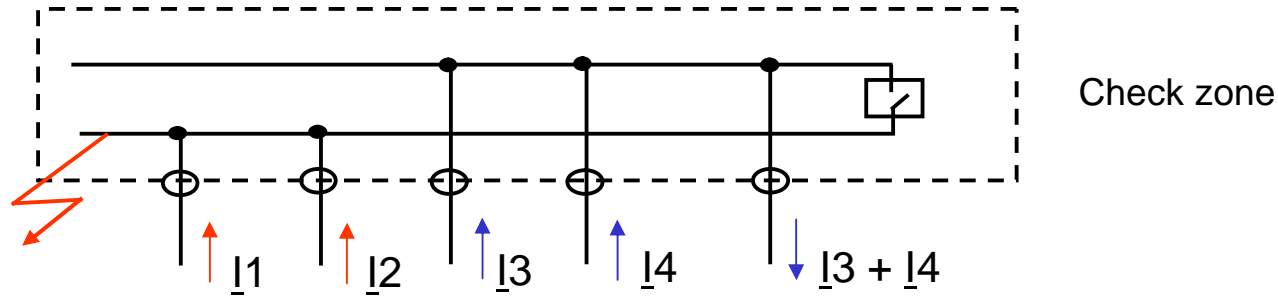
# 7SS52: special restraint algorithm avoids over-stabilisation



Normal restraint:  
Sum of all current magnitudes

$$I_{Res} = \sum |I| = |I_1| + |I_2| + |I_3| + |I_4| + |I_3| + |I_4|$$

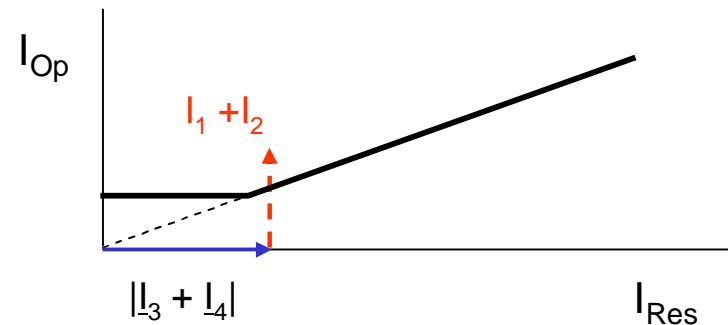


Special restraint algorithm:  
Positive and negative currents are added separately.

$$\sum |I_{-p}| = |I_1| + |I_2| + |I_3| + |I_4| \quad \sum |I_{-n}| = |I_3| + |I_4|$$

Smaller value is then taken:

$$I_{Res} = \sum |I_{-n}| = |I_3| + |I_4|$$
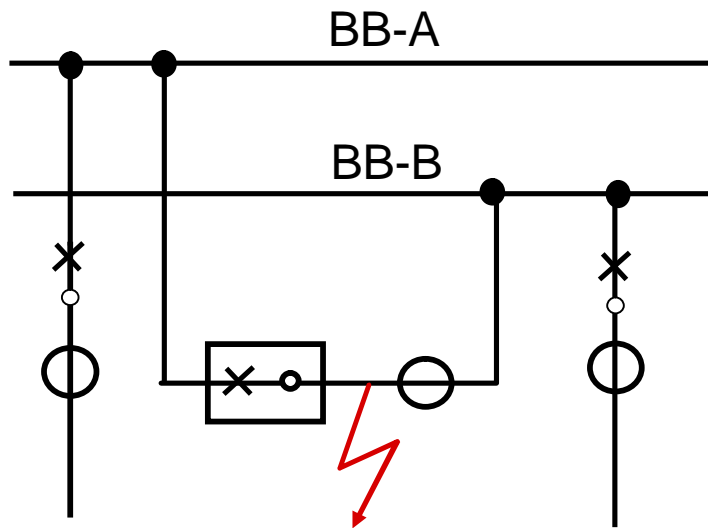
## 7SS52: Special treatment of dead zone faults (1)




Bus coupler CB aux. contacts **not** connected:

- 87-A trips bus coupler
- Current inverted in 87-B after T-BF.  
Subsequently 87-B trips BB-B

Coupler CB auxiliary contacts **connected**:

- 87-B trips immediately after opening of bus coupler CB because coupler current is removed from bus protection.  
→ time reduction (T-BF saved)
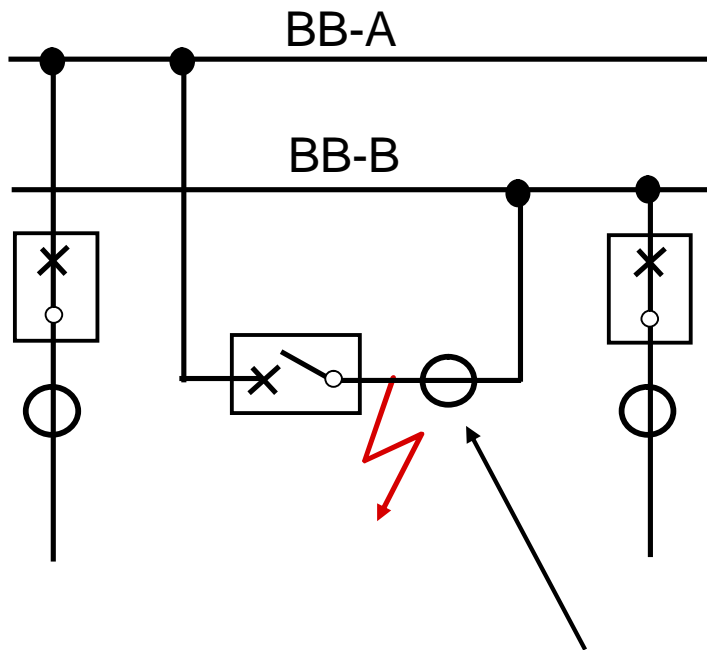
## 7SS52: Special treatment of dead zone faults (2)




- A) Bus coupler CB aux. contacts **not** connected:
- 87-A overfunctions and trips unnecessarily.
  - 87-B „sees“ an external fault and only trips finally through BF function (delay T-BF!)
- B) Bus coupler CB aux. contacts **connected**:
- 87-A remains stable („sees“ no fault current)
  - 87-B trips immediately

Coupler CB auxiliary contacts connected to 7SS52:  
Coupler current is removed from 87-A and 87-B current comparison with open coupler CB.
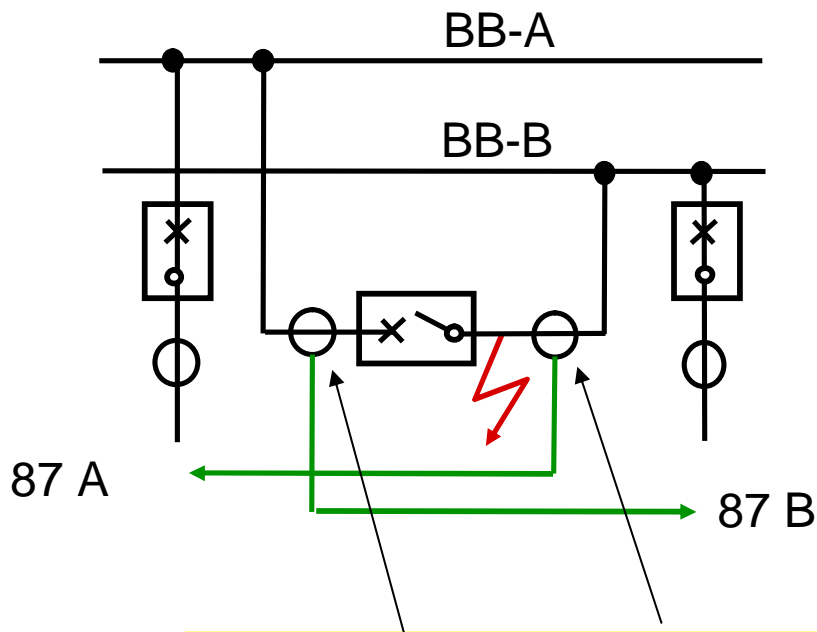
## 7SS52: Special treatment of dead zone faults (3)

Two CTs in coupling bay, overlapping protection zones




Coupler CB auxiliary contacts  
**connected:**

- 87-A „sees“ external fault and remains stable
- 67-B correctly trips BB-B

**Coupler CB auxiliary contacts connected to 7SS52:**

Coupler currents are removed from 87-A and 87-B current comparison with open coupler CB.

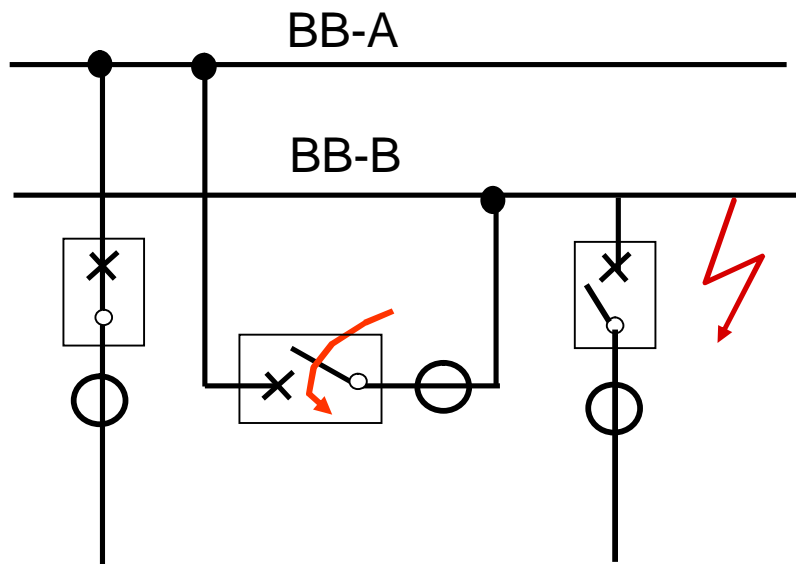
## 7SS52: Treatment of switch onto a faulted (earthed) bus



Coupler CB close command is detected by bus protection (change of binary input signal):

- Coupler current is immediately re-included in the 87 current comparison before CB contacts close.
- Selective tripping of BB-B by 87-B.
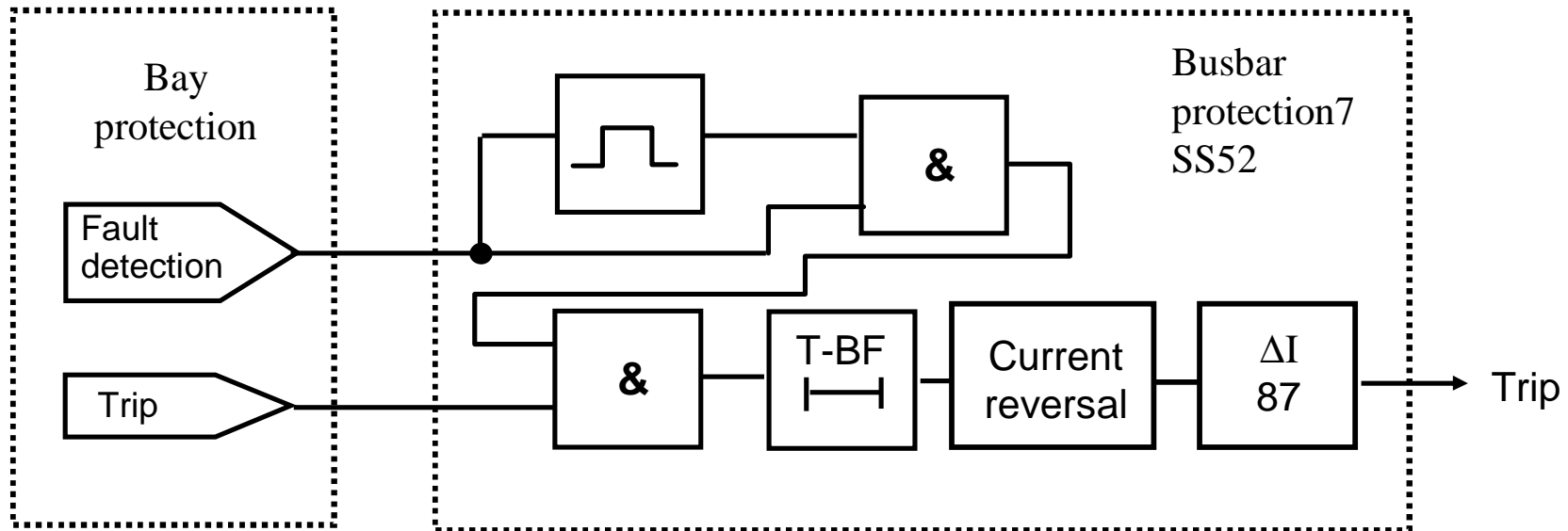
## 7SS52 : Integral breaker fail protection




With line fault and CB failure:

- Trip command of bay protection hangs on at BB protection
- Forced current reversal of the current of concerned bay after T-BF
- Zone selective tripping only of the concerned busbar
- Advantage: Reset time (overtravel time) of bay protection does not matter

## External bay dedicated BF protection

Zone selective tripping via isolator replica of 7SS52 busbar protection


Bay (feeder) protection

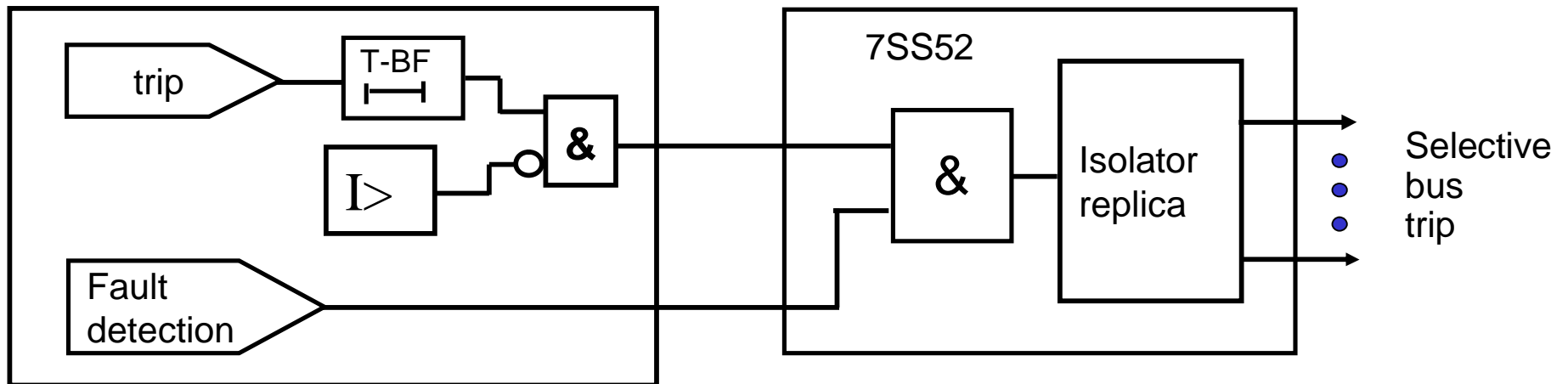


- BF trip command to busbar protection binary input (for security: fault detection signal as second criterion)
- Distribution of trip commands via isolator replica to breakers of concerned busbar
- è zone selective tripping of concerned busbar


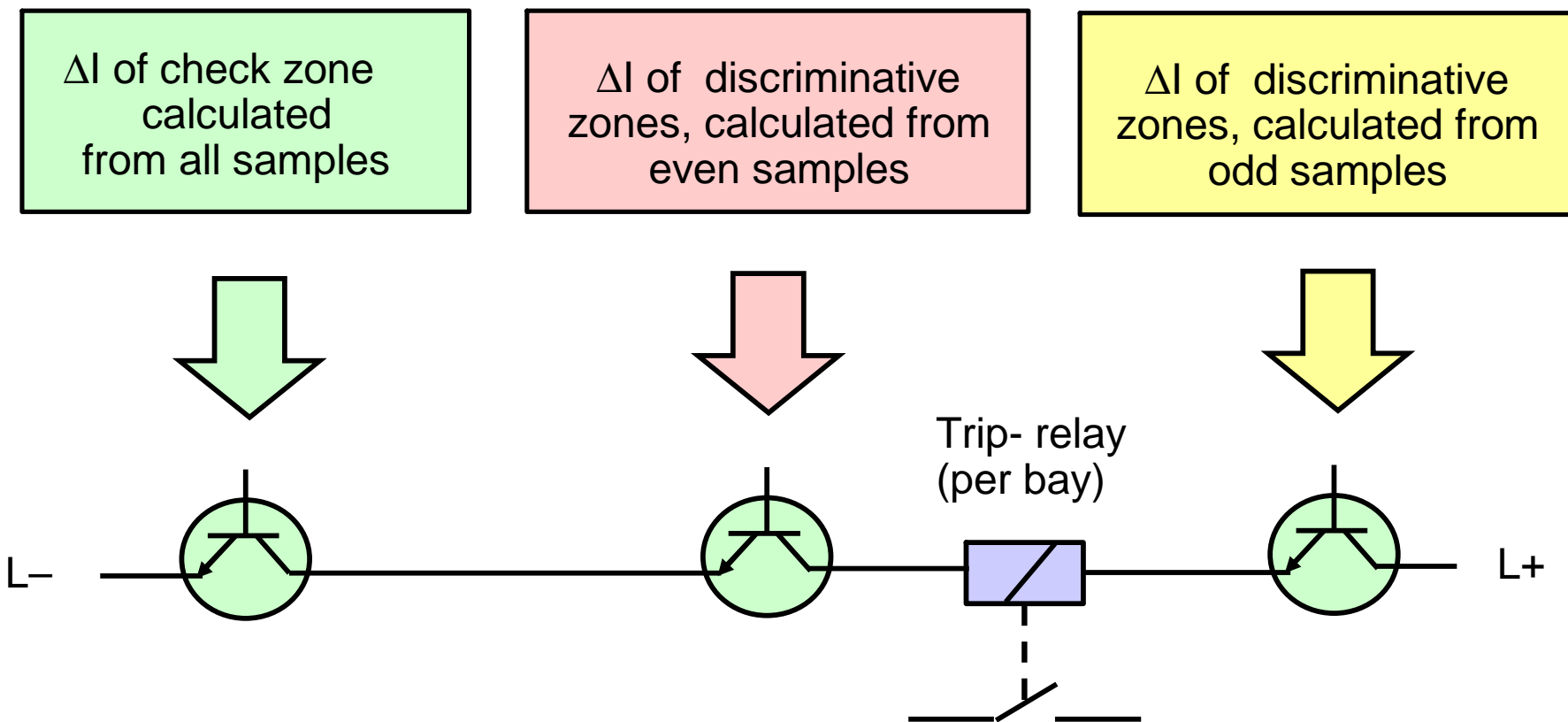
# Fail safe design: 3-out-of-3 decision per bay






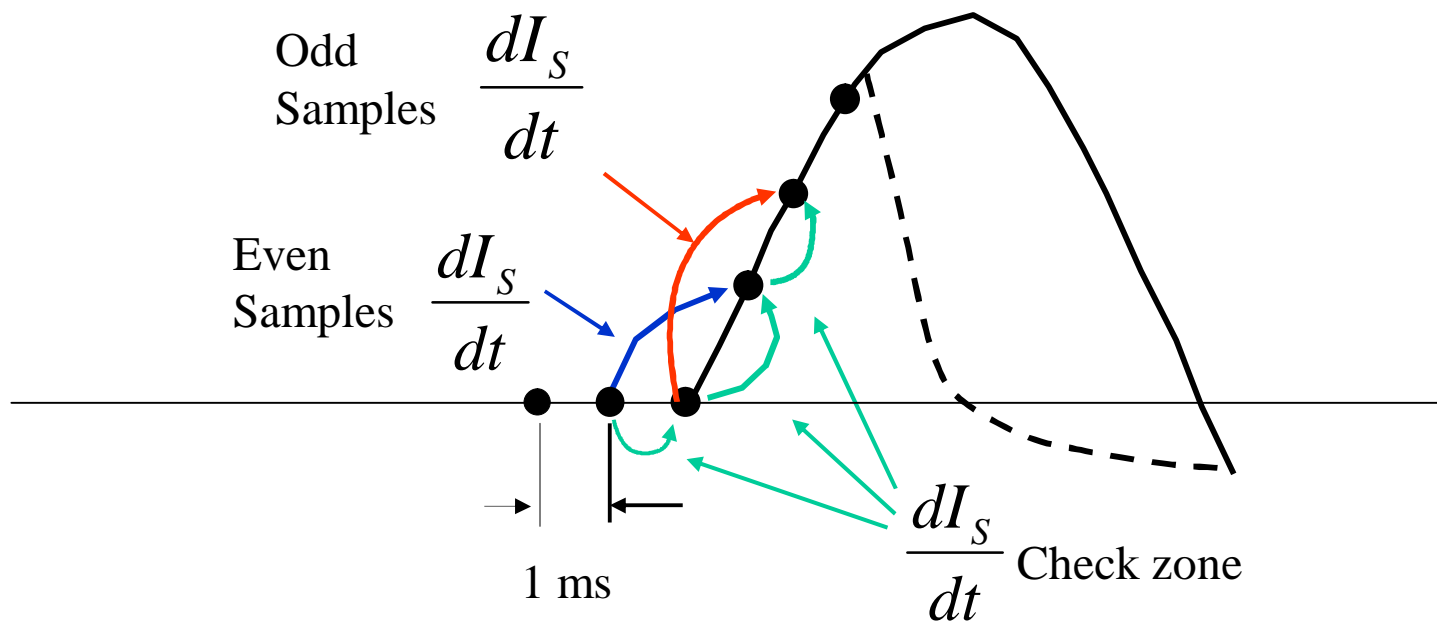
# Adaptive measurement (Booster circuit) (7SS5)




# Digital busbar protection 7SS5, Measuring technique

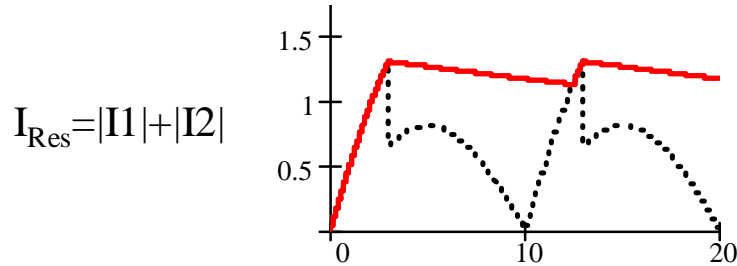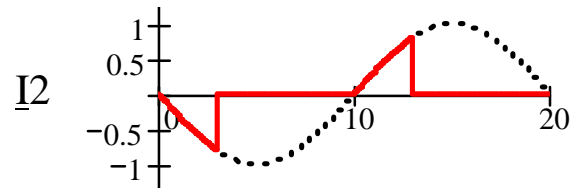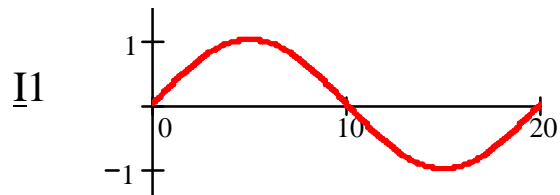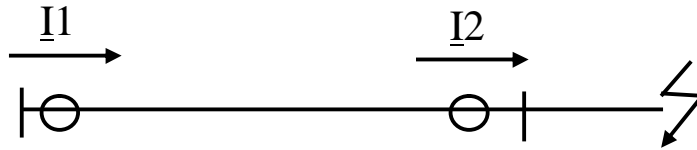
## External fault, symmetrical fault current




$$I_{Op} = |I_1 + I_2|$$

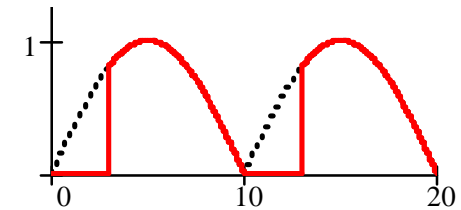

$$k \cdot I_{Res} = k \cdot (|I_1| + |I_2|)$$



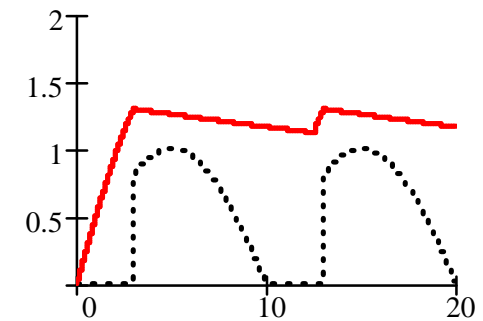


$$\Delta I = I_{Op} - I_{Res}$$

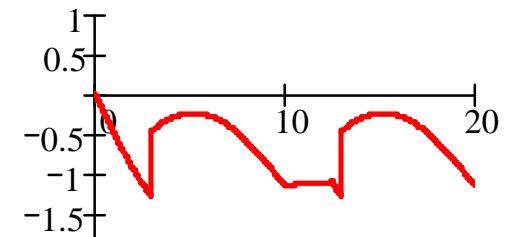


# Digital busbar protection 7SS5, Measuring technique

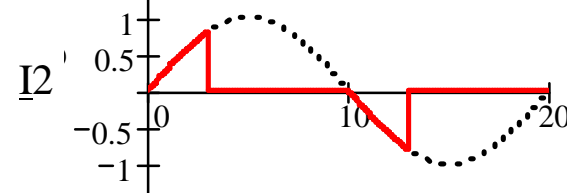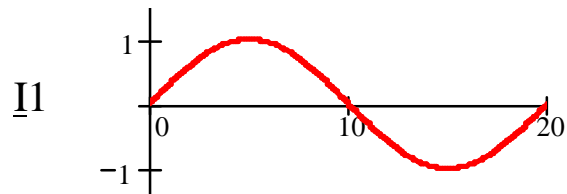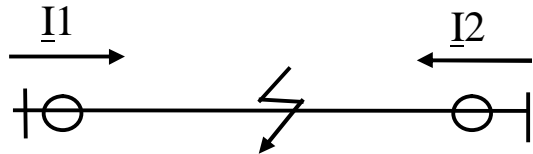
## Internal fault, symmetrical fault current




$$I_{Res} = |I1| + |I2|$$

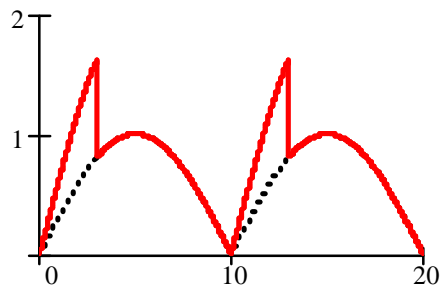


$$I_{Op} = |I1 + I2|$$

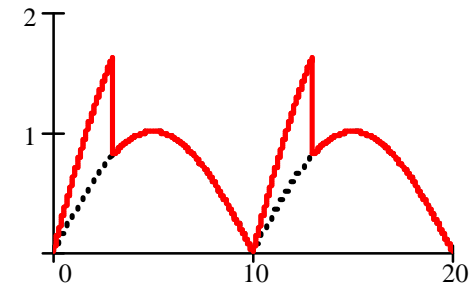


$$k \cdot I_{Res} = k \cdot (|I1| + |I2|)$$

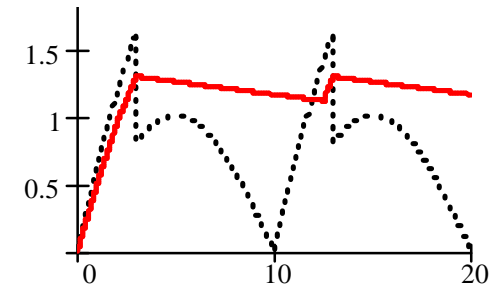



$$\Delta I = I_{Op} - I_{Res}$$

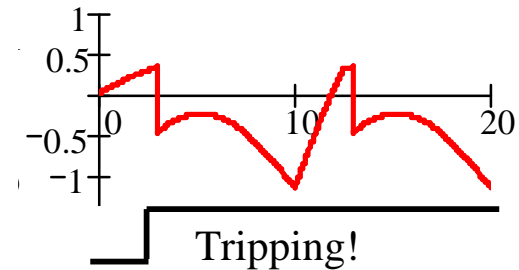
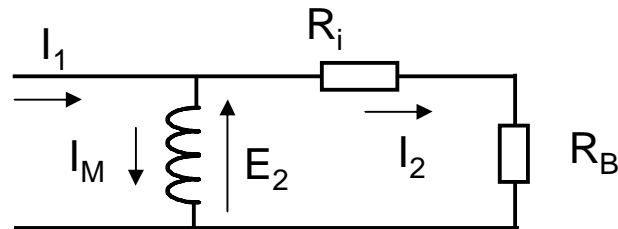
# 7SS5/6: Admissible over-burdening - Necessary dimensioning of CTs with regard to symmetrical fault currents


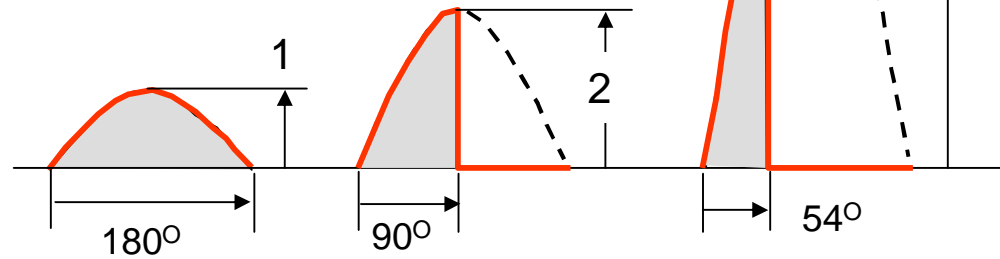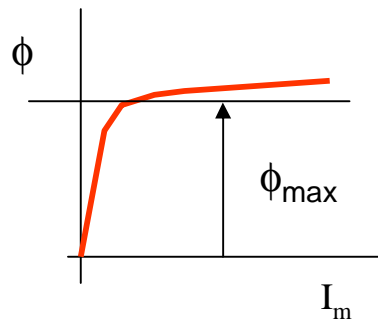
$$\Phi = \int e_2(t) = (R_i + R_B) \int i_2(t)$$



$$\Phi_{\max} \cong \int_0^{180^\circ} ALF' \cdot u_{2N}(t) \cdot dt = (R_i + R_B) \int_0^{180^\circ} ALF' \cdot i_{2N}(t) \cdot dt = (R_i + R_B) \cdot ALF' \cdot \hat{I}_2 \cdot \int_0^{180^\circ} \sin x \cdot dt = (R_i + R_B) \cdot ALF' \cdot \hat{I}_{2N} \cdot 2$$


$$\hat{I}_{2F} \int_0^x \sin x \cdot dt = ALF' \cdot \hat{I}_{2N} \cdot \int_0^{180^\circ} \sin x \cdot dt = ALF' \cdot \hat{I}_{2N} \cdot 2$$



$$\frac{I_{2F}}{I_{2N}} = ALF' \cdot \frac{2}{\int_0^x \sin x}$$

$$k_{OB} = \frac{I_{2F}/I_{2N}}{ALF'} = \frac{2}{\int_0^x \sin x}$$
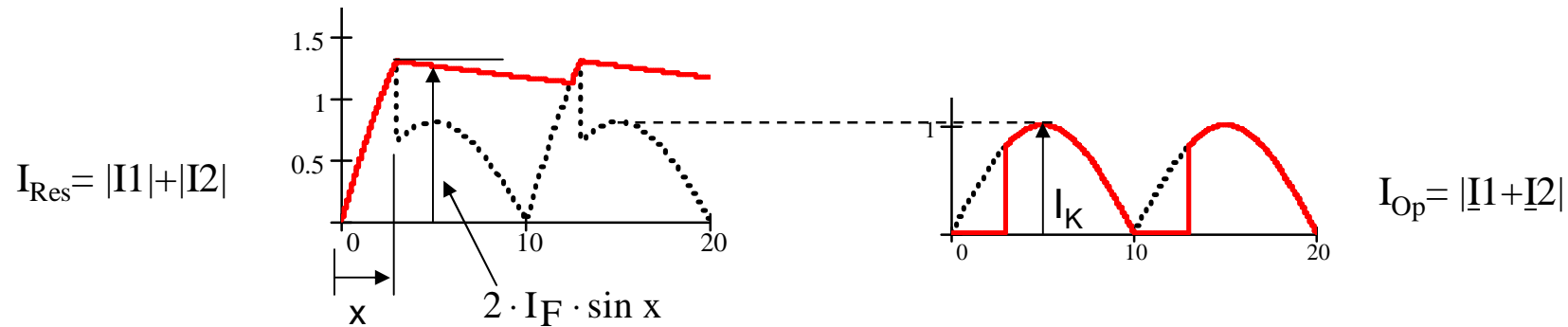
# Required restraining factor k dependent on over-burdening factor $K_{OB}$ (over-dimensioning factor $K_{TF}$ )



Condition for stability:

$$I_{Op} < k \cdot I_{Res}$$

$$I_F < k \cdot 2 \cdot I_F \cdot \sin x$$

①

①'

$$\sin x > \frac{1}{2 \cdot k}$$

②

$$\ddot{u} = \frac{I_2 K / I_2 N}{n'} = \frac{2}{\int_0^x \sin x} = \frac{2}{1 - \cos x}$$

from previous transparency)





$$k > \frac{K_{OB}}{4 \cdot \sqrt{K_{OB} - 1}} \quad \text{or} \quad k > \frac{1}{4 \cdot \sqrt{K_{TF} - K_{TF}^2}}$$

$K_{OB}$  = CT over-burdening factor

$K_{TF} = 1/K_{OB}$  = CT over-dimensioning factor

# Digital busbar protection 7SS5, Measuring technique

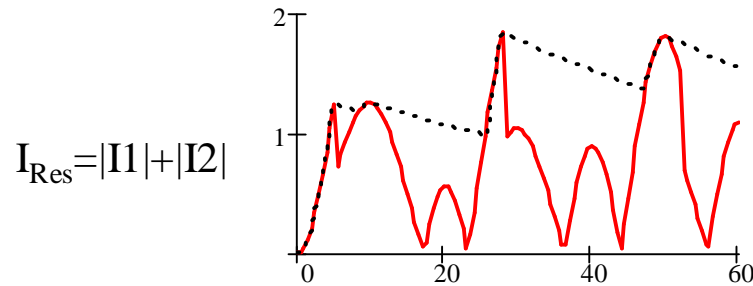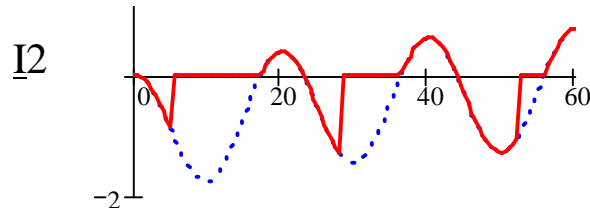
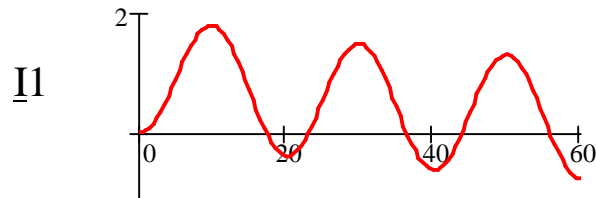
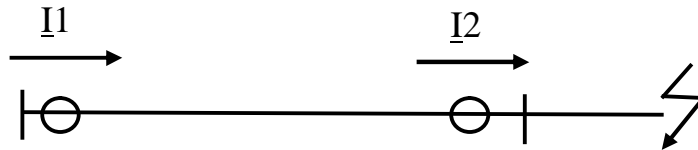
## External fault, fault current with DC offset



$$I_{Op} = |I_1 + I_2|$$




$$k \cdot I_{Res} = k \cdot (|I_1| + |I_2|)$$

$$\Delta I = I_{Op} - I_{Res}$$

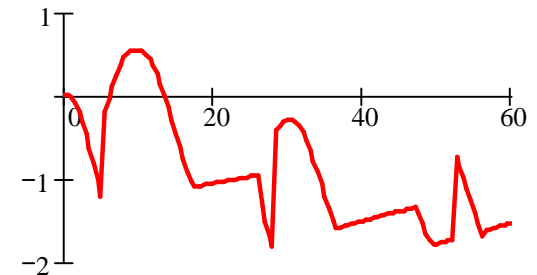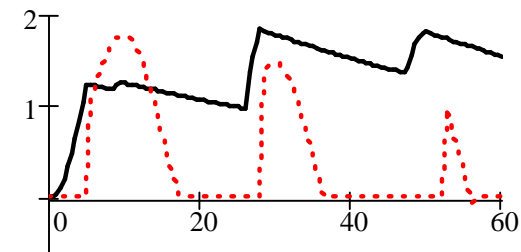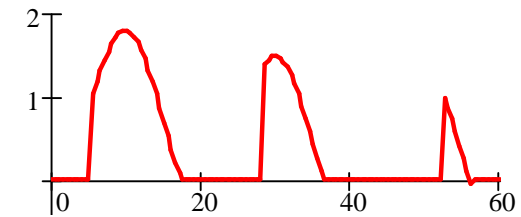


# Digital busbar protection 7SS5, Measuring technique
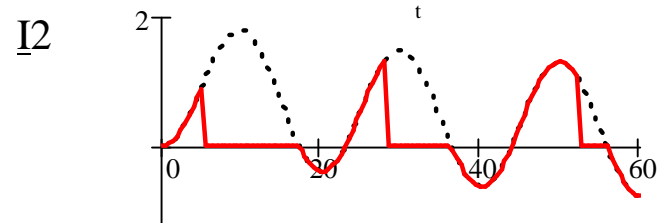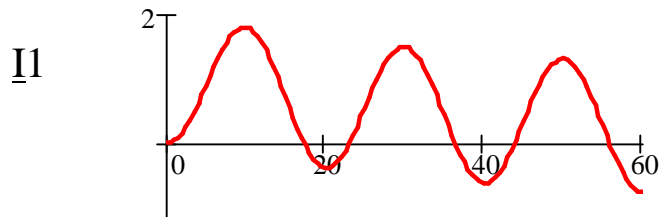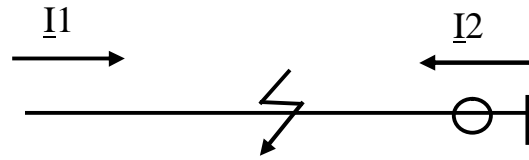
## Internal fault, fault current with DC offset






$$I_{Res} = |I1| + |I2|$$

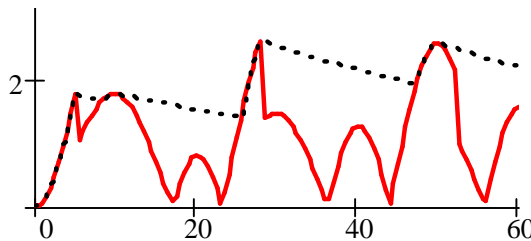

$$I_{Op} = |I1 + I2|$$

$$k \cdot I_{Res} = k \cdot (|I1| + |I2|)$$


$$\Delta I = I_{Op} - I_{Res}$$

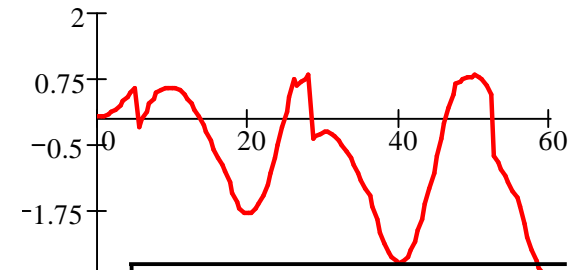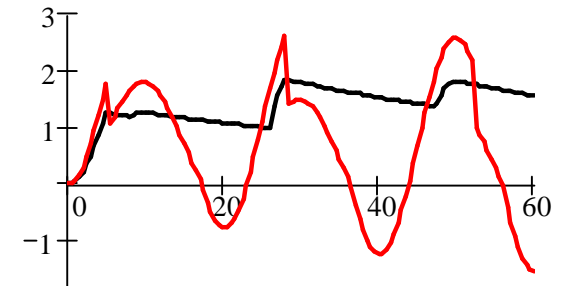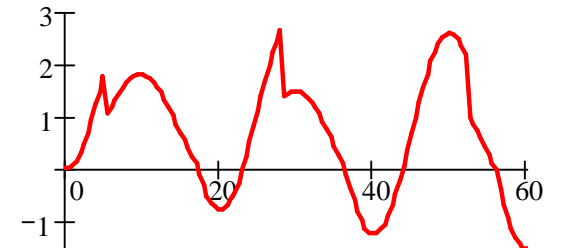

Tripping!


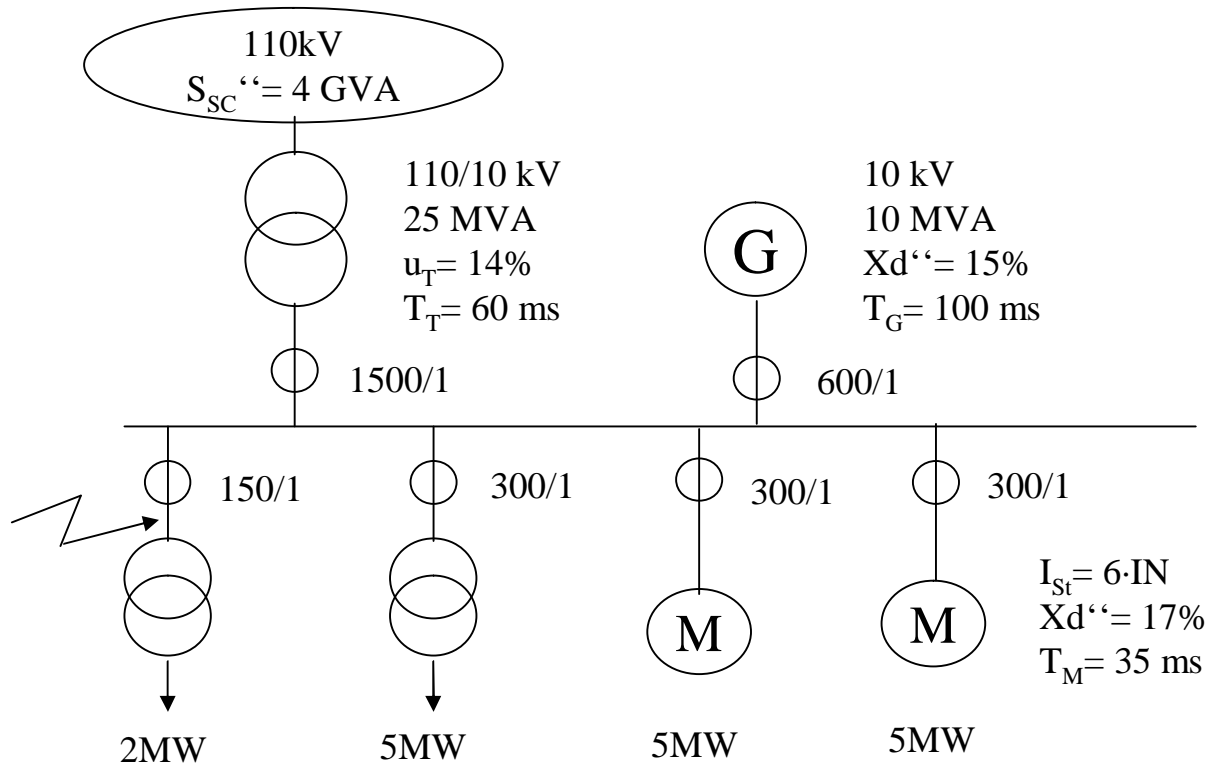
## CT dimensioning for busbar protection 7SS5, Example (1)



$$I_{N-T} = \frac{25 \cdot 10^6}{10 \cdot 10^3 \cdot \sqrt{3}} = 1440 \text{ A}$$

$$I_{N-G} = \frac{10 \cdot 10^6}{10 \cdot 10^3 \cdot \sqrt{3}} = 577 \text{ A}$$

$$\Sigma I_{N-M-HV} = 2 \cdot \frac{5 \cdot 10^6}{10 \cdot 10^3 \cdot \sqrt{3}} = 577 \text{ A}$$

$$I_{F-T} = \frac{1.1 \cdot 1440}{0.14} = 11.3 \text{ kA}$$

$$I_{F-G} = \frac{1.1 \cdot 577}{0.15} = 4.2 \text{ kA}$$

$$\Sigma I_{F-M} = \frac{1.1 \cdot 577}{0.17} = 3.7 \text{ kA}$$

## CT dimensioning for busbar protection 7SS5 and 7SS6, Example (2)

As worst case, the CT 150/1 A in bay 1 is considered.

Total fault current with a fault at the transformer HV terminals:

$$\Sigma I_F = I_{F-T} + I_{F-G} + \Sigma I_{F-M} = 11,3 + 4,2 + 3,7 = 19,2 \text{ kA}$$

Equivalent time constant:

$$T_{\text{Equiv.}} = \frac{I_{F-T} \cdot T_T + I_{F-G} \cdot T_G + \Sigma I_{F-M} \cdot T_M}{I_{F-T} + I_{F-G} + \Sigma I_{F-M}} = \frac{11.3 \cdot 60 + 4.2 \cdot 100 + 3.7 \cdot 35}{11.3 + 4.2 + 3.7} = 64 \text{ ms}$$

We consider a CT type 5P?, 30 VA, internal burden  $P_i = 15\%$  (4.5 VA):

Connected burden  $P_a = 1 \text{ VA}$

CT over-dimensioning factor for 3ms saturation free time:  $K_{TF}$  ca. 0.45

Corresponding to an overburdening factor of  $k_{OB} = 1/K_{TF} = 2.2$

Checking of the k-setting

(Stability with symmetrical fault currents):

$$k > \frac{k_{OB}}{4 \cdot \sqrt{k_{OB} - 1}} = \frac{2,2}{4 \cdot (2.2 - 1)} = 0.5 \quad (\text{chosen: } k=0.6)$$



$$ALF' = \frac{\Sigma I_F}{I_{N-CT}} \cdot K_{TF} = \frac{19.200}{150} \cdot 0.45 = 58$$

$$ALF = \frac{P_a + P_i}{P_N + P_i} \cdot ALF' = \frac{1 + 4.5}{30 + 4.5} \cdot 58 = 9.3$$


We finally choose: CT 5P10, 150/1, 30 VA,  $R_2 \leq 4.5 \text{ Ohm}$

# Transient performance of iron closed CT cores (type TPX)
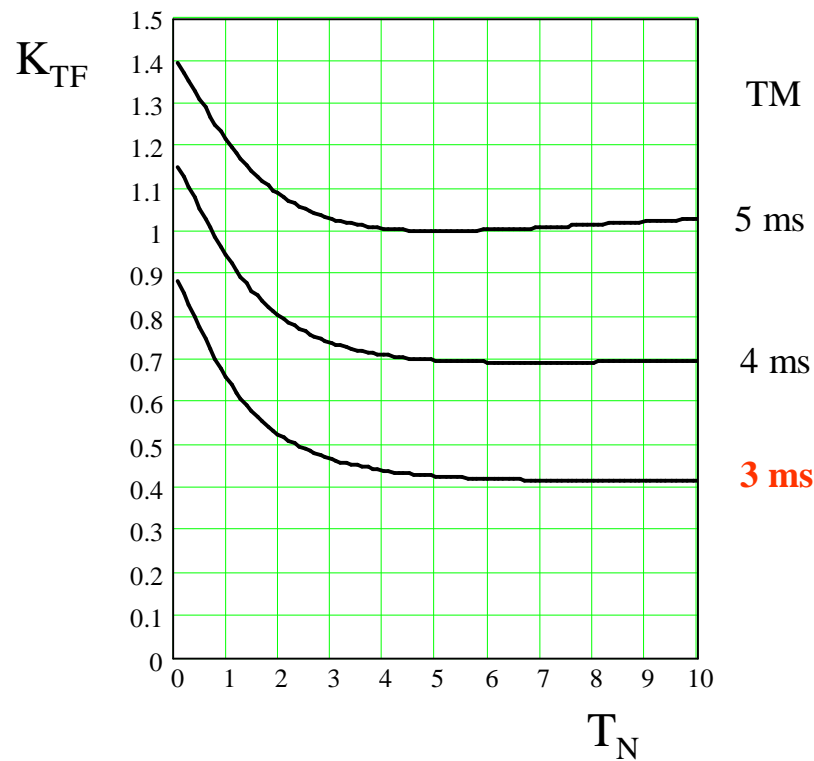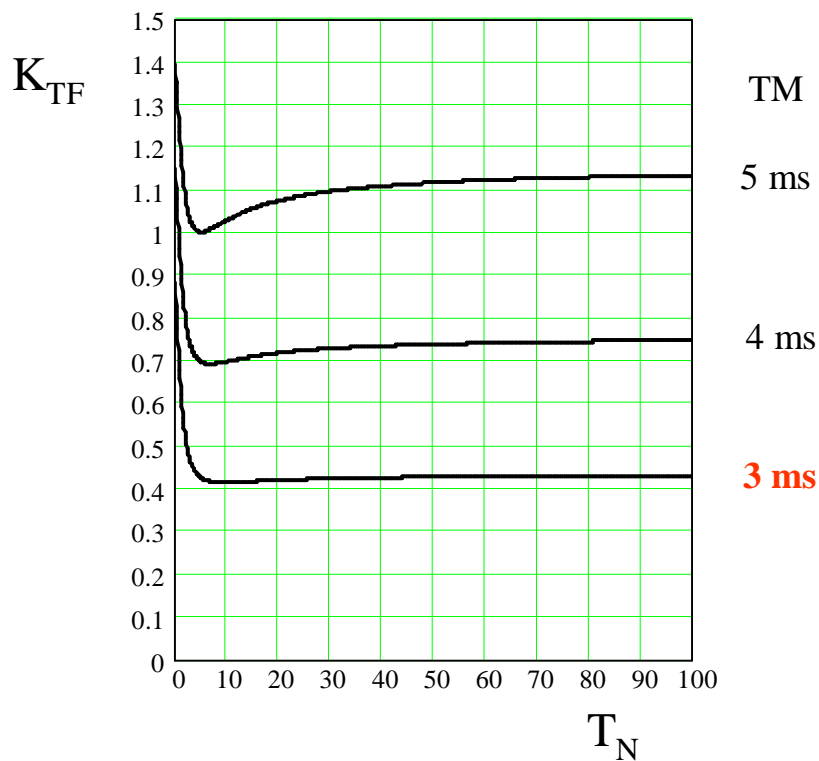
## Over-dimensioning factor $K_{TF}$ for short time to saturation



# High impedance busbar protection

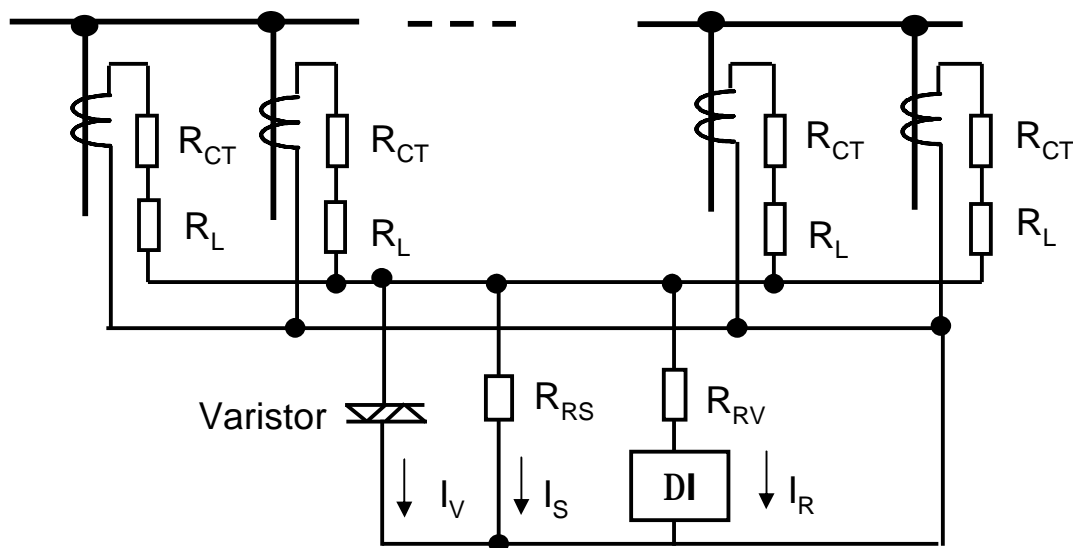

$R_{CT}$ : Resistance of CT secondary winding

$R_L$ : Connection cable resistance

$R_{RV}$ : Relay series resistance

$R_{RS}$ : Relay shunt resistance

## HI busbar protection, calculation example

---

**Given:** :n = 8 feeders

$$r_{CT} = 600/1 \text{ A}$$

$$U_{KN} = 500 \text{ V}$$

$$R_{CT} = 4 \text{ Ohm}$$

$$I_{mR} = 30 \text{ mA (at relay pick-up voltage)}$$

$$R_L = 3 \text{ Ohm (max.)}$$

$$I_R = 20 \text{ mA (fixed value)}$$

$$R_{RV} = 10 \text{ kOhm}$$

$$R_{RS} = 250 \text{ Ohm}$$

$$I_V = 50 \text{ mA (at relay pick-up voltage)}$$

Primary pick-up current:

$$I_{F-\min} = r_{CT} \cdot (I_R + I_S + I_V + n \cdot I_{mR})$$

$$I_{F-\min} = \frac{600}{1} \cdot (0.02 + 0.89 + 0.05 + 8 \cdot 0.03)$$

$$I_{F-\min} = 666 \text{ A} \cdot (111\% I_{N-CT})$$


Stability with external faults:

$$I_{F-\text{through} -\max} < r_{CT} \cdot \frac{R_R}{R_L + R_{CT}} \cdot I_R$$

$$I_{F-\text{through} -\max} < \frac{600}{1} \cdot \frac{10.000}{3 + 4} \cdot 0.02$$

$$I_{F-\text{through} -\max} < 17 \text{ kA} = 28 \cdot I_n$$
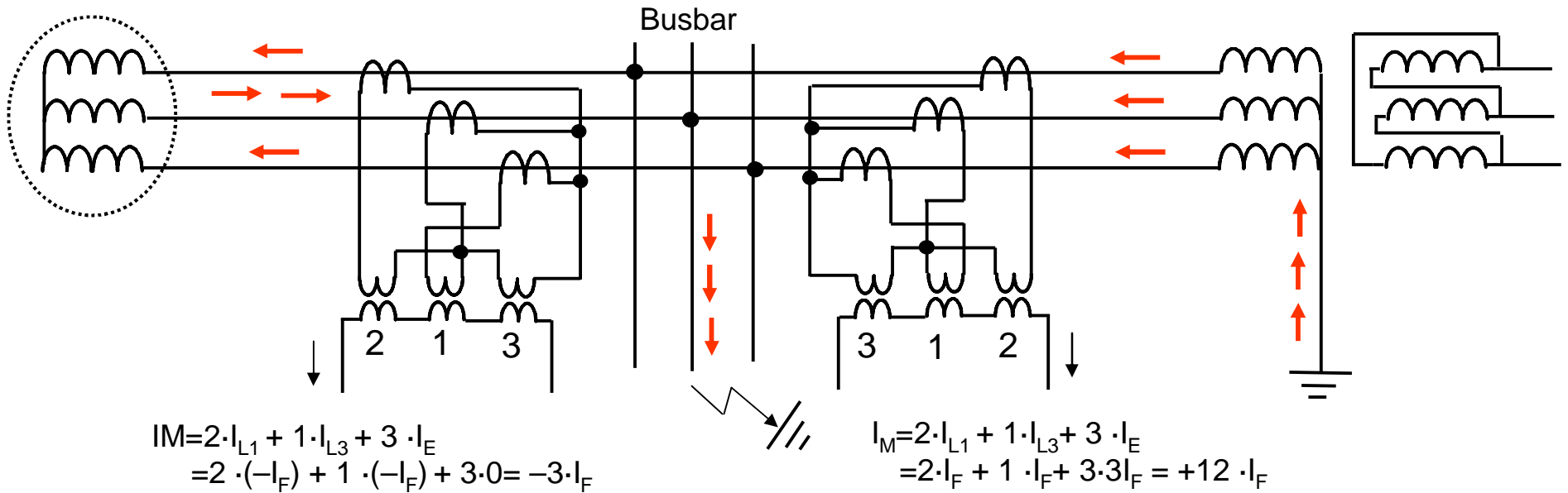
# Busbar protection, Composite current type (7SS600): Performance under unfavourable system earthing conditions




$$\left. \begin{aligned} I_{Op} &= |I_{M1} + I_{M2}| = 9 \cdot I_F \\ I_{Res} &= |I_{M1}| + |I_{M2}| = 15 \cdot I_F \end{aligned} \right\} k = 9/15 = 0.6$$


Faults in other phases:

$$\left. \begin{aligned} \text{Fault L1-E: } I_{Op} &= (3+12) \cdot I_F = 15 \cdot I_F, \\ I_{Res} &= (3+12) \cdot I_F = 15 \cdot I_F, \end{aligned} \right\} k = 1$$
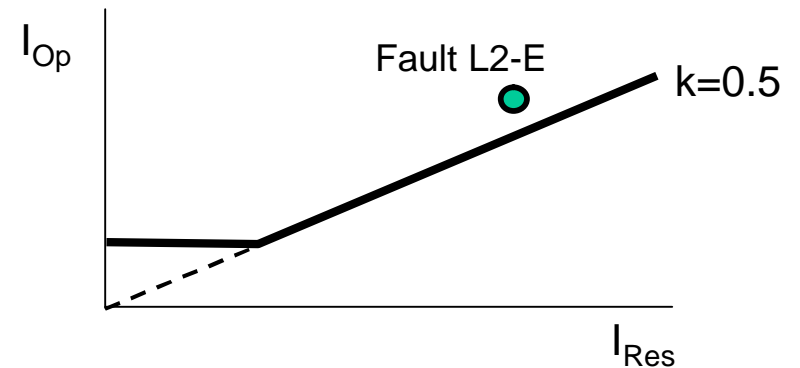
$$\left. \begin{aligned} \text{Fault L3-E: } I_{Op} &= (0+12) \cdot I_F = 12 \cdot I_F, \\ I_{Res} &= (0+12) \cdot I_F = 12 \cdot I_F, \end{aligned} \right\} k = 1$$


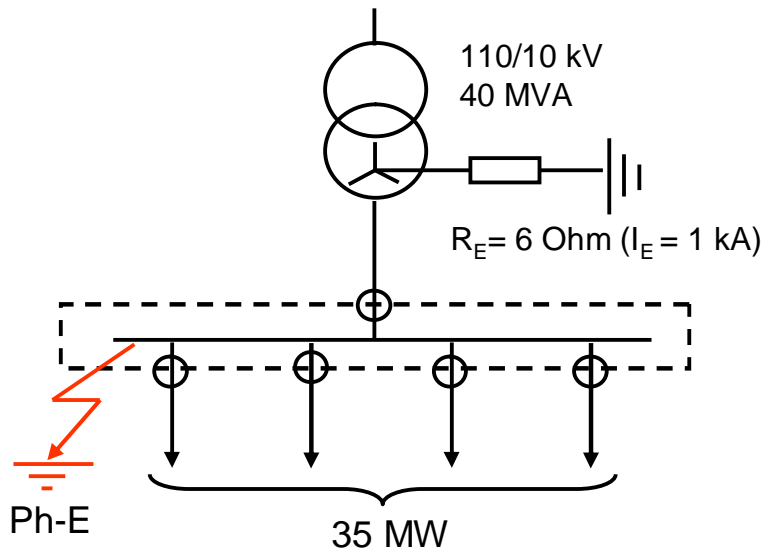
# Busbar protection, Composite current type (7SS600): Performance in networks with earth current limitation



$$I_L = \frac{35 \text{ MVA}}{10 \text{ kV} \cdot \sqrt{3}} = 2 \text{ kA}$$



$$I_F = I_E = 10 / \sqrt{3} \text{ kV} / 6 \Omega \approx 1 \text{ kA}$$

Worst case: Fault in phase L2

Restraint current:  $I_{Res} = 3 \cdot \sqrt{3} \text{ kA}$

Operating current:  $I_{Op} = 3 \cdot |I_{KE}| = 3 \text{ kA}$
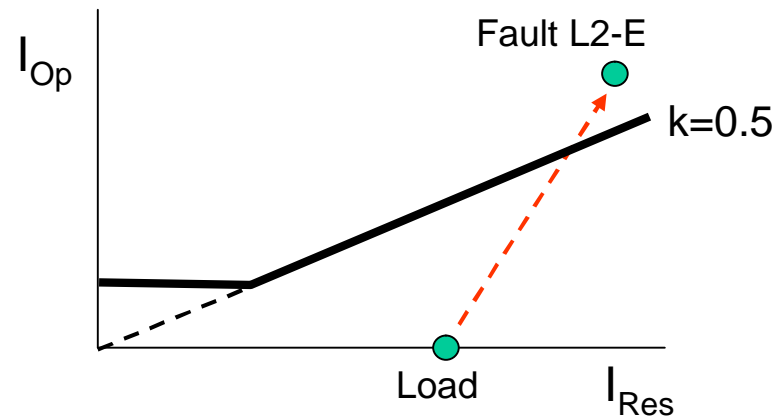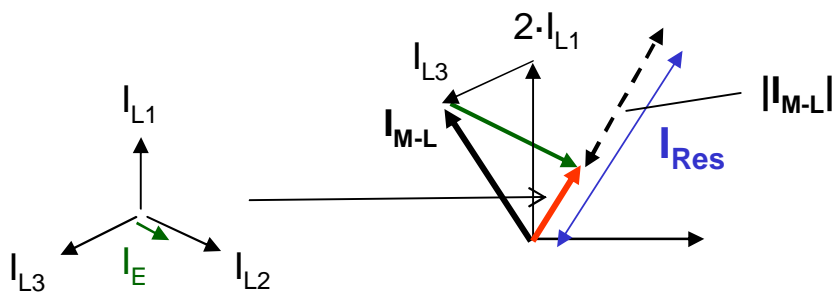
$$k = \frac{I_{Op}}{I_{Res}} = \frac{3}{3 \cdot \sqrt{3}} = 0,57$$



# Differential Protection 7UT6

## Remarkable Features





# The 7UT6 Family

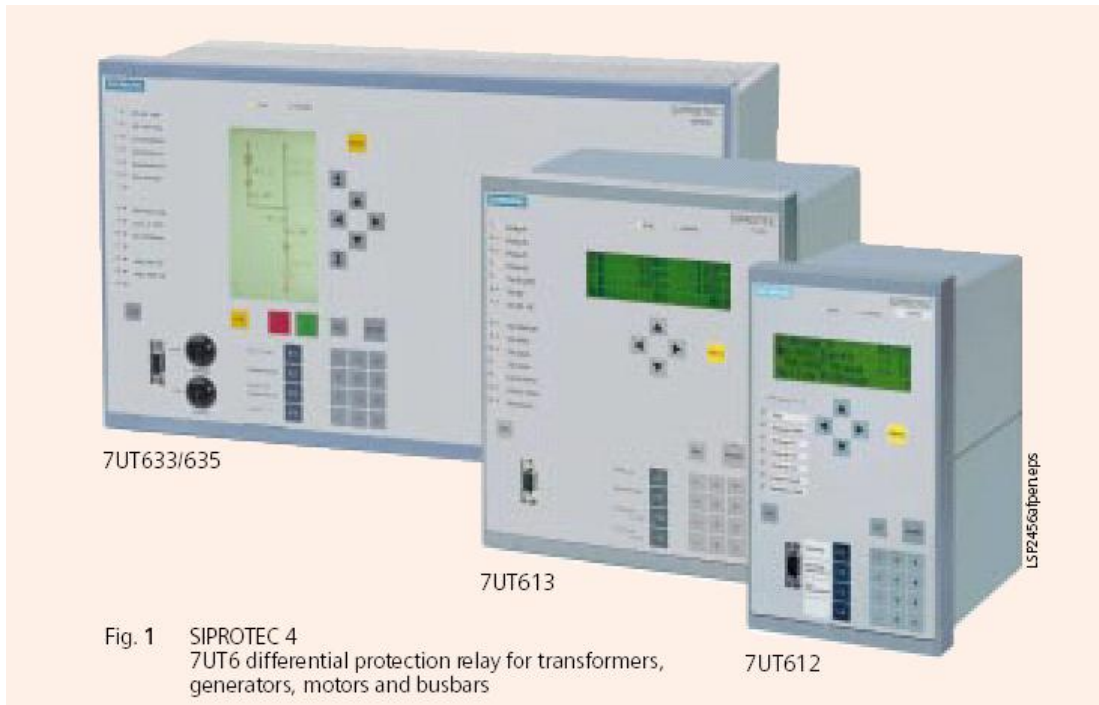


Fig. 1 SIPROTEC 4  
7UT6 differential protection relay for transformers,  
generators, motors and busbars

**7UT6** differential protection  
for

- Transformers
- Generators
- Motors
- Busbars

7UT612: for protection objects with **2 ends** (1/3 x 19" case 7XP20)

7UT613: for protection objects with **3 ends** (1/2 x 19" case 7XP20)

7UT633: for protection objects with **3 ends** (1/1 x 19" case 7XP20)

7UT635: for protection objects with **5 ends** (1/1 x 19" case 7XP20)

## 7UT6: Hardware options

■ Relay version	■ 7UT612	■ 7UT613	■ 7UT633	■ 7UT635
■ current inputs (normal)	■ 7 (7) <sup>1)</sup>	■ 11 (6) <sup>1)</sup>	■ 11 (6) <sup>1)</sup>	■ 14 (12) <sup>1)</sup>
(sensitive)	■ 1	■ 1 <sup>2)</sup>	■ 1 <sup>2)</sup>	■ 2 <sup>2)</sup>
■ voltage inputs (U <sub>ph</sub> / UE)	■ ---	■ 3 / 1	■ 3 / 1	■ ---
■ Binary inputs	■ 3	■ 5	■ 21	■ 29
■ Output contacts	■ 4	■ 8	■ 24	■ 24
■ Life contact	■ 1	■ 1	■ 1	■ 1
■ LC Display	■ 4 rows <sup>3)</sup>	■ 4 rows <sup>3)</sup>	■ Graphic	■ Graphic


1) 1A, 5A, (1A, 5A, 0.1A)

2) link selectable normal/sensitive


3) alpha-numeric

## 7UT6: Scope of functions


Function	ANSI No.	Function	ANSI No.
Differential	87T/G/M/L	Overfluxing V/Hz	24
Earth differential	87 N	Breaker failure	50BF
Phase overcurrent,	50/51	Temperature monitoring	38
Neutral overcurrent $I_N >, t$	50N/51N	Hand reset trip	86
Ground overcurrent ( $I_E, t$ )	50G/51G	Trip circuit supervision	74TC
Unbalanced current $I_2 >, t$	46	Binary inputs for tripping commands	
Thermal overload IEC 60255-8	49		
Therm. OL IEC 60354 (hot spot)	49		

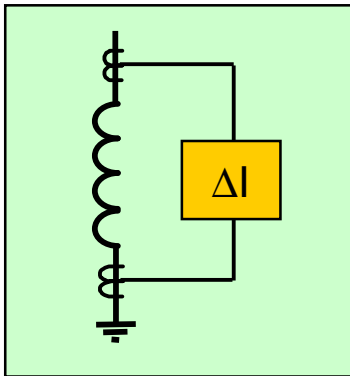


*Shunt Reactor*

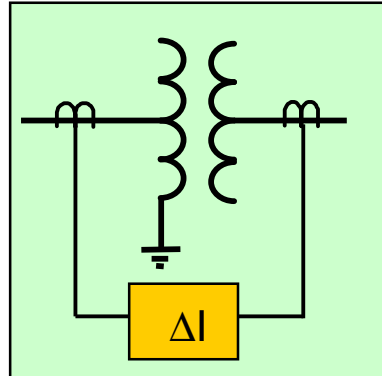


*Two winding transformer*

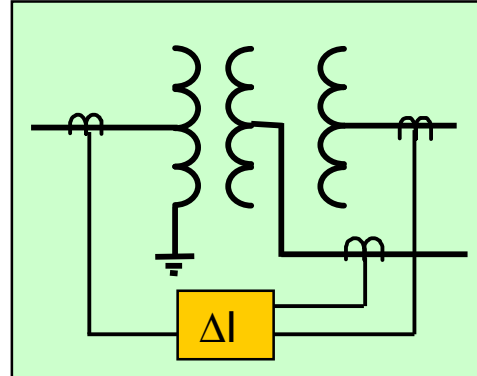


*Three winding transformer*

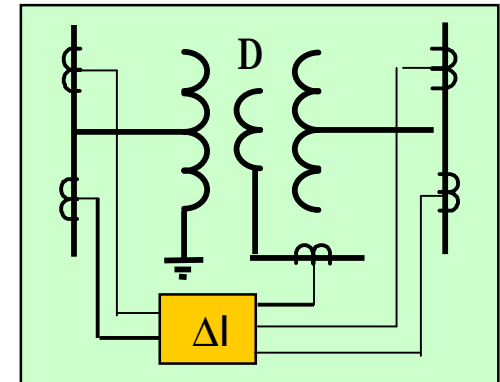

*Transformer bank (1-1/2-LS)*

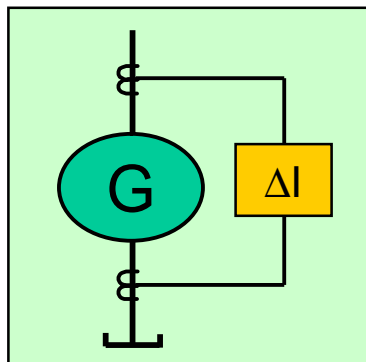


*Generator / Motor*

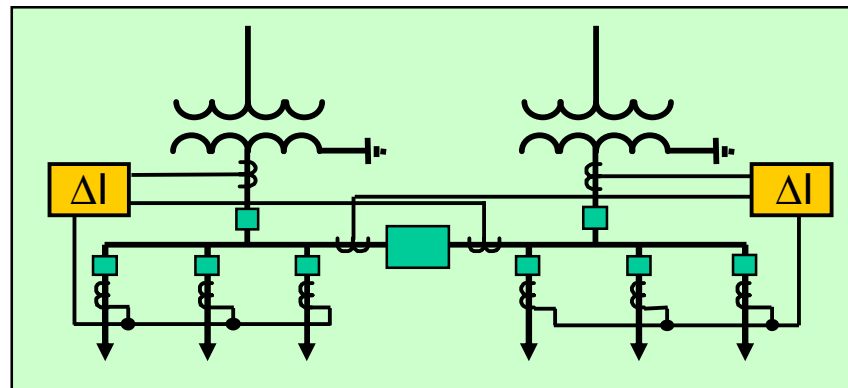


*Busbars*

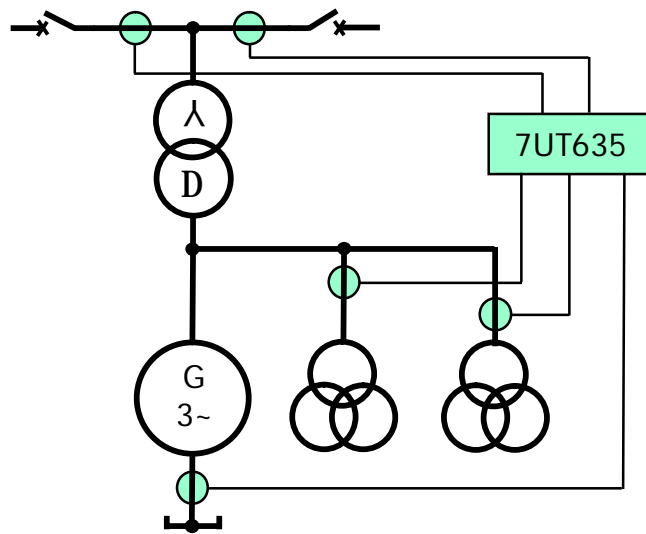Generation Unit protection  
(overall differential)




HI restricted earth fault protection

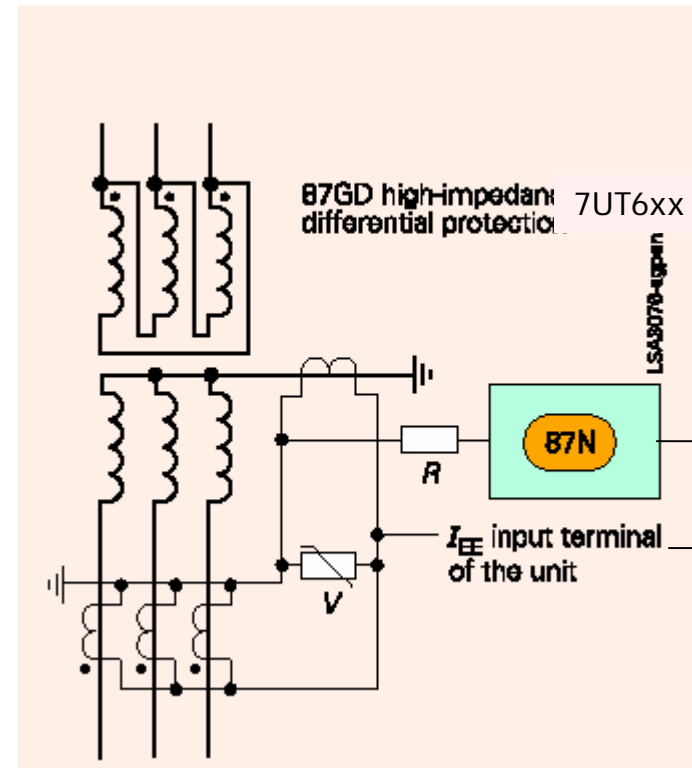


7UT6:

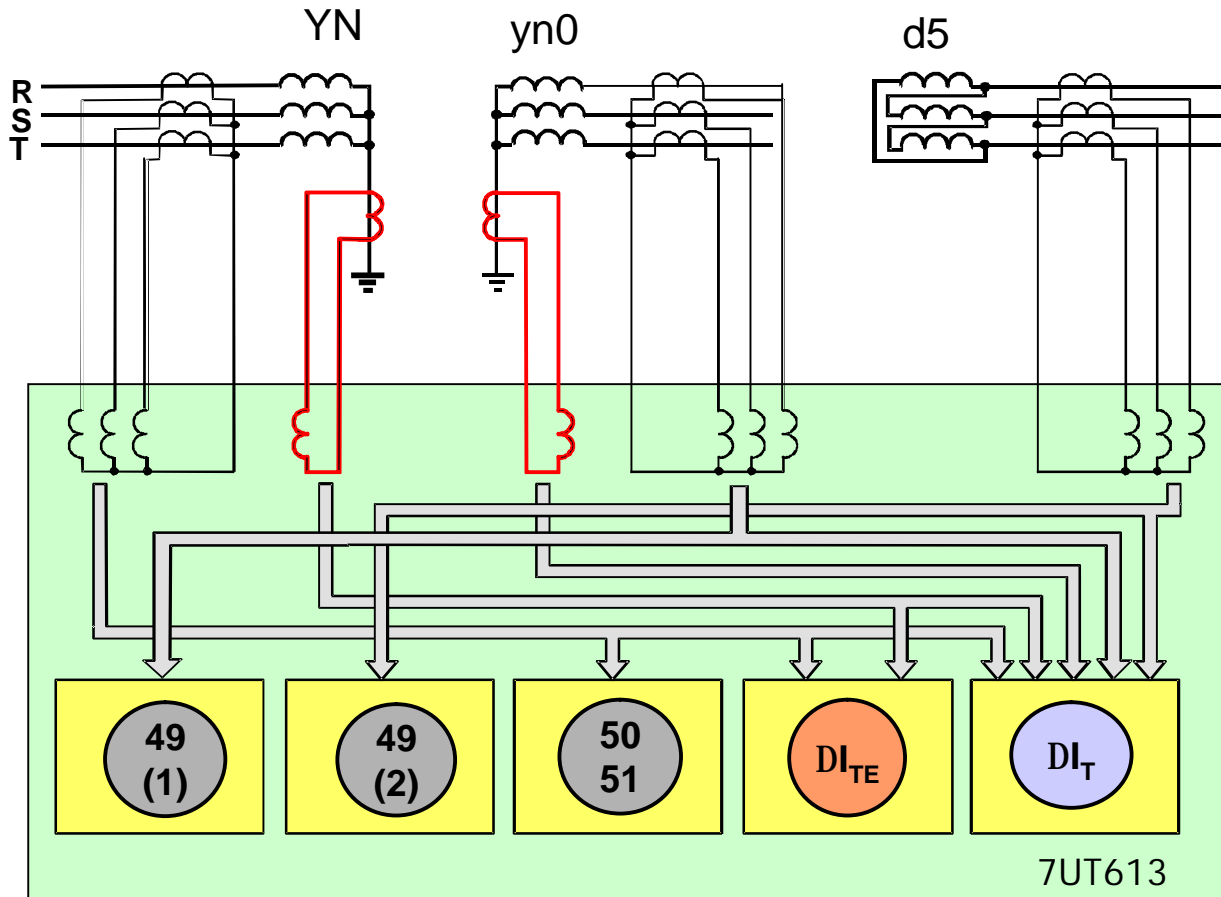selectable:  $I_0$ -correction or restricted earth fault protection




# 7UT6: operating characteristic

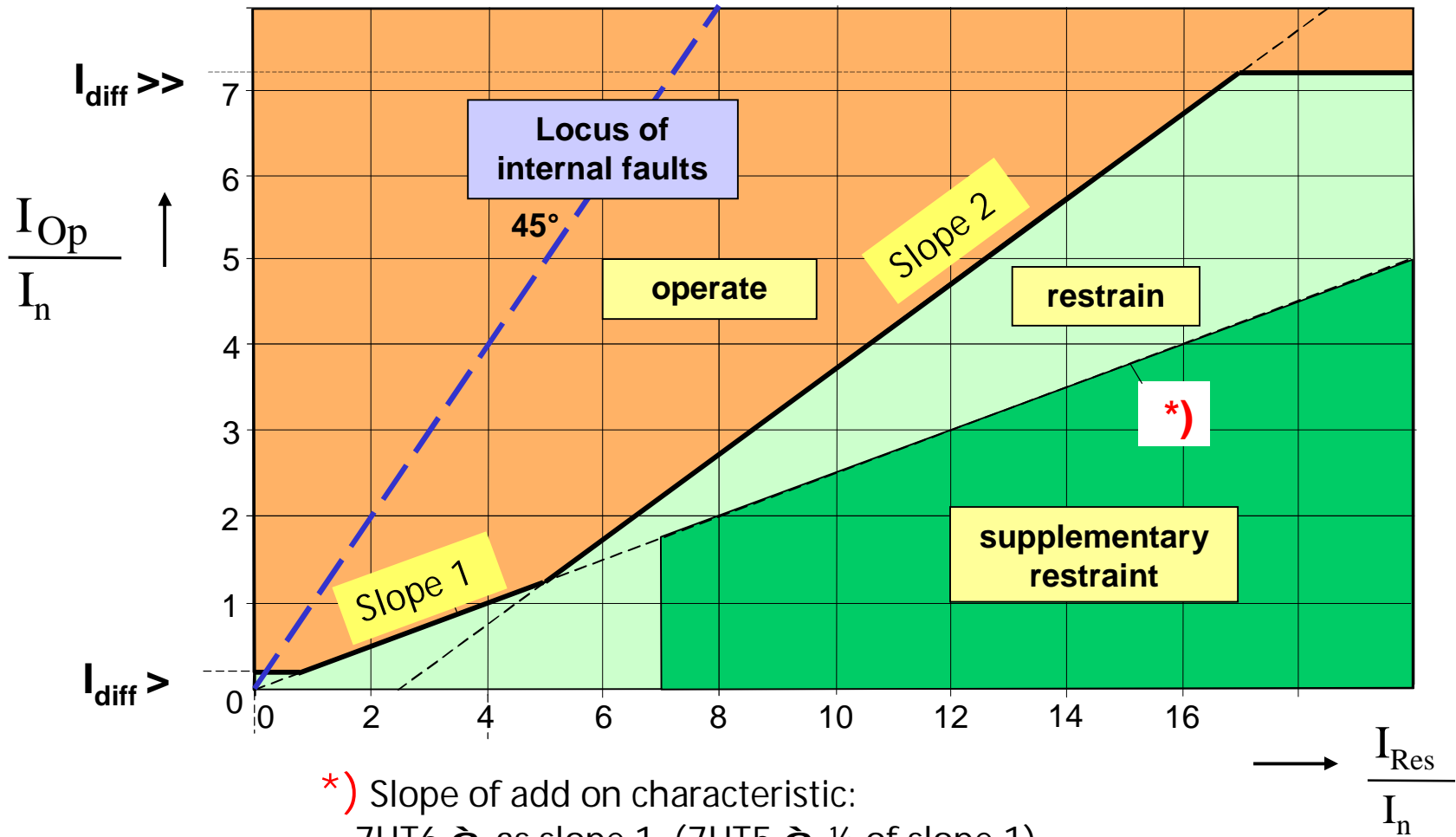


\* ) Slope of add on characteristic:  
 7UT6 à as slope 1 (7UT5 à ½ of slope 1)
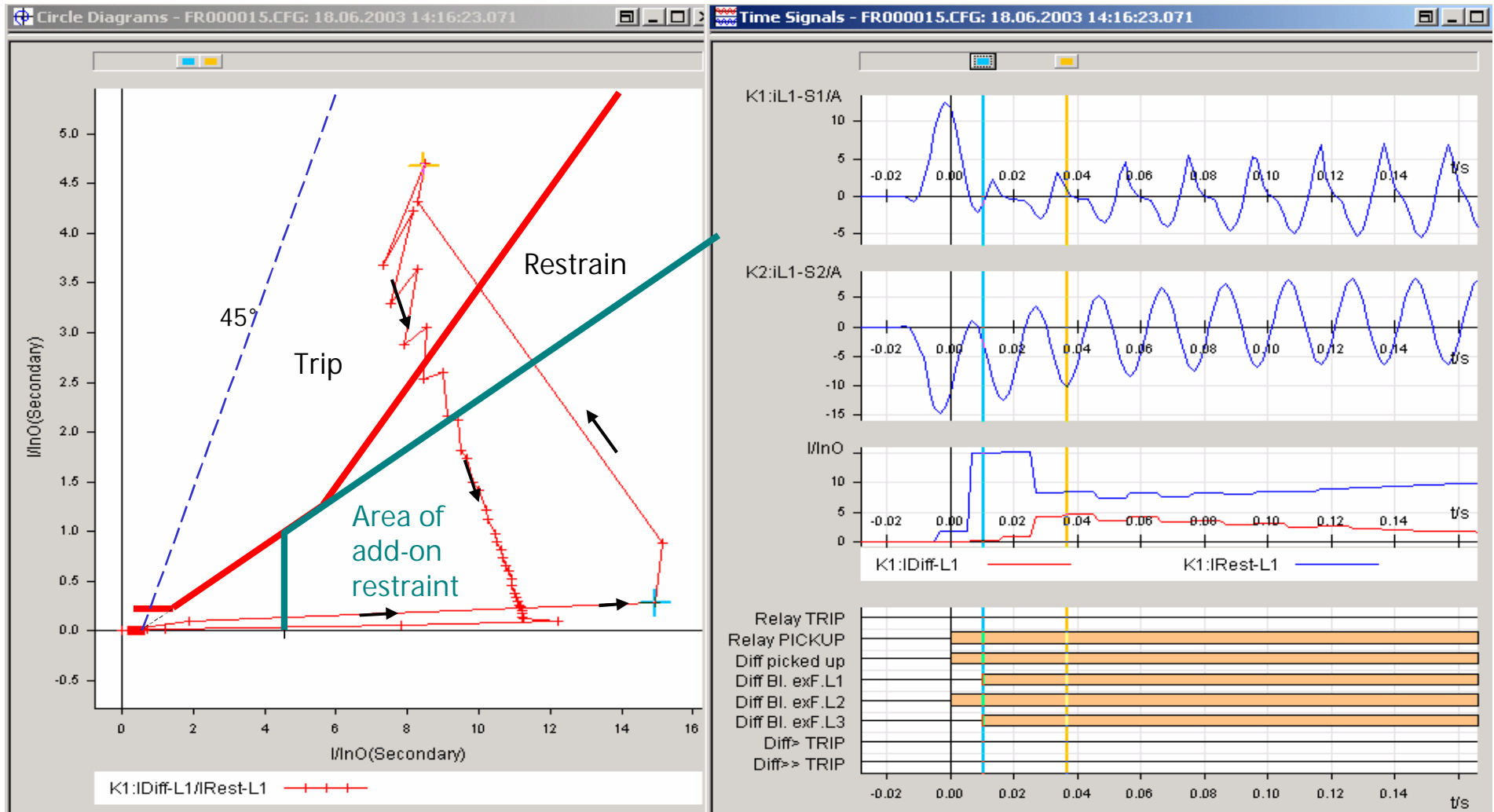
# 7UT6: Effect of supplementary restraint in case of CT saturation





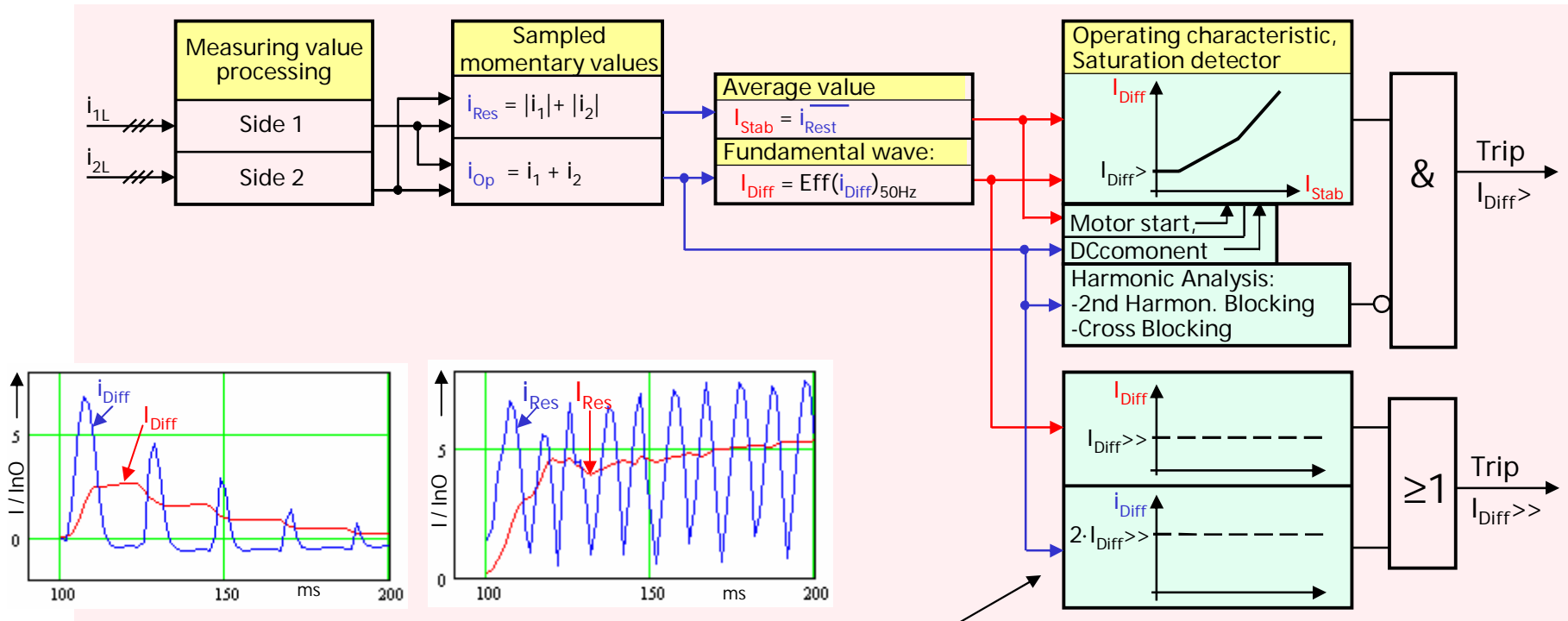
# Differential protection functions $I_{Diff}>$ and $I_{Diff}>>$



Fast tripping using sampled momentary values ensures dependable operation in case of extreme CT saturation!


## 7SA6: Temperature monitoring

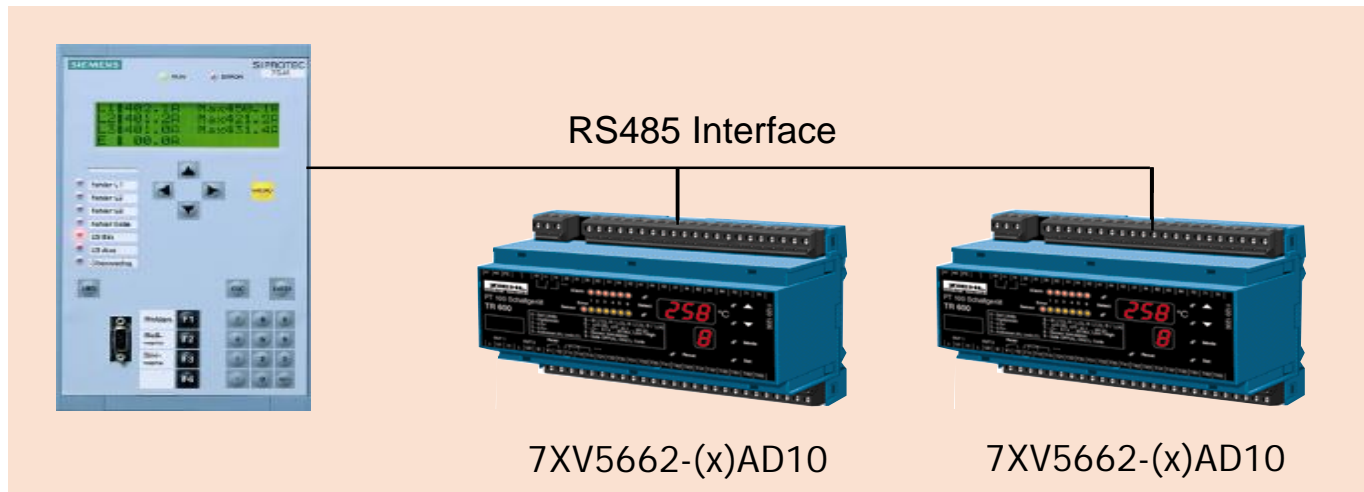

- Two thermo-devices can be connected to the serial service interface (RS485)
- Monitoring of up to 12 measuring points (6 per thermo-device)
  - each with two pick-up levels
- Display of the measured temperatures
  - directly at the thermo-device (which can also be used stand alone)
  - at the relay
- One input is reserved for hot spot monitoring (measurement of oil temperature)
- Thermistors: Pt100, Ni100 or Ni120

# 7UT6: Temperature monitoring with hot spot calculation (1)

## Example: Natural cooling

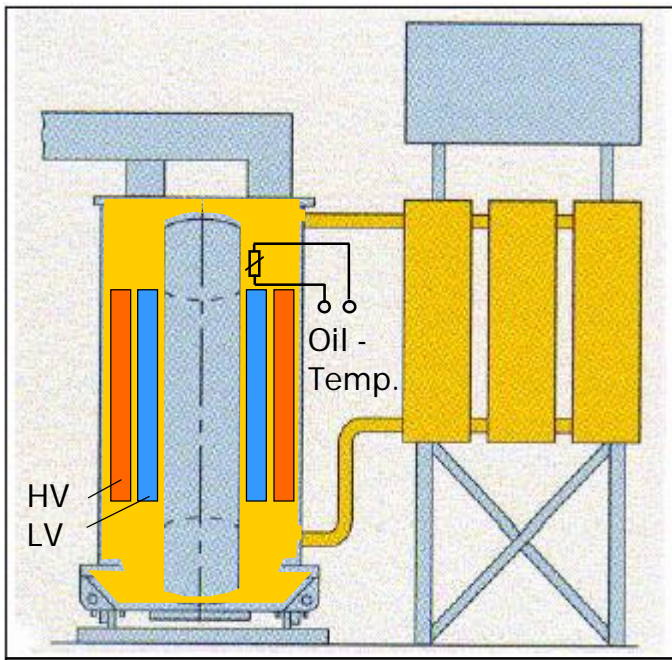

$$\Theta_h = \Theta_o + H_{gr} \cdot k^Y$$

$\Theta_h$ = hot spot temperature

$\Theta_o$ = oil temperature

$H_{gr}$ =hot-spot-to-oil temperature gradient

$k$ = load factor  $I/I_n$

$Y$ = winding exponent

Aging rate:

$$V = \frac{\text{Aging at } \Theta_h}{\text{Aging at } 98^\circ\text{C}} = 2^{(\Theta_h - 98)/6}$$

98° is reference for the aging of Cellulose insulation

Mean value of aging during a fixed time interval:

$$L = \frac{1}{T_2 - T_1} \cdot \int_{T_1}^{T_2} V \cdot dt$$

# 7UT6: Temperature monitoring with hot spot calculation (1)


## Example: Natural cooling

Number	Measured value	Value
01060	Hot spot temperature of leg 1	102 °C
01061	Hot spot temperature of leg 2	102 °C
01062	Hot spot temperature of leg 3	102 °C
01063	Aging Rate (L)	1.6
01066	Load Reserve to warning level	-10 %
01067	Load Reserve to alarm level	5 %


Number	Measured value	Value
01068	Temperature of RTD 1	73 °C

$$\Theta_h = \Theta_o + H_{gr} \cdot k^Y \approx 73 + 23 \cdot 1.15^{1.6} = 102^\circ\text{C}$$
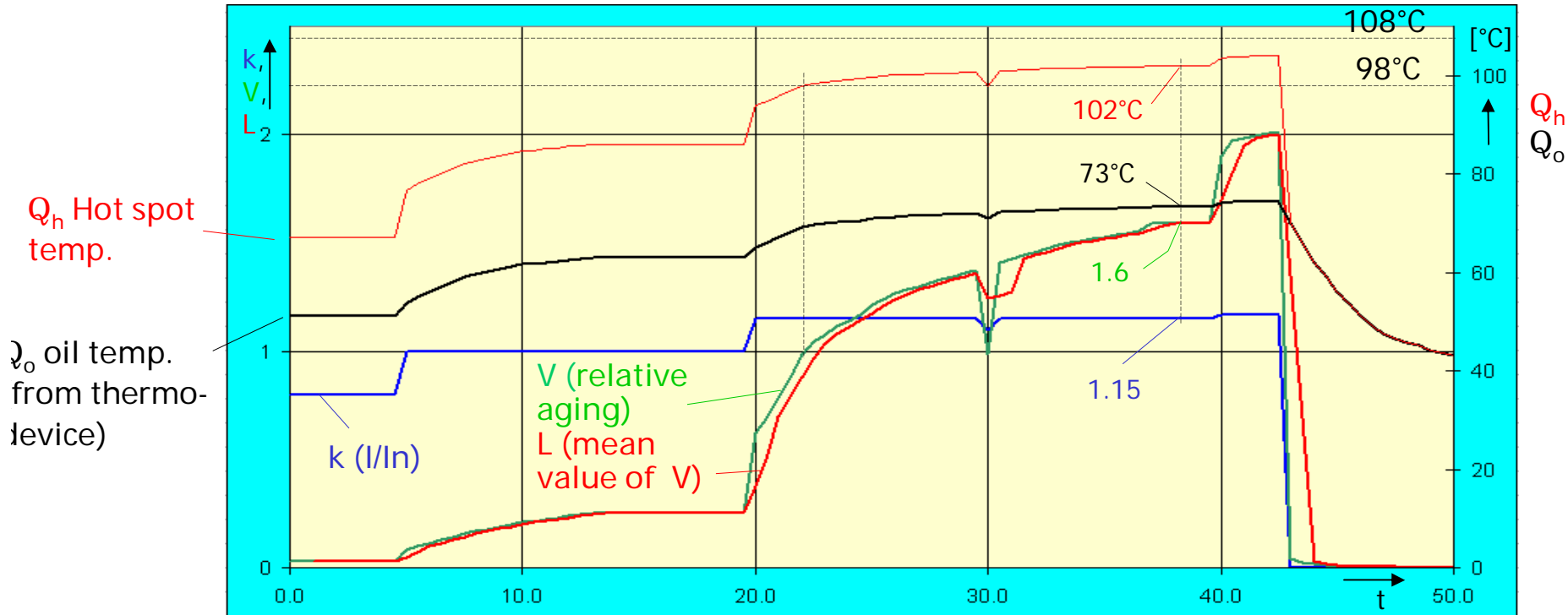
$$V = 2^{(\Theta_h - 98)/6} = 2^{(102 - 98)/6} \approx 1.6$$




## WEB-Technology

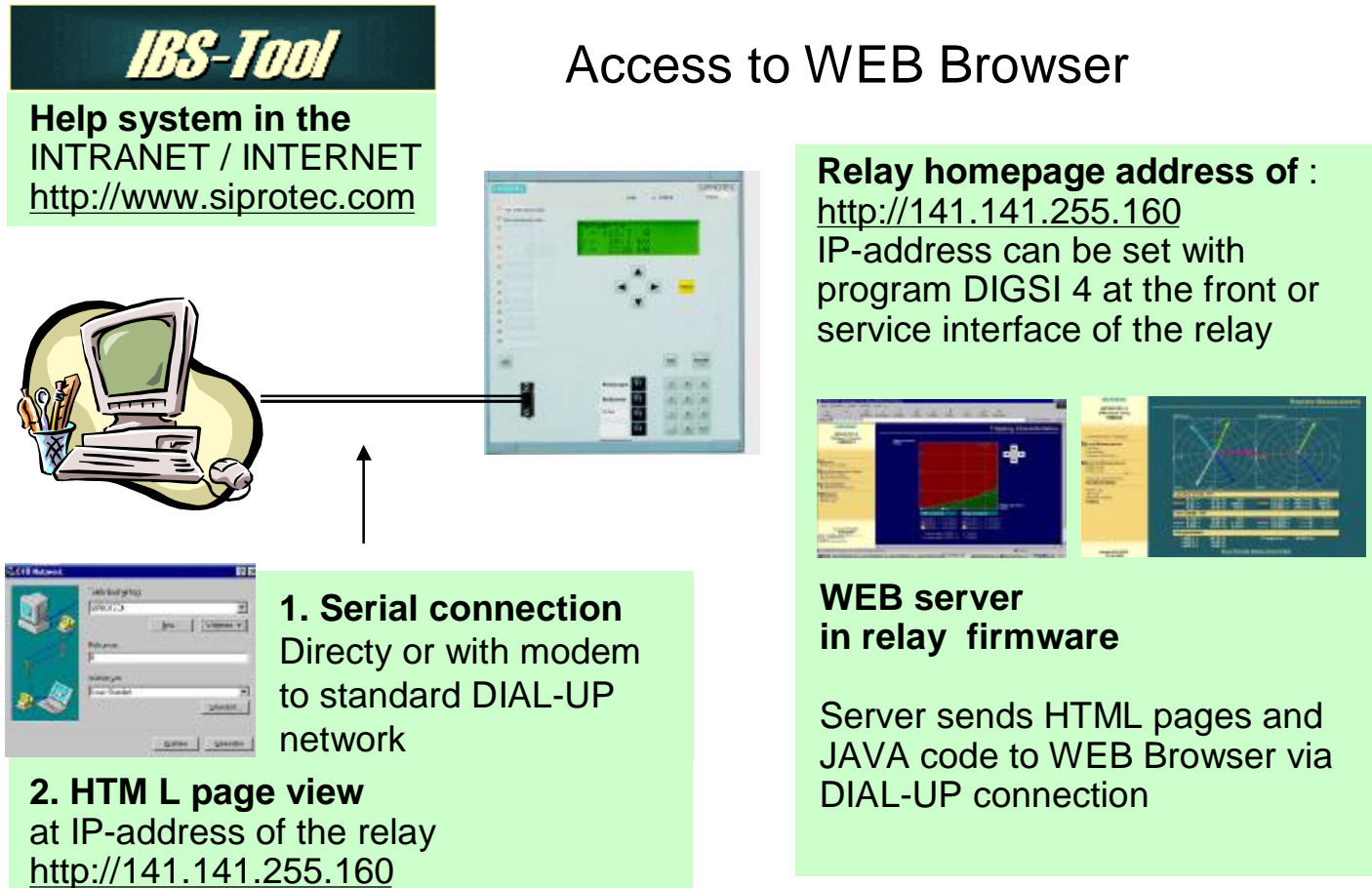
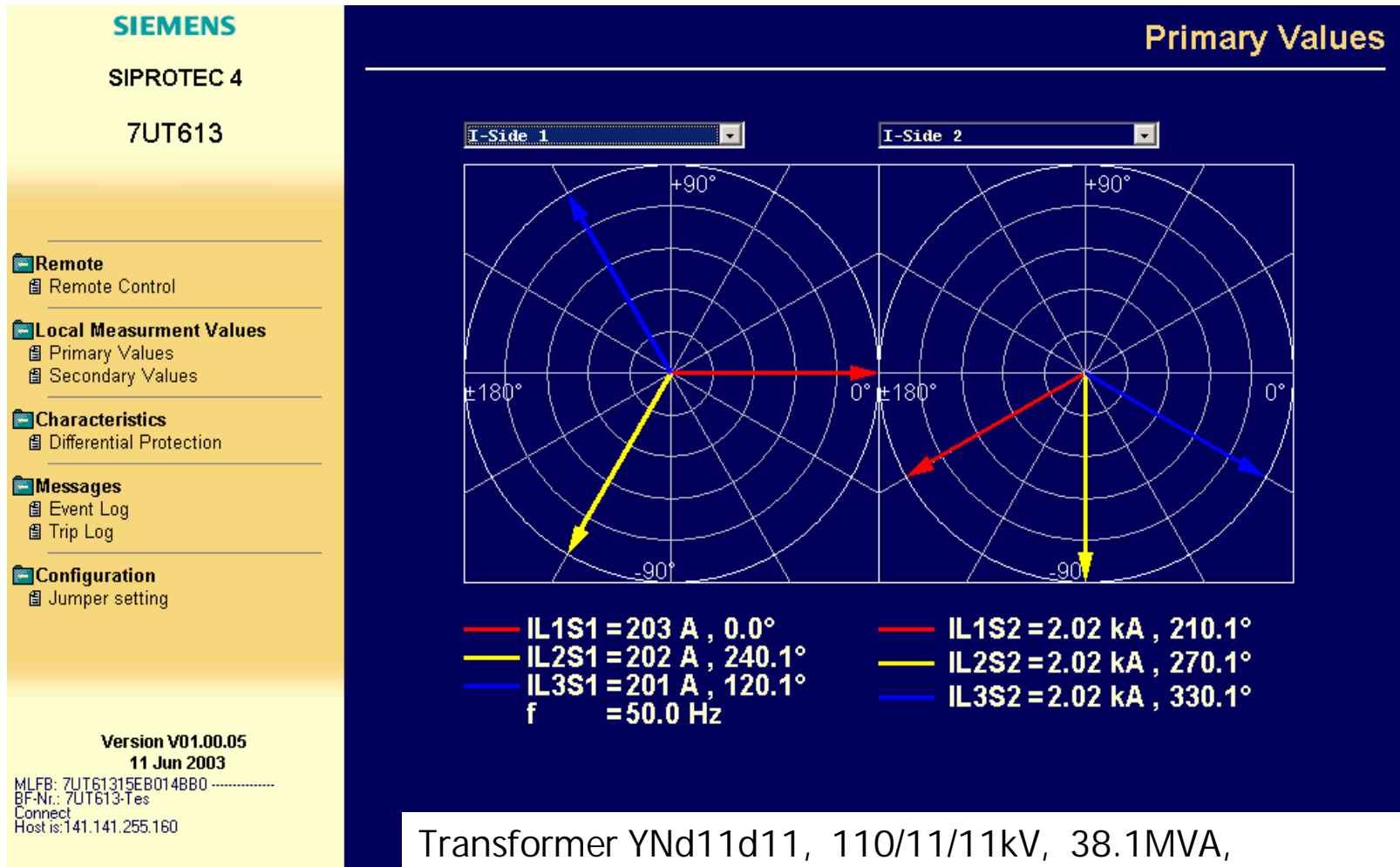
# 7UT6: Commissioning and service tool (2)


Current phasors of all terminals can be displayed



Transformer YNd11d11, 110/11/11kV, 38.1MVA,  
 IL2S2 → wrong polarity

# 7UT6: Commissioning and service tool (3)
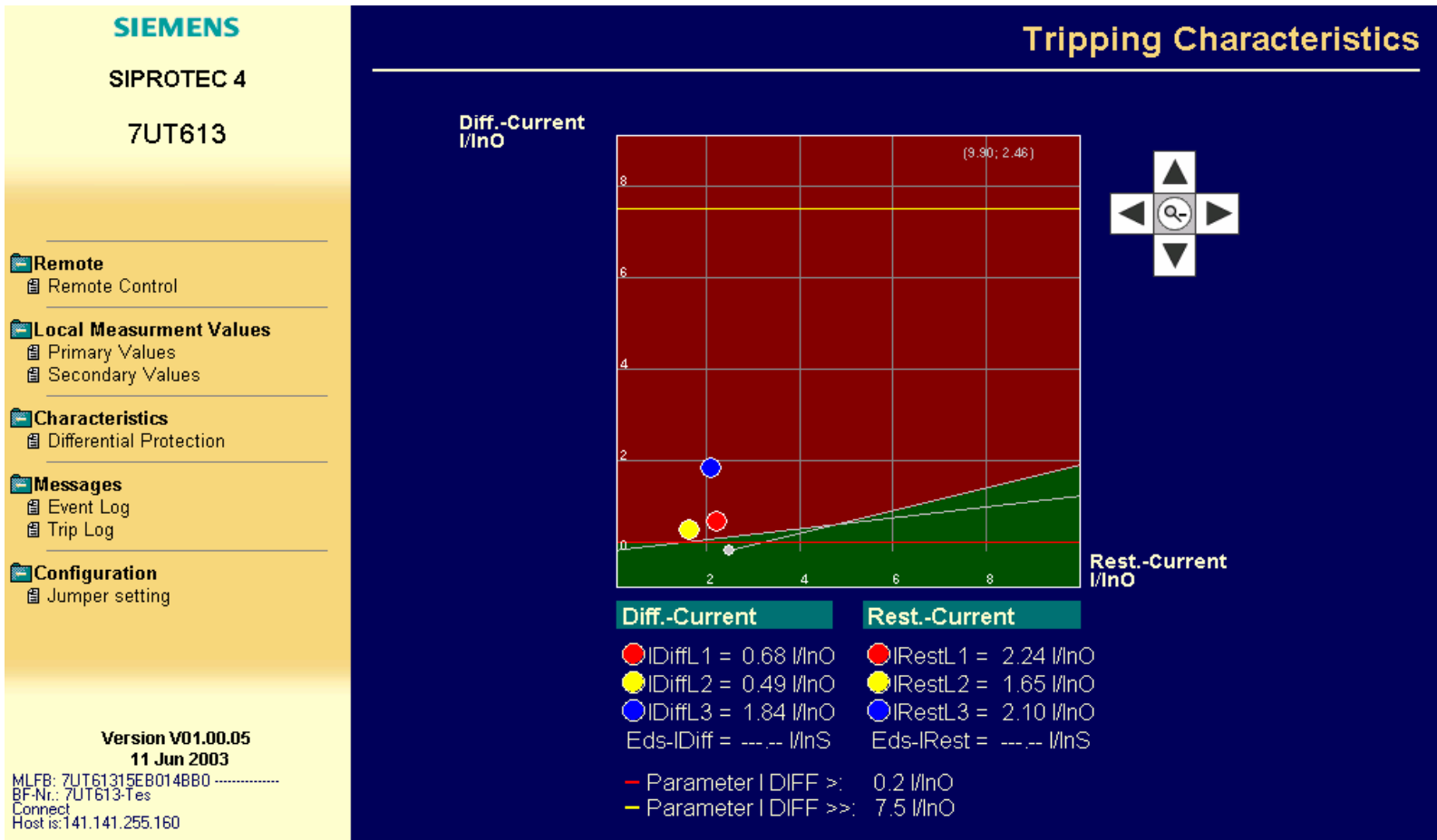
## Operating/restraint position can be displayed



Transformer YNd11d11, 110/11/11kV, 38.1MVA, IL2S2à wrong Polarität





Power Transmission and Distribution

# Differential Protection (7UT)


## Determination of the Transformer Vector Group

**SIEMENS**







## Transformer with Vector Group Yy0

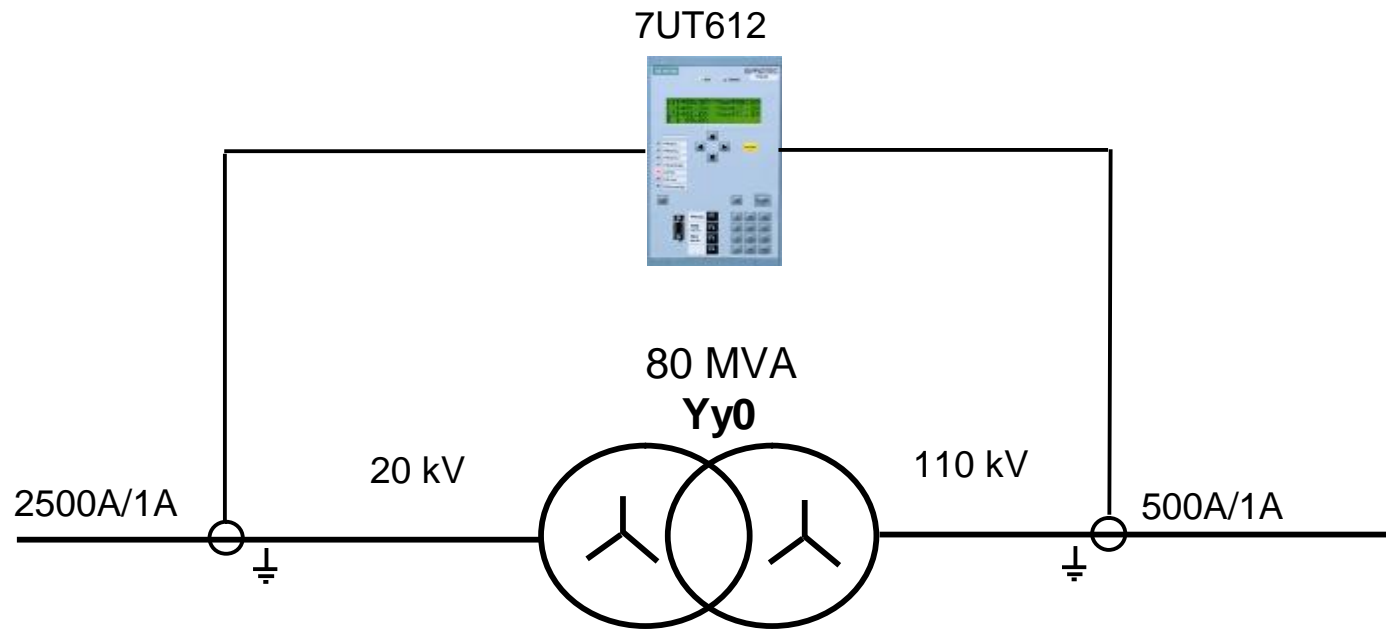



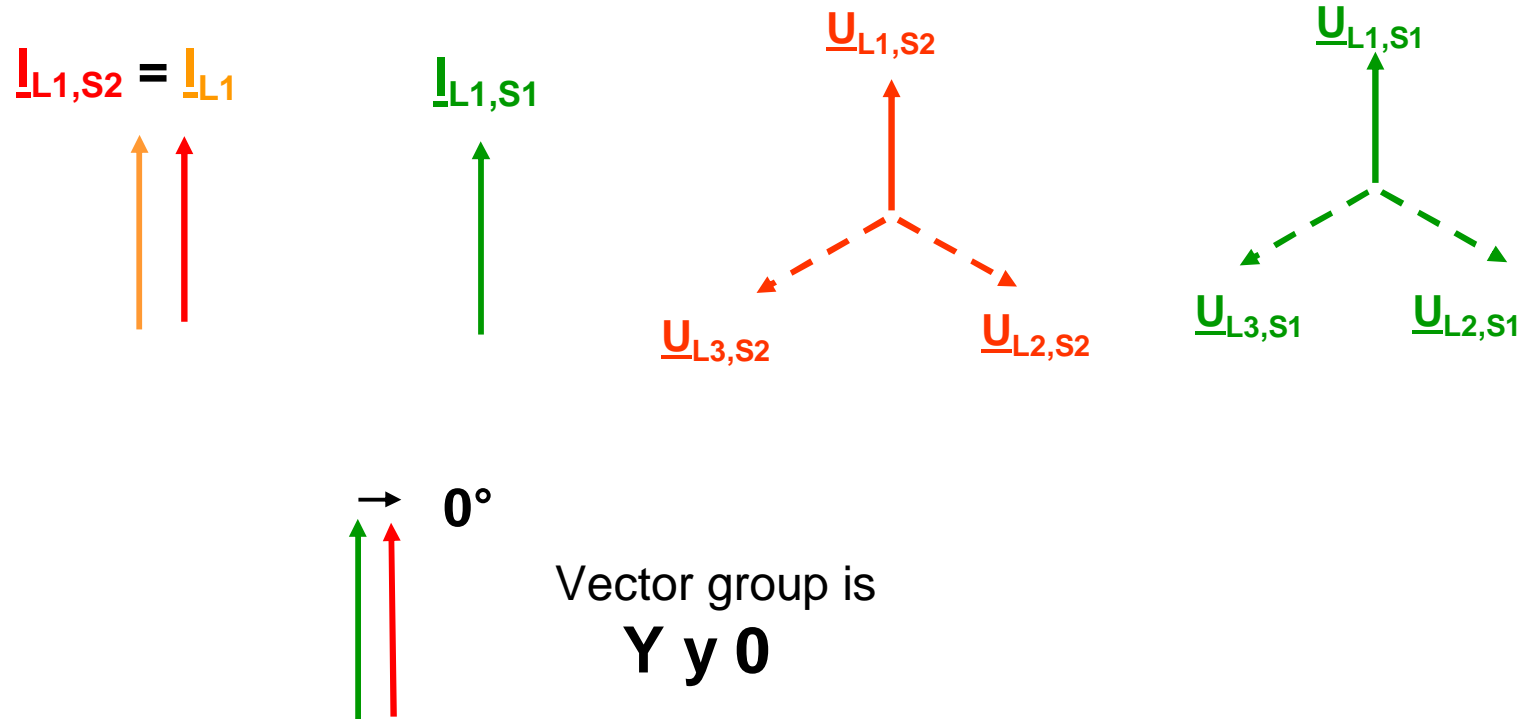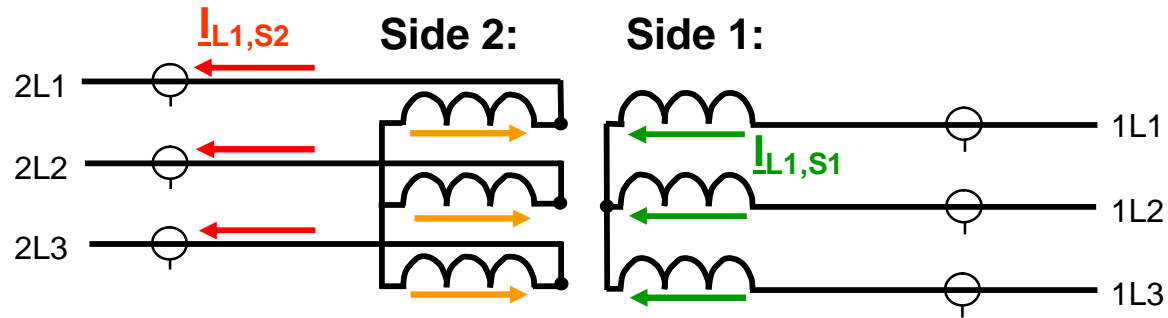
## Method of Vector Group Determination (Example Yy0)






# Transformer Protection

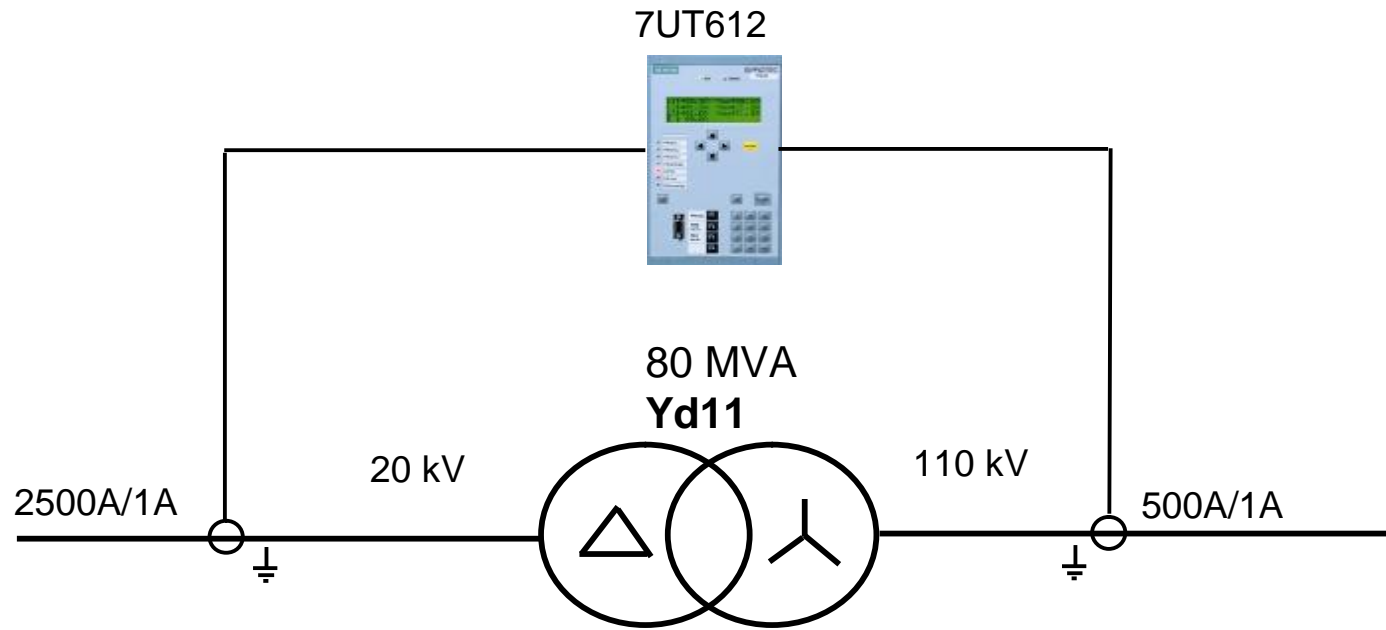



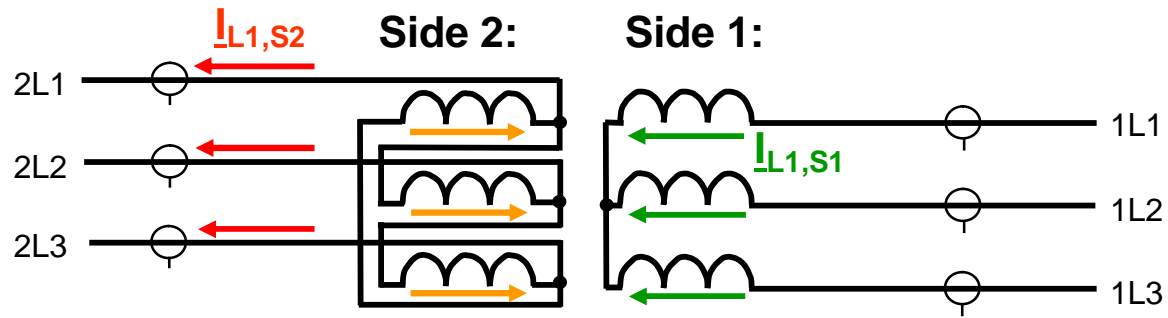
# Method of Vector Group Determination (Example Yd11)



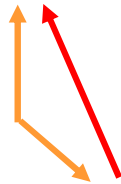
$$\underline{I}_{L1,S2} = \underline{I}_{L1} - \underline{I}_{L2}$$




$$\underline{I}_{L1,S1}$$




$$\underline{U}_{L1,S2}$$

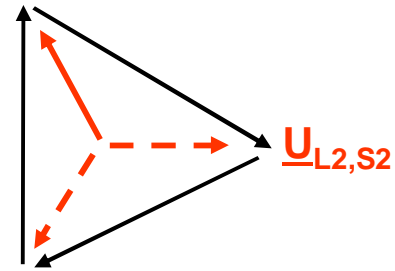

$$\underline{U}_{L3,S2}$$

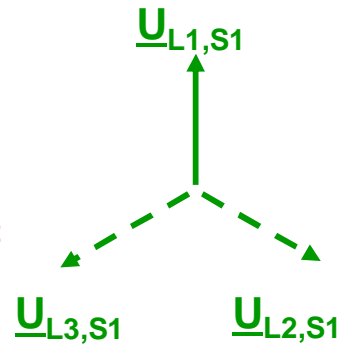

Vector group is  
**Y d 11**

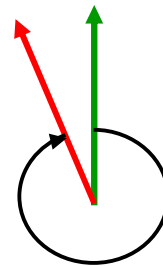

**330°**  
(n \* 30°)



## Definitions in SIPROTEC 4 Relays

Vector definition to a node is positive


The shown vectors or phase angles are transformed in this positive definition

The phase angle is displayed mathematics positive.


The reference phase is always phase L1 on side 1

### How to see the vector group Yd11?

Original

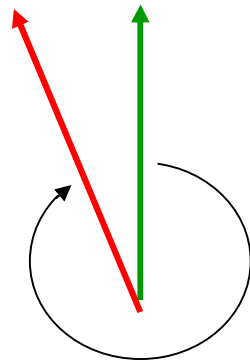

Siprotec 4 (Browser)

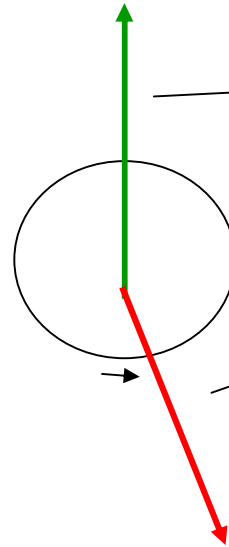

Phase angles

Side 1: 0°  
(reference phase)

Side 2: 210°


Please subtract 180°,  
than you get 30°  
(360° - 30° = **330°**)




# Web Tool (Browser) Vector group YNd11

## Secondary Values

Currents: Side 1

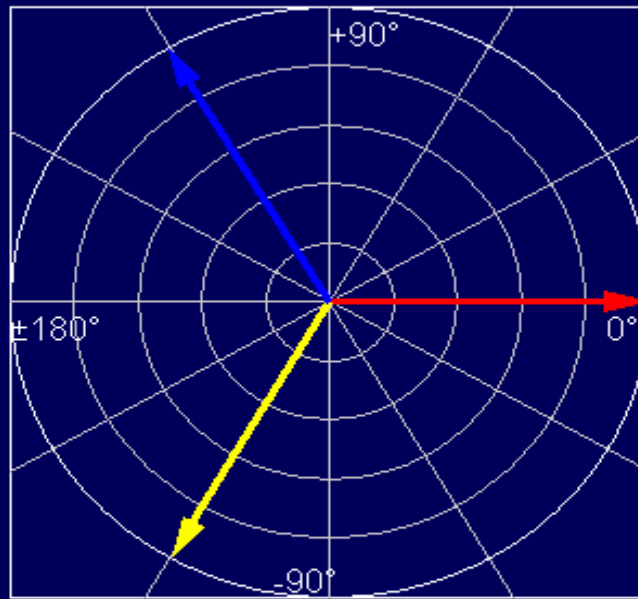

Currents: Side 2

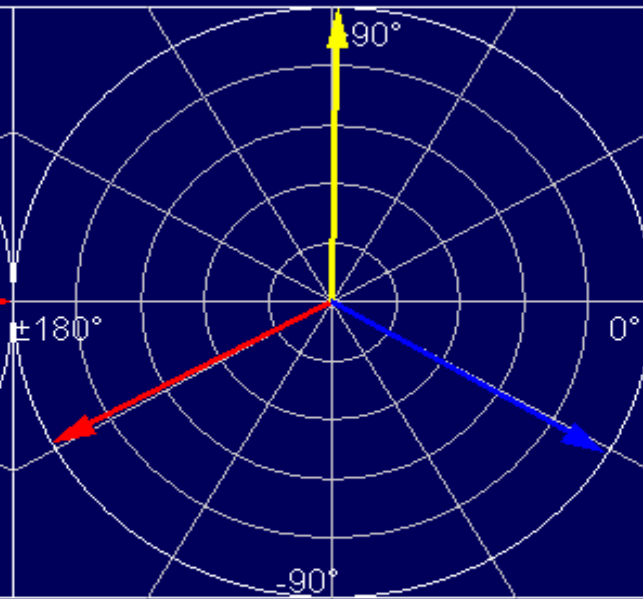



IL1S1 = 1.00 A, 0°  
IL2S1 = 1.00 A, 240°  
IL3S1 = 1.00 A, 120°  
I7 = 0.00 A, ---  
f = 50.00 Hz

IL1S2 = 1.00 A, 209°  
IL2S2 = 1.00 A, 89°  
IL3S2 = 1.00 A, 329°  
I8 = 0 mA

# Vector Group Determination via Fault Record

IL1;Side 2 lags 150° or leads 210°

Star point is towards the protected object

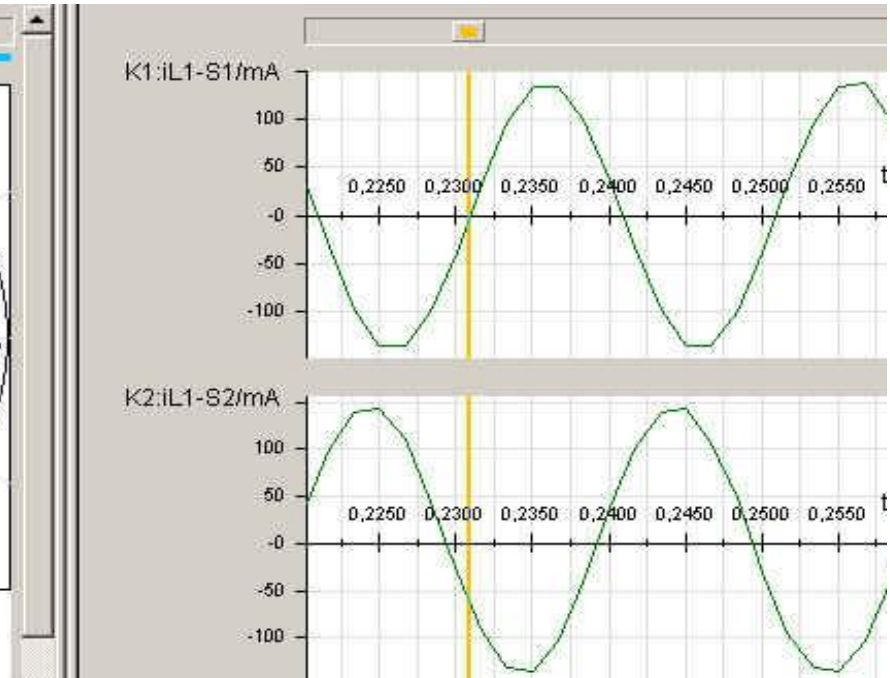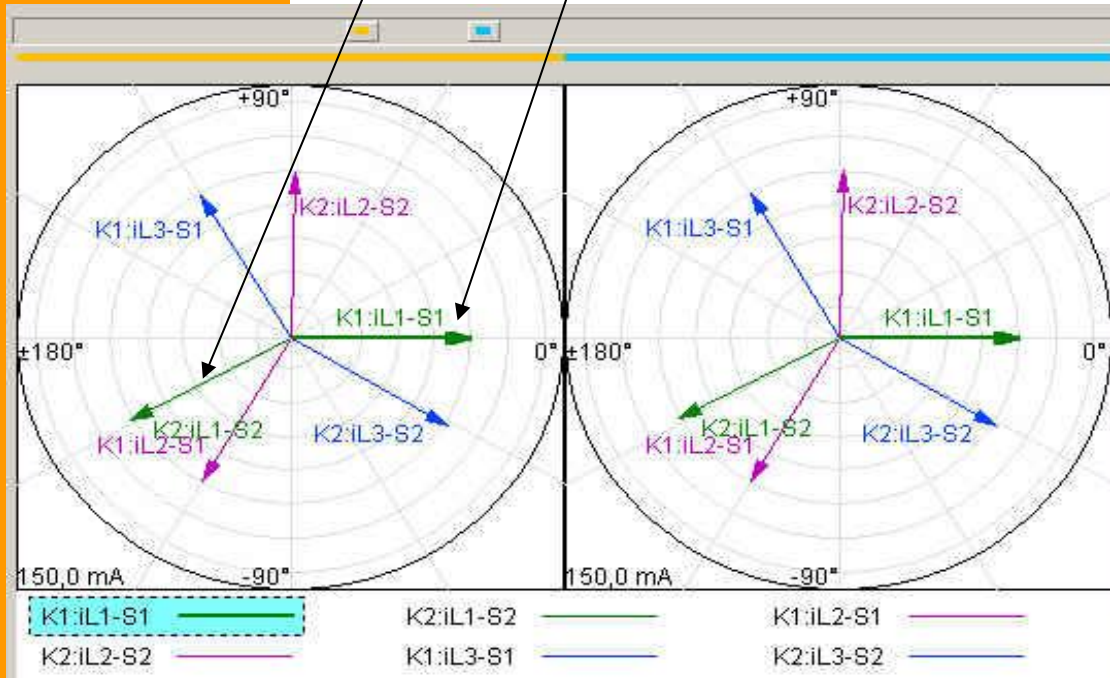

Way 1:  
IL1 Side:  $150^\circ + 180^\circ = 330^\circ$

Way 2:  
IL1 Side:  $210^\circ - 180^\circ = 30^\circ$   
leads  $30^\circ$  or lags  $330^\circ$

Phase shift is according the vector group definition  $330^\circ \rightarrow 11 * 30^\circ$



# Digital Transformer Differential Protection


**I0-correction  
+ vector group adaptation**

**SIEMENS**




# Transformer differential protection with I0-correction

## External fault

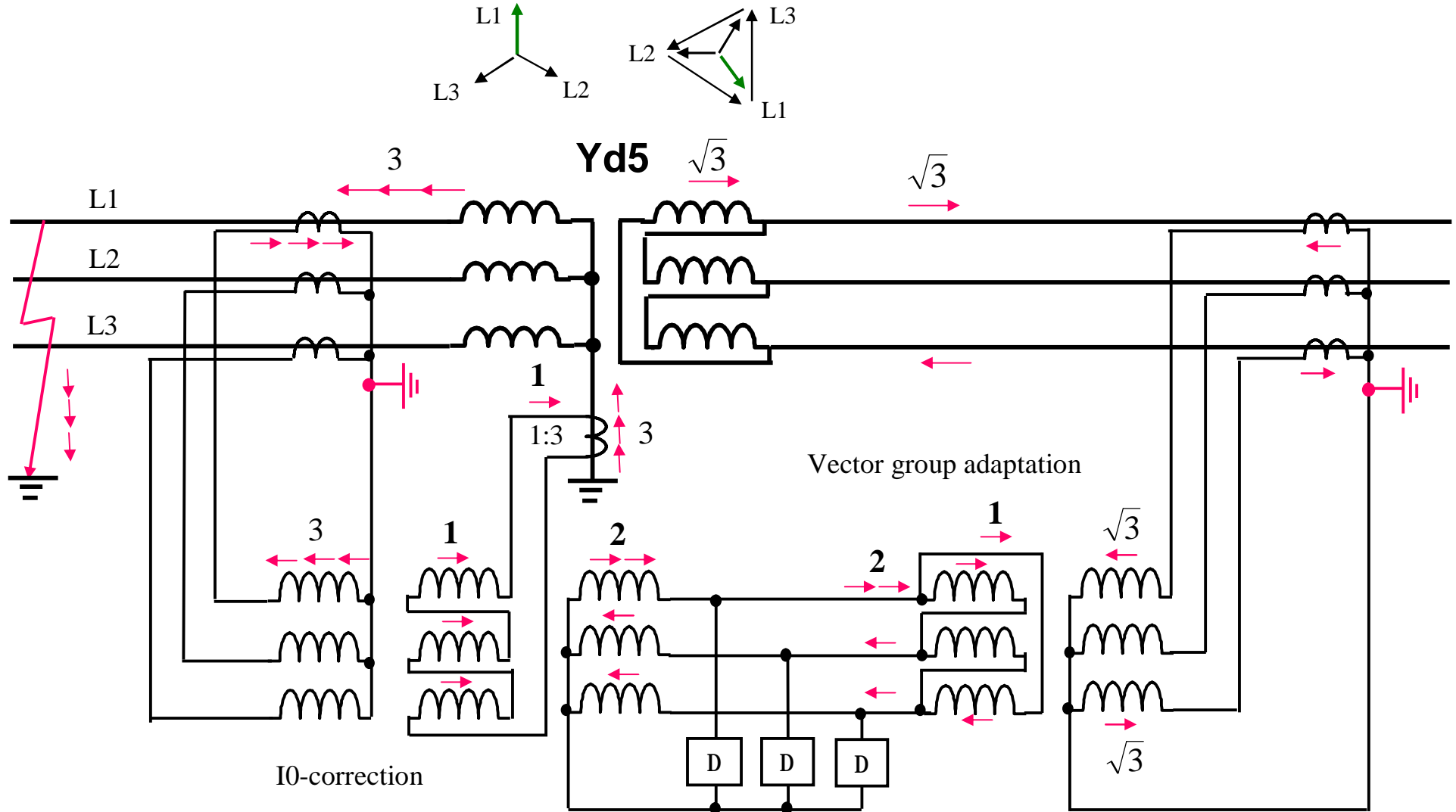

# Transformer differential protection with I0-correction

## Internal fault

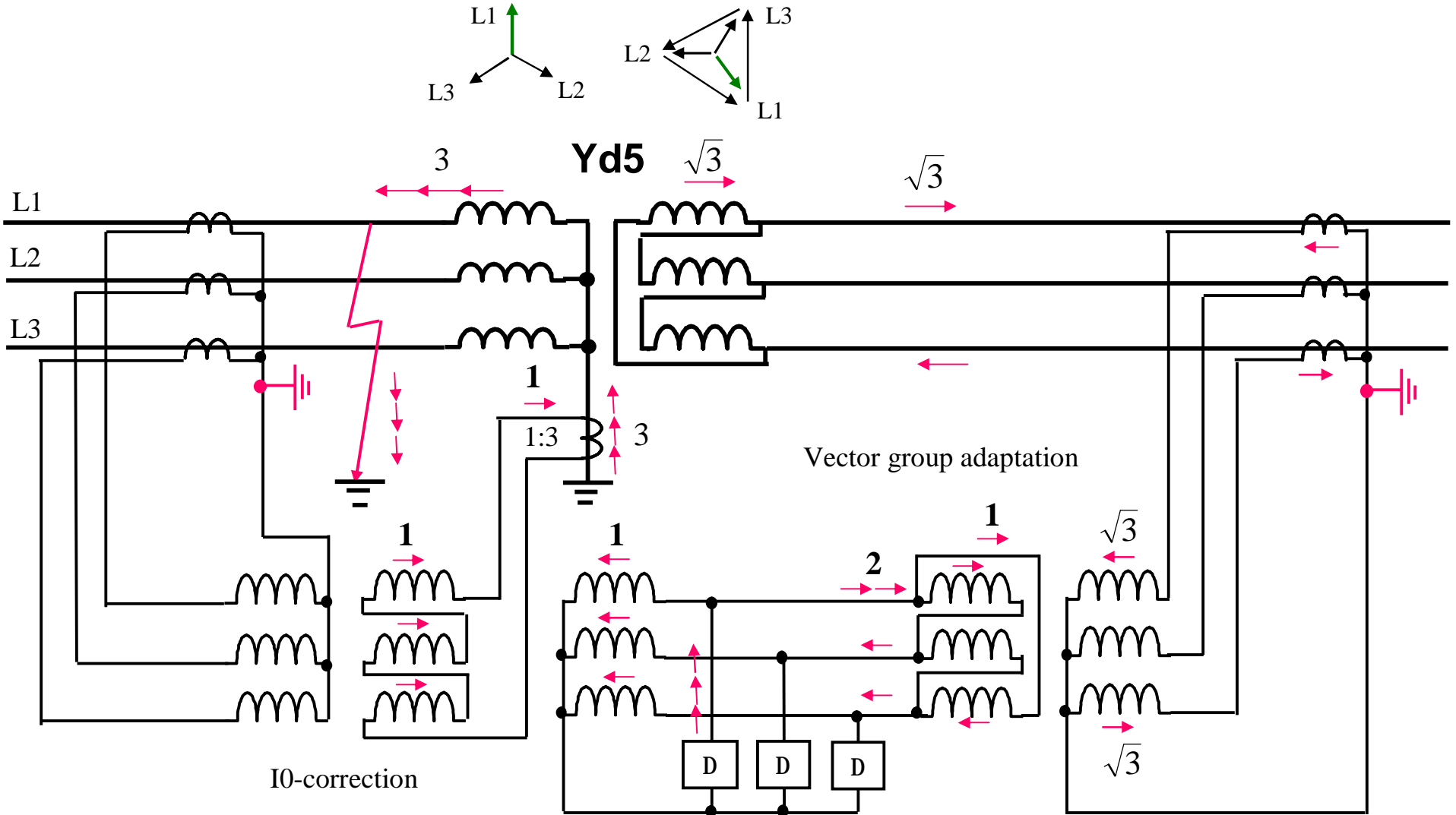



Power Transmission and Distribution


# Differential Protection (7UT)

## Determination of the Transformer Vector Group

**SIEMENS**






## Transformer with Vector Group Yy0

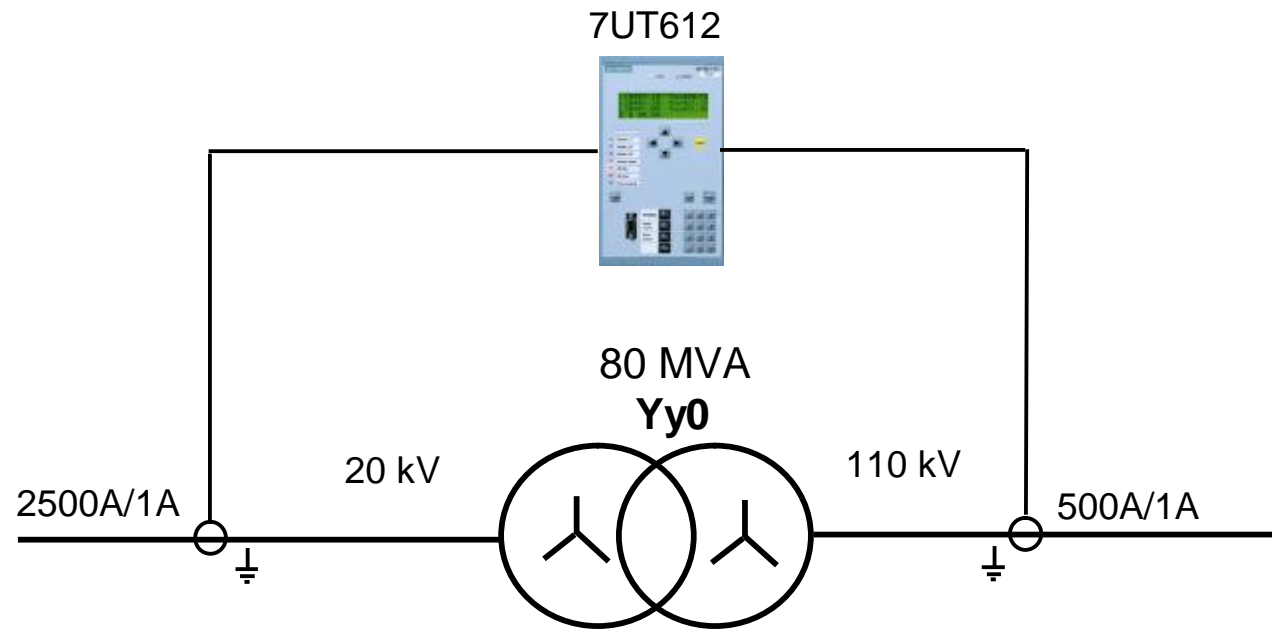



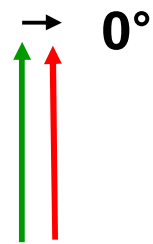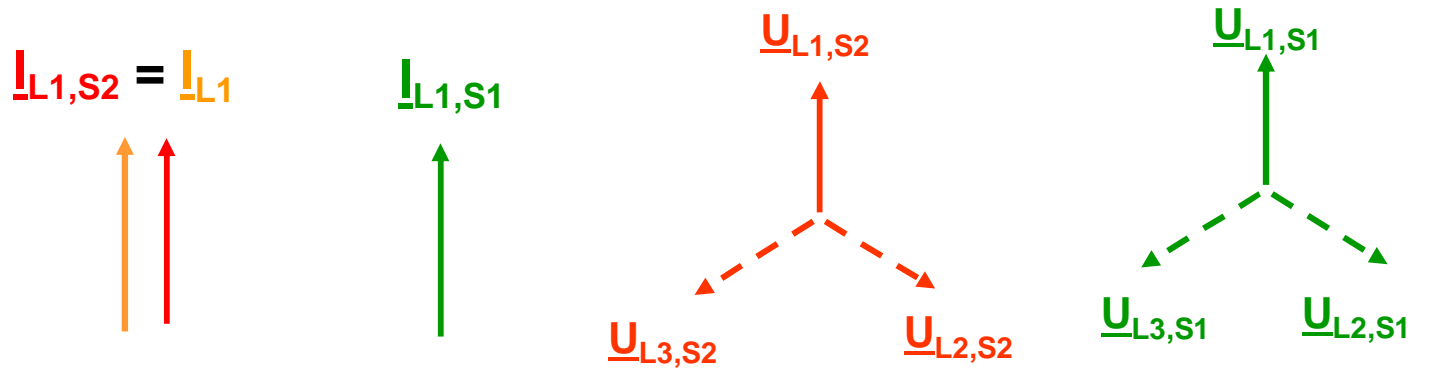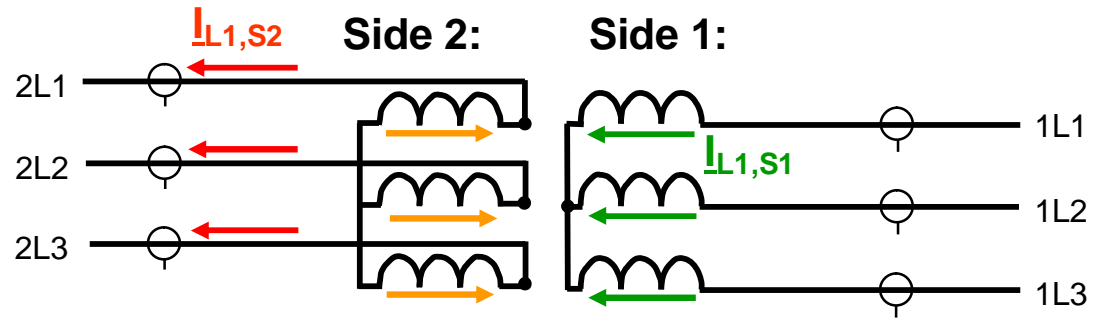
# Method of Vector Group Determination (Example Yy0)



Vector group is  
**Y y 0**




# Transformer Protection

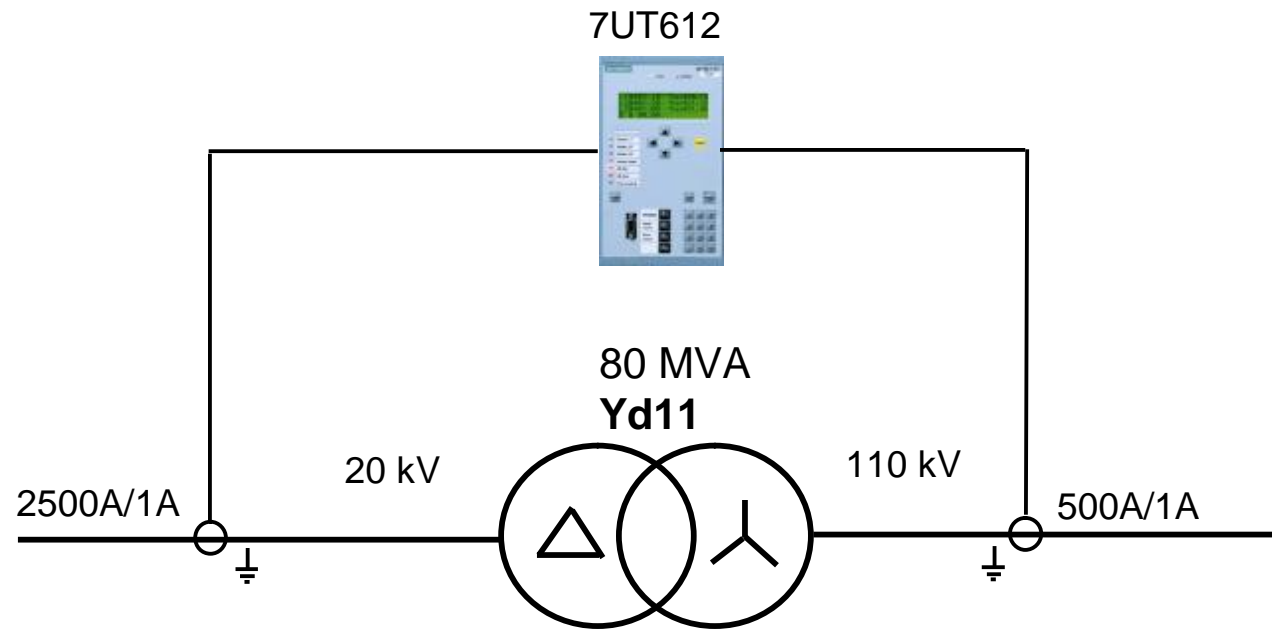


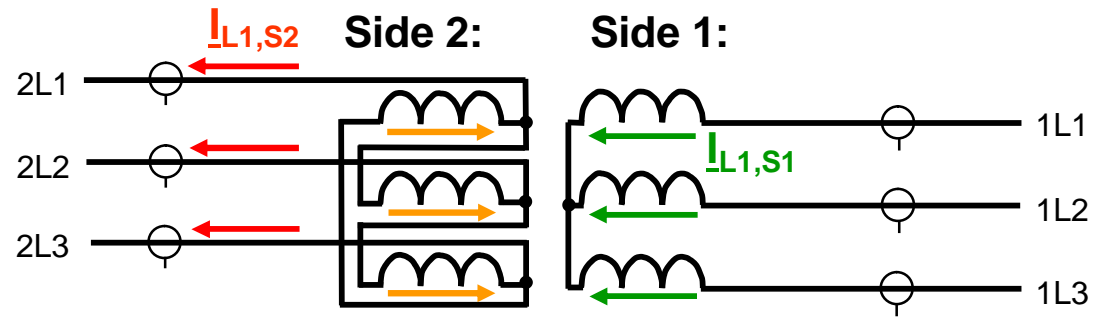
# Method of Vector Group Determination (Example Yd11)




$$\underline{I}_{L1,S2} = \underline{I}_{L1} - \underline{I}_{L2}$$



$$\underline{I}_{L1,S1}$$




$$\underline{U}_{L1,S2}$$

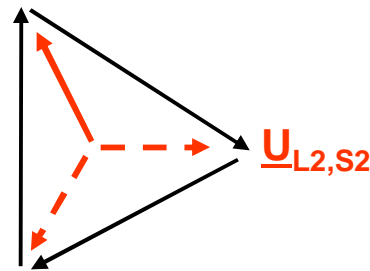


$$\underline{U}_{L3,S2}$$

$$\underline{U}_{L1,S1}$$

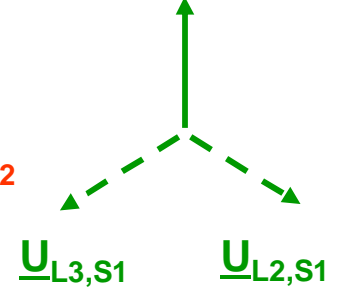

Vector group is  
**Y d 11**

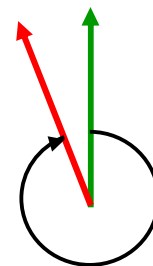

**330°**  
(n \* 30°)



## Definitions in SIPROTEC 4 Relays

Vector definition to a node is positive


The shown vectors or phase angles are transformed in this positive definition

The phase angle is displayed mathematics positive.


The reference phase is always phase L1 on side 1

### How to see the vector group Yd11?

Original

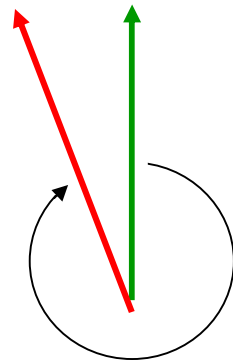

Siprotec 4 (Browser)

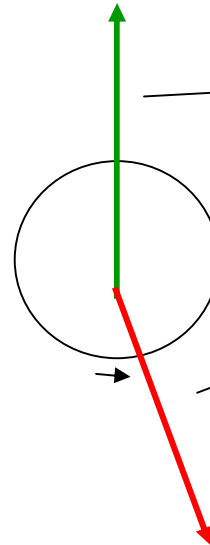

Phase angles

Side 1:  $0^\circ$   
(reference phase)

Side 2:  $210^\circ$

Please subtract  $180^\circ$ ,  
than you get  $30^\circ$   
( $360^\circ - 30^\circ = 330^\circ$ )







## Web Tool (Browser) Vector group YNd11

### Secondary Values

Currents: Side 1

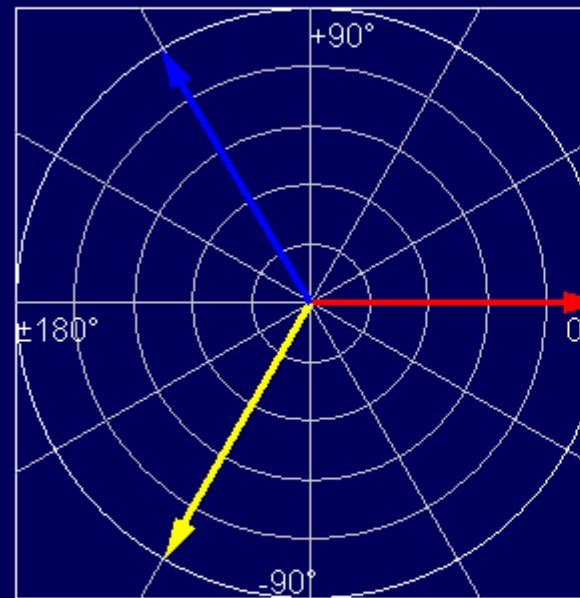

Currents: Side 2

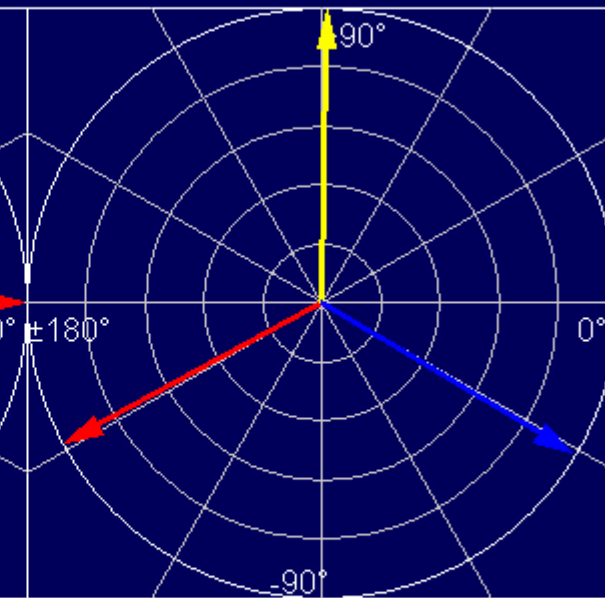

— IL1S1 = 1.00 A, 0°  
— IL2S1 = 1.00 A, 240°  
— IL3S1 = 1.00 A, 120°  
I7 = 0.00 A, ---  
f = 50.00 Hz



— IL1S2 = 1.00 A, 209°  
— IL2S2 = 1.00 A, 89°  
— IL3S2 = 1.00 A, 329°  
I8 = 0 mA



# Vector Group Determination via Fault Record

IL1;Side 2 lags 150° or leads 210°

Star point is towards the protected object

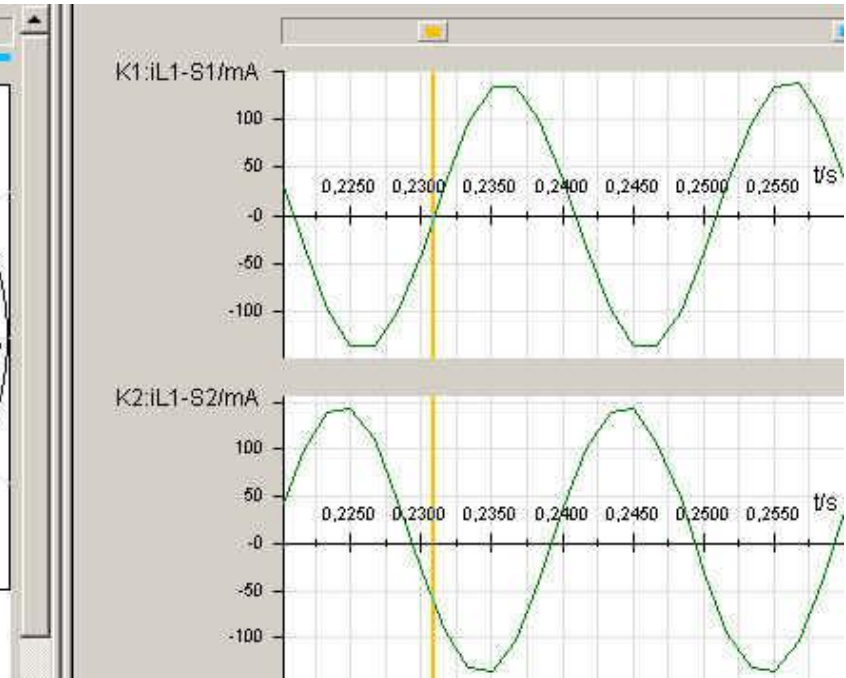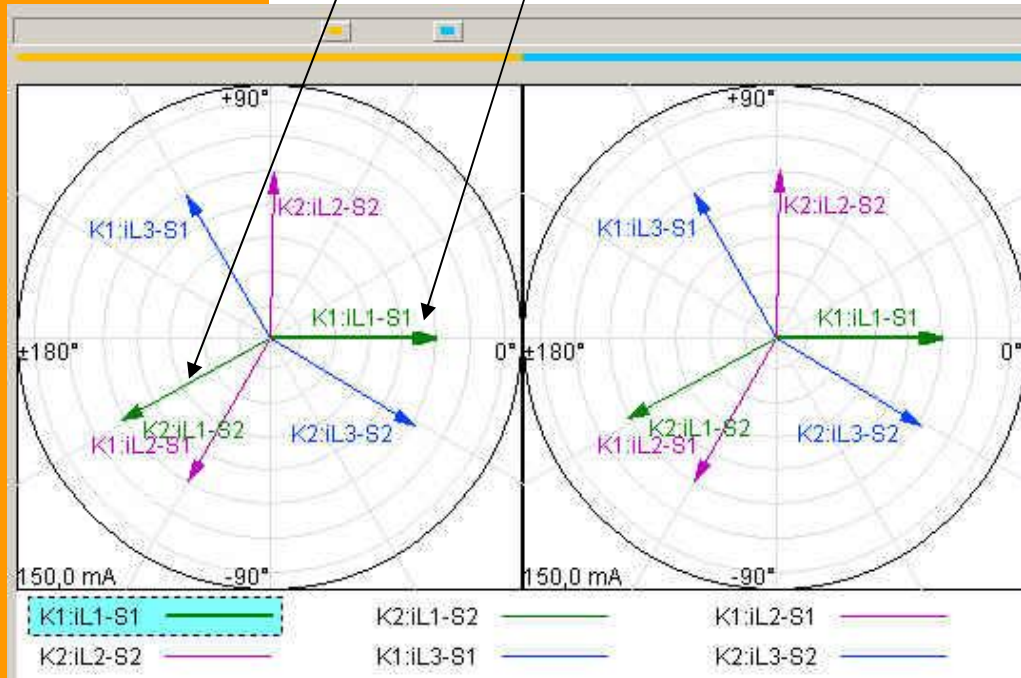

Way 1:  
IL1 Side:  $150^\circ + 180^\circ = 330^\circ$

Way 2:  
IL1 Side:  $210^\circ - 180^\circ = 30^\circ$   
leads  $30^\circ$  or lags  $330^\circ$

Phase shift is according the vector group definition  $330^\circ \rightarrow 11 * 30^\circ$